FREE INSIDE ~ HAM WALLCHART

electronics today

DECEMBER 1978 INTERNATIONAL

$1·25*

NZ $1.50

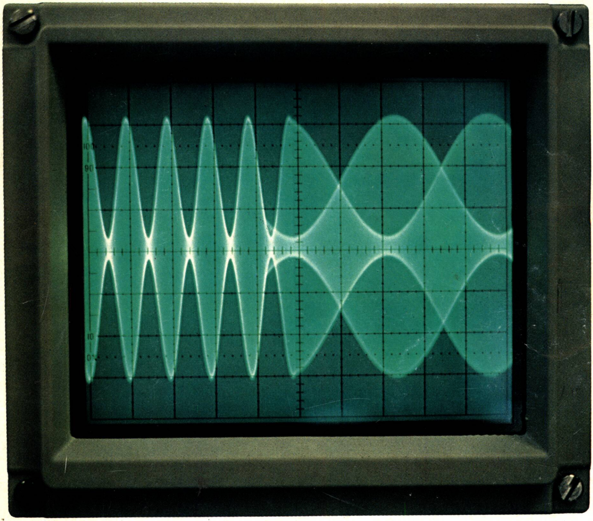

Designing Oscillators

Speech Compressor
Wheel of Fortune

NEWS, REVIEWS, HI~FI, COMPUTERS, SHORT WAVE RADIO...

WHAT EVERYBODY ASSUMED YOU ALREADY KNEW ABOUT TAPE RECORDING, BUT NEVER TOLD YOU...

...UNTIL **maxell**®
simply excellent

YES

I would like to learn more about tape recording. Please send me your 24 page Maxell Tape Booklet

...FREE!

Name..

Address..

....Postcode..................

Post this coupon to Maxell Advisory Service,
Post Office Box 307, North Ryde, N.S.W. 2113

WT83/78

AUSTRALIAN OWNED AND PRODUCED

December 1978, Vol. 8. No. 12

electronics today
INTERNATIONAL

Editorial: Les Bell
Managing Editor: Collyn Rivers

PROJECTS

556: Wind Speed and Direction Indicator 66
If you watch the weather, this is for you.
812: Wheel of Fortune 73
For the gamblers amongst you!
490: Audio Compressor 81
For amateur or CB use.
593: Colour Sequencer 89
For disco or theatrical effects.

FEATURES

Designing Oscillators 13
Not always as easy as it looks. . .
Special Offer: Chess Champion Mk 1 18
Special bonus if you get in quick.
Sound 21
Does it sound real?
Brains and Computers 31
How's your CPU?
Print Out 37
Various ramblings.
The Marisat System 45
It's not all at sea.
Special Offer: Hand-held Games 51
Car Race, Missile Attack, Basketball
ETI/Computerland Software Contest 52
Programming for fun and profit.
Introduction to PCM 57
It's changing telephones and hi-fi.
Nimbus Satellites 62
An eye on the ocean.
Data Sheet: LM324 78
Quad op amp.
Communications Section 97
For hams, SWL's, CB'ers.

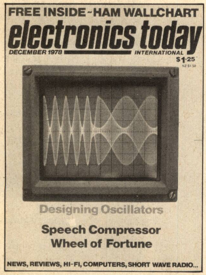

Cover: This month we're running an article on designing oscillators, but if you can design an oscillator to produce this kind of waveform, we'd like to know about it! If you're curious, we used a Tektronix 475A oscilloscope and a lot of ingenuity to get that waveform!

NEWS & INFORMATION

News Digest 4
Sound Briefs 29
Print Out News 37
Communications News 97
Propagation Predictions . . . 104
Kits for ETI Projects 109
PCBs for Projects 110
Mini Mart 112
Ideas for Experimenters . . . 124
Reader Services 130
Index to Advertisers 130

A Modern Magazines Publication
* Recommended retail price only.

Registered for posting as a publication — Category B

News Digest

The Inmos Saga

By now, many of our readers will have learnt of the formation of UK Government-sponsored Inmos, a British company which will attempt to catch up on US technology by producing a 64K dynamic RAM. In order to perform this feat, the management of the infant Inmos went head hunting in the Santa Clara Valley (Silicon Valley) for engineers who were already experienced in memory design, NMOS technology, etc. Having this kind of expertise is obviously crucial to the success of the venture. Several of the engineers they employed came from Mostek, who, understandably, felt that they were having their brains picked, and attempted to get an injunction against Inmos for misappropriation of trade secrets, in an effort to stop the raids for staff. However the charges were dismissed and Inmos seemed set to go.

The latest news, though, is that the three ex-Mostek engineers who were at the centre of the controversy have now left Inmos to set up their own design company, which will do work on a contractual basis for Mostek exclusively. Ward Parkinson, one of the founders of Micron Technology, claimed that he simply saw a better opportunity in working for himself. Although we hesitate to read between the lines, there is room for a lot of speculation in this story . . .

Datalogger 2000

United Systems Corporation, Dayton, Ohio, introduces their Datalogger 2000, a data information center that performs microprocessor-based functions such as signal processing, formatting, alarm assignment and interfacing.

The Digitec Datalogger 2000 measures up to four mixed parameters selected from temperature (Thermocouple, Thermistor, RTD), DC voltage, DC autoranging, AC voltage, True RMS and transmitter output. With up to 20 channels internal (expandable to 1000) and ± 25,000 count display of measured data, the Datalogger 2000 offers skip-channel capability and provides up to 1200 individually assignable alarms. It displays and records accurate time and date with a crystal controlled clock. Also displayed and recorded are channel number, measured data and parameter symbol with the printout of English messages that identify alarm status without look up tables. The 2000 offers data outputs that include isolated BCD, isolated RS-232-C or TTY compatible with selectable baud rates from 110 to 9600.

The Digitec Datalogger 2000 measures 430mm x 222mm x 355mm and weighs 9kg. A brochure is available with complete specifications from *NIC Instrument Company, Matthews Avenue, Airport West, Vic 3042.*

Earthquake Protection

How do you protect a nuclear reactor from an earthquake? The answer suggested by the UK's Malaysian Rubber Producers' Research Association is to mount it on giant rubber springs. In tests to be conducted jointly with the University of California at Berkeley, models of power stations will be constructed in the New Mexico desert and subjected to tremors from underground explosions. Instruments will record the performance of the rubber springs, which, if successful, will be installed in future reactor designs.

Student Scope Project

Students of the Electronics Department at Box Hill Technical College have combined talents to produce oscilloscopes for basic test equipment for students' personal use. Senior students are offered experience in the construction of complex equipment, design exercises, components research, board layouts, prototype testing and documentation under the guidance of staff.

The Department has quite a few student projects on the go; but the oscilloscope project has been the most adventurous and challenging due to the complexity of the oscilloscope as a piece of test equipment according to Jim Tregellas, teacher in charge of the project. Already a Power Supply project has been devised while a signal generato and an electronic voltmeter are other basic test equipment projects in the pipeline.

The technical specifications of the oscilloscope include:

Band width – DC to 5 MHz
Sensitivity – 10 mv/div.
Timebase – AC, DC, Auto and Line Triggering to 0.3 micro seconds per division
Probe – compensated (adjustable)

Cost of materials to students – approximately $130 tax paid.

The oscilloscope and other test equipment programs are produced by staff and students involved in the College's Certificate of Tehcnology (Electronics) course which is a post Year II, two year course plus 2 years of work experience. The 20 staff in the College's Electronics Department have had considerable industrial experience.

The photograph shows staff membe Jim Tregellas (centre) discussing the oscilloscope with Steve Edmonds (left) and Phillip Dew (right) graduate Certificate of Technology students of the College.

Portable TV/Radio

National Panasonic has just released the Model TR-5010A portable black and white TV receiver with 13cm screen and built-in AM/FM radio. This model, which sells at a recommended retail price of $215 can be operated from domestic AC mains, car or boat battery or its own internal batteries.

The unit is ruggedly constructed for the outdoor/portable life expected of such a versatile unit, and is available from selected electrical retailers, department stores and discount houses throughout Australia.

TI Embarassed

Rumours have been rife for an awful long time now about TI's personal computer, which will no doubt be the greatest thing since sliced bread, etc, etc, when it appears. The reason it hasn't is that TI are still suffering considerable embarassment following the unrelease of their processor-controlled CB, about which the technical press (that's us) went berserk. TI don't want the same thing to happen with their personal computer. However, here are the latest rumours, hot from the mill:

Since the project got under way, there have been no less than four major hardware design changes to provide performance improvements. The software specs were changed twice, giving Microsoft, who are developing the software under contract, a bit of a hard time. In fact they had to have their contract extended, and only delivered the final software in July.

Incidentally, TI are avoiding the phrase 'personal computer', preferring to use terms like 'home information system'. The magic box, when it appears, will work with a domestic TV set. Whether this will mean a delay while the system is redesigned or modified for the Australian market is not yet clear.

16K Static RAMs

Hot on the heels of Texas Instruments' announcement of a 16K static RAM design comes a similar product from Matsushita. The Japanese chip uses a double-layer cell structure and packs 101,000 transistor elements on a 15.7 mm^2 substrate. Access time is 110 ns and power consumption is 145 mA when running and 30 mA on standby. The package is a 24 pin type, and probably (though we don't know for certain) follows TI's lead in being pin compatible with the 2716/2516, with a 2K x 8 organization.

Advanced Submarine Communications

The latest technique to be investigated by the US Navy for communication with submarines is to use a high energy proton accelerator and aluminium bar system to produce a narrow beam of neutrinos which could be aimed through the earth at detectors on the other side of the world. The neutrinos would follow a straight path through the earth at the speed of light and radiation from the collision of neutrinos and water can be detected by submerged submarines. The system is expected to be jam-proof.

New Image for Dick Woods

Dick Woods Electronics is expanding its horizons. Now owned and operated by Dwell Pty. Ltd., the company is seeking (and achieving) a new image. The range of products handled has been expanded to include video cassette recorders, micro TV units, 'Snoopers' and an extensive range of car stereo systems, plus a range of components from TTL chips to nuts and bolts, many of which are directly imported.

Dwell has been appointed North Shore distributor for Plessey and have stocked a broad range of Foster speakers and speaker systems, in both complete and kit form.

Microcomputers will form a major part of the company operation. Systems handled at present include 'Synertek's VIM-1'; E&L MMD-1 8080 Mini-Micro Designer; 'Rockwell' AIM-65; a 6502 Micro System which includes a full ASC11 keyboard, a 20 digit alphanumeric display and a 20 column printer; and Micropolis 5¼ floppy disc systems, which store from 143,000 to 946,000 bytes (formatted) per drive.

Available shortly will be the Exidy 'Sorcerer' personal computer which is one of the most cost effective systems on the market. As standard it is fitted with a Z80 CPU, 20K bytes of memory, 1920 character display, graphics with a resolution of 122,880, a typewriter keyboard with a numeric cluster and full S100 capability.

Further details are available from:
Dick Woods Electronics, 77 Edgeworth David Avenue, Hornsby NSW 2077
Phone 4873111.

Chequebook Calculator

National Semiconductor Corporation has announced the Data Checker, a new thinline "cheque-book" calculator with three continuous memories. This unique memory feature allows a user to maintain and update both chequebook balance and balances for any two selected charge accounts. The three memories are simple to use, and do not interfere with usage of the calculator.

Balances are maintained even when the unit's power is off, and automatically updated as each new transaction is made. Balance figures, as well as calculator read-outs, are displayed on large Liquid Crystal Display (LCD), with 6mm digits.

Suggested retail prices for the Data Checker is $39.95 with Chequebook case and pen included.

News Digest

Microwave Exposure Levels

Research at the Institute of Occupational Medicine at Lodz in Poland is claimed to show that successive exposure to microwave radiation can have a cumulative effect, that excessive exposure can cause cataracts, and that the US Standard of 10 mW/cm^2 is too high. Researcher H. Mikolajczyk has found that RF fields below that level can alter the function of the pituitary gland in rats. Poland has introduced a system of RF standards to cover the frequency ranges 100 kHz to 300 MHz and 300 MHz to 300 GHz. In the higher range, 0.01 mW/cm^2 is reckoned to be 'safe' for the general population, while an 'intermediate' classification of 0.2 mW/cm^2 applies to electronics workers who may be exposed all day. 10 mW/cm^2 is the 'danger' limit at which 'exposure is not permissible except in urgent situations'.

Sanyo VCR

Sanyo Australia enters the colour video cassette recorder market early in December with their "Betacord" model. Developed after 10 years' design and production of VCR units, Sanyo were the first company to produce a truly portable video recorder.

The Sanyo VCR, using the Betacord system, is specifically applicable to Australian conditions. It utilises the U-shape loading system, the most widely used system in use in the world to-day. Among its special features are an "every-day" switch allowing you to go on holidays and record, for example, a half hour favourite programme for up to six consecutive days. Another important innovation is the remote pause switch which allows in-use editing while the programme is actually being recorded. With the Sanyo VCR, the remote pause unit is included as standard equipment and is not an optional extra.

The Sanyo VCR has a 12/12 warranty, comes complete with dust cover and a complimentary two-hour blank cassette. Sanyo will instal each unit at no cost to the consumer.

Fairchild Sues Data General

Remember Data General filed a suit against Fairchild over the Fairchild 9440 microprocessor, which executes the instruction set of the Data General Nova minicomputer? Well, just to even the score a bit, Fairchild have filed a $30 million dollar antitrust suit against Data General, charging unlawful marketing practices in the licensing of software for the Nova. Fairchild allege that this is designed to block competition with the 9440. Data General tie marketing of their software with that of the hardware, refusing to license their software to non-users of the Nova 1200 computer.

The Fairchild suit is backed up by similar charges filed by several other small computer companies, who manufacture computers which are software compatible with the Nova. Their case rests on whether it is reasonable for Data General to claim as 'trade secrets' the Nova instruction set, which they have published in manuals and books. The results of these cases could have very important consequences for the computer industry.

TI Calculator

A new calculator which has been released by TI in the UK stores the last 20 entries the operator makes. The TI-2550-IV is a four-function-with-percentage hand-held with memory which is designed to replace printing calculators by letting the operator review calculations and 'edit' them if necessary. The replay facility is activated by one key, and there is also a 'back-step' key. Corrections can be made at any point by keying in the correct entry and hitting the equals key.

Fibre Optic Kit

A new, complete fiber optic link for data communications applications that requires no expertise in optical design, calibration or adjustment, has been introduced by Hewlett-Packard.

The new HFBR-0010 low error rate fiber optic link system makes the use of fiber optics simple and practical for a broad range of customers. It comes ready to hook up, and consists of a digital transmitter, a digital receiver, a single fiber 10 meter connector/cable assembly and complete technical literature. Each of the components is available separately, and the connector/cable assemblies come in five standard lengths, with a maximum distance of 100 meters.

Typical applications of the new link include: Large computer installations; distributed processing systems; hospital computer systems; power plant communications and control; process control; voltage or electromagnetic field research; remote instrumentation systems; and factory data collection.

The new systems are point-to-point links intended for logic-to-logic communications over short to intermediate distances in industrial or laboratory environments. Processor-to-processor o processor-to-peripheral interconnection are prime applications.

"Applying a system design approach we were able to remove the complexities, to enable OEM systems designers or end users with data communications problems to begin using fiber optics links without having to become expert in the various discipline involved," said Peter Manno, product marketing manager for HP's Optoelectronics Division.

For further information, contact HP's representatives, Amtron Tyree.

Programmable Power Opamp

A programmable power operational amplifier with a unique electronic shut down capability that allows it to "float" in the "off" mode, passing only microamperes of current, has been developed by National Semiconductor. Designated the LM13080, the 50 by 50 mil bipolar device is internally compensated and can be programmed to allow the user to optimize the amplifier performance for his individual application.

The LM13080 has been designed primarily for those applications that require load currents from the output of 50 to 250 mA, either sink or source. Applications include audio amplifiers, power comparators, DC-DC converters and servo drivers for motor speed control.

According to Chris Mason, Applications Engineer, the user establishes the bias for the amplifier's input stage by means of an external resistor and as a result can control a number of the device's performance characteristics, including: input bias current, input offset voltage, and frequency response. Using resistors ranging in values from 100K ohms to 3M ohms, the input voltage varies up to 15 mV and the input bias current goes from less than 50 nanoamperes to 2 microamperes. With a 680k ohm resistor, for example, the amplifier is unity gain stable while the offset voltage is approximately 3 millvolts. If a tight offset voltage is needed, a 100k ohm resistor would allow an offset voltage of less than 1 millivolt, with minimum closed loop gain of 6.

Unlike similar devices on the market, the LM3080 has an electronic shutdown without the need to carry load currents in the control device. The device is unique, said Mason, in that the bias circuit for both input and output stages can be bypassed so that the entire circuit is turned off. This allows both stages to "float" while drawing only a few microamperes of quiescent current devices. By means of a saturated NPN switching transistor, the input programming (set) resistor and the output stage control pin are connected to ground for normal operation. In the "off" mode, the switching transistor is turned off and both the output and input stages are allowed to "float". This feature according to Peter Moon of NS Electronics, makes the LM13080 very useful in portable battery-powered applications. Because the average quiescent current in battery-powered systems may be 100 to 1000 times lower than that of other systems, using the LM13080 would result in less drain on the battery. Moreover, because it would not need to handle lead currents, the external switching device could be smaller and less expensive.

The LM13080 is designed to operate from both single and dual power supplies, and will operate from as little as 3 volts (DC). Available now, the LM13080 is priced at $0.72 each in 100-up quantities.

The new Grundig "Picture in Picture" 26" colour T.V. enables the viewer to watch two programmes at the same time – the normal programme plus a superimposed programme on the same screen. The main colour picture can be selected and, if required, an alternative programme which is visible on the same screen approximately the size of a postcard, in black and white. The alternative programme always appears in the same spot, in the middle of the bottom of the screen.

FAST Logic

Soon to be released is a new logic family called FAST – Fairchild Advanced Schottky TTL with low power consumption and propagation delays around 3 ns. 66 circuits will be available by the end of the year, at 'competitive' prices.

Gadget of the Month

Following hot on the heels of electronic popcorn and yoghurt, the latest gadget to be electronified is the cigarette lighter. A new design of solar-powered gas lighter has been announced by Yoshinaga Price Co. of Tokyo. It can run for six months, 40 lights per day, without requiring recharging. 5 min of bright sunlight will recharge this little marvel.

900 MHz CB for US?

The FCC Safety and Special Radio Service Bureau has ordered the drafting of a notice of inquiry for public comment on whether CB radios should be allocated a section of the spectrum around 900 MHz. The Commission reckons that expansion of the CB allocation is necessary, partly to stimulate the depressed CB industry.

Scribofoon?

The Scribofoon is a development of Philips Telecommunicatie Nederland which can transmit diagrams and written text over telephone lines. At the transmitter, a plastic pad, with X axis wires on the top side and Y axis wires below which are pulsed sequentially, is used to encode the position of a pen. A sequence of pen positions is transmitted over the phone lines to the receiver, for display on a screen. The system requires no modification to the telephones at each end, and will cost about the same as an ordinary colour TV.

Appliance Timer

General Instruments have announced the release of an appliance timer IC similar in concept to the STAC timer featured in last month's issue. Intended for use in cookers and similar appliances to replace the old stay clocks, the AY-3-1251 has keyboard entry, direct digit drive and four outputs. Further information from GI distributors.

INTRODUCING THE AR9. FOUR-ON-THE-FLOOR PLUS "ELECTRO-AUTOMATIC TRANSMISSION."

Bookshelf and mid-size speakers have been AR's act for 25 years.

Nobody builds them better, tests them more thoroughly or backs them with a stronger warranty.

But the flagship of most speaker lines is a big, floor-standing job. A heavy hitter that will blow your socks off. And our flagship has just come in.

The AR9 is a four-way, floor-standing speaker, 52¾ inches tall, with 5 drivers and the ability to handle amplifiers capable of delivering up to 400 watts *(gasp!)* continuous power per channel. (With amplifier being driven to clipping 10% of the time on normal music source material.)

The price: approximately $1250 a copy.

But the AR9 is a lot more than big and expensive.

The thing sounds simply fantastic.

Flat as a pancake all across the sound spectrum and virtually unaffected by room placement.

Each speaker contains two 12-pound, 12" diameter woofers. The two of them are linked by a kind of electronic automatic transmission." Deep in the low end where volume falls off as frequency goes down, the "automatic transmission" cranks up the woofers to maintain volume without the usual break-up and distortion.

Crossover points have been rearranged so that the 8" low mid-range driver handles the critical range of human voice . . . a design refinement that contributes to the startling clarity of the AR9 sound.

There is a new semi-horn on one high-frequency driver.

Improved liquid cooling.

A tweeter voice coil made with new high-temperature materials.

Refinements of proved AR engineering concepts abound throughout the system.

And the results are absolutely startling.

Our ears tell us, and our test instruments confirm, that the new AR9 is nothing less than the most perfect speaker system possible today.

To get a more complete write-up, contact your AR Dealer or us.

But better yet, listen to the AR9.

Then tell us it's not the fantastic speaker system you've ever heard.

ANOTHER TRIUMPH FOR TRUTH IN LISTENING.

Acoustic Research Australia
P.O. Box 21 — 7 Ford St.,
Greenacre. NSW. 2190
Phone: 642-3458

ar1.9

Portable TV Combo

National Panasonic has just released a versatile new portable unit which offers 3 programme sources as well as three separate power sources at very reasonable cost. The unit, designated Model TR-5000A is a combination black and white television, AM/FM radio and cassette recorder which can be operated from a domestic power unit, car or boat battery or its own internal batteries, which makes it ideal for outdoor living in car, camp, caravan or boat.

Television reception is excellent, even in bright outdoor locations on the 13 cm diagonal monochrome picture tube, and the powerful AM/FM radio receiver and cassette recorder give a wide choice of audio/video entertainment.

It comes complete with a sunshield for outdoor viewing, 3-way level/tuning meter and bass/treble controls, and at all all-up weight of only 4 kg (just under 9 lbs) without batteries it is light enough to go anywhere yet sufficiently strongly constructed to withstand the knockabout life of the portable. Recommended retail price from National dealers is $330.00.

Digital Watch Patents

Commodore (of PET fame) has received patents on two techniques for digital watch operation. One covers the use of a piezo-electric crystal to vibrate the watch as an alarm, while the other is more important and covers the use of one button to select the display of time, seconds and date – a technique used by virtually all manufacturers.

Home Computer Show

Box Hill Town Hall (Box Hill, Melbourne) will come alive to the sound of printers on the weekend of 9-10 December as it is the venue of the Home Computer Show being organised by Australian Seminar Services Pty Ltd of Melbourne. Judging by the bookings for stand space, the show is bound to be a success, with lots of interesting hardware on display. The success of the recent ACS-8 Computer Fayre in Canberra also augurs well for this show. Many companies who advertise in ETI will be there, and some interesting new products will be on display.

Among the exhibitors will be: Rod Irving Electronics, Abacus EDP Services, Futuretronics Pty Ltd, ASP Microcomputers, S M Electronics, Pennywise Peripherals, A J Ferguson, Sontron Instruments, the Byte Shop, the Caldor Corporation, Dick Smith Electronics, Warburton Franki, Philips, Computer Portraits, South West Electronics, Box Hill Technical College, Computerland, Texas Instruments, Delta Scientific Products, Automation Statham and, of course, ourselves – ETI.

We shall be displaying a selection of the ETI microcomputer related projects, including the ETI 640 VDU, the ETI 641 printer, the STAC timer from last month's issue, and some other goodies which we're sure you'll find interesting. The show is being held at the Box Hill Town Hall, Whitehorse Road, Box Hill, from 10 am to 10 pm on Saturday 9 December and from 10 am to 6 pm on Sunday the 10th. The admission fee is $2 for adults and 50 cents for children.

See you there!

Synergistic Beer Drinking

Well, last month we all turned up as usual, carrying bound volumes of ETI, ready to answer your questions, expecting to be overwhelmed, but we were rather disappointed by the turnout! We think the problem must be that we've arranged the Synergistic Beer Drinking for the first Wednesday of the month, but that is just before the magazine has been appearing, one month after the last one and so you've all forgotten about it. So, from this month, its going to be on the *second* Wednesday of the month; as you read this, that's probably next Wednesday. Now there's no excuse.

Here's all the relevant info, once again. The ETI technical staff will be at the *Bayswater Hotel, Bayswater Road, Rushcutters Bay,* (near the Rushcutter Bowl), on the *second* Wednesday of the month, to talk about electronics, hi-fi, computers, radio, anything! If you come along, we'll be glad to talk to you (we love a captive audience)!

ETI Price Increase

We regret that, starting with the January 1979 issue, the cover price of ETI will increase to $1.40. This is due to increasing costs, but we hope that you will continue to think that ETI offers good value for money.

ETI/Unitrex Calculator Contest

The October contest got a good response, and not many of you were stumped for the correct answer, which is, of course, $73.36. The winner for October is Mr Indry, of Kingsford, NSW, who will receive a Unitrex Calculator.

This month's problem was suggested by Mr B V Takach, of Wahroonga. He asks 'Our technical library displays the bound volumes of *The Diecasting Engineer.* Six issues, each of sixty pages, are bound into hard covers and placed on the book shelf in order. A busy bookworm chewed through the first page of Volume 22 to the last page of volume 23. How many pages have been chewed through?'

Seal an empty envelope, write your answer on the back of it, and send it to: Unitrex Calculator Contest (December), ETI Magazine, 15 Boundary Street, Rushcutters Bay, NSW 2011. The closing date is Friday, 5 January 1979.

How to crack a highly paid job as an electronics technician.

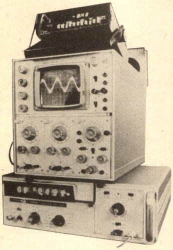

We'll give you excellent training - as good as you'll get anywhere in Australia.

We'll give you free medical, dental and hospital treatment.

We'll provide plenty of good tucker and a comfortable place to stay.

We'll give you substantial leave, and on top of all that, we'll pay you well while you're training.

On your side, you'll give us a period of hard, but interesting and rewarding work. And, when eventually you leave us, you'll find yourself a fully qualified and experienced Electronics Technician. Not a bad thing to be, these days.

So, if electronics is your idea of a great career and you are (at time of entry) approx. 15 to 17 for apprenticeship and over 17 for an Adult Trainee, join the Navy, Army or Air Force.

Phone us at:

Adelaide 223 2891. Brisbane 226 2626.
Canberra 82 2333 Hobart 34 7077.
Melbourne 61 3731. Perth 325 6222.
Sydney 212 1011.

Write to either the Navy, Army or Air Force Electronics Technician Counsellor, GPO Box XYZ in your nearest State Capital City (please include your date of birth).

Learn Electronics with us.

Authorised by Director-General of Recruiting. Dept. Defence.
TSAP15.FP.48

TDK's Revolutionary New Product — The HD-01 Head Demagnetizer Built into a Cassette Shell.

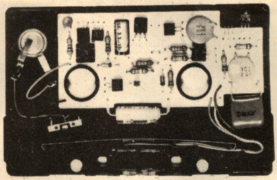

Simply load the HD-01 into any cassette recorder as you would a standard audio cassette and depress the 'play' button.

The HD-01 Head Demagnetizer was designed by TDK for easy, convenient head demagnetization of any cassette deck, insuring crystal-clear, perfect recordings every time.

The TDK HD-01 Head Demagnetizer features:

- A unique cassette format, designed to insure complete compatibility with any cassette deck.
- Powerful de-gaussing circuit instantly demagnetizes recorder heads the moment the play button is depressed. The above diagram depicts the oscillating waveform applied to the recorder heads, removing every trace of residual magnetism in only one second!
- A red LED (Light Emitting Diode) built into the HD-01 cassette shell will light up the moment your recorder heads have been completely demagnetized.

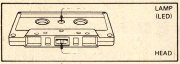

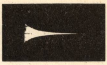

The TDK HD-01 Head Demagnetizer ends forever the fuss and mystique surrounding the demagnetization process and is much easier to use than conventional wand-type tools. Anyone can use the HD-01 and get perfect results every time.

The TDK HD-01 Head Demagnetizer is completely self-contained, battery operated and portable. It can be taken anywhere and stored with your present audio cassettes. The TDK HD-01 is ideal for all types of cassette decks especially those with heads located in hard to get at places such as:

- recorders with heads positioned in the front of the unit but which point to the rear.
- those with 'pop up' loading mechanisms which can not be detached, thus making the heads almost inaccessible.
- cassette decks with heads positioned laterally with respect to cassette loading (car decks are good example of this type).
- automatic loading machines.

WHY IS DEMAGNETIZING SO IMPORTANT?

TDK, in conjunction with many cassette deck manufacturers, recommend that cassette decks be maintained on a regular basis. Cleaning the heads, capstan and pinch rollers is one important aspect of that maintenance program. — Periodic demagnetizing, about every thirty hours of use, is the other. Failure to do so will cause a build-up residual magnetism on the heads, which can seriously affect tape and machine performance in the following critical areas:

1. The noise level in the low and midrange frequencies is increased by 5 to 7dB, thereby reducing the overall signal-to-noise ratio.
2. Pre-recorded tapes can also be affected with midrange and high frequency distortion, as well as attenuation by as much as 2 to 6 dB, virtually eliminating any hopes for clear sound reproduction.

The interaction of these factors will not only prevent both the tape deck and tape from displaying their true performance capabilities, but will severely limit the Dynamic Range properties of both, rendering pure sound reproduction an impossibility.

The following comparison data clearly demonstrates the effect of residual magnetism on recorder heads in the areas of both Noise Level and Frequency Response.

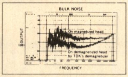

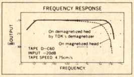

TECHNICAL DATA

Major Components:

Transistors (8)
Diodes (2)
LED (Light Emitting Diode)

Power Supply – Control Section – Oscillation Section – Head Section

Specifications:

Maximum Magnetic Flux Density	200 Gauss
Oscillation Frequency	630 Hz
Shape	(External Dimensions) Conform to IEC Standards
Battery for Power Supply	G-13 1.5 volt, Silver Oxide Battery (option)

Schematic Diagram of HD-01

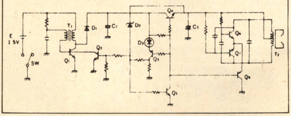

For additional information, direct all inquiries to:

CONVOY INTERNATIONAL PTY. LTD.
4 Dowling Street, Woolloomooloo, N.S.W. 2011
Telephone: (02) 358-2088. Telex: AA23111

The priceless gift of learning now has a price: $799.95 And a name: the Radio Shack TRS-80® Microcomputer. And now, at last, your child has a chance to discover Tomorrow on Christmas morning.

"Tomorrow" is an electronic world, based on computers—and it's already here. In it your child can be a number in a machine. A robot. Because he or she does not understand either the number or the machine. Or your child can be pleasurably elevated into this brave new world with a gift that has only become affordable in recent months

Advice for Parents Who Care

In your lifetime the possibility of owning or giving a computer—up to now—was unthinkable. A computer? That can teach? Remember? Display on its own screen? Play games? Complete with a standard typewriter keyboard? Unthinkable—up to now.

But now the Tomorrow Machine is not only thinkable but practical, affordable and available through every Tandy store and participating dealer. The TRS-80 personal computer system? For the kids? For Christmas?

TRS-80 manual, written by an educator, is 232 pages of instruction for a beginner.

TRS-80 system includes everything in this picture and, of course, the manual.

TRS-80 is expandable and can grow in power and utility. Everyone in the family becomes involved, entertained, informed.

INDEPENDENT TANDY ELECTRONICS DEALERS MAY NOT BE PARTICIPATING IN THIS AD OR HAVE EVERY ITEM ADVERTISED

TCDec78

DESIGNING OSCILLATORS

One of the problems in electronics is stopping amplifiers from oscillating, another problem is getting oscillators to oscillate . . . Tim Orr explains.

AN OSCILLATOR IS BASICALLY an amplifier with positive feedback applied around it. The feedback must be AC coupled otherwise a DC latch up condition would occur. Having got some sort of oscillation, one of two things can happen. The oscillation can build up in amplitude until clipping occurs due to the power supply voltage levels. At this point a stable, but truncated waveform will be generated. Alternatively if the gain of the amplifier is too low the oscillation will die away. To produce a pure sinusoidal oscillation the level of the signal in the system must be accurately controlled. There must be some amplitude limiting or automatic gain control such that when the peak signal level tries to exceed the reference voltage, the amplifier's gain is reduced. This is in fact what limiting does. To maintain stable oscillation, the overall gain of the system must be exactly unity. Any less and the oscillations will never start. If the gain is more than unity, the oscillations will occur, but amplitude limiting will cause gross distortion.

A very common method for stabilising the oscillations, which is often used in Wein bridge oscillators, is to employ a very sensitive thermistor as an AGC. However, the thermal time constant of this component often produces an annoying amplitude bounce with occurs when changing to a new frequency.

Other methods are diode limiters (which tend to cause large amounts of distortion) and FET AGC circuits. The latter method can be used to generate super low distortion sinusoids by allowing the system gain to stabilise over tens of seconds.

The oscillation frequency is mainly determined by the feedback around the amplifier. By making the feedback a reactive network, the phase of the feedback will vary as a function of frequency. Oscillations can only occur when the feedback is positive and thus the phase response of the feedback will determine the frequency of oscillation, assuming that the overall gain at this frequency is at least unity. By varying the phase response of the feedback, the oscillation frequency may be altered.

An oscillator should be thought of as being a circuit which continuously generates a waveform, no matter what the shape of the waveform. There are very many circuit techniques for generating these signals which range from relaxation oscillators to piece wise approximations using square waves. Some of these methods will now be illustrated.

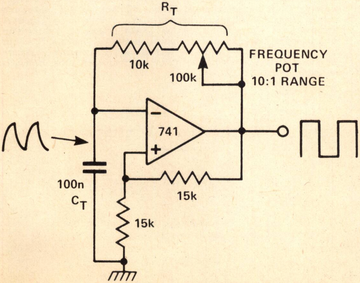

Manually Controlled Oscillator

In this circuit there are two feedback paths around an op-amp. One is positive DC feedback which forms a Schmitt trigger, the other is a CR timing network. Imagine that the output voltage is +10V. The voltage at the non-inverting terminal is +5V. The voltage at the inverting terminal is a rising voltage with a time constant of C_TR_T. When this voltage exceeds +5V, the op amp's output will go low and the Schmitt trigger action will make it snap into its negative state. Now the output is −10V and the voltage at the inverting terminal falls with the same time constant as before. By changing this time constant with a variable resistor a variable frequency oscillation may be produced.

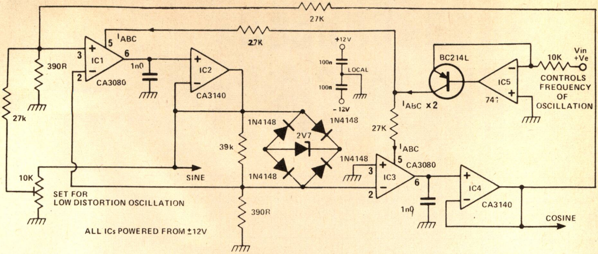

Dual Integrator Quadrature VCO

This is a sinusoidal oscillator which uses frequency dependent feedback and zener diode amplitude limiting. IC 1, 2, 3 & 4 form a dual integrator circuit which is an analogue model of a second order differential equation! There is some positive feedback around IC1,2 which is analogous to having a zero damping factor in the equation. This means that the oscillations will build up. The positive feedback is controlled by the 10k preset. IC1,3 are integrators and IC2 and IC4 are voltage followers with high input impedance. The phase shift produced by the integrator is 90° so there is no overall feedback around the loop (IC1 is non-inverting, IC2 inverts). Thus we have all the conditions for oscillation, and in fact oscillations will occur when the preset is adjusted to give the correct phase shift around the IC 1, 2 stage. Amplitude limiting is produced by the 2V7 zener inside the diode bridge. By placing it inside the bridge the same diode is used for both positive and negative signals and the limiting is symmetrical. The integrators are two quadrant multipliers (CA3080s), so the gain of the loop can be controlled by the current I_{ABC}. In the solution of this second order differential equation, the gain of the loop is proportional to the resonant frequency. Thus, by varying I_{ABC}, or rather by varying V_{IN}, the frequency of oscillation may be altered.

As the integrators produce a 90° phase shift, the two sinusoid outputs are in phase quadrature, i.e. one is a sinewave, the other a cosine wave. The cosine output is lower in distortion than the sinewave, because the amplitude limiting (and hence the distortion) is produced at the IC1,2 stage.

The second stage (IC3,4), acts as a filter and hence produces a purer sinusoid. Using this circuit a 1000 to 1 continuous frequency sweep can be obtained. However, the inaccuracies in the CA3080's will cause some amplitude variations and it may be necessary to set the positive feedback a bit high (and hence attract more distortion), to maintain stable amplitude limiting over the sweep range. This circuit is an oscillating filter and if you turn down the positive feedback and inject a small signal through a 100k resistor into IC1 pin 3, a bandpass and low pass response is obtained from the sine and cosine outputs respectively.

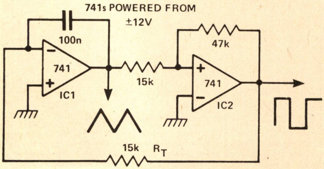

Simple Triangle Square Wave Oscillator

This circuit simultaneously generates a triangle and a square waveform. The triangle could be 'bent' by a diode function generator to produce a sinewave. The circuit is always self starting and has no latch up problems. IC1 is an integator with a slew rate determined by C_T and R_T and IC2 is a Schmitt trigger. The output of IC1 ramps up and down between the hysteresis levels of the Schmitt, the output of which drives the integrator. By making R_T variable it is possible to altar the operating frequency over a 100 to 1 range. Three resistors, one capacitor and a dual op amp are all that is needed to make a versatile triangle squarewave oscillator with a possible frequency range of 0.1Hz to 100kHz.

CMOS Oscillator

Two CMOS gates can be used to produce a simple oscillator. Imagine that output B is high. Then the input to A is also high due to it being coupled via the capacitor C_T to output B. Thus output A is low, input B is low and output B is high, which is as we would expect. However, capacitor C_T is being discharged via the 100k pot and 10k resistor to a logic 0. When this voltage reaches the crossover point for A, output A goes high, and thus output B goes low. Now the capacitor is charged up to a logic 1. Thus the process repeats itself. Varying the 100k pot changes the discharge rate of C_T and hence the frequency. A square wave output is generated. The maximum frequency using CMOS is limited to 2MHz.

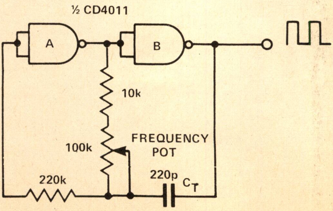

TTL Oscillator

A simple relaxation oscillator can be made using a TTL Schmitt trigger. The circuit (a) is the most simple version that can be produced. Imagine that the output is high. Capacitor C_T is charged up via R_T. When the upper hysteresis level (HyH) is reached, the output goes low. CT is now discharged until the low hysteresis level (HyL) is reached whereupon the output goes high. Thus the oscillator generates a square wave, with an uneven mark to space ratio, due to the input current requirements of the 7413. The frequency can be set at any value up to several megahertz by varying C_T and R_T. C_T can be an electrolytic but R_T must not be more than about 1k5 or it will not be able to pull down the Schmitt trigger inputs. (If you use a CMOS Schmitt this does not apply). The output is a nice fast squarewave capable of directly driving several TTL loads. One problem to be encountered is frequency jitter. When the input is very near to a hysteresis level, noise in the system may cause the oscillator to prematurely trigger, thus making that period slightly shorter and producing a noise induced frequency jitter. Also using two Schmitt triggers from the same IC is sure to cause interaction and thus jitter. To reduce power supply noise effects the IC should be decoupled with a 1uF tantulum capacitor actually at the V_{cc} and GND ins of the package.

Diagram (b) shows the same oscillator, but with a 10 to 1 manual control of frequency. The timing capacitor is charged up by the 10k pot and the 1k resistor. This voltage is then buffered by the emitter follower and fed to the Schmitt trigger. When the upper hysteresis level is reached the output of the Schmitt goes low and the capacitor is rapidly discharged via the diode until the lower level is reached. The process then repeats itself. As the discharge period is so fast, it can be as short as a few hundred nano seconds, the period can be thought of as being determined by the charging time, which is controlled by the 10k pot.

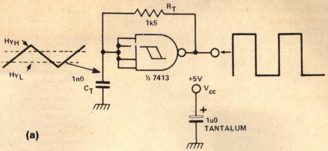

(a)

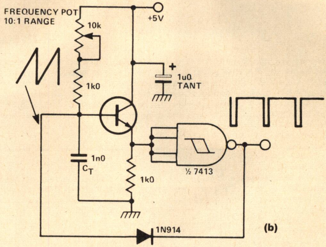

(b)

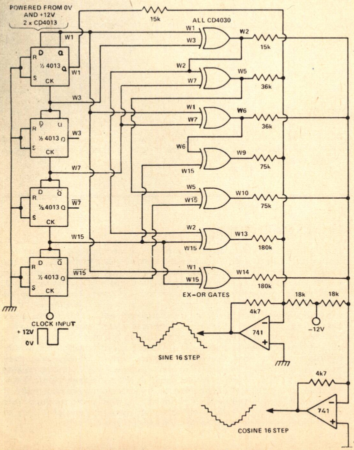

Walsh Function Generator

The mathematician Fourier said that any repeating waveform could be made up out of harmonic components. These components are sinusoids which are integrally related to the fundamental period of the waveform in question. This is a convenient conceptual approach, but as a way of practically synthesising waveforms it is not on. You would have to generate a whole series of harmonically related sinewaves which might prove a little difficult. However, a man called Walsh said that you could do the same thing as Fourier, but will square waves. So, instead of using sinusoidal Fourier sets, we can use square wave Walsh functions to synthesise waveforms. There are various techniques for calculating the Walsh function co-efficients for generating particular waveforms but these are beyond the scope of an article such as this. The diagram shows the circuit for generating a sine and cosine waveforms using 16 steps. Walsh functions are orthogonal functions, just as sine and cosine are orthogonal, and so the generation of these two waveforms is relatively simple using this technique. The 4013 dividers and the exclusive OR gates generate the Walsh functions, which in turn are converted into analogue waveforms by use of the correctly weighted resistor networks. Note that you only need 4 resistors to generate a 16 step sinewave approximation.

The resultant outputs can be easily filtered by fixed or tracking filters to produce pure sinusoids. The output frequency is 1/16th of the input clock frequency. The clock can be stopped and the outputs will remain fixed; try that with analogue trchniques!

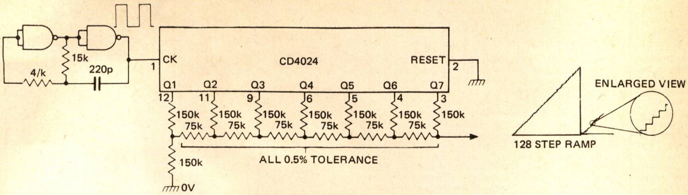

R-2R Staircase Generator

Waveforms can be constructed by building them up out of separate elements. In this case a linear ramp waveform is generated out of 128 steps. The CB4024 is a seven stage binary counter. It is being driven from a CMOS clock oscillator similar to that already described.

The Q1 to 7 outputs divide this clock frequency by 2,4,8,16,32, 64 and 128 respectively and the divided outputs are then fed into an R,2R ladder network. This is in fact a Digital to Analogue Converter (DAC) and as the counter is merely counting up, then the converter will generate a linearly rising waveform made out of 128 steps. When the counter overflows, the ramp waveform resets and the process repeats itself.

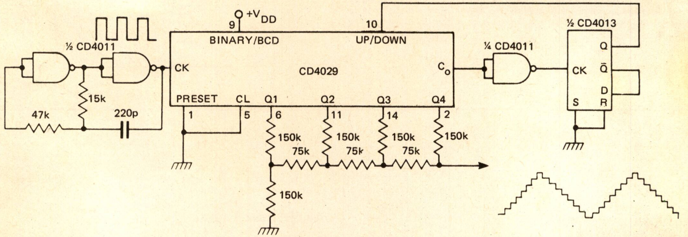

R-2R Triangle Generator

This circuit is similar to the previous except an up down counter is included. A clock signal is applied to the 4029 counter. When it has counted 16 clocks a Carry signal is generated. This clocks a D type flip-flop (4013), which changes state and reverses the up down mode of the 4029. Thus the circuit counts up, down up etc. The counter is converted via an R,2R ladder into an analogue output, a triangle waveform made up out of several steps.

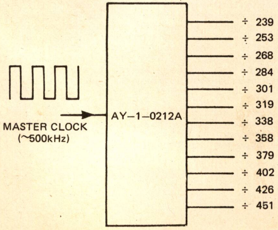

Master Tone Generator

If you have ever made an electric organ, piano or string machine you would have had to produce the twelve notes for the top octave by some means or other. More expensive organs might use 12 master oscillators which would be tuned to the top twelve semitones on the keyboard. This gives a nice free phase quality to the sound. The notes in the octaves below are made by using binary dividers and filtering. Very expensive organs would use an oscillator per note. This allows every note to be individually tuned and produces a very good sound quality. However, there is an easy way of producing the semitones and this is with a master tone generator chip. This is a pre-programmed divider having one input and twelve or thirteen outputs. A high frequency master clock is put into the chip which is deivded by numbers ranging from 239 to 451. These divisions produce the semitone outputs. Thus, by using one master oscillator and one master tone generator a lot of the work of making an organ is removed. It is possible to produce more accurate intervals using 12 oscillators, but the speed and efficiency of the chip usually wins in the lower price end of the market.

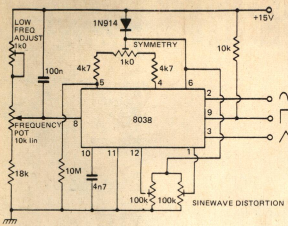

8038 Function Generator

There are several ICs available which perform some sort of oscillator function. One such is the Intersil 8038 which is a VCO with sine, tirangle and squarewave outputs. The basic oscillator is a triangle squarewave. The frequency is voltage controllable but is not a linear finction. The triangle symmetry and hence sinewave distortion are adjustable with a preset but change when the frequency is altered. Operation up to 1MHz is possible.

Triangle Squarewave ICO Using CA3080's

This circuit is very similar to that of the simple triangle/square oscillator, except that the operating frequency is controlled by a current I_{ABC}. (ICO stands for current controlled oscillator, as opposed to VCO, voltage controlled oscillator). Using this circuit, a sweep range of 10,000 to 1 is possible (for I_{ABC} 500 uA to 50 nA). The CA3080 is a two quadrant multiplier and the CA3140 is a MOS FET op-amp. IC1 is used as an integrator. IC2 is a high input impedance voltage follower and IC3 is a Schmitt trigger. The CA3080 has a current output which in the case of IC1 is used to charge up a capacitor. The voltage on this capacitor is buffered by the CA3140 and fed into the Schmitt IC3. The CA3080 (IC3) forms a very fast Schmitt trigger but as it has a current output, it cannot be loaded in any way without affecting the operating frequency. The output of the Schmitt is used to make the integrator inverting or non-inverting. Thus the operation is as follows. The integrator ramps upward until the positive hysteresis level is reached. The Schmitt flips over, the integrator then ramps downwards until the negative hysteresis level is reached. The Schmitt flips back and the process is repeated. The ramp rate is determined by the size of the current I_{ABC} and is linearly proportional to the oscillation frequency. At very low currents the triangle waveform may become very asmmetrical. This is due to current mirror mismatches inside IC1 and this device may have to be specially selected for continuous symmetry.

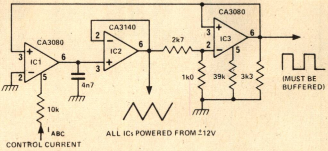

Precision Voltage Controlled Oscillator

The RC 4151 is a precision voltage to frequency converter. It generates a pulse train output which is linearly proportional to input voltage. The linearity for the circuit shown is 0.05%. The IC compares the input voltage with an internally generated one. It dumps controlled pulses of charge into a parallel RC network and compares this generated voltage with the input. If the input is greater it puts more pulses of charge into the RC network until the two are balanced. To get a larger sustained voltage in the RC network the frequency of the pulses must be increased. Thus the frequency of the pulses generated is made to be proportional to the input voltage.

The output is a pulse waveform and is intended to drive some sort of counting system, the chip being used as simple analogue to digital converter. It can also be used as a frequency to voltage converter. A maximum frequency of 10kHz has to be observed.

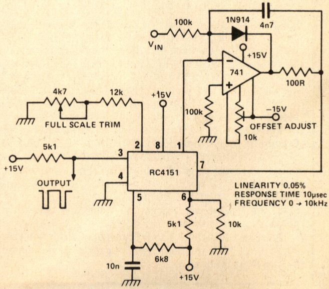

SPECIAL OFFER

Chess Computer

$149.95!!

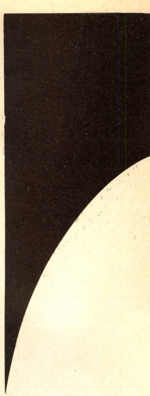

The Chess Champion Mk 1 is a self-contained microcomputer which has been programmed to play chess - and play it very well!

To play a standard game of chess, the machine is switched on and the desired level of play is entered - there are six levels, which vary the time per move from immediate response to the highest level, at which the Chess Champion Mk 1 will compute for up to two days! Once the level has been entered, the mode is keyed in. More on this later.

Play can now commence, with moves being entered in a standard notation. For example, the white king is on square E2 at the beginning of a game; if it is moved forward two spaces, the player keys in 'E', '2', 'E', '4', and then presses the 'PLAY' key.

The machine will now start computing its move, simultaneously flashing the level number. After a while it will display its move. You move its piece for it (you didn't think it was that smart, did you?), and can now make your reply.

The Chess Champion Mk 1 has provision for special moves, such as castling or taking 'en passant', through the use of a double move key. It also has a nasty habit of promoting any of its pawns that reach the last row to a queen - in fact, it doesn't miss a trick!

In Mode A, the machine sets up the board for a standard game, but in Mode B, the user can set up situations, using the 'EP' (Enter Pieces) key. This is of particular value in solving chess problems. There is also a 'Find Pieces' key, which lets the player locate all the pieces in case he suspects he has made an error (it couldn't have been the Chess Champion Mk 1).

The Chess Champion Mk 1 is a very competent chess player indeed, and will provide hours of amusement for even the most skilled chess players.

Electronics Today International has arranged for the Caldor Corporation to make the Chess Champion available to our readers for $149.95 (plus $3.95 postage, handling and insurance).

NOTE: This offer is made by the Caldor Corporation and this magazine is acting as a clearing house for orders only. Cheques should be made out to 'Chess Offer' and sent together with the order form or a copy thereof to 'Chess Offer', Electronics Today International, 15 Boundary St, Rushcutters Bay, NSW 2011.

This magazine will process the orders and send them on to the sponsor who will send out the goods by certified mail.

As a special incentive to ETI readers Caldor will refund $50 to the first twenty readers ordering these units! The full names and addresses of these readers will be made available to Electronics Today International.

SAVE $ $ $ $ $

HARMONIX

SPEAKER KITS

Simply a better sound.

PLESSEY/FOSTER COMPONENTS

Loudspeakers to satisfy the most demanding enthusiast.

Here they are — from the small HX8-2 way to the big HX15-3 way loudspeaker system. If you've ever heard from them, you'll know you've listened to the result of superb craftsmanship in the science of sound.

Model	Power	Frequency Range	Price Per Pair Kitform	Price Per Pair Assembled	Do-It-Yourself You Save Per Pair
HX8-2W	20W RMS	20 Hz-15 kHz	$166.00	$206.00	$40.00
HX10-3W	20W RMS	20 Hz-20 kHz	$225.00	$289.00	$64.00
HX12-3W	35W RMS	20 Hz-22 kHz	$267.00	$357.00	$90.00
HX12-3WA	45W RMS	20 Hz-21 kHz	$249.00	$359.00	$90.00
HX15-3W	70W RMS	18 Hz-40 kHz	$386.00	$485.00	$90.00

MAIL ORDER: NSW Country & Interstate – Freight extra.

For further technical information and your nearest dealer contact **Harmonix Acoustix** on (02) 519-5127 or write to 29 Vincent St, Marrickville. 2204.

TRADE ENQUIRIES WELCOME

DEALERS — the list grows.

- ***HARMONIX speaker kits now available from:***

• HI-FI CITY, 269 Elizabeth St, Sydney. 235-8401. • RADIO DESPATCH, 869 George St, Sydney. 211-0191. • SYDNEY HI-FI CENTRE, York St, Sydney. 29-1082 • MARTIN de LAUNAY, 289 Clarence St, Sydney. 29-5834. Also Newcastle and Wollongong. • HI-FI JUNCTION, Bondi Junction. 389-4000 • TERRY'S SOUND LOUNGE, Bowral, NSW • AUDIO EQUIP, 25 Shields Cres, Booragoon, WA. (09) 364-4736 • SOUND SPECTRUM, Darwin. • AUDIO EQUIP, Booragoon, WA. • SOUND CENTRE, Darwin, NT. • ECONOMY HI-FI, Woden, ACT.

HX15-3W

HX12-3WA

HX12-3W

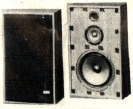

HX10-3W

HX8-2W

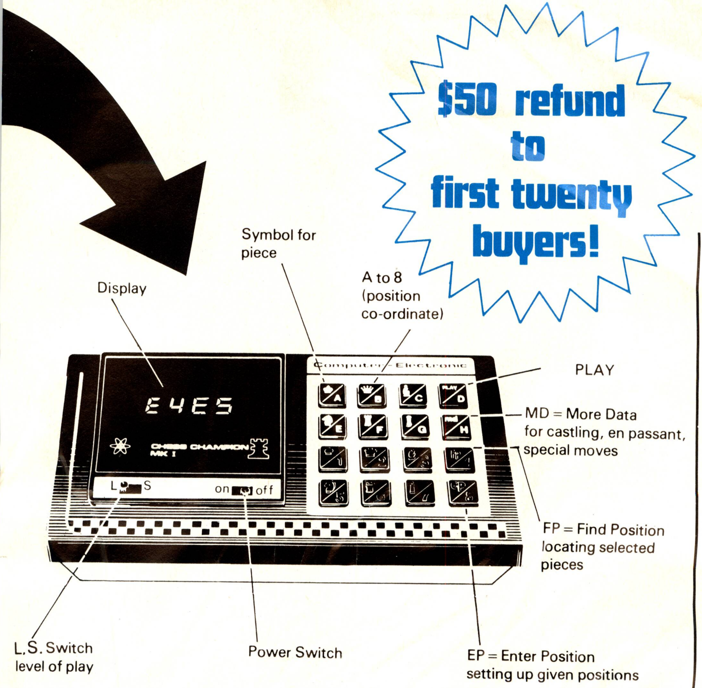
$50 refund to first twenty buyers!
Symbol for piece
Display
A to 8 (position co-ordinate)
PLAY
MD = More Data for castling, en passant, special moves
FP = Find Position locating selected pieces
L.S. Switch level of play
Power Switch
EP = Enter Position setting up given positions
E4E5
CHESS CHAMPION MK I
Computer - Electronic
L S
on off

CHESS OFFER

Electronics Today International, 15 Boundary Street, Rushcutters Bay, NSW 2011.

Please supply (quantity) . . . .

Chess Champions at $149.95 plus $3.95 post and packing — total $153.90.

Total: $ . . . .

NAME. . . . .

ADDRESS . . . .

. . . . . POSTCODE. . . . .

Please make cheques/postal notes payable to 'Chess Offer'.

SOUND

Reality?

Occasional Audio Correspondent Wally Parsons doesn't seem too troubled if he loses touch with reality.

IN ANY FIELD of endeavour based on sophisticated technology it's very easy to become so wrapped up in the technology itself as to lose sight of one's purpose, the end to which this technology is directed. This is especially true in a field such as audio which is not only in a state of rapid evolution but is also heavily consumer oriented. Thus we find hardware promoted for applications which are, at best, questionable, and at worst, quite impossible. Thus, persons may want to use graphic equalizers to correct frequency response irregularities caused by improper component mating (e.g. impedance mismatch), or simply bad design of a particular component, such as a speaker, or failure to deal with strong standing waves in the listening room.

Or perhaps we attempt to add "ambience" or equalization in a misguided effort to restore proper balance, without having the slightest idea of what the "proper" balance is. We want to obtain a reproduction which is "accurate", whatever that's supposed to mean, and faithful to the original, even though the original may never have existed; that is, the performance was created on the recording.

Now it is not my intention to knock progress. On the contrary; so many advances over the years have produced the capability of recording and broadcasting with a degree of fidelity inconceiveable not too many years ago. But much of this technology is wasted if we forget basics and lose sight of our aims. This may be why it's taken 70 years for some pressers to figure out how to put the centre hole in the centre of the record.

Listening

In these pages "Audio" is presumed to refer to those areas of sound reproduction which aim at a high level of performance quality. In establishing performance criteria attention must first be paid to the type of programme material to be reproduced most of the time.

The classical music concert goer is especially likely to be a purist. His reference standard is live music, heard with some frequency. This might give the impression of being a pretty tough act to follow, yet this is the audiophile most likely to be fooled into accepting reproduction which deviates grossly from his intended ideal. The reason is quite simple; human memory seems to be quite unreliable where sensory information is involved. If you go to a concert it's usually in the evening. Chances are you won't be operating your sound system before the next day, at least at concert hall levels. By that time your memory of last night's performance will have become less clear and unless your system has some gross obvious faults, it will sound pretty good. If the low bass is missing, your mind fills it in, or if a voice is projected a little too forward, your mind pushes it back. And then, if you can only get gallery seats and a recording was made with an up front perspective you no longer have a reasonable reference. This points to a need for considerable listening experience and helps explain the difficulty of becoming a first rate sound man at an early age.

Then too, it's so easy to be impressed by the extremely wide stage reproduced by two speakers and forget that at the live performance the stage angle was so much narrower that if you closed your eyes you really wouldn't know the exact location of the oboe and the trumpet. As for front to back depth, there really isn't much of that either.

Remember that speaker which reproduced such silky smooth string tones? Surprise: massed strings often have an edge to them which verges on the wiry. And why not; sound is produced by drawing a bow across stretched wire.

Many a great speaker has been criticized because cellos and basses have a resonant and woody quality often attributed to cabinet resonance. Well, it's resonance all right, the resonance of the belly of the instrument. Tympani really do sound hollow and a concert bass drum really is boomy. A good speaker does not reproduce its sound as a "Wump".

Production

The collector of predominantly rock music is in a different position. The technical key to set production is the multichannel recording chain, which, when used creatively, permits sonic effects which are quite impossible to produce by any other means, but which all too often makes possible the production of tracks by musically illiterate dullards who wouldn't be able to play the same tune together using conventional means. Unfortunately they are often put together by producers and engineers of similar mentality, who frequently exercise their toys on real music. With good material. engineered with taste, imagination, and good judgement, the result can often be magnificent. Obviously, the legitimate aim in reproduction is to realize the sonic image heard by the producer. In other words, to achieve what he wanted the listener to hear. The catch is, that you don't know what he wanted you to hear. So you may not be able to achieve it without duplicating the exact conditions which existed during the final mixdown. However, taste and judgement often prove to be a good guide here.

Where it becomes a little sticky is in the realm of more traditional popular music and some jazz forms in which these techniques have been used. Here we have at least the possibility of finding a live performance for comparison. With multitrack what we usually end up with is two channel monophonic sound which has been highly processed to produce an artificial stereo image. How successful these efforts are may be judged by the increasing number of equalizers, noise-reduction

"Why a frequency response of up to 40kHz when your ears can't handle 20kHz?"

In virtually all recorded music, there is little to listen to above a frequency of 16kHz, especially when you consider that few of us can hear beyond 15kHz anyway. The reason for the heightened response rate is to improve musical quality within the audible range. Music waveforms are complex, often with steeply rising and falling sides. Any vertical compression or attenuation of this waveform, as takes place in most average speakers, must cause a flattening of the wave with a consequent lack of sharpness and definition in the upper registers.

To solve this, Pioneer research arrived at the HPM-150 speaker with a frequency response ranging from a low of 25Hz to a high of 40,000 Hz. Pioneer developed the radically different supertweeter, shown opposite. In fact, it's the world's first made from high polymer film, made famous by Pioneer in their revolutionary SE-700 headphones. The three-inch cylindrical diaphragm of the supertweeter is loaded on a system of five vertical-sectoral horns for improved coupling and a horizontal dispersion of sound through 270°. With the HPM-150 you are assured of hearing all the super-highs which the human ear is capable of enjoying.

Taken all round, the HPM-150 is nothing short of remarkable. It's a four-way, four-speaker system rated at a nominal 125 watts input. Naturally, a speaker design of this sophistication needs power to perform. So it's no surprise that Pioneer advise a minimum of 50 watts per channel with a maximum input of 300 watts per channel on a continuous power basis.

A short specification
Enclosure: Bass-reflex, floor standing.
Speakers: 40 cm woofer, carbon fibre cone type.
10 cm mid-range, cone type.
4.5 cm tweeter, cone type.
7.5 cm supertweeter, high polymer film horn-loaded omni-directional.
Impedance: 6.3 ohms.
Frequency Range: 25Hz-40kHz
Input power: 125w nominal 50 to 300w recommended range.
Dimensions: 450w x 985h x 450d (mm)
Weight: 75 lb (37.3 kg)

All Pioneer speakers are covered by warranty for three years. Excellent service facilities are available throughout Australia via a network of Pioneer approved outlets.

Please mail me (Tick as required)
☐ HPM-150 Speaker Folder
☐ Folders on other components of equivalent compatibility.
☐ Other (please indicate).
....

To Pioneer Electronics
P.O. Box 295, Mordialloc,
Vic, 3195

Name ....
Address ....
.... State .... P'Code ....

PN150 HFR

PIONEER®
leads the world in sound

units, time delay devices and other signal processors commercially marketed and the demand for construction articles by readers of ETI.

An Art

I've long felt most of the art produced in any time to be worthless and generally forgotten with time. Perhaps in the area of music recording we must view software engineering from the same point of view. Like the discriminating music lover, then, we must establish clear values in our own minds as to what we are trying to accomplish, and evaluate new developments, equipment and concepts from this point of view.

I expect to get back to more specific aspects of this theme from time to time, but in the meantime, consider the virtue of the word "why".

Products And Developments

Basically there is little difference between the shape of the groove cut on the early Berliner disc and that of a modern stereo LP. Both are cut with a modified V-groove with some rounding at the bottom, and each modulation occurs on both groove walls. The only real differences have been in dimensions, included angle, and modulation angles.

Playback styli, too, have evolved from steel ploughs to precision instruments as more was learned about the dynamic relationship between stylus and groove wall. Generally, though, styli have been conically shaped with the tip ground to a spherical arc, and later an elliptical cross-section with bi-radial tip. This latter was developed mainly to improve the stylus' ability to trace high frequency modulations in the stereo groove. But even this proved inadequate to handle the very high frequencies (up to 45 kHz) involved in CD-4 recordings. Consequently other shapes were developed, most notably the complex Shibata and other types. With luck, most of the various four-channel systems will hibernate for a while, while we figure out what we really want to do with all these channels, but in the meantime some of the things learned have spun off and been applied to conventional two-channel stereo recording and play-back.

Quadrahedral

One of these was Stanton's "Quadrahedral^{TM}" stylus configuration, basically a stylus of elliptical cross-section with a very wide ratio of lateral to transverse dimension. Now, ordinarily this would result in a very small contact area and a consequently high unit contact pressure when used at any realistic tracking force. However, by forming the stylus into a hyperbolic shape, when viewed from the front, a larger area is placed in contact with the groove walls. The result is low unit pressure, and because this extended contact is along the vertical, smoother more extended high frequency response, with better tracking at high frequencies, aided by the improved groove wall contact.

In optimizing for CB-4 performance some sacrifice was made in tracking ability and transient response when playing stereo discs, with the result that Stanton's 780/4 DQ pickup lacked the presence and impact which characterized the 681 series. Even so, the new stylus shape combined with a redesigned pole structure did produce a certain smoothness and cleanness.

An outgrowth of this experience is the "Stereohedron^{TM}" stylus similar to the CD-4 unit but optimized for stereo use and available in the 681 EEE/S and the new Calibration Standard 881S. I've had the opportunity to use the EEE/S version for several months, and it seems to be an effective and worthwhile development which, if not in its present form, at least in some other variant, is likely to become as commonplace as the elliptical tip is now. So far I haven't found anything which it will not track including some pretty heavily equalized sibilants. Probably because of the different mating surface involved, recordings which showed signs of damage due to mistracking on previous plays either were cleaned up, or the noise component seemed to dissociate itself from the signal, thus reducing its obstrusiveness. The same is true of surface imperfections which appear as separate signals. The effect is something like noises which may come from an audience; one is aware of them, but they can be tuned out. Bright instruments like brasses and cymbals sound bright, yet there is no artificial effect added. Stereo imaging is wide, and solid, with a lovely but not exaggerated presence on voices and solo instruments, and a clean separation of individual voices on choral music.

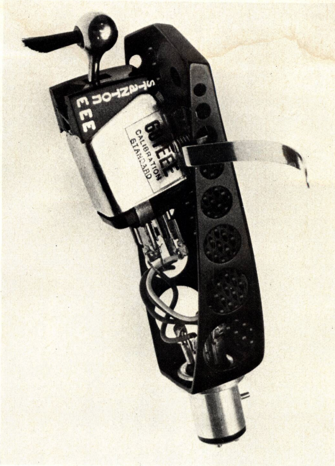

Now for the kicker. Stanton advises that the assembly be used **only** in the 681 EEE body. Well, I've got news; I'm using it in both the older 681 EE and the 780 Bodies. In the latter it performs to spec, although it requires a load of 27k and 100pF capacitance, while with the former it provided a significant up-grading in performance, and in both cases at considerably less cost than a complete 681 EEES. The different loading requirements are due to the different inductances used in each body. Now, Stanton has always designed their pickups for operation into a much lower capacitive load than most other manufacturers, using higher inductance coils to achieve reasonable output. This may account for the variable reports on performance. They tend to be a little tricky to install, and one wold be well advised to use very low capacitance cables even if it means adding lump capacitance to bring it up to the specified value.

Sansui's all-new integrated amplifiers have absolutely astounding specifications. Compare them with any others in their class, and Sansui comes out far ahead. But what really makes Sansui's new amplifiers so superior is that all these great specs have a single purpose — outstanding sound quality.

Take response speed, for example. Your amplifier doesn't move, but it does *respond*. The more rapid its response, the cleaner and the more accurate the sound. That's why the AU-717, for example, features an advanced DC power amplifier design. Sansui's DC amplifier eliminates all capacitors in the signal path and even in NFB loop so amplification is direct without coloration and phase delay. Response is astoundingly rapid — the proof is in the ultra-high (60v/μsec.) slew rate and ultra-rapid rise time (1.4μsec).

But Sansui didn't strive for such outstanding specs just to be able to print impressive figures. On the contrary, Sansui research showed that to achieve accurate reproduction and reduce signal loss, lightning-fast response was essential.

In addition, special circuits were incorporated to achieve new levels in stamping out TIM (transient inter-modulation distortion), a type of distortion that is now receiving high priority. Still another important benefit of Sansui's DC amplifier is the ultra-wide frequency response from zero (DC) to 200,000 Hz.

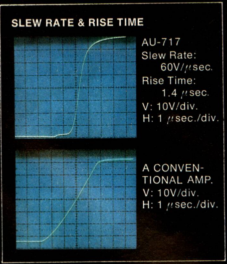

The final result is music with a purity and clarity that must be heard to be believed. All the dimensions of complex musical sounds — the wide dynamic range, the sudden pulsive signals, the nuances of barely perceptible but critical overtones in the ultra-high frequencies — all these are now crystal clear, all are proof of Sansui's new levels in superior sound quality. Impressive power is 85 RMS watts per channel, 20—20k Hz, and total harmonic distortion at rated output is 0.015%. That means it can be considered non-existent as far as the human ear is concerned.

Keep in mind that though the AU-717 is special, it's not special for Sansui. Each and every amplifier on the left-hand page embodies the same Sansui commitment to outstanding sound quality. All controls have been carefully thought out and designed for their specific purposes. Sansui has no place for gadgets and gimmicks in its dedication to the ultimate in hi-fi.

The AU-517 and AU-317 also feature the same DC power amplification as the AU-717, and offer 65 and 50 RMS watts respectively. The AU-217 and AU-117 offer 30 and 20 RMS watts respectively, but are not to be under-rated. In fact, they represent exceptional values in low distortion and true hi-fi performance.

Sansui for specs with a purpose — outstanding musical quality.

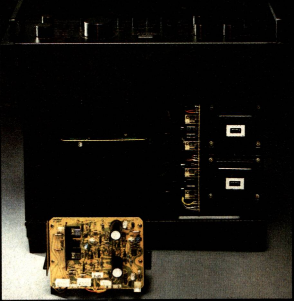

Sansui

Only hi-fi, everything hi-fi.

SANSUI ELECTRIC CO., LTD. 14-1 Izumi 2-chome, Suginami-ku, Tokyo 168, Japan
VANFI (AUST.) PTY. LTD. 162, Albert Road, South Melbourne, Victoria 3205, Australia Tel: 699 5473
Suite 5, Uniline House, 5 Northcliff Street, Milson Point, N.S.W. 2061, Australia Tel: 929 0293

Specs with a purpose!

Sansui's new amplifiers

Diagrams of stylus types.

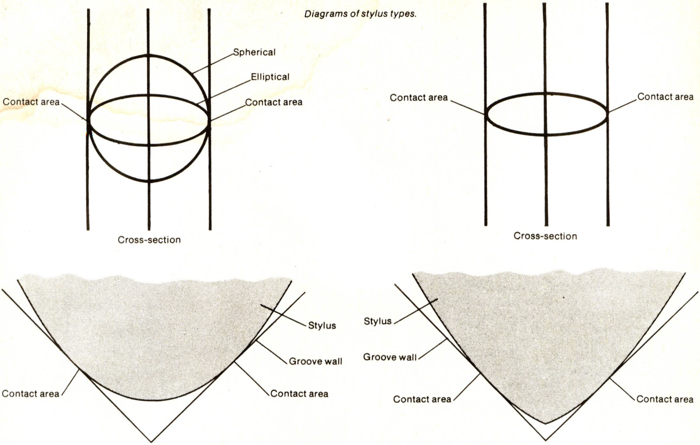

Elliptical and spherical styli.

CD-4 derived stylus (typical).

On the other hand, none of the products exhibit the excessive compliance which has become a fashionable design characteristic in recent years, so they can be used in arms of moderate mass.

Moving Magnet

The 881S represents a return to the moving magnet system, unlike Stanton's other products which use a moving iron principle. Therefore, its stylus cannot be used in the other bodies. They claim to have achieved a lower effective tip mass by using a very high energy magnet material and reducing its mass.

If you're using one of the earlier Stanton models this is a good way to upgrade. If not, but have considered using a professional pickup, the 681 EEE/S or the 881S would be worth considering. And incidentally, because of the close relationship between the companies many of the Stanton and Pickering styli and bodies are interchangeable. Thus, the Pickering 4500Q appears similar to the Stanton 780/4DQ, while XSV/3000 claims the same magnet system and stylus as the Stanton 881S. I'm not suggesting that you purposely mix and match bodies and styli, but if you already have the body, you might want to give it a new pointy head.

Shure Bros. has recently launched an advertising campaign which emphasises the point (if you'll forgive the pun) that there is a lot more to a good pickup than the stylus and its shape and other characteristics. This is one of those obvious things which most of us take for granted. After all, we no longer use thorn needles held in place by a set screw. However, it is only natural that a manufacturer should lay emphasis on some particular aspect of design which distinguishes a new product from others, and at the present time this happens to be stylus shape.

But it is equally true to say that there is more to a pickup than the pickup; there is its termination, which is also the interface with a pre-amplifier. All too often the only aspect of pickup termination considered is the load resistance. Since this has been essentially standardized for stereo pickups at 47k, it is no longer something with which we need concern ourselves. Figure 1 shows the equivalent circuit of a magnetic pickup including its load and the preamp. Coil inductance L and load capacitance (including cable, preamp and strays) constitute a resonant circuit whose Q is controlled by the internal resistance R_s and load resistance R_L (including preamp input resistance).

Complimentary Characteristics

All too often it's assumed that the recommended load capacitance for a pickup is a maximum figure, and it doesn't matter what actual value is used as long as it does not exceed this figure, and that too much capacitance will reduce high frequency response. Nothing could be further from the truth.

The moving system of any pickup has a natural resonant period which results from the effective mass of the moving system referred to the tip, and the compliance of its suspension. This produces a resonant peak which may be damped to a greater or lesser degree. This results in a particular response curve due to the mechanical system. In order to achieve a flat response to a constant velocity, the electrical circuit must have a response which is complementary, and this response is shaped by the circuit elements shown in Fig. 1. In order to achieve specified performance then, we *must* provide the specified loading conditions.

Nothing Is Ever Simple

Since R_L includes the preamp's in-out resistance, including it in the calculations of fixed resistance is simple, provided either that Rin is very high, or is a constant value. But this is seldom the case, especially when feedback is applied to the input stage, and is further complicated when equalization is incorporated in the feedback loop. Feedback alters the amplifier input impedance, and a feedback equalizer introduces a feedback factor which is frequency dependent, therefore, the input impedance is frequency dependent. It is important therefore that the preamp be designed in such a way as to ensure that its input impedance makes a negligible contribution to the pickup load. With commercially built equipment we rarely have any control over these characteristics, and in any case manufacturers seldom supply such information.

Is it any wonder then that a pickup may deliver outstanding performance with one preamp and prove quite disappointing with another of similar, or even better quality? It's worth noting that moving coil pickups when matched to a pre-preamp are less subject to these conditions, and the pre-preamp's output being resistive is affected less by the preamp-equalizer's input characteristics, as compared to other magnetic types, and this may be a major factor in the audibly superior quality of such units. It also goes a long way toward explaining the fact that many radio stations achieve excellent sound considering that pickups used are chosen with ruggedness in mind and frequently will deliver unacceptable performance in a home system.

Fig. 2. Impedance vs. frequency plot of source viewed by preamp.

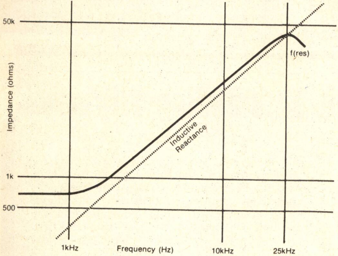

Looking From The Other Direction

The circuit shown in fig. 1 provides the source impedance for the preamp, and this impedance may look something like fig. 2. This is quite a bit different from the simple resistance often assumed when designing a preamp. Since most preamps in use today use series summing the feedback factor is modified by this impedance characteristic, and equalization accuracy is impaired. In addition, a complex and often unpredictable phase characteristic is introduced to affect the stability margin.

One solution is to use a differential input, but this is a noisier configuration. However, since the final noise figure is influenced by the source impedance this may not always be a problem. In other words, the noise figure which results from the variable source impedance may be sufficiently higher than the theoretical minimum that in reality we end up with the same noise figure no matter which circuit is used.

Another solution for use with preamps which already exist is the addition of series resistance to the input (figure 3a), although one would at first expect this to increase noise level, the more nearly constant source impedance allows input stage current to be optimized for the series resistance itself, with the additional benefit of allowing a better match to a wider variety of pickups. It can also be helpful in reducing rf pick-up, especially if circuit layout permits insertion directly at the base lead of the input stage. It also means that pickup load capacitance can be provided exclusively by the connecting cables and fixed capacitors. A suitable value for this resistance would be around 15k for most pickups, and should, if possible, be connected after the 47k load resistor, otherwise an additional load of 200k will be required, as in fig. 3c.

If a pickup-preamp combination does not perform as well as the quality of each component suggests it should, there is a good chance of the kind of hidden mismatch which many people seem to think is mysterious. It isn't really, it's just a matter of looking at all the facts, and considering the interaction of all circuit elements.

Fig. 3a. Preferred method of "swamping" cartridge inductance by adding series resistance Rs.

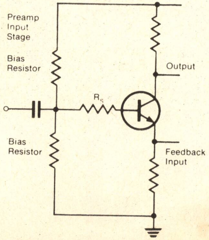

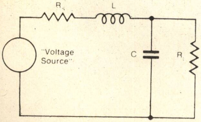

Fig. 1. Equivalent circuit of a magnetic pick up including load and preamp.

Fig. 3b,c. Two alternatives modifications to existing preamp input stages depending on bias resistor arrangement.

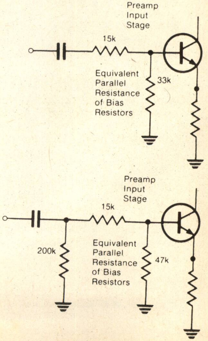
Preamp Input Stage
15k
Equivalent Parallel Resistance of Bias Resistors
33k
Preamp Input Stage
15k
200k
Equivalent Parallel Resistance of Bias Resistors
47k

THE BEST OF BRITISH!

NEW! G900 SUPER E MARK 2

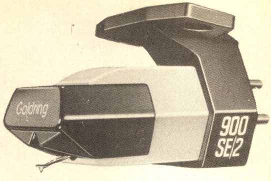

- Total weight only 4 grams.
- Genuine tracking weight 1 gram.
- New construction process (patent applied for) achieves lower inductance, resulting in even lower mass and flatter frequency response.
- Improved clearance between record and cartridge body, enabling even the most severely warped records to be played.
- Micro nickel tie bar welded to magnets acts as earth path and as movement control for the system.
- Specially shaped Butyl polymer pad provides optimised damping.
- Micro miniture magnet and ultra thin walled hard aluminium alloy tube fitted with elliptical, naked diamond point result in low intermodulation distortion with excellent tracking at both higher and lower frequencies.
- Every G900 SE Mk 2 is tested to exacting tolerances.

FOR TECHNICAL EXCELLENCE IN HI-FI PICK-UP CARTRIDGES AND REPLACEMENT STYLI LOOK FOR

BRITISH MADE **Goldring** ENGLAND

Australian Distributors for Goldring Products Ltd., U.K.

SOUNDRING DISTRIBUTORS

1/514 Miller St., Cammeray, 2062.
Tel. (02) 92-1990

AGENTS:

VIC: Jasper Coote Pty. Ltd., 304 Coventry St., Sth. Melbourne, 3205. Tel. (03) 699-4455
ACT: Jason Enterprises, 47 Wollongong St., Fyhwick, 2609. Tel. (063) 80-6519
QLD: Sound Accessories, 22 Dunbil Ave., Ferney Hills, 4055. Tel. (07) 351-4737 — Green Brothers (Wholesale) Pty. Ltd., 83 West St., Rockhampton. Tel. 27-3047: 467 Flinders St., Townsville. Tel. 72-1544

Special Offer on Two Outstanding Kits

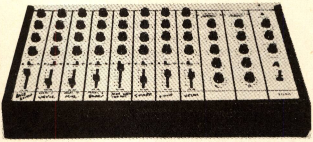

414 8-CHANNEL MIXER

With our special offer you will have 200 watts of power and an 8-channel mixer for P.A. or disco systems.

Complete kit of 414 master mixer only **$220.80** tax free
P&P $6.00 **$254.00** tax paid

Complete kit of 480 slave amplifier only **$91.30** tax free
P&P $4.00 **$105.00** tax paid

Special offer for December only:
One 414 kit and two 480 kits only **$374.00** tax free
P&P $12.00 **$430.00** tax paid

For December only we are offering a substantial saving on the purchase of two of our top selling kits for 1978. The 414 Mixer offers 8 input channels with tone controls and echo sound, stereo output with 5 stage equalisation and meters. The 480 is a compact 100 Watt Slave Amplifier ideal for use with the Master Mixer.

480 100-WATT SLAVE AMP

jaycar PTY LTD

P.O. Box K39, Haymarket, NSW. 2000.
405 Sussex Street, Sydney.
Tel: 211-5077.

Two New Technics Turntables

Two new high-performance elegantly styled, Technics belt-drive turntables have just been released in Australia by National Panasonic. They are the Model SL-220 semi-automatic and the Model SL-230 fully automatic types.

Both feature a recently-developed new-type **frequency generator servo-controlled DC motor** and advanced IC circuitry, which put them in a performance class approximating to top-quality direct drive models.

New Lathe Driver

Matsushita, working in conjunction with Teichiku Records Co, in Japan have developed a **new drive system for disc cutting lathes.** The system is said to reduce unevenness in the disc revolution to one eighth of present systems using a special kind of motor with a strong turning force and highly sophisticated electronic control of the speed. The system will be marketed world-wide by Matsushita.

PCM Standards

Several manufacturers have developed working **pulse code modulated record players** and records but none has been actually put into production due to lack of an agreed industry standard.

Present systems **vary in record size and playing speeds, recording methods, pick-up devices etc.** Hitachi, Mitsubishi, TEAC and Sony for instance use laser pick-up devices but Matsushita's recently exhibited device uses a mechanical arm.

Now though, a multinational digital audio disc council has been set up to try to formulate industry standards.

The first meeting was attended by representatives from RCA, MCA, Discovision, Thompson CSF, Philips, Victor, Sony, Sanyo, Toshiba, Matsushita, Pioneer, Hitachi, Mitsubishi, TEAC, Sharp, Atwa, Akai, Onkyo, Trio, Nippon, NEC ect etc.

Audio Adaptor For VCRs

An interesting highlight at the recent Tokyo audio fair was Sanyo's pulse code modulation audio adaptor which enables all types of video tape recorders (including Beta and VHS-format units) **to be used as super-fidelity audio systems** . . . A generally similar unit is currently available from Sony but is not compatible with VHS systems.

Sanyo's unit is still in prototype form but nevertheless Sanyo apparently intend to present it at the forthcoming Tokyo Audio Society Research Committee with the aim of having it accepted as **an industry standard**.

45 rpm Linn – official

Linn Sondek have at last accepted that some records do go round and round at 45 rpm and that owners of them would like to play them on their Linn's. Whilst the company still apparently claims that 45 rpm records are inherently inferior to 33s they've **bowed to the inevitable** and have produced a machined pulley sleeve adaptor. Involves removing the platter however. It's not quite as simple to use as Audiolab's two-speed frequency convertor (see this section ETI January 1978) but should be a **lot cheaper**.

Sound Cancellation

Many attempts have been made to produce 'anti-noise' – that is, audio signals 180° **out of phase with unwanted sounds**, such that they are substantially cancelled.

A research team at Britain's Chelsea College has been investigating the technique for some time using mock-ups of that traditional trouble maker, the noisy ventilator duct.

In simple form a microphone samples fan noise, this noise signal is then delayed sufficiently to phase invert it and then fed to a loudspeaker close to the open end of the duct. This **works to a point**, but standing waves set up in the duct cause the microphone to receive a cyclic signal thus reducing overall effectiveness.

A more advanced system is currently being experimented with – this involves a second speaker placed part way along the duct. This second speaker is fed with sound which is 180° out of phase with the total sound travelling down the duct. The result is an area of standing waves between the two speakers but **very little noise from the end of the vent.** Actual figure quoted are an average reduction of 16 dB over the range 30 Hz to 700 Hz and peak reductions of 20 – 25 dB.

FHONE

PROFESSIONAL AUDIO EQUIPMENT

FHONE MONO/STEREO GRAPHIC EQUALIZER

THE NEW 'FHONE' 20 ELEMENT ½ OCTAVE EQUALIZER (25Hz to 19.2KHz) IS A SOPHISTICATED ELECTRONIC UNIT, DEVELOPED AFTER INTENSIVE RESEARCH INTO TODAY'S PROFESSIONAL REQUIREMENTS, DESIGNED TO PLAY AN INTEGRAL PART IN RECORDING STUDIOS, SOUND REINFORCEMENT AND HI-FI EQUIPMENT.

- BALANCED AND/OR UNBALANCED INPUT/OUTPUTS.
- 14dB CUT AND BOOST (±1dB).
- CONVENIENT CENTRE STOP SLIDE CONTROLS.
- SIGNAL TO NOISE BETTER THAN -80dBA.
- OUTPUT LEVEL +18dBm. (MAX.)
- OPTICAL LED VU DISPLAY.
- 19" RACK MOUNT.
- OPTIONAL WOOD GRAIN CABINET FOR HI-FI USE.
- CHOICE OF SILVER OR BLACK BRUSHED FACE FINISH.

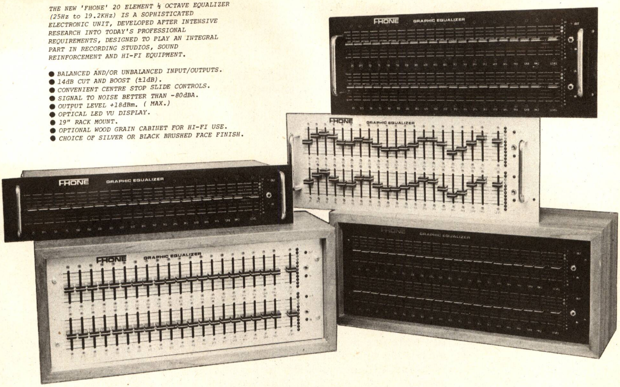

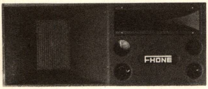

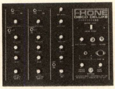

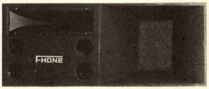

FHONE DELUXE DISCO

DESIGNED FOR RELIABILITY, APPEARANCE AND GUTSY PERFORMANCE, WITH UNIQUE ACOUSTIC FEEDBACK ELIMINATING CHARACTERISTICS.

- 250W RMS POWER AMPLIFIER.
- 2 x 3 WAY EXTENDED 45/60 VERTICAL OR HORIZONTAL SPEAKER UNITS, EACH CONTAINING 1 x 15" RCF SPEAKER, 1 x 100W 90° HORN, 2 x HIGH FREQUENCY RADIATORS.
- 3 WAY INTERNAL MUSIC MODULATED LIGHT SHOW.
- OUTLETS FOR EXTERNAL LIGHT SHOW (600W PER CHANNEL).
- RAP AROUND CONSOLE.
- 3 CHANNEL AUDIO MIXER - CHANNEL A, CHANNEL B, MICROPHONE.
- INPUT FOR AUX. SOURCE. e.g. TAPE DECK, CUEABLE ON CHANNEL A OR B.
- LED VU DISPLAY ON MIXER OUTPUT.
- HEADPHONE CUE PROVISIONS.
- 2 x 4W RMS HEADPHONE CUE AMPLIFIER.
- CROSS FADE SLIDE CONTROL.
- CROSS FADE BYPASS SWITCHES.
- FITTED WITH SHURE M55E MAGNETIC CARTRIDGES.
- HEAVY DUTY BLACK VINYL DESK TOP.

(4 WAY ELECTRONICALLY CROSSED UNITS ALSO AVAILABLE)

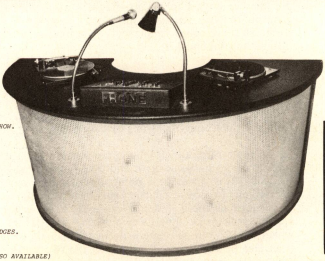

FOR FURTHER INFORMATION CONTACT :

FHONE AUDIO Pty. Ltd.
20 MAIN St. UPWEY Vic. 3158
03 754 2572   03 754 6268

AGENT :

ZEPHYR PRODUCTS
70 BATESFORD Rd. CHADSTONE
Vic. 3148
03 568 2922

BRAINS AND COMPUTERS

Man is just a machine, or is he? Is his brain the ultimate mechanism or could it be improved by bio-engineering techniques? How can we develop artificial intelligence to match the abilities our own brains and what do we have to learn from it? By S. McClelland.

EVEN IF THE HUMAN BRAIN is regarded as being a digital computer it must be considered to be far more complex than anything man can devise — or is likely to devise in the foreseeable future. In a volume of tissue far less than that of a football it packs some 10^{10} (that's 10 000 000 000) active elements, the nerve cells. In computer terms, its capacity to store information must run onto the 10 thousand megabit range *at least*.

Its organisation matches its abilities -- on average in a normal human being it's been estimated that 1 nerve cell dies every 10 seconds throughout our lives. It is never replaced, for brain cells alone in the body cannot reproduce, and yet we never notice the loss since the brain is so well organised that many of its circuits are redundant and can be replaced by alternative channels should they fail -- this has been the case even after serious injuries have been inflicted on the brain.

How much power does all this require? It's enough to make an engineer cringe — a meagre few watts!

What about the brain's higher capabilities — such as its capacity for inventiveness or 'original' thought? What was special about Mozart's brain circuits that enabled him to start composing music before he was 5 years old, or in Leonardo da Vinci's case, to design flying machines 500 years ahead of his time?

Sadly as yet we have no idea since so little is known about the brain!

Inputs and Outputs

All this uncertainty has not stopped a growing number of systems engineers and scientists from looking at the brain's organisation and operation (possibly with the idea of wanting to copy techniques in future systems!).

We can certainly find some aspects of central nervous system operation in common with computers. Both systems have of course what might be loosely termed 'input' and 'output' peripherals, for example. In the case of the brain the inputs are from the senses of the body, not only the primary ones of sight, hearing, smell and taste but also from many thousand of receptors near the surface of the body for various parameters such as temperatures and pressure.

Its outputs go to activate all the muscles in the body. This flow of information demands an enormous number of nerve fibres to convey it — up to a million nerve fibres are estimated to be associated with each major limb alone.

All of this of course prompts the question: "How does this information transfer take place?" To understand this we have to look at the most basic component of the whole system — the nerve cell itself.

Neurons

If we could remove a typical nerve cell from our bodies and look at it under a high power microscope, it would look something like Fig 1. Remember, this cell is probably only a few micrometres in diameter so what we're about to describe is a microscopic system-within-a-system.

The cell picks up signals from the other cells in its vicinity and these are fed down to the main part of the cell (containing the nucleus) and propogated along the long transmitter branch (axon) to the next cell.

It's along the inside of these long membranous branches that the electric impulses (or action potentials) are transmitted by the nerve.

The axon is no mere passive wire, however. If it was, the signals would soon be drastically attenuated by the leakage of the membrane to the outside after a very short travel. The cell membrane instead acts as its own signal booster to maintain the impulse at constant amplitude (about 100 mV) at any point on the axon. The action potential is either there or it isn't — there is no in-between state. A digital system? Perhaps. In fact, it's the frequency at which the action potentials are signalled that carries the information. We can now see why so many nerve fibres are needed to carry information. Each cell — and probably many others for the

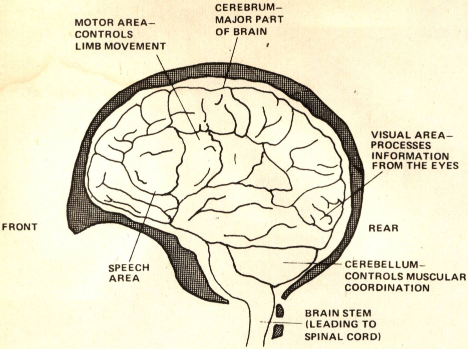
CEREBRUM– MAJOR PART OF BRAIN
MOTOR AREA– CONTROLS LIMB MOVEMENT
VISUAL AREA– PROCESSES INFORMATION FROM THE EYES
FRONT
REAR
SPEECH AREA
CEREBELLUM– CONTROLS MUSCULAR COORDINATION
BRAIN STEM (LEADING TO SPINAL CORD)

sake of redundancy – carries one 'bit' of information. The importance of this information depends on the frequency it is being signalled and it is likely that a high frequency signal establishes a higher priority than a lower frequency signal a particular context – rather like signalling an 'interrupt' in a computer system.

Simple as it is, a frequency-dependent system carries its own problems. The sense organs must make amplitude-to-frequency code conversions for transmission down the fibre and at the other end, the brain must find a way of coping with a frequency-dependent signal.

A secondary point is that all the nerve cells concerned with a particular function or sub-function work in parallel. The advantages of parallel processing are fairly evident. It's faster than serial and has a higher signal-to-noise ratio (even if it does need more channels).

So we can visualise action potentials – small spikes of voltage – being flicked up and down all the nerve fibres in the body at varying frequency, but not nearly as fast as electrical impulses through cables. However, even in this, nature squeezes all the performance it can out of the human nervous system. Each nerve cell is wrapped in several layers of fatty tissue with 'nicks' or 'breaks' in the fat at intervals along the axon. The effect of these 'breaks' or 'nodes of Ranvier' as they are known is to increase the speed of transmission of the action potentials down the nerve axon to about 100 metres per second.

Delaying Tactics and Logic Gates

If neurons propagate the action potentials, then it is the junctions between neurons (synapses) that route them. It's the synapses which work out if the incoming signals are of the right type and frequency to trigger the following cell to produce an action potential. From the point of view of the system, the synapses are the delay lines, one-way valves, triggers and gates all rolled into one.

It takes an electron microscope to even *see* the synapse regions and even then they don't look very special – they're merely bulbous terminations where nerve cells meet each other. Except that they don't meet each other – they're always separated by the absolutely microscopic distance of about 200 A – so tha action potential never gets across even the gap, let alone down the other side.

What actually crosses the gap is not the electric signal itself but a very small quantity of hormone which is released from the transmitter bulb. The hormone crosses to the receptor membrane where (by a process that's not fully understood) it causes the generation of another action potential. Even across so small a gap the chemical transmission takes a finite time and is susceptible to interference by foreign chemicals (drug addicts please note – your synapse may be switched off!).

Some synapses, instead of generating an action potential in the receptor membrane actually inhibit it from doing so – so we've found the on-off switches for the nervous system. Can we identify Boolean logic, gating arrangements in the nervous system? It's possible to speculate in thos terms and certainly the basic mechanisms seem to be there, but unfortunately not enough is known about even simple neuron groups to permit an answer to this question.

Don't Believe Your Eyes!

The nervous system can do some very sophisticated things to the input signals it receives by way of data processing. It can, for example, selectivity inhibit the triggering of neurons that carry no useful information in favour of ones that do.

This so-called 'lateral inhibition' not only cleans up potentially noisy channels by making them more 'contrasty' but in some animals is known to help the eye resolve very efficiently the boundaries between dark and light edges in an image. It probably occurs in the human nervous system as well where it is thought to give rise to some of the more common optical illusions as a by-product.

So much processing sophistication backing up the senses means that the brain can work on far less sensory information than it usually gets. For example, the brain really only requires a few per cent of the data it receives from the eyes in order to form a valid judgement as to the nature of the image. The same applies to the ear – speech has to be very badly distorted before the brain cannot recognise it. There is obviously a very close and complex interaction between the senses and the memory, which is continually generating possible 'best-fit' models to match the latest information received. Each model is discarded until the brain is satisfied with the result.

Our senses show a fantastic sensitivity to the world around us – we *can* hear a pin drop in a quiet room. More staggering still, the vibration amplitude of the ear drum which the miminum audible sound creates is *less than the diameter of one hydrogen atom . . .!*

Down Memory Lane

Digital computers have clearly-defined memory locations which are usually addressed under the control of a clocked pointer in the system. The human brain on the other hand seems to have no all-powerful organ of memory – attempts to find one have so far proved inconclusive. Rather, memory is a property of the system as a whole.

Secondly, data storage on a computer tape or disc is permanent until deliberately erased but information flow through the brain is far more dynamic and its retention more selective. Information floods into our brains from our senses at every living moment. Seen in this light it is neither desirable nor even possible to store it all. 'Store only the information that is important' the brain says to itself — but what is counted as being important?

Basically, we pick out the information about the *changes* in our environment, because it's the changes in it which may be threatening our immediate survival.

On a motivated level, we can store items deliberately. We remember by repetition (e.g. a telephone number). Most importantly we store information which is associated with something which has caused us great pain or pleasure in the past. How do we recall information once stored? It's clear that association plays a critical role. After all, we store not isolated events but connected ones — 'trains of thought' if you like. The memories are recalled when the right key of stimulus is provided. This stimulus may well be a piece of information associated with the group.

For example, the question "What do you remember about November 22nd 1963?" would probably elicit a blank reply from most people until (as various commentators have pointed out) they are told it is the day when President John F. Kennedy was assassinated. Many people can recall where they were or what they were doing — it's a memory that persists over 14 years because it is associated with such a traumatic incident.

In this way we can visualise the human memory almost as 'conglomerates' of memories — pieces of information tied together in some fashion only requiring the right input trigger to push it all out.

Some very intriguing hypotheses about how the memory operates have been suggested. One exciting and topical suggestion is that it records information as a hologram records 3-D images in laser light. A particular part of the image is not localised to a particular part of the hologram — in fact even a fragment of the hologram can theoretically recreate the entire image, a property which makes it very similar to the brain.

We must wait for more basic information on the brain to confirm or disprove this.

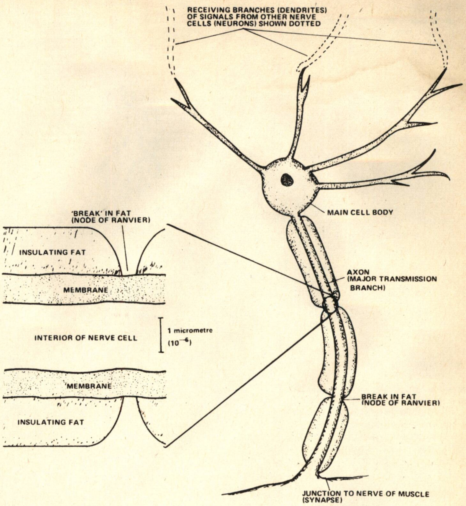
RECEIVING BRANCHES (DENDRITES) OF SIGNALS FROM OTHER NERVE CELLS (NEURONS) SHOWN DOTTED
MAIN CELL BODY
'BREAK' IN FAT (NODE OF RANVIER)
INSULATING FAT
MEMBRANE
INTERIOR OF NERVE CELL
1 micrometre (10^{-6})
MEMBRANE
INSULATING FAT
AXON (MAJOR TRANSMISSION BRANCH)
BREAK IN FAT (NODE OF RANVIER)
JUNCTION TO NERVE OF MUSCLE (SYNAPSE)

Tuning into Brain Waves

We can get some idea of what all this electrical activity is like by strapping electrodes — connected to a sensitive amplifier and chart recorder — to the skull.

We will obtain a rather confusing output of signals — referred to as an *electroencephalogram* or EEG. The EEG is usually a very weak signal — a few tens of uV amplitude at a range of frequency components are present.

The most well-known component of the EEG is the o-wave. Present in about 90% of all individuals, this signal (with a frequency between 8 Hz and 13 Hz) is at its most active when the subject is relaxed and his eyes closed. It disappears as soon as the subject opens his eyes or starts to concentrate on something like mental arithmetic.

What does it mean? Basically, we don't know. Nor do we know where or how it's generated, although its source (there may be more than one) *seems* to be located to the upper rear of the brain. Correspondingly little is known about the other EEG components.

Although the EEG doesn't give a great deal of information about the working of the brain (indeed we'll probably have to wait until further studies of the brain explain the EEG!), it has found great use in diagnosis of brain disorders such as epilepsy. But could the EEG have a more fundamental significance than that? My own pure piece of speculation — for what it's worth — it that it's the brain's clock, although it's too low in frequency to cope with many of the fast muscular actions of the body. Even so the 'ticking' of a brain might have a biological significance similar to a digital system's 'clock frequency'!

ETI
318
JULY '78

DIGITAL TACHO

SM ELECTRONICS
MELBOURNE

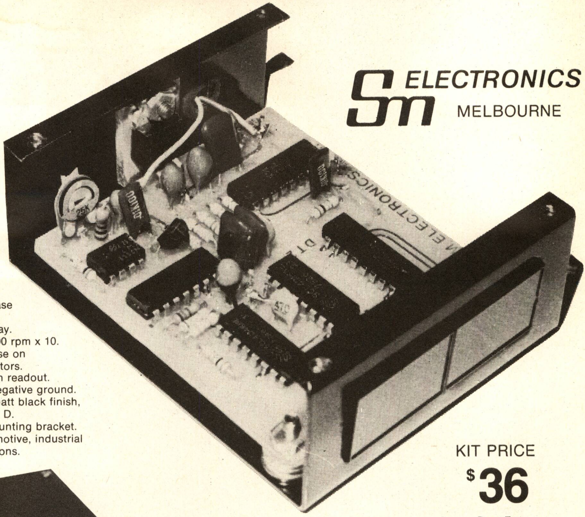

- Pre-punched steel case included in kit.
- 4 digit ½'' high display.
- Max reading — 10,000 rpm x 10.
- Link selectable for use on 4, 6 or 8 cylinder motors.
- 0.3 second update on readout.
- For use on 12 volt negative ground.
- *Cases supplied in matt black finish, 1¼'' H x 3'' W x 3¾'' D.
- *Universal swivel mounting bracket.
- Suitable for all automotive, industrial and marine applications.

KIT PRICE
$36
Post Free

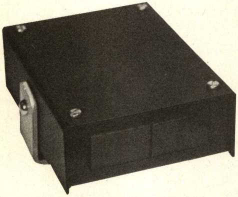

Assembled Price $48 Post Free

*Note: Painted case and mounting bracket supplied with assembled version only. When ordering please specify no. of cylinders, 4, 6 or 8. Designed and manufactured in Australia. Currently available ex stock.

S.M. ELECTRONICS
10 Stafford Crt, Doncaster East.
Box 19, Doncaster East, Vic. 3109.

(03) 842-3950

To: S.M. ELECTRONICS, (Please print)
Box 19, Doncaster East, Vic. 3109.

Please forward ☐ ETI 318 Tacho Kit(s) at $36.00 ea;
☐ Assembled Digital Tacho(s) at $48.00 ea. post free

I enclose cheque/postal order for total $............................
Please make cheques etc payable to S.M. ELECTRONICS

NAME ....

ADDRESS..

....Postcode ....

For assembled units, state no. of cylinders the Tacho is to be used on and we shall calibrate to suit.

No. of Cyl.	Kit.	Assemb.

Now. Two 3-way 40 watt speakers with nine tonal choices

Save about $50 per hour while you assemble them

Even if you didn't know them by number, you probably heard about the Philips AD12K12 MK11 Speaker Kits.

Because they are now a no.1 best-seller.

And here is the compact AD8K30, 8" 3-way compact system, with fine electronic and acoustic components (1" domed tweeters, 5" mid-range, super 8" bass drivers). Brilliant clean sound, with a frequency response closely following the ideal Bruel & Kjaer curve for hi-fi equipment measured in an actual listening room, using the "Third Octave Pink Noise Method".

Plus 9 combination tonal choices to adjust to the acoustics of your own listening-room.

You can assemble the AD8K30's in about two hours. You will get a professional result and save about $100 per pair over a comparable system.
Phone or send coupon now for full details of this and all our kits.

PHILIPS ELECTRONIC COMPONENTS AND MATERIALS
Sydney 427 0888 • Melbourne 699 0300 • Brisbane 277 3332
• Adelaide 45 0211 • Perth 65 4199

ELCOMA
Philips Electronic Components and Materials
P.O. Box 50, Lane Cove, NSW 2066

Please send me full details and brochures on your loud speaker kits and a list of retailers who stock them.

NAME ____________________

ADDRESS ____________________

____________________ STATE ________ P/CODE ________

ETA

Electronic Components and Materials

PHILIPS

BA.EL.3

DIODES/ZENERS

1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N4733	5.1v	1 W Zener	.25
1N753A	6.2v	500 mW Zener	.25
1N758A	10v	"	.25
1N759A	12v	"	.25
1N5243	13v	"	.25
1N5244B	14v	"	.25
1N5245B	15v	"	.25

SOCKETS/BRIDGES

8-pin	pcb	.20	ww	.35
14-pin	pcb	.20	ww	.40
16-pin	pcb	.20	ww	.40
18-pin	pcb	.25	ww	.75
22-pin	pcb	.35	ww	.95
24-pin	pcb	.35	ww	.95
28-pin	pcb	.45	ww	1.25
40-pin	pcb	.50	ww	1.25

Molex pins	.01	To-3 Sockets	.25
2 Amp Bridge		100-prv	.95
25 Amp Bridge		200-prv	1.95

TRANSISTORS, LEDS, etc.

2N2222	NPN (2N2222 Plastic .10)	.15
2N2907	PNP	.15
2N3906	PNP (Plastic - Unmarked)	.10
2N3904	NPN (Plastic - Unmarked)	.10
2N3054	NPN	.35
2N3055	NPN 15A 60v	.50
T1P125	PNP Darlington	.35
LED Green, Red, Clear, Yellow		.15
D.L.747	7 seg 5/8" High com-anode	1.95
MAN72	7 seg com-anode (Red)	1.25
MAN3610	7 seg com-anode (Orange)	1.25
MAN82A	7 seg com-anode (Yellow)	1.25
MAN74A	7 seg com-cathode (Red)	1.50
FND359	7 seg com-cathode (Red)	1.25

C MOS

4000	.15
4001	.15
4002	.20
4004	3.95
4006	.95
4007	.20
4008	.75
4009	.35
4010	.35
4011	.20
4012	.20
4013	.40
4014	.75
4015	.75
4016	.35
4017	.75
4018	.75
4019	.35
4020	.85
4021	.75
4022	.75
4023	.20
4024	.75
4025	.20
4026	1.95
4027	.35
4028	.75
4030	.35
4033	1.50
4034	2.45
4035	.75
4040	.75
4041	.69
4042	.65
4043	.50
4044	.65
4046	1.25
4049	.45
4050	.45
4066	.55
4069/74C04	.25
4071	.25
4081	.30
4082	.30
MC 14409	14.50
MC 14419	4.85
4511	.95
74C151	1.90

– T T L –

7400	.10
7401	.15
7402	.15
7403	.15
7404	.10
7405	.25
7406	.25
7407	.55
7408	.15
7409	.15
7410	.15
7411	.25
7412	.25
7413	.25
7414	.75
7416	.25
7417	.40
7420	.15
7426	.25
7427	.25
7430	.15
7432	.20
7437	.20
7438	.20
7440	.20
7441	1.15
7442	.45
7443	.45
7444	.45
7445	.65
7446	.70
7447	.70
7448	.50
7450	.25
7451	.25
7453	.20
7454	.25
7460	.40
7470	.45
7472	.40
7473	.25
7474	.30
7475	.35
7476	.40
7480	.55
7481	.75
7483	.75
7485	.55
7486	.25
7489	1.05
7490	.45
7491	.70
7492	.45
7493	.35
7494	.75
7495	.60
7496	.80
74100	1.15
74107	.25
74121	.35
74122	.55
74123	.35
74125	.45
74126	.35
74132	.75
74141	.90
74150	.85
74151	.65
74153	.75
74154	.95
74156	.70
74157	.65
74161	.55
74163	.85
74164	.60
74165	1.10
74166	1.25
74175	.80
74176	.85
74180	.55
74181	2.25
74182	.75
74190	1.25
74191	.95
74192	.75
74193	.85
74194	.95
74195	.95
74196	.95
74197	.95
74198	1.45
74221	1.00
74367	.75
75108A	.35
75491	.50
75492	.50
74H00	.15
74H01	.20
74H04	.20
74H05	.20
74H08	.35
74H10	.35
74H11	.25
74H15	.45
74H20	.25
74H21	.25
74H22	.40
74H30	.20
74H40	.25
74H50	.25
74H51	.25
74H52	.15
74H53J	.25
74H55	.20
74H72	.35
74H101	.75
74H103	.55
74H106	.95
74L00	.25
74L02	.20
74L03	.25
74L04	.30
74L10	.20
74L20	.35
74L30	.45
74L47	1.95
74L51	.45
74L55	.65
74L72	.45
74L73	.40
74L74	.45
74L75	.55
74L93	.55
74L123	.85
74S00	.35
74S02	.35
74S03	.25
74S04	.25
74S05	.35
74S08	.35
74S10	.35
74S11	.35
74S20	.25
74S40	.20
74S50	.20
74S51	.25
74S64	.15
74S74	.35
74S112	.60
74S114	.65
74S133	.40
74S140	.55
74S151	.30
74S153	.35
74S157	.75
74S158	.30
74S194	1.05
74S257 (8123)	1.05
74LS00	.20
74LS01	.20
74LS02	.20
74LS04	.20
74LS05	.25
74LS08	.25
74LS09	.25
74LS10	.25
74LS11	.25
74LS20	.20
74LS21	.25
74LS22	.25
74LS32	.25
74LS37	.25
74LS38	.35
74LS40	.30
74LS42	.65
74LS51	.35
74LS74	.35
74LS86	.35
74LS90	.55
74LS93	.55
74LS107	.40
74LS123	1.00
74LS151	.75
74LS153	.75
74LS157	.75
74LS164	1.00
74LS193	.95
74LS367	.75
74LS368	.65

LINEARS, REGULATORS, etc.

MCT2	.95
8038	3.95
LM201	.75
LM301	.45
LM308 (Mini)	.95
LM309H	.65
LM309K (340K-5)	.85
LM310	.85
LM311D (Mini)	.75
LM318 (Mini)	1.75
LM320K5 (7905)	1.65
LM320K12	1.65
LM320T5	1.65
LM320T12	1.65
LM320T15	1.65
LM324N	1.25
LM339	.75
7805 (340T5)	.95
LM340T12	.95
LM340T15	.95
LM340T18	.95
LM340T24	.95
LM340K12	1.25
LM340K15	1.25
LM340K18	1.25
LM340K24	1.25
78L05	.75
78L12	.75
78L15	.75
78M05	.75
LM373	2.95
LM380 (8-14 PIN)	.95
LM709 (8, 14 PIN)	.25
LM711	.45
LM723	.40
LM725N	2.50
LM739	1.50
LM741 (8-14)	.25
LM747	1.10
LM1307	1.25
LM1458	.65
LM3900	.50
LM75451	.65
NE555	.35
NE556	.85
NE565	.95
NE566	1.25
NE567	.95

9000 SERIES

9301	.85	95H03	1.10
9309	.35	9601	.20
9322	.65	9602	.45

MICRO'S, RAMS, CPU'S, E-PROMS

74S188	3.00
1702A	4.50
MM5314	3.00
MM5316	3.50
2102-1	1.45
2102L-1	1.75
2114	9.50
TR1602B	3.95
TMS 4044-	9.95
8080	8.95
8212	2.95
8214	8.95
8224	3.25
8228	6.00
8251	8.50
8255	10.50
8T13	1.50
8T23	1.50
8T24	2.00
8T97	1.00
2107B-4	4.95
2708	9.50
Z80 PIO	8.50

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd., San Diego, CA 92111 U.S.A.

No Minimum

All prices in U.S. dollars. Please add postage to cover method of shipping. Orders over $100 (U.S.) will be shipped air no charge. Payment should be submitted with order in U.S. dollars. All IC's Prime/Guaranteed. All orders shipped same day received.

SPECIAL DISCOUNTS

Total Order	Deduct
$35 - $99	10%
$100 - $300	15%
$301 - $1000	20%

Phone (714) 278-4394

BarclayCard / Access / American Express / BankAmericard / Visa / MasterCharge

PRINTOUT

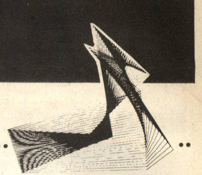

ETI's COMPUTER SECTION

NEWS

16K 2716 PROM Card

This versatile memory card from Pennywise Peripherals provides 16K of 2716 PROM storage together with an integral programmer which can program any PROM location on the card. The card is extremely easy to use. It plugs directly into the microprocessor bus and needs no other control signals apart from the normal memory READ/WRITE lines. It looks, to the processor, just like ordinary RAM memory.

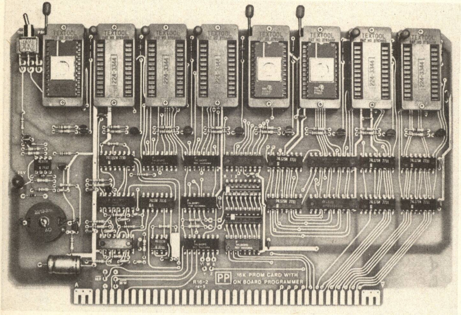

PROMs can be read, using ordinary memory reference instructions, or have programs executed out of them just as for a simple PROM memory card. All PROMs not actually in the process of being read or programmed are automatically held in the "power-down" mode thereby minimising power consumption.

To program a location in any of the PROMs, the microprocessor simply stores, with a normal memory write instruction, the required data in the actual address on the PROM Card. The data and address are latched, V_{pp} is raised to 25V, and the selected PROM is automatically pulsed for the correct time. All setup and hold times can detect when programming of the location is complete simply by reading the same address and checking the validity of the data: invalid data is automatically returned until the programming cycle is completely over.

The 25V supply required during programming is generated on-board by a switching supply so that the whole Card runs from only +5V. Because any of the 16K locations on the Card can be programmed by a single store instruction, data can be "typed" straight in using the usual microprocessor monitor command to "change memory" or "insert in memory".

The 16K bytes on the Card are divided into two 8K blocks each of which is switch selectable to any 8K area within 64K. A write protect switch is provided to prevent accidental programming of

COMPUTER CLUB DIRECTORY

Sydney: Microcomputer Enthusiasts Group, P.O. Box 3, St. Leonards, 2065. Meets at WIA Hall, 14 Atchison St., St. Leonards on the 1st and 3rd Mondays of the month.

Melbourne: Microcomputer Club of Melbourne, meets at the Model Railways Hall, opposite Glen Iris Railway Station on the third Saturday of the month at 2 p.m.

Canberra: MICSIG, P.O. Box 118, Mawson, ACT 2607 or contact Peter Harris on 72 2237. Meets at Building 9 of CCAE, 2nd Tuesday of month at 7.30 p.m.

Newcastle: contact Peter Moylan, Dept. of Electrical Engineering, University of Newcastle, NSW 2308. (049) 68–5256 (work), (049) 52–3267 (home).

Brisbane: contact Norman Wilson, VK4NP, P.O. Box 81, Albion, Queensland, 4010. Tel. 356 6176.

New England: New England Computer Club, c/- Union, University of New England, Armidale, NSW 2351. (New club; not restricted to students)

Auckland: Auckland Computer Club, P.O. Box 27206, Auckland, N.Z.

Computer clubs are an excellent way of meeting people with the same interests and discovering the kind of problems they've encountered in getting systems 'on the air'. In addition, some clubs run hardware and software courses, and may own some equipment for the use of members. Try one — you'll like it!

If your club is not listed here, please drop us a line, and we'll list you. The same applies if you are interested in starting a club in your area. Also, if established clubs know their programme of forthcoming events, we can publicise them.

Centaur Industries

THE S100 SPECIALISTS
PO Box 37243, Winnellie, N.T. 5789

SEATTLE COMPUTER PRODUCTS, INC.

S-100 static RAM. Top quality assembled and tested boards backed by a full year's warranty — will work in any known S-100 system: no clocks, no refresh, no problems with DMA peripherals, no "hidden gotchas"!

16k-250 ns	$439	8k-450 ns	249
16k-450 ns	399	4k expansion kit (450 ns)	83
8k-250 ns	279	4k expansion kit 450 ns)	93

GUARANTEED FOR ONE FULL YEAR

S.D. SYSTEMS

Top quality S-100 kits at unbeatable prices (also available assembled and tested). All boards feature sockets for all ICs, and first quality plated-through PCBs.

Z80 STARTER KIT

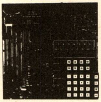

The ideal choice for the beginner, this is a complete Z80 system on a board. Includes 1k static RAM with sockets for another 1k, powerful 2k ZBUG monitor, extra PROM socket PLUS on-board PROM programmer. There's also a Kansas City standard cassette interface, hex keyboard and six digit display, twelve command keys, four counter/timer channels, two eight-bit parallel I/O ports, and room for you to expand: a generous 2½" x 8" wire-wrap area for custom circuitry AND S-100 INTERFACE WITH POSITIONS FOR TWO S-100 EDGE CONNECTORS ON BOARD.

Comprehensive documentation including full operating and programming guides. Power requirements: +5v at 1A, +25v at 30 ma. (for PROM programming).
ALL THESE FEATURES FOR ONLY $249

assembled and tested $399

SBC-100 SINGLE BOARD COMPUTER — much more than just a CPU board, it combines the Z80 CPU with 1k RAM, four PROM sockets for 4k or 8k of ROM storage, fully programmable synchronous/asynchronous serial I/O (RS232 or 20 ma. current loop), parallel input and output ports, 4 counter/timer channels and 4 vectored interrupts.

Replaces 3 or 4 boards in many systems!
PRICES REDUCED: KIT $239

assembled and tested $369

VERSAFLOPPY FLOPPY DISC CONTROLLER — Controls both 8" standard and 5" minifloppies. Directly controls Shugart SA-400, SA-800; Persci 70 and 277; MFE 700/750 and CDC 9404/9406. Listings of control software are included in the price.
THE BEST VALUE IN FLOPPY DISC CONTROLLERS $159

assembled and tested 239

SHUGART FLOPPY DISC DRIVER

SA-400 5" minifloppy	$379	SA-400 cable	35
SA-800 8" std. floppy	575	SA-800 cable	39

SOFTWARE

CP/M disc operating system — the industry standard, complete with 8080/Z80 assembler and BASIC-E plus editor and utilities, on 5" or 8" floppy disc	$125
Versafloppy control software on 2708 EPROM	25
SD Monitor (includes Versafloppy control) on PROM	50
Z80 Disc based assembler	70

LOW COST CASSETTE INTERFACE

Kansas City 2400/1200 Hz, 300 Baud. Comes partly assembled with oscillator and phase locked loop pre-tuned for trouble-free assembly. Mates with either 22 pin edge connector of 8 pin Molex connector $19.95

NEW RELEASES:

VDB-8024 VIDEO DISPLAY BOARD — Full 80 x 24 character display, complete cursor control, forward and reverse scroll, blinking, underline, reverse and field protect.

Controlled by a dedicated on-board Z80, it includes keyboard power and signal interface, plus both composite and separate video and sync.
KIT PRICE $319

assembled and tested $369

S-100 EDGE CONNECTORS — Imsai type, gold plated to suit Starter Kit and our motherboards $6.00

MEMTECH CO.

MEMTECH ARITHMETIC PROCESSOR INTERFACE

This unique product brings the number crunching power of the fabulous AM9511 arithmetic processing chip to the S-100 computer user. Full 32 bit floating point multiply in as little as 42 us. — and a full complement of transcendental functions, all far faster than software routines.

Also available is BASIC-M, a modified\BASIC-E on CP/M compatible diskette which takes full advantage of the APU performance.

APU interface (without 9511 chip) $159
assembled and tested$179
APU interface with 2 MHz 9511..$385
assembled and tested $399
APU with 4 MHz 9511 .... $485
assembled and tested $499
BASIC-M on 8" CP/M format floppy disc $29

Available soon: modified versions of CP/M compatible FORTRAN and PASCAL compilers

CENTAUR INDUSTRIES

CENTAUR S-100 POWER SUPPLY

Professional quality power supply with rugged, generously rated transformer, top grade filter capacitors (the ones NASA use!), fully fused, transient protected, AC line filter — gives+8v at 22A, ±16v at 3A, AND+28v at 3A for floppy discs and/or PROM programming supplies $349

(Power supplies shipped freight collect)

Add 15 percent sales tax where applicable — we pay postage on prepaid orders — orders accepted prepaid or COD

Z80B CPU BOARD $149

assembled and tested $235

EXPANDOPROM BOARD — Takes either 2708 or 2716 EPROMS for up to 32k. Comes complete with all support chips and sockets etc. (EPROMS not included). KIT PRICE $99

assembled and tested 189

EXPANDORAM — High density dynamic RAM, compatible with SD Systems Z80 CPU boards and the Versafloppy controller. Designed to work with 8080 and 8085 CPUs as well, these boards come in 32k and 64k models, which can be purchased partly populated for later expansion if needed.

32k model (uses 4115 RAM)			64k model (uses 4116 RAM)		
Size	**Kit**	**A&T**	**Size**	**Kit**	**A&T**
8k	$199	$379	16k	$499	$595
16k	299	449	32k	689	849
24k	399	519	48k	869	1099
32k	475	599	64k	1049	1299

STRUCTURED SYSTEMS GROUP — Quality business-oriented software designed for use under the CP/M operating system.

CBASIC — Runs on any 8080 or Z80 system with 20k or more and CP/M. Powerful disc access features — random and sequential files including variable length records. Enhanced control structures (WHILE . . . WEND, optional ELSE clause and STATEMENT LIST improvements to the IF statement), source library facility, machine language routine linkage, powerful PRINT USING, 14 BCD digit arithmetic for accurate financial calculations, and many more powerful features make this the BASIC for business applications. CBASIC is a compiler, so your programs run faster, use less memory, and are much more secure against software piracy
ON 8" CP/M FORMAT DISKETTE WITH USER MANUAL $99.95

QSORT — Runs on any CP/M system. A full disc sort/merge package — easy to use and very flexible.
ON 8" CP/M FORMAT DISKETTE WITH USER MANUAL $95

NAD — A complete name and address database system with a number of powerful user options. Requires CP/M, 32k and a 132 column printer — it can select records on any field including a user-definable field — print mailing labels — many powerful uses can be easily programmed.
ON 8" CP/M FORMAT DISKETTE WITH USER MANUAL $79

WAMECO, INC: QMB-12 S-100 MOTHERBOARD — 13 slot motherboard complete with all parts and connectors. Features extensive ground plane and termination of all signal lines, I/O area with 3 regulated voltages.
KIT PRICE $125

assembled and tested $145

COMING SOON —

Centaur 2000 disc based S-100 business system.
Post, packing and insurance included in price — add 15 percent sales tax. Dealer enquiries invited.

PROM locations. All bus signals are buffered with low powered schottky TTL and the bi-directional data bus is driven by tri-state buffers.

The PCB is 247.5 x 152.5mm and has plated through holes with a solder resist coating. The edge connector is for the Motorola EXORcisor^R bus (43 x 2 way 0.156") and used by the popular MEK 6800D2 Kit. However, the read/write control logic is jumper selectable for a variety of schemes other than the M6800, such as 6502, 8080/85, 2650, SC/MP.

The Card is available fully assembled and tested with low insertion force sockets standard for the 2716s. Zero insertion force sockets are provided as an optional extra. The standard price is expected to be $197.30 excluding sales tax plus $38.70 for all zero insertion force sockets. 2716s are extra. Pennywise Peripherals, 19 Suemar St, Mulgrave, Vic, 3170. (03) 546 0308.

Marrickville Microcomputer Society

On the 11th September, the Marrickville Microcomputer Society was formed at the Addison Road Community Centre (in Marrickville, obviously). The initial meeting featured a display of four of the more popular microcomputer systems, and was well attended, mainly by local supporters of the centre. The objectives of the Society have not yet been formally set out, but obviously involvement with youth and community is high on the list of priorities. As the Society's secretary, Justin Walsh, told us, 'The young unemployed members of the centre were a little untimidated by all the expertise and I suppose that was to be expected; after all, computer people are all supposed to be super whiz kids with above average intelligence. A lot of patience will be needed to convince these kids that they, too, can learn to use these machines and a university degree is not absolutely necessary'.

Although the club does not yet have a regular meeting place, plans are in hand for fund raising activities, including a raffle with a TRS-80 computer as first prize. Anyone interested in assisting the club in their various endeavours should contact Justin Walsh at 26 Malakoff Street, Marrickville 2204 or phone him on 569 5689.

Monash Club

A new club, the Monash Personal Computer Club, is now operating at Monash University. At present all members are students at the University, but membership is open to any member of the public. Contact them at: Monash Personal Computer Club, c/- Union Building, Monash University, Clayton, Vic 3168.

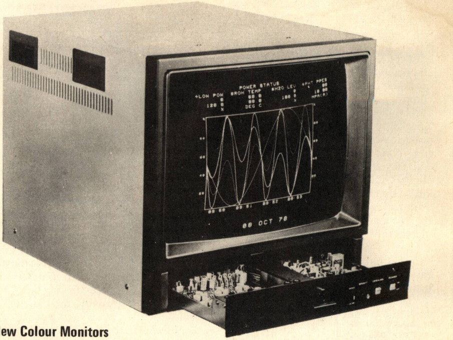

New Colour Monitors

Aydin Controls of Fort Washington, Pennsylvania, has released a series of new high resolution red-green-blue colour video monitors which are specifically designed for the display of computer-generated text, graphics and image data, with displayable resolutions of up to 1024 elements or 1024 raster lines. This performance is made possible through the use of ultra-fine pitch shadow mask CRT's and extremely stable video deflection circuits.

The Model 8024 13" and Model 8025 19" monitors have a 15 MHz video bandwidth and a horizontal frequency of 15 kHz to 18 kHz. The Model 8026 is a fast-scan monitor with a 25 MHz video bandwidth and 28.3 kHz to 34.6 kHz horizontal frequency. All units provide easily adjustable, extremely stable convergence circuitry. The convergence adjustments are sectorised to correspond to 10 areas of the CRT screen with independent RGB controls for each of the 10 screen areas which are independent of each other, thus making adjustment of convergence simple and straight-forward.

Full details are available from *Datatel Pty. Ltd., Suite 4, 3 Raglan Street, South Melbourne, 3205.*

IBM Pips TI

Although TI have released their 64K dynamic RAM, they weren't as quick off the mark as IBM, who are not only making the chips, but have released their first product using them. The giant computer manufacturer really shook industry observers by releasing the 8100, a distributed processing system, at half the price everyone expected – partly due to the use of large dynamic RAMs. Looks like the giant wasn't as sluggish as everyone thought; maybe he was only sleeping! If IBM have the technology to make 64K RAMs, it stands to reason they have similar technology in microprocessors. Watch this space . . .

Bit Pad for TRS-80

Computer hobbyists may have noticed ads in US magazines for the Bit Pad, a digitizer which can be used to enter graphics into a microcomputer. A major problem for users of the PET, Apple-II and other 'software oriented' computers has been the construction of a suitable interface to get the data into their system. Summagraphics are now offering an interface for the Bit Pad to the TRS-80 which is supplied with a cassette containing the necessary software. The interface, which costs US$175 in the States, allows the use of all other TRS-80 accessories. Summagraphics, 35 Brentwood Ave., Fairfield Conn. 06430.

PRINTOUT

Silicon Cast Pascal Processor

Western Digital Corporation has developed a 16-bit computer chip set that directly executes Pascal object programs at least five times faster than is possible with conventional system software and eliminates the previously required host operating system and interpreter. The company will sell its state of the art development both as a chip set and as a packaged software development computer to both OEM's and personal computing stores.

Designated the Pascal *Microengine* product line, the chip set standardizes the version of Pascal offered by the University of California at San Diego. UCSD's language for business, industrial and computer aided instruction applications. It was derived from (and is source compatible with) the original Pascal developed in 1971 at the Swiss Institute of Technology.

'The heart of the UCSD system is the 'ideal' pseudo machine called the 'P-machine' ', Dr. Lotito, Vice President and General Manager, Computer Products Division, explained, and we have implemented this idealized machine directly in a chip set using LSI technology. You might say we have made the first 'sand-casting' of something that previously had been available only as a software product.'

The UCSD software system includes a complete Pascal operating system: Pascal compiler, BASIC compiler, file manager, screen-oriented editor, debug program and graphics package, all written in the Pascal language.

In addition to the expanded business opportunity for Western Digital, Dr. Lotito sees the *Microengine* concept as making a number of important contributions to the computer industry. 'First, we have built an engine to drive well-established, field-proven software,' he said. 'That, in itself, is a major innovation in the computer industry, which has been talked about for many years. We have further increased the performance level of microcomputers to a point where they are competitive with larger, more expensive systems for business applications, industrial control, educational systems, and so forth.

'We have significantly lowered the cost of computer power at the system level by utilizing LSI technology in the disk controller, communications controller, DMA controller and other processor support functions, as well as in the processor itself.' The *Microengine* approach also reduces memory requirements of the UCSD system by a minimum of 25 percent by eliminating the host operating system and interpreter.

'Pascal is becoming one of the world's most popular languages, and we expect that the Western Digital development will contribute toward even more widespread acceptance,' Dr. Lotito said.

UCSD Professor Ken Bowles, who has been deeply involved in development of Pascal in the US, agreed that the Western Digital announcement should 'go a long way towards boosting Pascal's popularity among the user community.

'We are very excited; we've been hoping this would happen,' he said. 'The original version of Pascal was designed for teaching programming, and there were no provisions, for example, for using it with rotating disk storage files. We have attempted to outfit the language with these 'missing links' to make it commercially suitable,' he continued.

Bowles noted that there are more users of UCSD's Pascal today than users of all other versions combined. Western Digital and UCSD have agreed to mutually support this LSI implementation as the true UCSD standard.

Technical Information

The chip set is comprised of four LSI (MOS) components:

An arithmetic chip that contains micro-instruction decode, ALU, and the register file.

A micro-sequencer chip that contains macro-instruction decode, portions of the control circuitry, micro-instruction counters, and 1/0 control logic.

Two MICROM chips (each 22 bits x 512) that contain the micro-instruction ROMs and micro-diagnostics.

Additional features of the *Microengine* chip set include user-defined bus configuration, four levels of interrupts, single- and multi-byte instructions, hardware floating point, stack architecture, 3.0 MHz four-phase clock (75 nanoseconds per phase), and a TTL-compatible three-state interface.

The desktop computer features the 16-bit *Microengine* processor, 32K words (64K bytes) of RAM memory, full DMA control functions, fully-integrated floppy disk controller, two RS-232 asynchronous ports, and two 8-bit parallel ports – all on a single 8 x 16 board, and three power supplies (+12V, +5V and –5V) packaged in a low-profile (5¼ inches high x 16¼ x 13½) stylized enclosure.

Further details will soon be released by *Daneva Control Pty. Ltd., PO Box 114, Sandringham, Vic, 3191* Western Digital Corporation's representative in Australia.

UK Micro Impact Survey

A recent survey by National Opinion Polls Ltd. in the UK has turned up som interesting facts about people's attitude to automation, microelectronics and computers. These topics have been the subject of intense discussion by Government, unions and the media in Britain, and of course, hit the headlines here during the recent strike by Telecom technicians.

In April the BBC's documentary series 'Horizon' showed a 50 minute film entitled 'Now the Chips are Down' which dealt with the employment consequences of microelectronics and data processing, and the poll was the first indication of public opinion on the matter The theme of the film was that the microprocessor will change the face of employment and that by the 1980's, unless something is done soon, the UK could face unemployment three to fou times higher than the present 6%.

The survey was conducted on a sample of 1 001 people in various type of employment nationally. It showed that 25% of people expected computer to put 'lots' of people out of work and 41% expected them to put 'some' people out of work. Only 16% expect computers to create more jobs.

Breaking the sample down accordin to type of employment revealed that fears of unemployment are highest among the unskilled. 16% of management expect computers to put 'lots' of people out of work, compared to 35% of unskilled workers who held the sam opinion.

On the other hand, when asked 'Should we have more or fewer computers?', 39% said 'more', and 38% saic 'fewer', with 23% undecided. Again, differences emerged between the employment classes – management were 56% 'more' and 17% 'fewer', while unskilled workers were 24% 'more' and 48% 'fewer'.

Several other interesting points emerged: when asked 'If you had the opportunity to give up work without loss of pay, would you do so?', 40% said yes and 56% no. The no vote was strongest in the 15 to 24 age group.

The statistics indicated that 7.5 million people, based on current labour statistics, would be willing to undergo retraining providing they suffered no financial loss. This would help to cushion the effects of technology as people move to employment in other areas.

Whatever the survey indicates, it is certain that the introduction of microprocessors-based automation will bring a lot of headaches and cost a lot of money.

64K Dynamic RAM

Sample quantities of a new 64K dynamic random-access memory (RAM) priced at US $125.00 each are now available in the US, Texas Instruments Incorporated announced today. Volume production is scheduled for the first quarter of 1979.

Organized as 64K x 1, the TMS 4164 is expected to be the first available single 5 volt 64K dynamic RAM on the market. It comes in a 16-pin, 300-mil standard dual-in-line package, complying with JEDEC standardized pin-out requirements and allowing upward compatibility with the 16K dynamic RAM.

The TMS 4164 single 5-volt power supply design is TTL compatible, offers considerably lower power dissipation and is more immune to system noise. Five-volt operation also reduces the effective electric field across the gate oxide offering higher system reliability. In addition, a compact layout and optimized design/process combination for 5 volt only operation results in improved performance.

Access times range from 100 to 150 nanoseconds (ns) maximum with minimum cycle times of 200 to 250 ns. Power dissipation is 200 milliwatts (mW) maximum or three microwatts maximum per bit. Comparing the 462 mW power dissipation of the 16K RAM at 375 ns cycle time, total maximum power dissipation of the new 64K RAM is reduced by 60 percent with improved cycle times while bit density is quadrupled. This advancement allows practically an order of magnitude power per bit improvement.

The TMS 4164 features a 256 cycle refresh with a 4 millisecond maximum refresh period, as a result of the lower power dissipation. This refresh period is a 100% improvement over the 2 millisecond refresh period of current 4K and 16K RAMs. The small chip size of 33,000 square mils is a significant contributing factor to lower production costs and improved reliability.

Due to TMS 4164 refresh compatibility with the 16K RAM, the basic refresh controller timing does not require major changes. The only provision required is for an 8-bit refresh counter/multiplexer when upgrading to 64K from a 16K system. Also contributing to higher system operating efficiency is a 1.3 to 1.6% refresh overload time, compared to 2.4 percent on the 16K RAM.

Two clocks, RAS (row address select) control the gating of the 8-bit addresses so that timing characteristics are essentially identical to the TMS 4116 16K RAM. Row address set-up time is zero nanoseconds; hold time, 15 ns. Column address set-up is –5 ns and RAS/CAS spacing is 15 and 50 ns. This allows the system designer a full 35 ns interval to change addresses and bring CAS low, without extending access time beyond 150 ns.

Photomasks for TMS 4164 volume production will be manufactured with electron-beam equipment to control geometries to better than 0.25 microns. Projection printing will also be employed to avoid direct contact between photomask and wafer. Additionally, geometries at several critical levels of the TMS 4164 are 2.5 to 3 microns, demanding use of positive photo-resist for resolution and delineation control as well as dry processing at critical levels. Further details from Texas Instruments.

The Thinker Toys Econoram III

Les Bell reports on a popular, low cost dynamic memory board.

AS I HAVE commented in these pages before (and no doubt will do so again), the biggest and most expensive part of a computer system usually turns out to be memory. Every computer needs memory to store and execute programs, and if you are a computer hobbylst, you will often find yourself in the exasperating position of having insufficient memory to run the programs you want. Most computer hobbyists, in fact, once they have got their system up and running with the basic I/O requirements, spend most of their money thereafter on memory — at least until they start to get I/O-bound because they want to control their ham shack, or some such application.

The pattern is fairly predictable: eager computer freak gets his CPU board, evaluation kit or whatever up and running, using serial I/O to a VDU, and starts writing and running simple programs in machine code using the kit's small monitor program. He's probably only got 256 or 512 bytes of memory, and he's unlikely to fill that if he's programming in machine code, so for a while he's happy writing short games programs or clocks or whatever. But he gets bitten by the bug that gets us all in the end, and wants to write longer programs, preferably using an assembler.

That starts it. He needs more memory, so he buys a couple of 4K boards or maybe an 8K. Now he can run an assembler and all kinds of things become possible. But now is he satisfied? No way, he's had a taste of power, and now he wants to run BASIC.

This is fine; he *can* get a BASIC that will run in 8K, but soon he notices that all the great programs that appear in the American mags use Extended BASIC with all the fancy string handling functions, PRINT USING, etc. And of course there's no way it will fit in his 8K, which now seems very tiny indeed. So off he goes for another 8K. And so it goes on. . .

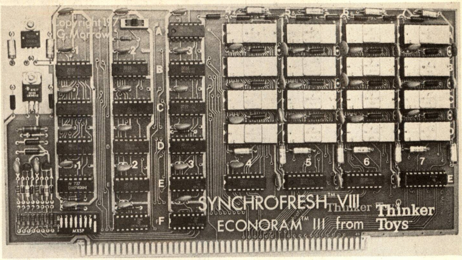

The Cure

There's no cure for Memory Madness. You can't do without it. Even if you take up photography instead, you'll just end up with Lens Madness. The only thing you can do is give in to the craving, while trying to stop it bankrupting you.

Being in the market recently for 8K to give my system some 'get up and go', I looked around at what was available, and my eyes came to rest on the Thinker Toys Econoram III 8K RAM card.

Now, this card was designed by George Morrow, alias Morrow's Micro Stuff, whose front panel design was given good reports in this magazine back in August 1977. In fact, a Morrow front panel forms the heart of my system, and based on my experiences with it, and the very cunning logic design on that card, I figured that the Econoram III was a pretty safe bet.

The Econoram III utilises dynamic memory devices of the 2107 type, which offer two major advances over static types — they are cheaper, and they consume less power. Of course, there is a drawback to dynamic memory in the form of the refresh circuitry that is required, and this has been the problem with most dynamic memory cards that have been produced to date, and indeed, is the reason why, even now, most new designs use static RAMs. Early dynamic memory boards suffered from extremely complex refresh logic — one had 35 ICs and a delay line, while another design had to be laid out on a five-layer board!

The Econoram III, however, doesn't have masses of complex logic — instead George Morrow has been very cunning in the design of the refresh circuitry. Many boards operate asynchronously with respect to the system bus, and this is the reason for the use of complex circuitry to arbitrate bus contentions when the processor and the refresh logic both try to access the memory at the same time. Instead of this scheme, Morrow has designed the Econoram III to operate in synchronism with the bus, using a scheme called Synchrofresh.

Synchrofresh

The refresh circuitry of this board assumes that the bus signals are being generated by an 8080 or 8080A microprocessor; in other words, that it is a 'genuine' S100 bus (whatever that is!). The 8080 does not access the memory during certain machine states, for example, when it has just done an instruction fetch and is decoding the instruction to decide what to do next.

Using a finite state machine (really just a counter IC) to decide what type of memory cycle the processor is executing, the circuitry 'weaves' the refresh timing into the processor's memory accesses, without interfering at all.

Because of this, the refresh circuitry is less complex and is more reliable; in fact, it is virtually foolproof.

Of course, there is a drawback: the Z-80 CPU produces slightly different timing waveforms from the 8080, and this can trick the Synchrofresh circuitry; however, Thinker Toys warn of this problem in the manual, and give a list of other boards which are known to 'confuse' the Econoram III, such as the Cromemco Dazzler.

Construction

The board was supplied fully assembled and tested — in the US, Thinker Toys actually charge $10 more for the kit than the assembled version, reflecting the fact that people often have problems with kits this complex, find themselves out of their depth, and have to return them for service. The board is double sided, through hole plated, and finished with a solder mask and silk screening to indicate component locations. The dynamic memory array occupies the top right-hand side of the board, with te refresh circuitry to the left and bus buffers towards the lower edge of the board. All ICs are socketed.

The manual supplied with the board is excellent, and based on it, there would probably be little difficulty in building up a kit, although getting it to work is a different matter, as the circuit operation is extremely cunning. The manual describes the operation of the circuitry in some depth, and covers the configuration of the board, which is basically just setting up the two 4K blocks of memory at the required addresses.

A memory diagnostic program is given which is specially written to punish the address drivers of the dynamic RAMs and will show up any faulty bits. Listings of this program are thoughtfully provided in both octal and hex (there aren't many of us octal freaks around any more you know!).

Upon plugging the card into a system, it got up and ran with no problems at all, although, as mentioned above the CPU is also a Morrow design and one would expect the two to be compatible. From all reports, however, the Econoram III works reliable with a variety of other CPUs.

Thinker Toys warrant the board for one year if it is purchased assembled, or six months in kit form. In addition, if the board turns out to be incompatible with your system, they ask that it be returned for a refund. The price in Australia is approximately $180, assembled and tested, which is extremely good value. The board is available from *Automation Statham, 47 Birch Street, Bankstown, NSW 2200.*

ADVANCED COMPUTER PRODUCTS

THE FIRST TO OFFER PRIME PRODUCTS TO THE HOBBYIST AT FAIR PRICES NOW LOWERS PRICES EVEN FURTHER!

1. Proven Quality Factory tested products only, no re-tests or fallouts. Guaranteed money back. We stand behind our products.

2. Same Day Shipment All prepaid orders with cashiers check, money order or charge card will be shipped same day as received.

S100 PRODUCTS

LOGOS I 8K STATIC RAM

- ★ Low Power
- ★ Selectable Memory Protect
- ★ Totally Buffered
- ★ Battery Back-up
- ★ Address on 1K boundary
- ★ Requires no front panel
- ★ No wait states

ASSEMBLED & TESTED

250ns.	199.95
450ns.	179.95

KIT

250ns.	149.95
450ns.	125.95

WE OFFER GROUP DISCOUNTS

Bare PC Board w/Data **$21.95**

Now over 1 year successful field experience

"Special Offer" Buy (4) 8K 450ns. Kits $117.00 ea.

IMS 16K STATIC RAM

- ★ Memory mapping
- ★ Phantom
- ★ Address 16K Bound
- ★ Use with or w/o front panel
- ★ Power 2.1 amps typ.
- ★ Uses 2114

ASSEMBLED & TESTED ONLY

450ns. $439.95 250ns. $495.95

S-100 32K STATIC RAM

- ★ Address 32K Boundary
- ★ Power 450ns. 2.8 amps typ.
- ★ No wait states on 2MHz
- ★ Fully Buffered
- ★ Phantom can be added
- ★ 2114/TMS4045 or 9135

ASSEMBLED & TESTED	KIT
250ns. $849.00	250ns. $790.00
450ns. $769.95	450ns. $625.00

Bare PC Board w/Data $59.95

SPECIAL OFFER:

Kit without Memory only $99.95.

Add 2114 Memory for 8 @ $7.50 ea.

PARATRONICS LOGIC ANALYZER KIT

MODEL 100A (analyzes any type of digital system)	$219.95
Trigger Expander Model 10	$229.00
Baseplate	9.95
Model 10 Manual	4.95
Model 150 Bus Grabber Kit	369.00

DC HAYES DATA COMMUNICATIONS ADAPTER

★ Telephone/TWX ★ S-100 compatible

★ Bell 103 freq. ★ Originate & answer mode

Assembled & Tested	$279.95
Bare PC Board w/data	$ 49.95

Z-80/Z-80A CPU BOARD

- ★ On board 2708
- ★ Power on jump
- ★ 2708 included (450ns.)
- ★ completely socketed

Assembled and tested	$185.00
Kit	$129.95
Bare PC Board	$ 34.95

★ For 4MHz Speed Add $15.00

MICRODESIGN MR-16 2716 EPROM BOARD

(MR-8 Also Available at same price)

- ★ Individual Prom Address
- ★ Uses Low cost 16K TI EPROMS
- ★ Optional 1K RAM ★ Phantom-control

Assembled and Tested	174.95
Kit	99.50

SPECIAL SPECIAL SPECIAL

2708-6 Eprom	8 @ $ 5.50 ea.
416 16K Ram	32 @ $16.95 ea.
1771-01 Floppy	5 @ $25.95 ea.
Pet Connector Set	5 @ $ 7.95 ea.

BYTE USER 8K EPROM BOARD

★ Power on Jump ★ Reset Jump

Assembled & Tested	94.95
Kit	64.95
Bare Pc Board	21.95

Special Offer: Buy 4 kits only $59.95 each

NOTE: 2708-6 only $5.95

TARBELL FLOPPY INTERFACE

★ S100 Compatible ★ Uses CPM

★ Jumper Selectable ★ Persci,Shugart,etc

Assembled and tested	$269.95
Kit	$179.95
Bare PC Board	$ 39.95

NOTE: For CPM Add $70.00
Documentation Add $20.00

TRS 80 UPGRADE KIT

16K Memory with Jumpers and Instructions (Specify Level I or Level II)	$159.95
APPLE II 16K UPGRADE KIT	$149.95

PET TO S-100 ADAPTER

Allows Pet to be interfaced to popular S-100 Bus.

Kit	$189.95
Assembled	$269.95
For Low Cost 8 Slot Bus to expand your Pet only	$149.95 Kit

DATABOOKS & MANUALS

NSC TTL Data	$ 3.95
NSC Linear Data	4.95
NSC Linear APP/note I	3.95
NSC Linear APP/note II	3.95
NSC CMOS Data	2.95
NSC Audio Data	3.95
NSC Volt. Reg. Data	2.95
NSC Memory Data	3.95
NSC MOS/LSI Data	3.95
NSC Power Transistors	2.95
Intel Databook	3.95
Intel MCS85 Manual	7.50
Intel MCS80 Manual	7.95
Intel MCS40 Manual	4.95
AMD 8080 Handbook	5.95
AMD Linear Data	4.95
AMD Schottky Data	4.95
AMI MOS/LSI Data	3.95
GI MOS/LSI Data	4.95
Osborne Intro to Micro Vol. 0	7.50
Osborne Intro to Micro Vol. I	7.50
Osborne Intro to Micro Vol. II	7.50
Osborne 8080 Programming	7.50
Osborne 6800 Programming	7.50
Osborne Z80 Programming	7.50
TI Powr Semi's Data	7.50
TI TTL Data	6.95
TI Transistors & Diodes	8.50
TI Memory Data	3.95
TI Optoelectronics	3.95
TI Linear Data	3.95
TI Bipolar Memory	3.95
TI Interface Data	4.95
Motorola Semi Data 1, 2, 3	9.95
Mot. Vol.4 Mecl Data	3.95
Mot. Vol. 5 CMOS Data	2.95
Mot. Vol. 6 Linear Data	3.95
Mot. Vol. 9 Schottky TTL	2.95
Mot. MPU Applications	25.00
Mot. MPU Prog. Ref. Manual	3.95
Mot. Power Data	2.95
Mot. Rectifier Data	2.95
Mot. Switching Tran.	2.95
Mot Zeners	2.95
Basic Software SRI Vol. I or II	24.95
Basic Software SRI Vol. III	39.95
Basic Software SRI Vol. IV or V	9.95
Basic Software SRI Vol. VI	49.95
Basic Software SRI Vol. VII	39.95
1978 IC Master	47.50

DISKETTES

5" MINI
- ★ Soft Sector
- ★ 10 Sector
- ★ 16 Sector

$4.50 each $3.90/10

NORTH STAR MINI

$4.95 each $4.50/10

8" STANDARD
- ★ Hard
- ★ Soft

$4.50 each $4.10/10

6800 DESIGNER BOARDS MODULES PROTO BOARDS

★ Motorola Compatible Modules*,

MEK 6800 D2 Kit	$235.00
9600 6800 MPU Module	495.00
9601 16 slot Mother Bd.	175.00
9602 16 slot Card Cage	75.00
9603 8 slot Mother Bd.	99.00
9604 System Power Supply	250.00
9610 Prototype Board	36.00
9615 4KEprom Module	250.00
9620 16 port parallel I/O	375.00
9626 8K Static RAM	295.00
9626K 8K Static RAM Kit	225.00
9630 Extender Card	60.00
9640 Multiple Tuner Prog.	395.00
9650 8 port Duplex Asyn. I/O	395.00
Mot 43/86 Connectors w/w or s/t	5.95
AMI EVK 99* 6800 sub Kit	99.00
AMI EVK 200 Kit	249.95
AMI EVK 300 Assembled	275.00
EVK Kluge Board	95.00
EVK 16K Byte Ram Board	75.00
EVK 6 Slot Motherboard	35.00
EVK Extender Board	45.00
EVK Solid Frame Chassis	129.00
EVK Connectors	6.50
AMI 6800 Proto Rom	30.00
AMI 6800 Micro Assembler Rom	30.00
6800 Tiny Basic Paper Tape	20.00
6800 Tiny Basic Eprom	125.00

Hi PLOT LOW COST DIGITAL PLOTTER

- ★ RS 232
- ★ Plot Size 7" x 10"
- ★ Digitizer Avail. Soon
- ★ High Resolution
- ★ 2.4"/sec Plot Speed

NEW

List: $1085.00

OUR PRICE $999.00

SPECIAL KEYBOARD BUY WHILE THEY LAST

"Clare Pender 62 Key ASCII w/26 Pin & 34 Pin Output Conn." $54.95

SUPPORT DEVICES

AM9511 Arith. Processor	$195.00
AM9517 DMA Controller	71.95
AM9519 Universal Interrupt	24.95
3881 (Z80 PIO)	10.45
3881-4 (4MHz)	14.95
3882 (Z-80 CTC)	10.45
3882-4 (4MHz)	14.95
8205/74S138 Decoder	2.95
8212 8 bit I/O	2.50
8214 Priority Int.	6.95
8216 Bus Driver	2.50
8224 Clock Gen.	2.95
8224-4 (4MHz)	9.75
8226 Bus Driver	3.95
8T26 Bus Driver	2.39
8228 Sys. Control	6.95
8238 Sys. Cont.	6.95
8251 Prog. I/O	11.50
8253 Int. Timer	19.50
8255 Prog. I/O	11.50
8257 Prog. DMA	19.50
8259 Prog. Int.	19.50
8275 CRT Controller	74.95
8279 Prog. Keyboard	19.95
6810-1 128 x 8 RAM	4.75
6820 PIA	7.20
6821 PIA	7.25
6828 Priority Int.	11.95
6834-1 512 x 8 Eprom	12.95
6850 ACIA	7.20
6852 Serial Adapter	9.95
6845/HD46505 CRT Contr.	39.95
6860 Modem	14.50
6862 Modulator	14.50
6871A 1.0MHz OSC	25.95
6875	8.25
2350 USRT	9.95
6880 Bus Driver	2.39
1821 SCD 1K RAM	25.00
1822 SCD 256 x 4 RAM	16.95
1824 CD 32 x 8 RAM	9.95
1852 CD 8 bit I/O	10.95
1856 CD I/O	8.95
1857 CD I/O	8.95
6520 PIA	7.50
6522 Mult.	9.95
6530-002	15.50
6530-003	15.50
6530-004	15.50
6530-005	15.50
3851 F8 Prog. Store	14.95
3853 F8 Memory I/O	14.95

PROMS

2708	9.95
2708-6	5.95
1702A	3.95
1702A-6	3.50
2716-5V	44.95
2716-5V, 12V	24.95
2758 5V	25.95
5203AQ	11.95
5204AQ	9.95
6834-1	12.95
IM 5610	2.95
82S123	2.95
82S126	4.50
82S129	4.95

RAMS DYN.

4116 16K x 1	17.95
4115 8K x 1	6.95
4050 4K x 1	4.45
4060 4K x 1	4.45
4096 4K x 1	4.25
2104 4K x 1	4.95
2107B-4 4K x 1	4.25
5261	1.95
5262	1.95
5270	4.95
5280	4.95
1103	1.95
4008L	4.95
TMS4070 16K x 1	19.95
4027-3	4.95
MCM6605 4K x 1	4.95

FLOPPY DISK I/O

1771-01 8" & Minifloppy	27.95
uPd372 Nec Floppy	49.95
1781 Dual Floppy	39.95

CHARACTER GENERATORS

RO32513-001 (5V) Upper	9.50
RO32513-002 (5V) Lower	10.95
RO32513-ADM3 (5V) Lower	14.95
MCM6571	10.75
MCM6571A	10.75
MCM6574	14.50
MCM6575	14.50

KEYBOARD ENCODERS

AY5-2376	13.75
AY5-3600	13.75

UARTS/USRTS

TR1602B (5V, 12V)	3.95
AY51013 (5V, 12V)	5.50
AY51014A/1612 (5-14V)	6.95
AY51015A/1863 (5V)	6.95
TMS 6011 (5V, 12V)	5.50
IM6402	9.95
IM6403	9.95
2350 USRT	9.95
1671B Astros	24.95
SALE TR1472B	**9.95**

BAUD RATE GENERATORS

MC14411	11.25
4702	14.95
WD1941	9.95

TV CHIPS

MM5320 TV Synch	7.95
MM5369 Prescaler	3.95
LM1889 Modulator	3.95
CW300 Saw Function	1.50
MM57100 Color TV Game	6.95
MM57104 Clock	3.75
AY38500-1 TV Game	5.95
AY38600 Color TV Game	24.95
AY38615-1 Color Converter	8.95
AY38700-1 Tank Chip	29.95
RF Modulator with Audio	8.95

A/D CONVERTERS

8700	8 bit Binary	13.50
8701	10 bit Binary	22.00
8702	12 bit Binary	36.95
8705	12 bit TS	42.95
9400	Volt to Freq. Conv.	7.25
8750	3-1/2 Digit BCD	13.95
8038	Multifunction	3.95
1408L6	6 bit	3.95
1408L8	8 bit	5.95
DACOI	A/D	5.95

TV INTERFACES

Pixie-Verter	8.50
TV-1 Video Interface	8.95
Pickles & Trout TV Mod. Kit	20.00
Multiverter	35.00
M&R Modulator	35.00

MICROPROCESSORS

Z-80	**$19.95**
Z-80A	26.95
F-8 (3850)	16.95
2650	24.95
CD1802	19.95
8080A	9.95
SALE 8085	**18.95**
8008-1	14.95
2901	21.95
2901A	29.95
TMS 9900JL	69.95
CP1600	39.95
6502	13.95
IM6100	29.95
6800	**19.95**
6802P	32.95
8035	17.50

SOCKETS

8 Pin W/W	.32	8 Pin S/T	.17
14 Pin W/W	.37	14 Pin S/T	.20
16 Pin W/W	.38	16 Pin S/T	.22
18 Pin W/W	.60	18 Pin S/T	.31
20 Pin W/W	.90	20 Pin S/T	.34
22 Pin W/W	.93	22 Pin S/T	.35
24 Pin W/W	.85	24 Pin S/T	.41
28 Pin W/W	1.15	28 Pin S/T	.49
40 Pin W/W	1.49	40 Pin S/T	.63

CONNECTORS

6 Pin Single S/E	1.49
15/30 Dual S/E	1.95
18/36 Dual S/E	2.35
22/44 Dual S/E	2.95
40/80 W/W	4.95
43/86 Dual W/W/S/T	6.50
50/100 IMSAI W/W	4.75
50/100 IMSAI S/T	4.75
50/100 Altair W/W/S/T	5.95
IMSAI Card Guides	4/1.00

25 Pin-D Subminature	
DB25P	3.25
DB25S	3.75
Hood	1.25
Set w/Hood	6.50

NEW CTS DIPSWITCHES

CTS206-4	$1.75	CTS208-8	$1.95
CTS206-5	$1.75	CTS209-9	$1.95
CTS206-6	$1.75	CTS209-10	$1.95
CTS207-7	$1.75		

8080 USER'S IT'S HERE LIVERMORE BASIC

ON 65K ROM
THAT'S RIGHT ON ROM!!!

OUR PRICE only $95.00

PCG PROGRAMMABLE CHARACTER GENERATOR

The hottest version of STARWARS available.

S-100 Compatible 2MHz Kit with object code on tarbell or cuts $169.95

NAKED PC BOARD SALE S-100

Z-80 CPU (ITHACA)	34.95
Z-80 CPU (TDL comp.)	34.95
8080A CPU	34.95
8K Static Logos	21.95
8K Eprom Byteuser	21.95
32 Static S-100	59.95
Tarbell Floppy I/O	39.95
Tarbell Cassette	29.95
Vector 8800 Proto	19.95
ACP Proto Bd.	27.95
ACP Extender w/conn	15.95
Realtime Clock	34.95
WMC 13 Slot Mother Bd.	33.00
S-100 8 Slot Mother Bd.	34.95
Vector 8803 11 Slot M. Bd.	29.95
SSM Video I/O	27.95
SSM I02 Parallel I/O	27.95

UV "Eprom" Eraser

Model UVs-11E **$64.95**

Holds 4 Eprom's at a time.

Backed by 45 years UV experience

Model S-52T **$219.95**

Professional Industrial Model

ATTENTION KIM USERS

KIMSAI-expansion to S-100	125.00 Kit/165.00
KIMSI to KIM Connector	5.75/pair
KIM 1 6502 Single Board Computer	245.00
KIM 1 Power Supply	89.00
KIM Memory Plus - (consists of 8K Ram, 8K 2716 Eprom, Programmer, I/O etc.)	245.00

KIM SOFTWARE

• Please package (cassette) 12 games	16.95
• Help Editor package (cassette)	16.95
• Help Mailing List pkg. (cassette)	16.95
• Help Info Retrival pkg. (cassette)	16.95
• Microchess (cassette)	16.95
• Microaid Assembly/Disassem/Editor	27.95
• Microaid Source Listing (cassette)	27.95
• Tiny Basic for KIM (paper tape)	10.95

ATTENTION PET USERS

BETSI-pet expansion to S100	105.00 Kit/160.00
PET Connector Kit. Includes (4) Connectors for memory expansion, IEEE 488 I/O, cassette I/O and parallel user port	9.95/set

ATTENTION TRS-80 USERS

Now in stock the hard to find 20/40 Memory Expansion Connector with contacts 7.95

ATTENTION APPLE II USERS

APPLE II w/16K (get a spare)	$1125.00
416/4116 16K Memory Module	8/200.00
Floppy Disc II w/Controller	495.00
Applesoft II Firmware Card	100.00
Video Monitor II (B/W)	205.00
Printer Centronics Micro	695.00
Printer Centronics 779	1445.00
Apple II Prototype Board	24.00
Parallel Interface Card	180.00
Communications Interface Card	180.00
PR40 Printer I/O w/cassette	49.95
2716 Eprom Burner	89.95
requires 2716 Socket Adaptor	10.00
Apple II to MFE tape I/O	197.50
Coresident Assembler cassette	19.95
Apple II Softech Software Exchange Membership includes 8 pack of cassettes	39.95

All Shipments FCM or UPS. Orders under $100.00 add 5% handling and postage. Orders over $100.00 add 2.5% handling & postage. Mastercharge/Bankamericard/COD accepted w/25% deposit. California Residents add 6% tax. Foreign Orders add 8% handling. All parts prime factory tested guaranteed. Same day shipment. Add 25 cents for Data.

Retail pricing may vary from Mail Order Pricing.

STATIC RAM HEADQUARTERS

	1-24	25-99	100
21L02 450ns.	1.30	1.25	1.15
21L02 250ns.	1.59	1.55	1.45
2102	1.25	1.15	1.10
91L02APC	1.75	1.65	1.50
21L11-1	4.10	3.95	3.75
211-1	3.75	3.65	3.55
21L12-1	4.25	4.10	3.95
2112-1	2.95	2.85	2.65
21L01-1	3.95	3.75	3.65
2101-1	2.90	2.70	2.55
2114-3 300ns.	9.95	9.75	8.25
2114-4 450ns.	7.95	7.50	5.50
TMS4044	9.95	9.75	8.25
TMS4045	9.95	9.75	8.25
EMM4200A	12.50	11.95	9.95
EMM4402	7.95	7.25	6.25
5101C-E	7.95	7.95	7.25
upd410 (4200)	10.95	10.25	9.25
AMD9140/41	10.95	10.25	9.25
AMD9130/31	12.95	11.95	10.25
FSC 460/46416K CCD Only $18.95 Each			
1101	1.95	1.75	1.25
P2125/93425 (45 ns.)	7.95	7.35	7.25
6508 1K x 1 CMOS	7.95	7.95	7.25
6518 1K x 1 CMOS	7.95	7.95	7.25
74S189 64 bit Ram	3.95	3.25	2.50

WAVEFORM GENERATORS

8038 Function Gen.	3.95
MC4024 VCO	2.45
LM566 VCO	1.75
XR2206 Function Generator	5.25

CHARGE COUPLED DEVICES

16K CCD - First time offered Fairchild 460 CCD 16K Memory (now you can experiment with CCD technology at a reasonable price. 17 page Application note supplied with each order. Quantity limited)

$18.95 each (reg. 43.00)

CRYSTALS

Microprocessor Timebases TV Game

Frequency	Price	Frequency	Price
1.0MHz	$5.85	6.0MHz	$ 4.95
1.8432	4.95	6.144	4.95
2.0MHz	5.85	6.5536	4.95
2.01MHz	2.95	10.0MHz	4.95
2.097152MHz	5.85	13.0MHz	4.95
2.4576MHz	5.85	14.31818	4.95
3.579545MHz	1.50	18.0MHz	4.95
4.0MHz	4.95	18.432MHz	5.95
4.194304MHz	5.95	20.0MHz	4.95
4.91520MHz	5.95	22.1184MHz	5.95
5.0MHz	4.95	27.0MHz	5.95
5.0688	4.95	36.0MHz	5.95
5.7143MHz	5.95	48.0MHz	5.95
		100KC	12.95

DISPLAYS/OPTO

DL 704/707/CC/CA .300	1.25
FND359 CC .357	.95
FND 500/507/CC/CA .500	1.35
FND 503/510 CC/CA .500	.95
FND 800/807 CC/CA .800	2.50
Bowmar 9 digit bubble	.99
FSC 8024 4 digit CC .800	4.95
HP7340 HEX Display	19.95
TIL 305 5 x 7 Array	4.50
TIL 306 7 seg w/logic	8.95
TIL 308 7 seg w/logic	8.95
TIL 309 7 seg w/logic	7.95
TIL 311 HEX Display	12.95
MA 1003 12 auto clock	17.95
MA 1002 4 digit clock module	9.95
MA 1010 4 digit clock module	9.95
Bezel for above	4.95
NSN 373/374 dual CC/CA .300	2.20
NSN 583/584 dual CC/CA .500	2.60
NSN 783/784 dual CC/CA .700	3.00
4N25 Opto Isolater	1.10
MCT 2 Opto Isolater	.89
4N33 Darlington ISOL	1.75
Red Led's .185 Dia.	5/1.00
Green/Yellow	4/1.00
HP 5082/7731 7 seg.	.90

MONTHLY SPECIALS

14 Pin W/W 100 pcs.	19.95
14 Pin S/T sockets 1000 pcs.	.10
16 Pin S/T sockets 1000 pcs.	.11
22 Pin S/T sockets 1000 pcs.	.12
FSC460/464 16K CCD's	18.95
AMD 9140CDC Static Ram	10.95
4116/416 16K Dynamic Ram's	8 for/149.95
1488 or 1489 RS232 Driver	.95
8T97 Buffer	1.25
8130 or 8131	2.45
8833 or 8835	1.99
74367 or 74368	6/5.00
75451/52/53	10/2.50
8T26 Bus Driver	2.39
78L05 Regulator	2/1.00
MCT2 Optoisolator	.89
2510A Shift Register	2.95
2519A Shift Register	2.95
MM5056 Shift Register	2.95
LM760N-14 Compartor	1.10
DS0025CN Clock Driver	1.49
DS0026CN Clock Driver	2.50
8T20 Bidirect oneshot	3.49
1403AN Shift Register	1.50
9368	2.95
Intel 8155 22 I/O w/Ram	17.95
ICL 7107 CPL 3½ Dig. A/D	11.95

NEW
1978 CATALOGUE
SEND 25¢ POSTAGE

DISCOUNT COMPUTER CORNER

	Discount Cash	Computer Credit Card
Apple II/16K	$1125.00	$1155.00
TEI PT208	4599.00	4699.00
TEI MCS122	450.00	462.00
Cromemco Z-2	536.00	551.00
Cromemco SYS III	5499.00	5561.00
Decwriter II	1475.00	1525.00
Persci 277	1230.00	1266.00
Shugart 800/801	495.00	512.00
Pertec FD200	299.00	319.00
MFE Dual 751	730.00	744.95
Shugart 400	325.00	315.00
Horizon I	1439.00	1479.00
North Star	599.00	617.00
Low Cost S-100 Bus	149.95	155.95
ADM 3 Assem.	829.95	865.00
Soroc IQ 120	895.00	945.00
Teletype Model 43	1199.00	1230.00
AM100	Contact sales desk	
Imsai w/22 slots	599.00	617.00
Oliver 2708/16 Programr.	275.00	288.00
Pennywhistle Modem	129.95	129.95
Cromemco 16K Ram	449.00	462.00
Hazeltine 1500	1175.00	1195.00
Okidata 110 w/TFR5232	1675.00	1705.00
Okidata 22 w/TFR5232	2705.00	2810.00
MEK 6800 D2 Kit	235.00	Same
KIM I 6502	229.95	Same
Intercept Jr 6100	281.00	Same
Technico 9900 Kit	299.00	Same
RCA VIP Cosmac	249.00	Same
Rockwell AIM	375.00	Same
Synertek VIM-1	269.00	Same

P. O. BOX 17329 Irvine, California 92713 New Phone (714) 558-8813
TWX: 910-595-1565

Retail Store Open Mon. – Sat.
Located at 1310 "B" E. Edinger,
Santa Ana, CA 92705

Over the past two years customer acceptance of Vector Graphic microcomputers has just grown and grown and grown. It isn't terribly surprising, really. After all, it does make life a lot easier when you have reliable cost effective equipment.

So it is with our new Vector MZ business system with both data processing and word processing available all in one trouble-free system.

That's good because:

By having one interactive stand-alone system with optional software for all your business functions including Accounts Payable, Accounts Receivable, General Ledger, Financial Statement, Inventory and more, plus... word processing for mailing labels, text editing of manuals, catalogs, etc., collection letters, contracts and proposals – you'll have big business power.

Known throughout the industry for highly reliable equipment, Vector Graphic's new business system incorporates: the Z-80 based Vector MZ microcomputer with built-in dual-disk quad-density storage enough to handle as many as 4,000 customers and 12,000 inventory items; Vector Graphic's "Mindless terminal"; and a Centronics 120 character per second printer. Optional Diablo letter-quality printer is also available.

That's Vector Graphic – cost effective, versatile, reliable systems. When you get right down to it – nobody does it better.

☐ Send me details immediately

Name ____________________

Company ____________________

Address ____________________

City/State ____________________

Dealer inquiries invited
MICROCOMPUTER DIVISION
A.J. & J.W. DICKER PTY. LTD.
VECTOR GRAPHIC 5245639
24 Woodfied Bvde., Caringbah 2229

BUSINESS
Small ^ Wonder

The Marisat System

Three satellites provide navigational and communications facilities to users around the world. Special ETI report.

THE INSTALLATION OF radio communication equipment on ships has consistently proved its worth since the sinking of the Titanic, when wireless was used to contact the rescue ships. Although we have progressed somewhat from the days of rotary spark gap transmitters and coherer receivers, even the use of sophisticated MF and HF single sideband equipment and VHF radio for inshore communications has not yet provided consistently high quality communications. Although ships are rarely out of communication with essential services such as weather reports, the vagaries of propagation due to the ionosphere often disrupt communications. Because of this a considerable amount of maritime communications is by Telex and even the trusty Morse Code.

The variation of performance on a particular band varies considerably with time of day (as a glance at our propagation predictions will show), and this means that communications with a particular shore station at a particular time must be on the right band. Again, signals are often subject to severe fading as well as interference from other stations, cross-modulation and all kinds of problems. This has essentially been the situation for some time now; there have been very few significant advances in the technology of marine radio since the introduction of single sideband.

The problems are aggravated by the progress that has been made in land based communications. Shipping companies are able to use computers in data communications networks to transmit information between their offices around the world, yet radio communication is unable to carry the volumes of information to ships that the operators would wish.

But here comes the answer to many of these problems – a satellite communications network called Marisat.

A close-up of the fibreglass radome which houses the above-decks antenna assembly.

The Satellites

On February 19th 1976, a Thor Delta 2914 launch vehicle lifted the Atlantic Marisat satellite into its position above the equator at 15 degrees West longitude. The first users of the satellite were the US Navy on March 25th and the first commercial voice message went through on July 9th, 1976.

The satellite, which is one of three which also cover the Pacific and Indian Oceans, weighed almost 655 kg at launch, and just over half that on station in orbit. The Atlantic satellite, from its stationary orbit 35 584 km above the earth, covers an area encompassing the entire Atlantic Basin, and western portions of the Indian Ocean, as well as Pacific Ocean areas off the west coast of South America. Each of the satellites covers an area of approximately one third of the earth's surface – the Pacific Ocean satellite, which is positioned at 176.5 degrees East longitude, covers from the west coast of the US across the Pacific Basin to the Malaysian Peninsula. The Indian Ocean satellite, which at present is only used by the US Navy is situated over the equator at 73 degrees East longitude. The satellites operate on three bands. On C-band the receive frequencies are 6420 – 6424 MHz, and the transmit channels from 4195 – 4199 MHz. On the lower L-band, the frequencies are 1638.5 – 1642.5 MHz and 1537 – 1541 MHz, respectively. There is also a UHF service which is used exclusively by the US Navy.

Each satellite is 3.8 m high and 2.16 m in diameter, and has a triple antenna system mounted on top.

The satellites, however, are only part of the story. What is significant about Marisat is the provision of satellite earth stations on board ships at sea – a hostile environment for equipment of this nature.

The Marisat System

Radio Officer Ed Watkins, on the 'Robert Miller' operates the Marisat terminal.

The Shipboard Installation

The Marisat terminal on board ship is in two sections – the below decks electronics console and the above-deck antenna assembly. The antenna is a 1.3 m diameter parabola, mounted inside a fibreglass radome along with ship motion sensors which operate with gearless servomechanisms to keep the antenna accurately and automatically tracking the satellite.

Since the position of the satellite is accurately known, and the latitude and longitude of the ship is also known, reference to a table will give the true bearing and elevation of the satellite. Once the antenna has been set up correctly the receiver is left on, and thereafter tracking is accomplished automatically. This is done by monitoring the automatic gain control voltage in the receiver, and using it, via servomechanisms to drive stepper motors, thus compensating for changes in the ship's position. Balance against pitch and roll is provided by a motor driven stabilised platform and rate and level sensors.

The 226 kg antenna assembly has an RF amplifier mounted behind the antenna with 32 W output, and the antenna itself has a gain of 23.5 dB. The receive figure of merit is 4 dB/K at 5 degrees elevation.

Below decks is a 150 kg console which contains the bulk of the non-RF electronics – a telephone communications chassis, status and operating panel, antenna control unit, teletype and power supplies.

The Marisat network provides several major communications services:

Voice. The telephone service is of a very high quality and is linked with many international telephone networks.

Telex. The international 50 baud telex network is linked to the Marisat satellite system, and provides a round-the-clock facility for the transmission of important messages. The Marisat telex system is extremely sophisticated and offers many special features. For example, abbreviated dialling is possible, using single or double letter or number codes rather than typing out lengthy numbers and area codes. Multiple addressing allows messages to be 'broadcast' to several points, a camp-on facility will automatically re-try busy numbers, and finally, the system will accept and store messages for later transmission in case delays are expected.

Facsimile. The facsimile facility is extremely useful because of its ability to transmit drawings, daily reports, manifests, weather maps, and other graphic material.

Data. The use of computers in teleprocessing and communications makes the provision of data transmission of increasing significance. Marisat provides a capability for alternate voice/data communications at 1200 and 2400 bits per second.

Further services are under development, for example a high speed data transmission service which would allow data from oil exploration or survey vessels to be transmitted to computers on the other side of the world for analysis in real time.

The Ground Stations

There are two main ground stations which handle the ground-to-satellite end of the communications link, as well as the control signals for the satellites. One is situated at Southbury, Connecticut and the other is at Santa Paula, California. Both stations are equipped with 12.8 m diameter dish antennas.

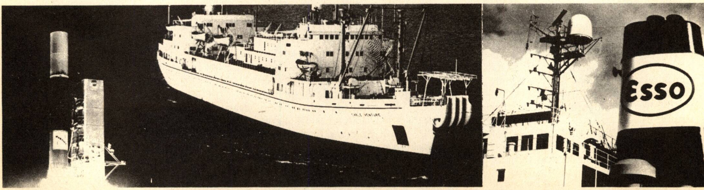

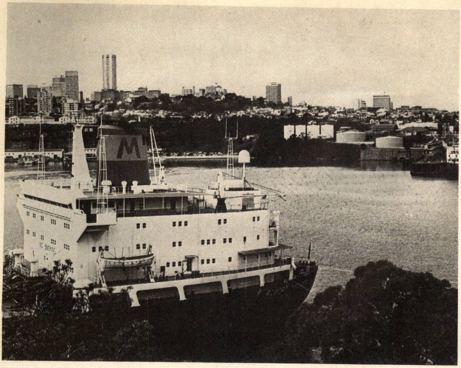

The Marisat antenna assembly can be seen above the stern of the Robert Miller, berthed at Sydney's Gore Bay.

Each station is a 'network control' point for commercial traffic in its area, and controls the assignment of satellite channels to a particular ship or offshore rig, transmits or receives messages on these channels, and then returns the channels to a common pool for reassignment to other users. Thus, the system is available to a large number of ships.

Offshore Facilities

Marisat is especially useful to offshore exploration and construction industries, because of the integrity of data communicated through the system and because of the reliability of the service. Users range from pipeline projects in the Straits of Magellan to highly sophisticated at-sea construction projects off the north of Scotland.

The 24-hour availability of instant reliable communications provides better management methods, with consequent cost savings because of the enormous daily running costs of these rigs.

Other advantages of Marisat communications include the capability for instant data analysis, which can save days in drilling, well-logging and downhole analysis time; the ability of crews to call home and speak to family and friends; the ability to make on-site changes in engineering drawings using the facsimile equipment; the ability to transmit payroll data and other information such as the morning report; and improved safety through the Marisat 'Distress' capability which provides immediate contact with Coastguard offices on both sides of the US.

US Navy

A major user of Marisat (and indeed the only user of the Indian Ocean satellite) is the US Navy, which has an exclusive UHF band allocation well clear of the commercial frequencies. Military Sealift Command, for example, hurtled into the 20th Century in 1977 with the installation of Marisat on five of their ships. These oceanographic survey ships were a natural choice for the installation of Marisat because of the large volumes of data technical crews compile at sea.

With the Marisat terminals on board, MSC survey ships can transmit compiled data to computer centres on a daily basis. Previously, mapping and charting data was stored on magnetic tapes and mailed to the data processing centres whenever a ship put into port. Gaps in the coverage might not be discovered for days or even weeks, sometimes requiring a ship to return to an area to repeat part of the survey at great expense. Marisat permits much quicker detection of these problems.

Robert Miller

Two Sydney-based oil tankers are already fitted with Marisat terminals: the 'Robert Miller' and the 'Australian Endeavour'. Thanks to the cooperation of R.W. Miller & Co., and AWA's Marine Division, we were able to take a look at the Marisat terminal on board the Robert Miller in Gore Bay, Sydney, recently. The Robert Miller regularly runs around the South Coast from West Australia we were able to get some good photographs of both the above decks antenna assembly and the console.

Step Forward

Because of its ease of operation, and the high quality of the communications services it provides, Marisat represents a major step forward in maritime communications.

We would like to thank COMSAT General Corporation, R.W. Miller & Co., and AWA Marine Division for their assistance in preparation of this article.

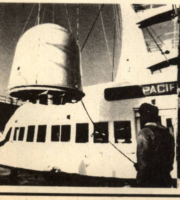

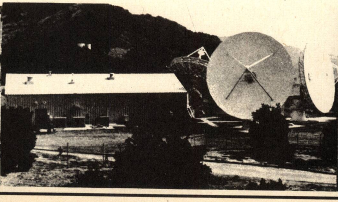

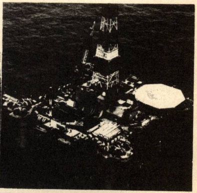

University
MULTIMETERS

EVERYTHING FOR THE HOME HOBBYIST

MVA-50 'Professional Meter'
50 k^/Volt – 46 ranges
D.C. Volts – 12 ranges to 1 kV
A.C. Volts – 10 ranges to 1 kV
D.C. Amps – 10 ranges to 10A
Resistance – 4 ranges to 16 M
db – 1 mW in 600^ to + 62 db.
Price: $38.00+15% Sales Tax

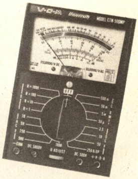

CTN 500 MP 'Popular Meter'
20 k^/Volt – 4 mm. Terminals
D.C. Volts – 6 ranges to 5 kV
A.C. Volts – 5 ranges to 1 kV
D.C. Amps – 4 ranges to .5A
Resistance – 4 ranges to 10 M
db – 1 mW in 600^ to + 62 db
Price: $26.50+15% Sales Tax

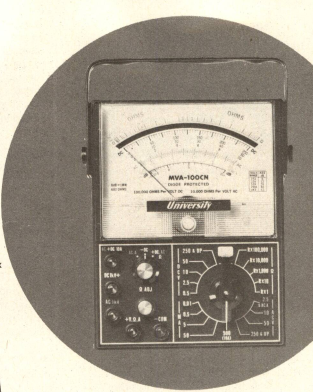

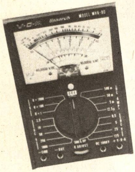

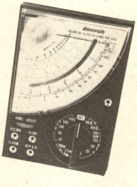

MVA-80 'Handyman's Meter'
80 k^/Volt – Recessed Meter
D.C. Volts – 6 ranges to 1 kV
A.C. Volts – 5 ranges to 1 kV
D.C. Amps – 4 ranges to .5A
Resistance – 3 ranges to 10 M
db – 1 mW in 600^ to + 62 db
Price: $27.50 + 15% Sales Tax

MVA-100 CN 'Deluxe Meter'
100 k^/Volt – Reversing Switch
D.C. Volts – 6 ranges to 1 kV
A.C. Volts – 5 ranges to 1 kV
D.C. Amps – 6 ranges to 10A
A.C. Amps – 1 range to 10A
Resistance – 5 ranges 0.1 to 200 M
db – 1 mW in 600^ to + 62 db
Price: $50.00 + 15% Sales Tax

ALL UNITS HAVE DIODE OVERLOAD PROTECTION AND MULTI-COLOUR MIRROR SCALES

MVA-5/73 'Pocket Meter'
20 k^/Volt – Unbreakable Case
D.C. Volts – 6 ranges to 2.5 kV
A.C. Volts – 5 ranges to 1 kV
D.C. Amps – 3 ranges to 250 mA
Resistance – 2 ranges to 6 M
Capacitance – 10 uuf to .1 uf
Price: $21.00 + 15% Sales Tax

HIGHEST QUALITY AT THE LOWEST PRICE, BACKED BY OVER 30 YEARS' SALES & SERVICE

TO: Mr . . . .
Address: . . . .
. . . . Post Code. . . . .
Quantity: . . . . Model . . . .
Enclosed cheque/postal note for above unit, or send C.O.D. post. Please allow $2.50 for packing, post and insurance UG-1

UNIVERSITY GRAHAM INSTRUMENTS PTY. LTD.

106 Belmore Road, Riverwood 2210
Telex: 21398 Phone: 53 0644

MAD MAL'S BEST BUYS

DECEMBER MADNESS!

MAD MAL

MAD MAL © 1978

JUST RELEASED! 2 FABULOUS NEW DE-LUXE SPEAKER KITS - WOOD VENEERS
•HAND-CRAFTED & FINISHED •CONTOURED FRONT GRILLES •FULLY ASSEMBLED •JUST ADD SPEAKERS OF YOUR CHOICE!
650x410x310 mm $49.50 EA
'LIVE SOUND' 760x480x360mm $65 EA
* GENUINE WOOD VENEERS •ASH •TEAK •MAPLE •WALNUT ETC

5" TV TUBE
150CB4 B/W TUBE $5.95 EA
NEW! LAST FEW. 2 FOR $11 OR

BY PLESSEY
23 WAY 2 SIDED PC EDGE CONNECTORS
GOLD PLATED (USE AS 46 WAY) EA $1

NT-3102 Eht Trans.
Brand new Philips EHT Transformers Popular Model
$6.50 EA

SYSTEM PRICE $55
BUILD YOUR OWN SPEAKERS LIKE THESE!

6" BASS + 3" TWEETER KITS TO BUILD YOUR OWN SPEAKERS - 10W EA. $7

SUPER CARTRIDGES... MAD MAL'S Bargains
'A' $1.80 STEREO CERAMIC
'B' 90¢ MONO CRYSTAL
'C' $1.80 STEREO CRYSTAL

Telescopic Aerial
TOP QUALITY CHROME
TOTAL LENGTH 3'6"
SCOOP 2 FOR $1

5" HI-FI MID-RANGE OR TWEETER 15W
8/15 OHMS 4KH-19KHz TWIN-CONE $3.50

LOOK SUPER SCOOP!
2 Gang Condenser
200pf + 90pf
3/4" x 3/4"
25¢

U-BEAUT POWER TRANSFORMER
240v IN, 12V 1A plus 26V 1A OUT
$3.95 EA OR 2 for $7
BRAND NEW & G'TEED, WITH SHIELD.
Lots of uses eg: Amplifiers, Power Supplies, Test Equipment etc. Ask our price for quantity - total 800 available.

CORAL SPEAKERS
High quality, complete speaker kits, X'overs, mtg screws, wire etc

6SA-1	6"	30w,	50Hz-20KHz	$52 PR
8SA-1	8"	35W,	70Hz-20KHz	$59 PR
8SA-5A	8"	35w,	50Hz-20KHz	$65 PR
10SA-1	10"	50w,	40Hz-20KHz	$97 PR
10SA-5A	10"	50w,	40Hz-25KHz	$109 PR
12SA-1	12"	60w,	30Hz-20KHz	$133 PR
12SA-5A	12"	50w,	35Hz-20KHz	$139 PR

SAVE HEAPS!
IF YOU BUY CORAL SPEAKERS WITH ANY OF OUR HUGE RANGE OF CABINET KITS, WE WILL CUT-OUT FRONTS FOR YOU FREE

MUSICOLOUR MKIII COLOUR ORGAN KIT
SAVE $10 OFF OUR NORMAL PRICE of $59.90 $49.90
See E.A. Sept '76

HI-FI STEREO SYSTEM KIT
3W+3W AMPLIFIER
Volume, Bass, Treble Controls - also h'phone and 5pin din Rec/Play socket - all parts and instructions are supplied - includes teak finish wood base suit BSR or Garrard $19
DE-LUXE TURNTABLE
Complete with cer. cartridge - will suit above ampfifier $22

NEW Garrard
TURNTABLE BASES
in beautifull TEAK!
Size 21"x14"x3½"
Plenty of room for amplifier
JUST MAD! $3

New! UF-411
PHILIPS AM RADIO TUNER MODULE UF-411
3 Sil Trans. Just add Ferrite Rod Aerial $1.00 ea plus Tuning Gang $2.50 ea, 6v or 9v, etc to build complete tuner.
ONLY $2.50

SWITCH BARGAINS!

MINI-SLIDER DPDT	DPDT ROTARY	SPST FOOT-SWITCH	DPDT De-Luxe Toggle
25¢	40¢	30¢	55¢

ELECTRICAL TERMINAL BLOCKS (12 FOR 50¢) IN MULTIPLES OF 12 50¢

FUSEHOLDERS 15¢ ea STD 3AG FUSE

ROTARY WAFER SWITCHES
$1 ea
3 Pole 3 Pos 3 Bank
6 Pole 2 Pos 1 Bank
4 Pole 2 Pos 3 Bank

Hot-Line Filter
SUIT CB or CAR STEREO $2.50 EA
Reduces Ignition Noise

6.5mm STEREO SOCKET 50¢ EA $4 FOR 10

NEW! ECONOMY TONE ARM WITH STEREO CARTRIDGE $5.50

3.5mm SOCKETS 10¢ EA OR 80¢ FOR 10

PACK/POST: 50¢ plus 10% ORDER

NEON BEZEL 40¢
Std 3/8" Mounting New, top quality 250VAC
NE-2 NEONS 10¢

15V 2AMP POWER SUPPLY KIT $12.50
Comprises: Trans, 4x2.5A Sil Rectifiers, 3300uF Electrolytic. Plus instructions to build a CB Power Supply etc.

NEW! Push-Button 250v AC Switch
PUSH-ON, PUSH-OFF 1 AMP 20¢

MAL'S VALU-PACKS
LUCKY DIP ASSORTMENTS FOR VALUE CONSCIOUS EXPERIMENTERS

500 ½W RESISTORS $2	200 1W RESISTORS $2	250 MIXED ¼, ½, 1 WATT RESISTORS $2	40 5W RESISTORS Also 3W, 7W, 10W $2
25 NEW PRESET POTS $2	12 NEW SLIDER POTS $2	40 RADIO, TV KNOBS $2	20 ASST. POTS $2
100 CAPS CERAMIC $2	45 CAPS ELECTROS $2	20 P.F, I.F, OSC COILS $2	20 ASST VDR'S + insts. $2
50 ASST. TAGSTRIPS $2	20 ASST. LOW VOLTAGE DIAL LIGHT GLOBES $2	30 6" PCES SPAGHETTI TUBEING. $2	20 MINI POTS $2

BUY 10 PACKS + EXTRA ONE FREE!

MAD MAL'S BONANZA * PAK
A VAST ASSORTMENT OF GOODIES FOR ALL YOU ASPIRING HOBBYISTS!
All new, all high quality parts, samples, specials, end-of line, useful components, incl semiconductors, transformers, resistors, capacitors, pots, IC's, switches, relays etc. etc. etc. WORTH $$$$$
Over 2Kgm weight, size approx 11"x7"x6"
$9.98
NEW!

KRAZY Semiconductor PRICES
All top quality brands full spec - Equivalents may be supplied.

7400	20¢	2N3053	35¢
7401	20¢	2N3643	30¢
7441	$1	2N4250	40¢
7473	70¢	BC337	25¢
7490	70¢	BC338	25¢

MAD

IR60	600 PIV	25A	Rect.		75¢
IN5404	400 PIV	4A	Rect.		55¢
VJ148	100 PIV	10A	Bridge		$3.75
MDA3504	400 PIV	35A	Bridge		$4.13
C122D	400V	8A	SCR		$1.34
SC146D	400V	10A	Triac		$2.20
TIC44	40V	600mA	SCR	4 for	$1

MPF102 Fet 75¢ MPF105 Fet 75¢

HEATSINK PLIERS 2 FOR $1.95 WHILE THEY LAST

2 NEW C-CORE TRANSFORMERS
a) 50v 2A or 100v 1A plus 6.3v 2A
b) 15v 2A or 30v 1A
EA $8
AUST. MADE
LAST FEW! SPECIAL OFFER!
2x 12v 6A TRANSFORMERS 110v PRIMARY, SERIES FOR 240v $12 PR.

NEW, DE-LUXE STEREO H'PHONES
SAVE 33⅓% NOW ON ALPHA H'PHONES $15
Vol, Tone adj
NOW REDUCED FROM $22.90

MASTER/SLAVE INTERCOM SETS
Instal Yourself, Complete Kits with all wire, battery, insts. etc. LIMITED QUANTITY

2 WAY	3 WAY	4 WAY
$12	$20	$25

VORTEX STEREO CASSETTE MECHANISM
LAST SHIPMENT OF THESE TOP QUALITY DECKS - Ideal for computer enthusiasts or build your own cassette recorder. 120v ONLY $29.50
240v-120v TRANSFORMER, also 15v 1A and 6.3v 1A windings $7.50 EA
RECORD/PLAYBACK KIT NOW Reduced $15 EA

COMPUTER * BOARD SALE
A SPECIAL PACK OF 10 BOARDS WITH APPROX 600 ASST. PARTS FOR $5
LESS THAN 1¢ PER ITEM FOR -
300 RESISTORS mostly 2%
220 DIODES various germ. and silicon
70 TRANS TO5 and TO18 germanium
30 ELECTROS highest quality
IDEAL FOR SCHOOLS, HOBBYISTS, EXPERIMENTS.

2W+2W STEREO AMPLIFIERS
Volume, tone control all parts on PCB, 2x LM-380 IC's, 12v-18v supply, add only transformer if required (extra $4.50), 100mV input, T.H.D. 1% at 1KHz at 1.5W. Ideal mounting under turntable for cheap home stereo!
$5.95

12V DC RELAYS
10 AMP 3 POLE Contacts
Coil: 110Ω
Small Size
All new, top grade
Popular style.
QTY 1-9 $2 EA
QTY 10-24 $1.80 EA
QTY 25+ $1.70 ea
Be early, limited supply available now.

* * * APOLOGY * * * * *
THE PRICE OF THE HONEYWELL STROBE FLASHER IN LAST MONTH'S ADVERTISEMENT SHOULD HAVE BEEN $14 NOT $1 AS WAS SHOWN - MAL MADE ANOTHER BLUNDER - WE APOLOGIZE FOR ANY INCONVENIENCE
* * * * * * * * * * * * * * *

WOW! ASST. TRANS RADIO OUTPUT & DRIVER TRANNIES 50¢

VALVE OUTPUT TRANNY General Purpose $1 EA

INSTRUMENT CASE $3
Plastic mantel radio cabinets with metal front panel etc.
Size 12"x4½" x 4¾" Few Only

NUMERICAL * KEYBOARD KIT
Ideal for keyless entry lock systems, burglar alarms, all microprocessor applications etc.
Keys 0-9 and CLR key, top quality, low profile, keys are 18mm x 18mm
$5.90 ea.

MAD MAL
c/- PRE-PAK electronics
P.O. BOX 43, CROYDON 2132
718 Parramatta Rd. Croydon NSW
PH: 797-6144 Open 7 Days

Supa-Specials

2 TRANS RADIO KITS $2.50

NEW PUSH-BUTTON PERMEABILITY TUNERS 4 Coils $2
Suit Synchrodynes
MANUAL Tuners $1

¼" TAPE SPLICER $2.50
Cuts & trim Easy to Use

6-10 Henry DC FILTER CHOKES $1
Brand New, Suit most valve TV's etc!

JADE *Computer Products*

EPROM BOARD KITS

RAM'N'ROM (16K any EPROM)	$117.00
MR-8 (1K RAM, uses 2708)	$99.50
MR-16 (1K RAM, uses 2716)	$99.50
EPM-1 (uses up to 4K of 1702)	$59.95
JG8/16 (uses 2708 or 2716)	$69.95

MICROPROCESSORS	
F8	$16.95
Z80 (2MHz)	$20.00
Z80A (4MHz)	$25.00
CDP1802CD	$17.95
2650	$19.95
AM2901	$20.00
6502	$11.95
6800	$16.95
6802	$25.00
8008-1	$12.95
8035	$20.00
8035-8	$21.00
8080A	$10.00
8085	$23.00
TMS9900TL	$49.95
8080A SUPPORT DEVICES	
8212	$2.90
8214	$4.65
8216	$2.75
8224 (2MHz)	$4.30
8224-4 (4MHz)	$9.95
8226	$2.75
8228	$6.40
8238	$6.40
8243	$8.00
8251	$7.50
8253	$20.00
8255	$8.50
8257	$20.00
8259	$20.00
8275	$75.00
8279	$18.50
USRT	
S2350	$10.95
UARTS	
AY5-1013A	$5.25
AY5-1014A	$8.25
TR1602B	$5.25
TMS6011	$5.95
IM6402	$9.00
IM6403	$9.00
BAUD RATE GENERATORS	
MC14411	$10.00
14411 Crystal	$4.95
6800 PRODUCT	
6810P	$4.00
6820P	$6.60
6821P	$6.60
6828P	$11.25
6834P	$16.95
6850P	$8.65
6852P	$11.00
6860P	$9.25
6862P	$12.00
6871P	$28.75
6875P	$8.75
6880P	$2.50
68B10P	$6.00
KIM SUPPORT DEVICES	
6102	$8.00
6502	$11.95
6520	$10.00
6522	$9.25
6530	$15.95
6530-002	$15.95
6530-003	$15.95
6530-004	$15.95
6530-005	$15.95
6532	$17.95
CHARACTER GENERATORS	
2513 Upper (-12+5)	$6.75
2513 Lower (-12∓5)	$6.75
2513 Upper (5 volt)	$9.75
2513 Lower (5 volt)	$10.95
MCM6571 up scan	$10.95
MCM6571A down scn	$10.95
PROMS	
1702A	$8.00
2708	$9.95
2716 (5+12) TI	$25.00
2716 (5v) INTEL	$60.00
2758 (5v)	$23.40
DYNAMIC RAMS	
416D/4116 (250ns)	$12.50
2104/4096	$4.00
2107B-4	$3.95
TMS4027/4096 (300ns)	$4.00
MM5270	$4.50
MM5280	$3.60

STATIC RAMS	1–15	16-100
21L02 (450ns)	$1.50	$1.20
21L02 (250ns)	$1.75	$1.50
2101-1	$2.95	$2.60
2111-1	$3.25	$3.00
2112-1	$2.95	$2.65

FLOPPY DISK CONTROLLERS	
1771B01	$39.95
1781	$69.95
KEYBOARD CHIPS	
AY5-2376	$13.75
AY5-3600	$13.75
MM5740	$18.00
MM5743	$18.00

EXPANDOR'S BLACK BOX PRINTER

This 64-character ASCII impact printer with 80-column capability is portable and uses standard 8½" paper and regular typewriter ribbon. Base, cover and parallel interface are included. Assembled and complete with manual and documentation.

only $430.00
(90 day manufacturer's warranty)

TRS—80 Interface Cable for Black Box Printer
with mating connectors: **$48.00**
(must be used with expansion module, +8v/1 amp power supply required).

Power Supply for TRS—80/Black Box Printer $49.00

★ STATIC RAM SPECIALS ★

2114's, low power (1024x4)

	1-15	16-99	100 +
450ns	8.00	6.95	5.50
250ns	9.00	8.00	6.50
TMS4044/MM5257, low power			
450ns	8.00	7.50	6.50
250ns	9.95	8.75	8.00
4200A (4Kx1, 200ns)			
	9.95	8.50	8.00

Look!

DYNAMIC RAM BOARDS EXPANDABLE TO 64K

32K VERSION • KITS

Uses 4115 (8Kx1, 250ns) Dynamic RAM's, can be expanded in 8K increments up to 32K.

8K	$199.00
16K	$255.00
24K	$310.00
32K	$369.00

64K VERSION • KITS

Uses 4116 (16Kx1, 250ns) Dynamic RAM's, can be expanded in 16K increments up to 64K.

16K	$292.00
32K	$432.00
48K	$578.00
64K	$721.00

JADE PARALLEL/SERIAL INTERFACE

S-100 compatible, 2 serial I/O ports, 1 parallel I/O.

Kit JG-P/S	$124.95
Ass. & Tested JG-P/SA	$179.95
Bare Board with manual	$30.00

FLOPPY DISK INTERFACE

JADE FLOPPY DISK (Tarbell board)

Kit	$175.00
Assm. & Tested	$250.00

S.D. Computer Products "Versa Floppy"

Kit	$159.95
Assm. & Tested	$189.95

STATIC RAM BOARDS

JADE 8K

Kits:	450ns	$125.95
	250ns	$149.75
Assembled & Tested:		
	450ns	$139.75
	250ns	$169.75
Bare Board:		$25.00

16K - Uses 2114's (low power)

Assembled & Tested:

RAM 16 (250ns)	$375.00
RAM 16B (450ns)	$325.00
MEM-2 Kit: 250ns	$285.00

16K with memory management

Assembled & Tested:

RAM 65 (250ns)	$390.00
RAM65B (450ns)	$350.00

32K Static

Assembled & Tested:

250ns	$795.00
450ns	$725.00
250ns Kit	$575.00

ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

JADE *Computer Products*

4901 W. ROSECRANS AVENUE
Department "E"
HAWTHORNE, CALIF. 90250
U.S.A.

Telephone:
(213) 679-3313
Telex:
18-1823

Discounts available at OEM quantities. All prices above are quoted in U.S. $ F.O.B. Hawthorne, Calif., U.S.A. To expedite shipments please include international money order or bankers check payable against any U.S. bank in U.S. $, or use your Barclay, Access or American Express credit card (include card number, expiration date, and signature). Add 20% of total order for postage.

WRITE FOR OUR FREE CATALOG

TRS-80 apple II MEMORY EXPANSION KITS

4116's
(16Kx1, 250ns)
8 for $85.00

TRS—80 KIT
includes connectors and instructions **$98.00**

JADE 8080A

with full documentation

Kit	$100.00
Assm. & Tested	$149.95
Bare Board	$30.00

JADE Z80

with provisions for ONBOARD 2708 and POWER ON JUMP

2 MHz	
Kit	$135.00
Assm. & Tested	$185.00
4 MHz	
Kit	$149.95
Assm. & Tested	$199.95
Bare Board	$35.00

MD-690a CPU BOARD

S-100 Compatible 6800 MPU 1K x 8 RAM, PROM expandable to 10K.
$199.95

Shugart DISK DRIVES

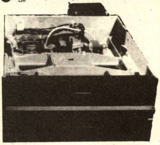

SA 400 **$295.00**
Single-density 5¼", 35 track drive.

SA801R **$495.00**
Single-sided 8" floppy disc drive.

DM 2700-S **$750.00**
Includes SA801R disk drive, 10" x 10" x 16" cabinet, power supply, data cable, fan, AC line filter.

S—100 MOTHER BOARDS

JADE 6-SLOT

Kit	$41.95
Assembled & Tested	$56.95
Bare Board	$24.95

9—SLOT "LITTLE MOTHER"

Kit	$85.00
Assembled & Tested	$99.00
Bare Board	$35.00

13—SLOT "QUIET MOTHER"

Kit	$95.00
Assm. & Tested	$110.00
Bare Board	$40.00

22—SLOT "STREAKER"

Assm. & Tested	$149.00

JADE VIDEO INTERFACE

S-100 Compatible Serial Interface with Sockets Included.

Kit	$117.95
Assm. & Tested	$159.95
Bare Board with manual	$35.00

Video Games

A Major breakthrough in portable electronic fun

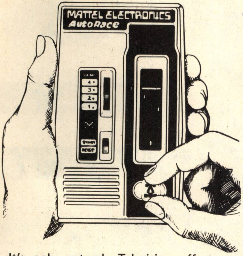

It's only natural. Television affects our lives in an extraordinary number of ways. It is today's major communication vehicle with the world. Innovative scientific efforts have expanded the possibilities of the television receiver console. Teletext, home computers, and programmable video games are just some of the more recent examples.

The Video Trauma

Perhaps most obvious has been the use of television receivers for the playing of video or television games. These games which utilise dedicated chips, often cause family frictions during prime time viewing hours as siblings fight to secure the use of the monitor either as VDU (visual display unit) for game use, or to watch a desired programme on the favourite channel.

The Discovery

MATTEL Scientists realised the possibilities. Using a combination of available microprocessor technology and special miniature circuits, they were able to develop a sophisticated, challenging, portable video game that does not even need a television set.

The Challenge

These little microprocessor marvels are lightweight; you can carry them in your hand, take them out with you to picnics, long car rides, or just sit in the corner while others are watching their favourite television programme.

The Excitement

Beat the Clock!

Shift into first gear and you're off. Dodge the oncoming cars or watch out. You've got just ninety-nine seconds to complete four laps of the electronic track. Hear the roar of the crowd – GO!!

Electronic Video Experience

These electronic games are the latest in a series of space age non video video games, and are backed by the world wide Mattel organisation, so that you may have confidence in the high quality of the product.

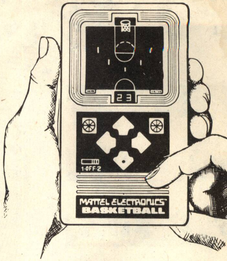

Now for ETI Readers

We have made arrangements with the Caldor Corporation, who represent Mattel in Australia, for them to offer these games to ETI readers at special low prices – $27.95 for Electronic Car Race or Missile Attack, and $34.95 for Basketball, plus $1.50 postage, handling and insurance for each game. To order, simply fill out the coupon and send to: Video Game Offer, Electronics Today, 15 Boundary St., Rushcutters Bay, NSW 2011, enclosing a cheque made out to Video Game Offer for the correct amount. Please allow three weeks for delivery. The offer closes on the 19th January, 1979.

Send to: Video Game Offer, Electronics Today, 15 Boundary St, Rushcutters Bay, NSW 2011.

Please forward:

...... Electronic Car Race Games at $29.45 inc. p&p each ....
...... Missile Attack Games at $29.45 inc. p&p each ....
...... Basketball Games at $36.45 inc. p&p each ....
Total ....

Please make cheques, etc. payable to 'Video Game Offer"

Name ....

Address ....

.... Postcode ....

The offer closes on Friday, 19th January 1979 and is open to Australian residents only.

eti/computerland software contest

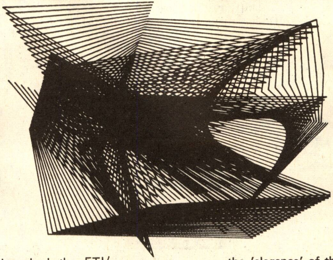

Last minute exhortation! We launched the ETI/ Computerland Software Contest back in April, and since then it seems to have stimulated considerable interest but, frankly, not as many entries as we'd hoped. For this reason, we have decided to set back the closing date of the contest to the 19th of January 1979, and encourage readers to send in their recent software efforts. They don't have to be very complex; quite short programs could well 'scoop the pool'.

We really aren't looking for professional-style brilliance, just software that works and can be used by people to *do* something with their computers.

The type of applications software we're seeking can be anything from a spelling or arithmetic demonstration program or a mortgage repayment program to the kind of sophisticated software we list here:

- * *Mailing list processor.*
- * *Address/telephone file.*
- * *Point of sale terminal.*
- * *Recipe file.*
- * *Inventory control.*
- * *Circuit analysis.*
- * *Music synthesis.*
- * *Calendar/clock/reminder list.*
- * *Chequebook balancing program.*
- * *Applications to help the handicapped.*
- * *Small business accounting package.*
- * *Computer communications set.*
- * *Amateur radio station control.*
- * *Burglar alarm with police notification.*

The idea is to get your computer doing something that is in some way useful. The only stipulation we'd like to make is that software must be written either in BASIC or in the form of a well-annotated assembly language listing for one of the popular microprocessors such as Z-80, 8080, 6800, 6502 and 2650. This means that we stand some chance of running your software to check it out. For the same reason, specialised hardware should be kept to an absolute minimum.

The criteria the judges will use to decide upon the winning entries will be: the value of the software to the user; its complexity, i.e. the size of the program; the 'elegance' of the software; the degree of 'human engineering' in the design of software features; and the quality, amount and presentation of the documentation supplied. It is likely that other factors will also influence the judges to some extent, as different criteria will apply in varying degree to different programs. The judges will be Dr R Graham, of NSW Institute of Technology, Rudi Hoess, of Computerland, and Collyn Rivers and Les Bell of ETI.

The prizes? Overall first prize is a Cromemco ZPU Z-80 CPU card while the second prize winner will receive a Vector Graphics 8K RAM kit. Third prize is a Vector Graphics 260 x 260 graphic display generator and fourth prize is a PROM/RAM card from Vector Graphics. In addition, each of the prizewinners will receive a two year airmail subscription to the US computer magazine of their choice and a two year subscription to ETI.

There will also be three special prize categories — the awards for 'Best Documentation' and 'Most Original Application' will each be a two year subscription package, while the 'Most Marketable Software' winner will, subject to agreement, be marketed on a royalty basis. In addition, the winning entries will be published in ETI, and payment for this will be made at our usual (excellent!) rates.

With the promise of all these super prizes, fame, and fortune, it's well worth while tidying up some of the software you've written recently, writing it up and sending it in. You've got nothing to lose and a whole lot to gain!

The closing date for the contest is now Friday, 19th January 1979, which should give plenty time to 'polish up' existing programs. The winners will be announced in the March or April 1979 issue of ETI, but if (as we hope) there is a lot of entries to be checked this may be delayed.

EMONA *enterprises*

Room 208/661 George Street, Sydney Phone: 212-4815

P.O. Box 188, COOGEE. NSW. 2034.

FOR PROMPT MAIL ORDER SERVICE!

CHECK OUR CHRISTMAS SPECIALS

RUSH WITH YOUR ORDERS NOW!!!!

NEW! NEW! NEW!

Sinclair Digital Multimeters DM235

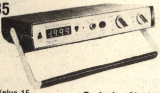

Only $130 (plus 15 percent sales tax)

Exclusive Sinclair 12 months guarantee!

FEATURES:

• 3½ digit resolution • Large, bright, wide angle LED display reading to ± 1999 • Automatic polarity selection • Industry standard 10M ohms input impedance • 0.5 percent of reading basic accuracy • Full multimeter facilities including AC current • Resistance measurement up to 20M ohms. • Direct reading of semi-conductor forward voltages at 5 different currents • Simple, unambiguous controls with readings always in volts, mA or k ohms. • Selection of all functions from a single input terminal pair • Automatic overrange indication • Automatic decimal point placement • Operation from disposable or rechargeable cells, or from AC adapter/charger - • Facility for battery condition test.

Six functions in 26 ranges
DC Volts — 1mV to 1000V; AC Volts — 1mV to 750V; DC Current — 1 uA to 1A; AC Current — 1 uA to 1A; Resistance — 1 ohm to 20 M ohms; Diode test — 0.1 uA to 1mA; 10M ohms input impedance.

Reading rate: 2½ per second
Temperature coefficient: less than 0.05 degrees C of applicable accuracy specification.
Dimensions: 10" x 5.8" x 1.6" (225 x 148 x 40mm)
Weight: Less than 1½ lbs (640 gms)
Sockets: Standard 4mm for resilient plugs, ¾" (19mm) spacing
Power Requirements: Four 'C' or R14 size disposable cells, or approved AC adaptor or Sinclair rechargeable cell pack

Supplied Complete with test leads and prods, and operator's instruction manual
Options A/C adaptor/charger units for 240V; Rechargeable battery pack; Eveready carrying case with neck strap and lead stowage compartment; 30kV High voltage probe.

PDM35

Only ~~$65~~ $55
(plus 15 percent S/T.)

Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment. The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-sized case, ready to go anywhere. **Features:** 3½ digit resolution reading to plus/minus 1999. Automatic polarity selection. 10M ohm input impedance. Full multimeter facilities. Resolution of 1mV and 0.1nA. Semiconductor junction test facility. 1 percent of reading accuracy. Genuine pocket format. **Ranges:** DC volts; 1mV to 1000V. AC volts; 1V to 500V. DC current; 1nA to 200mA. Resistance; 1 ohm to 20M ohms. **Contents:** PDM35; test leads with probes; owner's operating manual — protective carrying pouch. **Power Requirements:** 9 volt transistor radio battery or 9 volt approved AC adaptor.

Exclusive Sinclair 12 month guarantee!

CALCULATORS

from TEXAS INSTRUMENTS

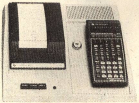

PC100A with TI-58/59

	Excl. S. Tax	Incl. S. Tax
T.I.-25	$32.00	$35.00
T.I.-30	19.00	20.50
T.I.-30 Student Pack	23.00	25.00
S.R.-40	28.00	32.00
T.I.-55	53.00	59.00
T.I.-57	74.00	85.10
T.I.-58	109.00	120.50
T.I.-59	247.00	275.00
T.I.-5050M	81.00	90.00
T.I.-BA Business Analyst	33.00	37.95
Little Professor	16.00	17.90
Data Man	23.00	25.00
T.I.-MBA	75.00	87.40
T. I. Programmer	53.00	59.00
T.I.-MM Money Manager	21.00	23.50
PC-100A Printer	213.00	236.00
Library Modules for T.I.-58/59	31.00	35.00
Blank Mag. Cards for T.I.-59	14.00	16.10
Programming Forms — Pads	2.20	2.80
TP-30250 (3 rolls of paper, PC100A)	10.00	11.50

The new SINCLAIR Enterprise — Programmable!

- Real computing power.
- A comprehensive program library: General, Finance, Statistics, Mathematics, Physics, Engineering and Electronics.

(For more details see Sept. '78 ETI)

Excl. S/Tax **$69** Incl. S/Tax **$79.35**

THE ULTRASLIM NS 108 by National

Semiconductor. For details see Sept. '78 ETI.

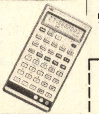

Excl. S/Tax ~~$44~~ **$40** Incl. S/Tax ~~$50~~ **$46**

BMC

LCD-8W, Billfold Pocket Calculator with clock/stopwatch & alarm. (See May '78 ETI)

Excl. S. Tax ~~$41.74~~. $35 Incl S. Tax ~~$48~~ $39

LCD-8M, Billfold Pocket Calculator

Excl S. Tax ~~$16.95~~. $15 Incl S. Tax ~~$19.50~~ $17

1212PD, 12 digit Display Printer

Excl. S. Tax $108.70 Incl S. Tax $125

TRADE ENQUIRIES WELCOME

DIGITAL LCD WATCHES

- Gents, Ladies, Chronographs, Solar, etc.
- LED Digital Clocks
- Check availability of all models before ordering. (See our ad in Nov '78 ETI)

NEW

CORONA

AD 7802 AUTOMATIC TELEPHONE DIALLER

$340
incl s/tax.

Features:

- Dial directly through the keyboard.
- Redial the number only by one touch.
- Automatically repeat the call.
- 40 easy to operate memories to store telephone number.
- Easily connect to any rotary-dial telephone.
- Stand-by power supply for memory protection
- Reliable LSI circuitry.
- Telecom approved.

FRG-7 COMMUNICATIONS RECEIVER ONLY **$339**

NOTE: For all goods; P&P, Int. $3, NSW $2 (up to $50 value) Int. $4, NSW $3 (up to $100 value). Goods valued over $100 delivered by courier — freight paid by receiver.

To: EMONA ENTERPRISES
PO Box 188, Coogee, NSW. 2034.

welcome here

Please send me ....
....
....
I am enclosing cheque ☐ money order ☐
or debit my Bankcard, Number ....
Signature ....
Name ....
Address ....
....
.... P/code ....

THE DICK SMITH CHRISTMAS GIFT SELECTOR

Tear out, encircle the item(s) you want and leave where your wife/husband/in-laws/girlfriend etc, will see it.

AM/FM STEREO CASSETTE

A fantastic NEW AM/FM stereo cassette radio. Has battery or power operation plus demo cassette and a fully comprehensive instruction manual. Look at our price compared to the others.

$149.95 DON'T PAY $200 OR MORE FROM THE OPPOSITION!

Cat. A-4020

AMAZING MINIATURISATION

Contains 1,000's of transistors. . .

NEW

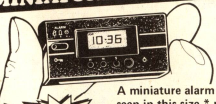

SCOOP PURCHASE
Buy direct from the importer - no duty on this unit. . . .

$29

A miniature alarm clock never before seen in this size * runs on two small batteries for thousands of hours * very loud alarm * complete with dust case and vinyl slip-in case. Cat. X-1042

SUPER THIN CALCULATOR

NEW

Ultra slim (4.5mm) compact LCD type calculator. Not much larger than a Bankcard! Batteries are supplied and will last a long time. Complete 8 digit calculator in case.

Q-3022 $29.50

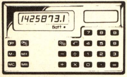

SOLAR TIME

NEW

Cat. X-1040

$39.50

"Right On" is the latest solar watch and Dick Smith has it. There are 6 functions - hours, minutes, seconds, day, month and AM -PM. Ultra thin and stainless steel band plus extra long battery life. For late nighters there is a light built-in.

COMPUTER CHESS

YOUR CHESS COMPUTER COMES COMPLETE WITH BOARD AND CHESS MEN.

Cat. X-1250

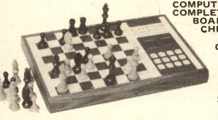

$299

Ideal gift for the person who has everything - incredible computer controlled chess game with three levels of difficulty. Match wits against the computer - YES you can win!

WASP CB

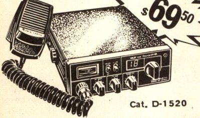

$69.50

Cat. D-1520

18 CHANNEL CB RADIO AT NEAR COST!
What more could you want from a CB radio - the 'Wasp' has LED channel readout plus RF gain control, switchable blanker and noise filter plus many more features that you would expect from a top class CB radio. Not just 90 days warranty either - with the 'Wasp' you get a two year warranty - the set is right and so is the price, don't miss out get your 'Wasp' today

HITACHI 'SCOOP'

Why pay too much for your Hitachi cassettes when you can get them from Dick at a price that won't hurt!

DON'T PAY TOO MUCH FOR QUALITY CASSETTES:

C60LN Cat.C-3060 $1.50ea
C90LN Cat.C-3065 $1.95ea
C60UD Cat.C-3070 $2.40ea
C90UD Cat.C-3075 $2.85ea
Limit 5 per customer.

MICRO CASSETTE

One hand operation * Uses micro cassettes available @ $2.95 ea. Cat. C-3360. Ideal for dictation. Built-in mic. Top Value.

$39

A-4040

RADAR ALARM

$49.50

A-8500

ALL NEW 10 TRANSISTOR MODEL WITH IMPROVED RANGE . . .
Simply clip the Dick Tracer to your sun visor and be prepared for those police radar traps. Built-in rechargeable battery - simply plug into cigar lighter socket and recharge over night.

CASSETTE LIBRARY

NEW

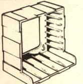

$6.50

BOX OF 6 UNITS.

The new easy mount cassette library * 6 units interlock to give either 30 cassette mountings with case or 48 cassettes without case * supplied with screws for wall mounting.
Cat. C-3800

THE GENTLE ALARM

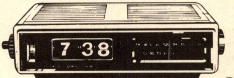

LESS THAN $30!

LIMITED STOCKS. $29.95

Just look at this superb digital leaf movement clock radio for less than $30! Tune into your favourite AM or FM station for a great sound. Use the buzzer or radio to wake you - softly and gently. Cat. A-4446

$24.50
X-1047

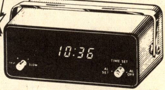

DIGITAL CAR CLOCK

12V DC operation * Use it in your car, boat, plane * Comes in an easy to install case * Crystal controlled digital readout electronic clock with alarm * Why not go digital and be the first in your street!

Cat. X-1045 .. Clock module only $19.50

CLOCK KIT BARGAIN

CHEAPEST WITH SECONDS DISPLAY

NOW $15

Cat. K-3364

FANTASTIC SAVING - WAS $\$29^{75}$

ALMOST HALF PRICE!

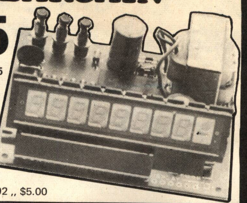

This 240 volt digital clock kit is amazingly simple to build. 12 or 24 hour operation and seconds display with BIG (10mm) bright orange numerals. Kit includes full instructions - build it yourself in a couple of hours!

Handsome plastic case to suit Cat. H-3192 ,, $5.00

Amazing New Multimeter Measures CAPACITANCE Too!

33 RANGES COVER:

DC and AC volts, DC and AC current, resistance up to 50M ohms full scale, Decibels, transistor measurements of h_{FE} and I_{CEO}, plus capacitance from 50pF and up to 50uF. Reverse polarity switch, large 4 colour scale, diode protection plus safety fuse. Complete with 2 sets test leads, batteries and 16 page instruction manual. Why not give yourself a present - you deserve it!

Cat. Q-1140

$\$69^{50}$

RF PROBE

Enables your Q-1140 or Q-1136 to be used as an accurate RF voltmeter up to 30MHz - ideal for CB service work!

Cat. Q-1138 .. .. $12.50

HI-VOLT PROBE

Want to measure TV EHT or vehicle ignition HT? Use this probe to extend the capability of your multimeter to 50kV.

Cat. Q-1025 .. .. $22.50

WATCH THIS SPACE

AND FIND OUT WHAT YOU MISSED

Each month all of our stores feature an outstanding special which is actually BELOW COST! N.B. Specials are strictly while store stocks last. Don't miss out!

LAST MONTH:

A USEFUL ELECTRONIC BUZZER FOR ONLY 55c - Normally $1.75

SAVING $1.20

WHAT'S THIS MONTH'S SPECIAL? CALL IN AND FIND OUT YOURSELF!

WHAT'S NEW?

Get her in the mood

$\$9^{95}$

Set the scene with subdued room lighting. Lamplite dimmer switch plugs into light globe socket of your table lamp, globe plugs into dimmer. Turn the knob to the lighting level you want - and you're away! No wiring necessary - takes lamps to 150W.

Cat. X-1114 .. .. $9.95

Incredibly cheap Mercury switch

$1

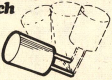

NEW PLASTIC ENCAPSULATION

Ideal for car alarms, cutouts, safety switches. Mercury blob inside switch makes circuit between two contacts when switch is upright, breaks circuit when switch is tilted over. Rugged plastic case. At this price you can afford to buy lots, then figure out all sorts of clever uses for them.

Cat. S-1935 .. .. Bargain at $1.00 ea.

Buy 10 or more and pay 75c ea.

PARTS FOR NEW KITS

PLAYMASTER AM/FM TUNER (See Nov/Dec EA)

Complete kit, including instructions	Cat. K-3494	$159.50
SEPARATE PARTS		
Pre-wired and aligned tuner module	Cat. F-4610	$59.00
Set of 4 PC Boards	Cat. H-8357	$9.75
Signal strength meter	Cat. Q-2100	$4.95
Tuning meter - centre zero	Cat. Q-2095	$4.95

Most other electronic parts for this project in stock.

MODEL TRAIN CONTROLLER (See October EA)

Not produced as a kit – all parts available from stock:

PCB only	Cat. H-8355	$3.75
Zippy box	Cat. H-2752	$3.75
2N3055 transistor	Cat. Z-2145	$0.95
2N3053 transistor	Cat. Z-2130	$0.80

UNIVERSAL MOVIE MIXER (See September EA)

Complete kit, including instructions	Cat. K-3492	$49.50
SEPARATE PARTS:		
PC Board (only)	Cat. H-8354	$2.95
50k A curve 45mm slider pot	Cat. R-1980	$0.85
Knobs to suit slider pot	Cat. H-3780	$0.40

FET INPUT AC-DC VOLTMETER (See September EA)

Not produced as a special kit - all parts available ex-stock:

PC Board (only)	Cat. H-8353	$2.75
1mA MRA-65B panel meter	Cat. Q-2060	$12.50
Fabricate your own meter scale using the Scotchcal process:		
8005 black Scotchcal photo-sensitive aluminium	Cat. H-5694	$6.00
CA-3140 FET op-amp	Cat. Z-5417	$2.50

VARI WIPER Mk 2 (See September ETI)

Not produced as a kit - most parts available from stock:

Relay	Cat. S-7125	$4.80
C106YI SCR	Cat. Z-4315	$1.00
2N2646 (DS2646) unijunction	Cat. Z-1786	$1.20

UPGRADED 40/200MHz FREQ. COUNTER (See August EA)

Same style as previous kit, but new circuitry means it is easier to build, set up and is more sensitive. Basic counter is 40MHz – by adding a single 95H90 IC the range is extended to 200MHz.

Complete kit for 40MHz, inc. instructions	Cat. K-3437	$99.50
95H90 IC to extend range to 200MHz	Cat. Z-5360	$12.50
SEPARATE PARTS:		
PC Boards (set of two high quality boards)	Cat. H-8346	$8.50
MC-10116L IC (triple differential amplifier)	Cat. Z-5415	$1.95
MM-5369M IC (oscillator - divider)	Cat. Z-5781	$2.50
74C926 IC (4 digit counter)	Cat. Z-5414	$6.50
3.579545MHz crystal (new low price)	Cat. K-6031	$3.00
LT-303 7 segment display	Cat. Z-4103	$1.50

All other components are normal stock lines at all of our stores.

PHOTO TACHOMETER (See August EA)

Although we do not produce a full kit for this project, all parts are normal stock lines at all of our stores.

PCB (only)	Cat. H-8352	$1.80
FPT 100 phototransistor	Cat. Z-1950	$2.00

NEW 10 GAME TV GAME KIT (See July EA)

Complete kit, including instructions	Cat. K-3491	$49.50
SEPARATE PARTS:		
PCB (only)	Cat. H-8344	$3.95
Fully built RF modulator	Cat. K-6040	$3.00
Fully built audio modulator	Cat. K-6042	$4.50
AY-3-8600 IC	Cat. Z-6852	$15.00

TANK TV GAME (See October ETI)

Complete kit, including instructions	Cat. K-3475	$39.50
SEPARATE PARTS:		
PCB (only)	Cat. H-8620	$3.85
AY-3-8710 IC	Cat. Z-6856	$17.50
Fully built RF modulator	Cat. K-6040	$3.00
Fully built audio modulator	Cat. K-6042	$4.50

DICK SMITH ELECTRONICS

bankcard welcome here

SYDNEY
125 York Street, SYDNEY. Ph. 290-3377
147 Hume Hwy, CHULLORA. Ph. 642-8922
162 Pacific Hwy, GORE HILL. Ph. 439-5311
30 Grose Street, PARRAMATTA. Ph. 683-1133

MELBOURNE
399 Lonsdale Street, MELBOURNE. Ph. 67-9834
656 Bridge Road, RICHMOND. Ph. 42-1614

BRISBANE
166 Logan Road, BURANDA. Ph. 391-6233

ADELAIDE
203 Wright Street, ADELAIDE. Ph. 212-1962

SHOPS OPEN 9AM to 5.30PM
(Saturday 9AM – 12 noon)
BRISBANE 1/2 Hour earlier.

· ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

Many lines available from the Dick Smith Electronics Centres at

GRACE BROS ®

Broadway · Bondi · Chatswood · Liverpool
Miranda · Mt Druitt · Parramatta · Roselands
and Warringah Mall

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

MAJOR DICK SMITH DEALERS: Listed below are the names and addresses of dealers who stock a large range of our products - however we cannot guarantee that the dealers listed will have all items in stock and at the prices advertised.

Overland Communications	11/53 Wollongong St, Fyshwick ACT. Ph 804307
Brian Bambach Electronics	68 William St, Gosford NSW. Ph 247246
Crystal TV Rentals Pty. Ltd	66 Crystal St, Broken Hill NSW. Ph 6897
D.G.E. Sales	44 Brown Rd, Broadmeadow, Newcastle NSW. Ph 691222
G.M. Electronics	99 Fitzmaurice St, Wagga NSW. Ph 213044
Mid States Radio Pty. Ltd	638 Dean St, Albury NSW. Ph 213888
Sound Components	78 Brisbane St, Tamworth NSW. Ph 661363
Trilogy Electronic Supplies	40 Princes Hwy, Fairy Meadow NSW. Ph 831219
Hunts Electronics	18 Neil St, Toowoomba QLD. Ph 326944
Tropical TV	249 Fulham Rd, Vincent QLD. Ph 791421
Sumner Electronics	95 Mitchell St, Bendigo VIC. Ph 431977
A.E. Cooling	6 Trimmer Rd, Elizabeth South SA. Ph 2552249
Gawler C.B. Centre	51 Hillier Rd, Evanston SA. Ph 222149
Hutchesson's Communications	5 Elizabeth St, Mt. Gambier SA. Ph 256404
Altronics	105 Stirling St, Perth WA. Ph 3281599
Hocks TV Rentals	87 Hannan St, Kalgoorlie WA. Ph 211906
Aero Electronics	123a Bathurst St, Hobart TAS. Ph 348232

425EA1278

SEALED, RECHARGEABLE, MAINTENANCE-FREE BATTERIES...

Internationally accepted YUASA BRAND batteries have such features as —
● no maintenance, never need topping up ● unspillable, may be charged/discharged in any position ● wide range of capacities.

SEALED NICKEL CADMIUM BUTTON CELLS

- Various types available for —
  Standard rate discharge
  High rate discharge
  Trickle charge
- Large range, 1.25 cells available in single or multi cell stacks from 10 MAH to 500 MAH
- May be charged and discharged over a wide temperature range

SEALED NICKEL CADMIUM SINTERED PLATE CELLS

- Various types available for —
  High temperature operation,
  Rapid recharging,
  High rate discharge
- Self resealing gas release safety venting system
- Large range 1.25 volt cells from 140 MAH to 3500 MAH
- 'AA', 'C' and 'D' sizes available

SEALED LEAD CALCIUM BATTERIES

- Long life, 1200 cycles or 5 years float service life possible
- Self resealing gas release safety venting system
- May be continuously cycled or float charged
- May be charged and discharged over a wide temperature range
- Long shelf life, capable of prolonged open circuit standing
- Large range —
  6 volts from 1.2 A.H. to 10 A.H.
  12 volts from 1.9 A.H. to 20 A.H.

ADDRESS ALL ENQUIRIES TO:

New South Wales: I.E.I. Pty. Ltd. 109 Alexander Street Crows Nest, 2065 Phone: 438 2722, 438 2932
Victoria: I.E.I. Pty. Ltd. 29 Stafford Street Huntingdale, 3166 Phone: 544 8411
Queensland: Bob McKnight (Trading) 23 O'Connell Terrace Bowen Hills, 4006 Phone: 52 7600
Western Australia: R.F. Datodi & Associates 16 Prowse Street West Perth, 6005 Phone: 321 4429
South Australia: Aquavia Controls Pty. Ltd. 61A Baden Terrace O'Sullivans Beach, 5166 Phone: 384 1444
Tasmania: George Harvey Electric Pty. Ltd. 76 York Street Launceston, 7250 Phone: 31 6533. 162-164 Argyle Street Hobart, 7000 Phone: 34 2233

IMPORTED BY **CHLORIDE** Chloride Batteries Australia Limited

now the most complete range available in Australia

PCM Explained

Don Rost explains how pulse code modulation will revolutionize the telephone system.

IN THE 19TH CENTURY certain transmission experiments were performed that involved the coding of speech and music into digital electrical signals using telegraphic techniques. The experiments weren't too successful but these were actually early attempts at *pulse code modulation*, a technique that is much used by the telecommunications industry and recently by recording and audio firms. The basic principles outlined here particularly concern the telephone industry but they are basically the same for most PCM systems.

One of the real problems in telecommunications has been noise and crosstalk (a type of noise induced from adjacent channels), problems that are costly, difficult and often impossible to eliminate using analog transmission methods. Because PCM uses digital signals not dependent on signal amplitude, these problems are eliminated to a high degree.

Time Division Multiplexing

Suppose as in Fig. 1 there are three separate phone signals, on three separate "channels," and they are transmitted to their respective destination each down a pair of wires. Further, suppose that these three calls are being made from two cities located 40 km away from each other.

It would be nice if just one cable pair could carry all three calls instead of three separate pairs. There have been different analog techniques for doing this, the one we will concern ourselves with, because it leads us to PCM, is called *time division multiplexing*. We are still talking analog, the speech signals vary in amplitude as the persons are talking. By sampling portions of these signals at regular intervals all three signals can be broken up and sent along the same transmission line. This is illustrated in Fig. 2.

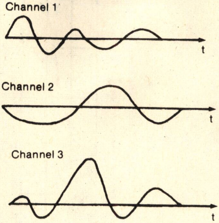

Fig. 1.a. Examples of three signals on separate channels.

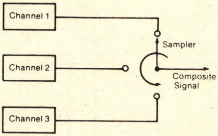

Fig. 1. b. Three channels multiplexed onto a single line by a sampler, here represented as a continuously rotating switch.

This type of composite signal is known as *pulse amplitude modulation* (PAM) because it uses the amplitude samples of the signals multiplexed. The problem with PAM is that it is subject to the same noise and distortion problems as any analog signal. Fig. 10llustrates this. After a signal has travelled a fair distance the signal will have become attenuated to a great degree and will require amplification along the line. Unfortunately, not only will the signal be amplified but also any distortion and noise now associated with the signal.

To get around this problem a method of digitally encoding the signal was developed. Although Alec H. Reeves patented PCM in 1938, it was not until the development of high-speed solid state switching devices and in particular integrated circuits that the system became practical. PCM changes analog signals into digitally coded pulses and then reverses this process at the receiver to recover the original analog signals. This is accomplished in 3 basic operations: sampling, quantizing and encoding. The basic operation is shown in Fig. 3.

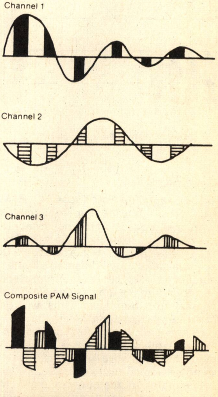

Fig. 2. An example of time division multiplexing using pulse amplitude modulation.

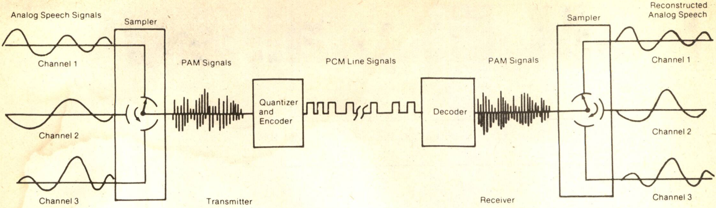

Fig. 3. Basic operation of a time division multiplexed PCM System.

Sampling

For accurate reproduction of the signal a sampling rate of twice the highest frequency is required (this according to a theorem from Nyquist) and in telephone channels this works out to an 8kHz sampling rate. This means that once every 125 microseconds (1/8000s) a channel is sampled. Since telephone lines typically multiplex 24 channels on one line 24 channels are sampled successively in that 125 us time slot, called a *frame*. (Fig. 4)

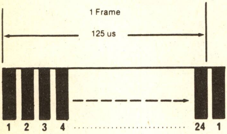

Fig. 4. Twenty four channels multiplexed into 125us "frame".

Quantizing

The sampling produces a PAM signal; to prepare these analog samples for digital processing it is necessary to assign values to each of the samples. This assigning of a value is accomplished by establishing a limited number of levels called *quantum steps* and rounding the amplitudes off to the nearest quantum level. This will be more clearly explained by Fig. 5a.

Channel 3 has samples taken of the following quantum values: 3,5,3,3, 2. A reconstructed wave using just these samples would look like Fig. 5b.

The major source of noise in a PCM system is the *quantizing error* which randomly occurs because the quantum

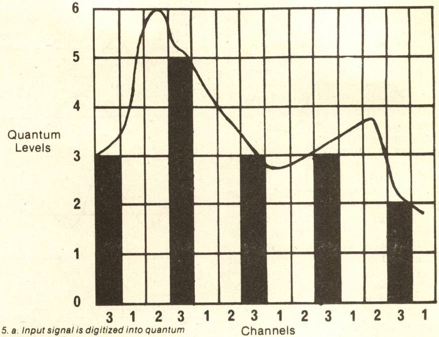

Fig. 5. a. Input signal is digitized into quantum levels on channel 3.

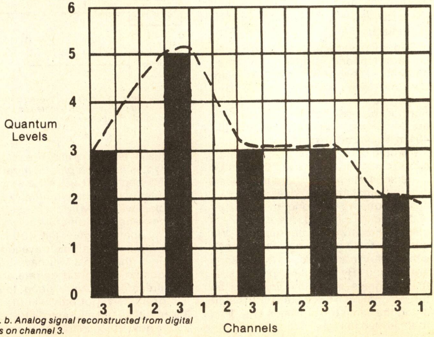

Fig. 5. b. Analog signal reconstructed from digital values on channel 3.

steps are only approximations. By increasing the number of quantum steps the quantizing noise decreases but at the cost of increased bandwidth required in transmitting the data. If quantum steps. are assigned in a straight linear fashion (uniform size) approximately 2048 (11 binary bits) are required to provide sufficient signal fidelity. Such a system, however, is impractical in telecommunications due to the large bandwidth involved. To get around this we can do one of two things. Assign small quantum steps at the low amplitudes where it's needed the most and larger steps to the remainder, or what is usually done, *compress* the amplitude *range* before uniform quantization and then *expand* the signal at the receiving end (*companding*). More gain is applied to weak signals than to stronger ones and typically this reduces the amplitude ratio from 1000 to 1 to 63 to 1 or in terms of dB, from 60dB to about 36dB. By using this technique, the number of quantum steps can be reduced from 2048 to 128 (only 7 bits) with the same noise performance. (Fig. 6)

Coding

Once a numerical value is assigned to the samples we can convert this to a binary form. Since $2^7 = 128$ we need a 7 bit code to represent the 128 different levels. As an example of how this works suppose we wish to represent the quantum level 101 in binary form. In binary, $101 = (1 \times 2^6) + (1 \times 2^5) + (0 \times 2^4) + (0 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0)$. (Fig. 7).

So instead of sending an analog pulse amplitude signal on the transmission line we send its equivalent in binary pulses or if you like, 1's and 0's. Another bit, used for signaling and supervision of the previous channel, is added to make a total of 8 bits per sample; this is actually an older system called the "D1." More commonly used today is the D2 system where all 8 bits are used 5 out of every 6 frames to give a larger quantum range (and therefore less quantum noise in the system). This gives the system 256 quantum levels 5/6 of the time and the one bit in every 6 frames is then used as the signaling bit.

Before sending these pulses one further step is encountered and that is to change the pulses to *bipolar* format. This just means that every other 1 is inverted as in Fig. 8. Now the positive and negative pulses are the 1's and the spaces 0's.

There are several advantages to converting to bipolar format. Most of the energy in the bipolar system is concentrated at ½ the pulse repetition frequency, which results in less energy

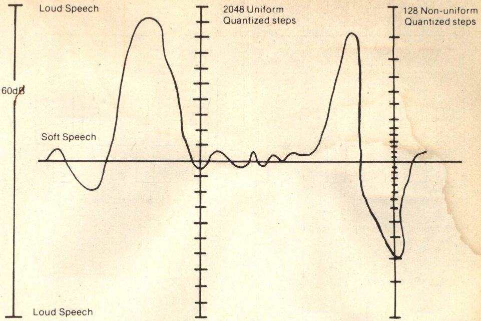

Fig. 6. a. Use of uniform and logarithmic or non linear quantization steps.

Fig. 6. b. An example of compression.

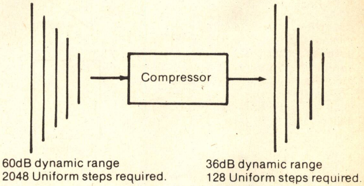

Fig. 7. Quantum level 101 shown in digital form.

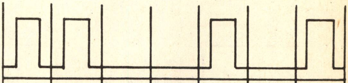

Binary	**1**	**1**	**0**	**0**	**1**	**0**	**1**
Decimal	**64**	**32**	**0**	**0**	**4**	**0**	**1**

Fig. 8. In bipolar format every other binary one pulse is reversed in polarity.

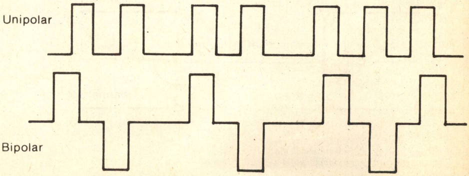

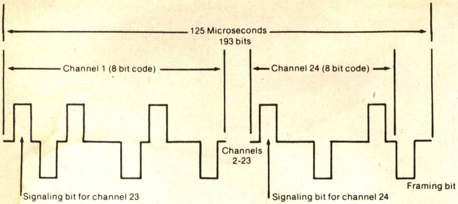

Fig. 9. Typical PCM line signal for a D1 system.

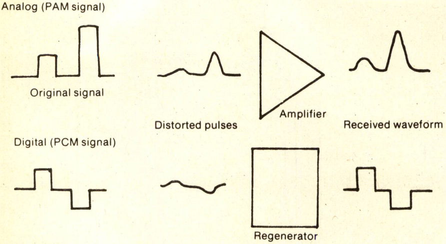

Fig. 10. In a PCM system repeaters regenerate the attenuated signals to look like the original transmitted data.

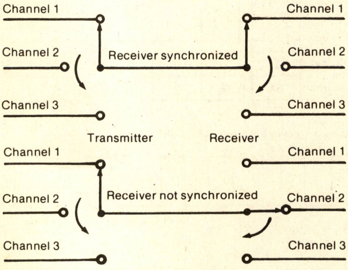

Fig. 11. Inproper synchronization with the transmitter will result in random channel selection.

being coupled into adjacent pairs of wire in the cable as crosstalk. There is no DC component so transformer coupling is possible. And error detection is easy since every other 1 bit will be reversed in polarity.

In every frame one additional bit is added as a *framing pulse* to synchronize the receive system with the transmit. Such a 24 channel system then uses 24 x 8 bits + 1 sync bit for a total of 193 bits. Since the sampling rate equals 8KHz, the transmission rate equals 193 x 8,000 = 1,544,000 bits per second. A typical D1 system line signal would look something like Fig. 9. A D2 system would be similar, except every 6th frame would have the signaling bits instead of every frame as in the D1.

Repeaters

Unlike analog signals that would have to be amplified along with their accompanying distortion, PCM signals are regenerated at repeater stations enroute to their destination. Regeneration involves reshaping the pulses to look like the original signal, so even if the pulses accumulate noise before reaching the repeater the regeneration process cleans them up at each repeater. Remember, in a digital system all that counts is either a pulse or no pulse hence the problem of accumulative distortion and noise are greatly reduced in a PCM system. These repeaters are positioned about every 1.8 km. (Fig. 10)

Receiver

The receive side of a PCM system merely operates in the reverse of the transmit section. The PCM line signal is decoded into PAM and then sampled to each respective channel. The key to PCM operation is synchronization so this is where that extra framing bit is important, without it your call would be randomly selected to any one of the 24 channels. (Fig. 11)

This description of PCM has been basic — the complexity of the logic, the analog-digital and digital-analog conversions, and other intricacies of a PCM system make it impossible to go into any great detail here. It should give you some idea, though, of how this technique has benefited the telecommunications industry and promises the audio one with new avenues to reducing noise. Above all, it should be mentioned that because it is a digital method, PCM or something similar can be used extensively in connection with computer based systems. In addition, with fiber optic systems now being field tested PCM lends itself readily to communication via the light spectrum.

2650 HOBBY COMPUTER THE LOGICAL CHOICE

NEW RELEASE

RA 1000 MICROPROCESSOR CONTROLLED CRT/TERMINAL FULLY ASSEMBLED/TESTED **$325.00**

At last! a versatile, low cost terminal for hobby computer users The RA1000 operates with any monitor or modified TV set offers full keyboard facilities and produces serial ASC11 ready for most microprocessor systems.

The RA1000 uses a SC/MP II microprocessor to control keyboard scanning and VDU update. Internal EPROM program storage makes possible maximum versatility because a simple PROM changeover produces various options such as baud rate selection, alternate scrolling formats, lower case, limited graphics and even baudot operation.

Features:

Full information keyboard (self contained)
110/220 baud operation (easily altered)
64 character, 16 line screen.
x, y cursor addressing (for table updates etc.)
ASC11 bell facility built in.
HORIZONTAL TAB
RUBOUT
CLEAR SCREEN
CRYSTAL CONTROLLED TIME BASE
SELF CONTAINED POWER SUPPLY
ATTRACTIVE ABS CASE WITH METAL BASE.

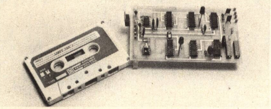

SECI Low Cost Cassette Interface **$24.50**

For the bulk storage of programmes onto tape the SECI kit is ideal. Based on the Kansas City Format the SECI operates reliably from below 110 baud to 1200 baud.

The SECI kit comprises double sided P.C.B. all components and a test tape for easy alignment.

LEVEL A Price $299.00

	NORMAL PRICES
EA VDU Described in EA Feb 78 a Hardware VDU, 16 lines by 32 Characters	**$97.50**
78UT4 KEYBOARD ENCODER KIT Described in EA April 78 ASCII Encoder & Uart for Serial 1/0	**32.50**
KB04 KEYBOARD KIT A 55 Key ASR33 Format keyboard, suitable all micro's	**59.50**
EA 2650 CPU KIT 1K ROM, 1K RAM, Kit expandable to 4K RAM, A great beginners kit.	**55.00**
TRANSFORMER Suitable low profile transformer for micro's.	**17.50**
CASE Low profile case as per Electronics Australia.	**24.50**
GAMES PAK 1 Listing of ten games suitable for use with this system.	**12.50**
PROGRAMMING COURSE Write your own programs after only a weeks study with this course.	**12.50**

LEVEL B Price $449.00

	NORMAL PRICES
RA 1000 Made and tested CRT terminal - see across page under new releases.	**$325.00**
EA 2650 1K ROM, 4K RAM Described in EA May 78 A versatile powerful CPU.	**115.00**
TRANSFORMER S100 Designed outputs are + 5 @ 10 AMPS + 12 and — 12 @ 1 AMP.	**22.00**
SECI Fast Cassette Interface capable of rates up to 1200 Baud.	**24.50**
GAMES PAK 1 Listing of Ten Games lots of fun for all ages.	**12.50**
PROGRAMMING COURSE Learn to write your own programmes an easy to follow course.	**12.50**

LEVEL C Price $699.00

	NORMAL PRICES
KB04 KEYBOARD 55 Key ASR 33 format ASCII Encodable. Ideal kit for any system.	**$59.50**
78UT4 Keyboard Encoder/Uart, 90 key encoder with serial input and output.	**32.50**
KT9500 Full CPU, 1K ROM, 2 1/0 PORTS, TTY and RS232 inputs, easy expansion.	**115.00**
DG640 VDU Software controlled, memory map, 16 x 64 characters, 64 x 128 graphics	**149.50**
RSMB A Motherboard for Ramsticks decodes 16K of RAM, crystal clock	**35.00**
RAMSTICKS 2K VERSION 4 Ramsticks comprising 8K of RAM allows system to use basic.	**198.00**
SECI A Cassette interface can use rates up to 1200 baud to dump and load.	**24.50**
EPS100 A 5v @ 10 AMP power supply also giving + 12 and — 12v @ 1 AMP.	**55.00**
BASIC 4K medium size basic, 10 digit floating point packing and more.	**29.50**
PROGRAMMING COURSE Learn machine language and write your programs after only a week.	**12.50**

APPLIED TECHNOLOGY PTY. LTD.

POST & PACKAGING	**$2.00**	**all orders**
CERTIFIED MAIL	**0.50**	**extra**
REGISTERED MAIL	**2.00**	**extra**

POSTAL ADDRESS—P.O. Box 311, Hornsby 2077
HEAD OFFICE/SHOWROOM—109-111 Hunter St.,
Hornsby (9.00—5.00, MON. to SAT.)

bankcard welcome here

PHONE: (02) 476 4758 General Enquiries — (02) 476 3759 (Technical Information)
PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE

Nimbus Satellites Monitor the Earth

Brian Dance explains how the Nimbus satellites will help us to better understand the ecology of the oceans.

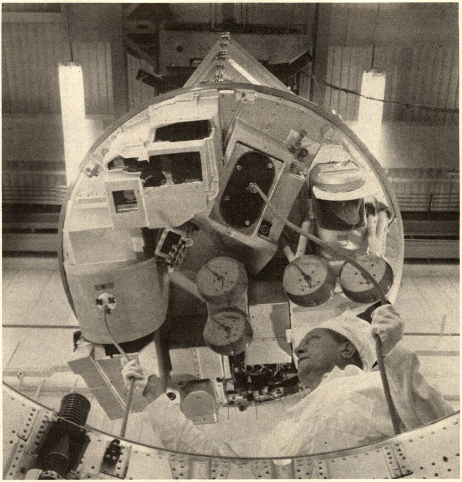

THE NIMBUS-7 SATELLITE launched in September 1978 has joined six earlier Nimbus satellites which relay television pictures, infra-red and ultra-violet data, etc. back to earth. This information is required to enable weather scientists to understand the dynamics of the ocean-atmosphere system and the balance of energy received by and transmitted from the earth. Other applications include such diverse fields as tracking oil spills at sea, monitoring air pollution and helping to locate good fishing areas.

The new satellite has been constructed mainly by the General Electric Company's Space Division at Valley Forge, Pennsylvania. It was launched by a McDonnell Douglas Delta 2910 rocket with 9 Castor II strap-on solid fuel motors into a circular orbit 1 110 km above the earth. This 933 kg satellite is 3.05 m high by 3.35 m wide (with solar panels extended) and has a 1.52 m diameter sensory ring for housing experiments and the electronics. It has an orbital period of 107 minutes.

The primary task of Nimbus-7 is to gather data from the atmosphere, oceans and coastal waters on a global scale from selected regions using 8 sensing instruments. Apart from the U.S., participating nations include Belgium, France, West Germany, Italy, United Kingdom, South Africa, The Netherlands, Switzerland and Canada. The data will be received by earth stations in Alaska, Hawaii, Ascension Island, Guam, Goldstone (California), Quito, Santiago, Orroral and Madrid. This data will be processed and analysed by some 60 members of the Nimbus Experiment Team (NET) in nine different countries.

The CZCS

One of the sensors aboard Nimbus-7 is a "Coastal Zone Colour Scanner" or CZCS which will be made available on a top priority basis for the identification and tracking of oil spills over eleven of the major ocean areas traversed by oil tankers. NASA will support the U.S. Environmental Protection Agency in this application during emergencies.

The CZCS on Nimbus-7 will be used to investigate how well it can detect areas with good fishing potential, measure industrial waste dumping and chemical pollution, offshore sewage outfalls and red tides. In addition, this experimental sensor will map chlorophyll concentration, sediment distribution and temperature gradients of coastal waters and the open ocean. This information can be used to compute the extent of pollution and the location of large fish shoals.

Some of the main areas in which the CZCS will be used in investigations include the Mediterranean coastal waters, the North Sea, the English Channel, the Atlantic Ocean, New England and California river estuaries and coastal waters, the Gulf Stream, the Great Lakes and Cape Hatteras.

Another sensor on board the Nimbus-7 craft will track the earth's energy exchange as an indicator of long term climate changes. This Earth Radiation Budget experiment is designed to measure incoming solar, reflected solar and emitted terrestrial energy simultaneously during different seasons of the year. Other sensors will probe the atmosphere at various altitudes and investigate the sea surface. Gas concentrations and temperature profiles will be monitored, aerosols in the stratosphere measured, ozone mapped, water vapour determined and sea ice observed. A 6 channel infra-red scanning radiometer will be used on the satellite, together with a scanning multichannel microwave radiometer, etc.

Earlier work

The Nimbus programme has compiled more data for the study of the earth's weather and climate from space than any other NASA programme. The six earlier Nimbus spacecraft have transmitted more than 400 000 television images of the earth's cloud cover, provided more than 51 000 hours of infra-red data, more than 42 000 hours of ultra-violet data, more than 185 000 hours of 'sounder' data on atmospheric temperature and pressure, more than 16 000 hours of data on the earth's heat balance and relayed more than 60 000 messages from remote ground and data collection platforms to the receiving stations.

The Nimbus programme began nearly 20 years ago at the General Electronic Space Division and NASA's Goddard Space Flight Centre. Nimbus-1 was launched in August 28th, 1964, but had a much shorter life than the other Nimbus satellites, as shown in Table 1.

The success of the Nimbus craft for providing stable remote sensing platforms for viewing the earth from near space has directly led to the adaption of this type of craft for the development of Landsat craft which have been designed for the analysis and inventory of the natural resources of the land of this planet. Three Landsat craft based on the Nimbus design have been successfully orbited and two of these three continue to provide resource data to some 100 different countries.

A contract has been issued to General Electric for the construction of the first Atmospheric Cloud Physics Laboratory (ACPL) to fly on a future Spacelab Shuttle flight. This vehicle will enable scientists to study the microphysical processes of cloud formation in a manned spacecraft with a gravity reduced environment. *Work has also* commenced on a LIDAR system in which a space borne laser instrument will be used to measure cloud top heights, pollution concentrations, atmospheric aerosols and wind velocities.

One of the major benefits being derived from space research is the more detailed view we are able to obtain of our own planet. Satellites can provide the data we require to predict large floods and hence to save lives.

NIMBUS	Launch date	Active orbital life	Operational orbits	Remarks
1	August 28, 1964	27 days	371	
2	May 15, 1966	2 years 6 months	13 029	Spacecraft retired
3	April 14, 1969	2 years 8 months	13 575	Spacecraft retired
4	April 8, 1970	7 years 4 months	36 923	In reserve
5	December 11, 1972	5 years 8 months	28 100	Still in service
6	June 12, 1975	3 years 2 months	15 746	Still in service

Table 1. List of Nimbus satellites excluding the new Nimbus-7.

Electronics Today International

4600 and 3600

SYNTHESIZERS

Complete plans for the Electronics Today International 4600 Synthesizer are now available in book form.
Many hundreds of these remarkable synthesizers have been built since the series of construction articles started in the October 1973 issue of Electronics Today.
Now the articles have been re-printed in a completely corrected and up-dated form.
The International Synthesizers have gained a reputation as being the most flexible and versatile of electronics instruments available.
They have been built by recording studios, professional musicians, university music departments and as hobby projects.
This book is available now as a limited edition of 2000 copies only.

Ensure your copy!

Send $12.50 to Electronics Today International,
15 Boundary Street, Rushcutters Bay, 2011.

silicon valley

THE STABLE OF THOROUGHBRED MICROS

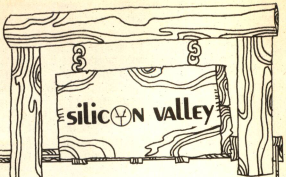

SYM-1 SIRED BY KIM (A SURE STARTER)

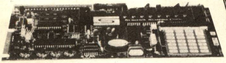

In performance. In quality. In availability. OEMs, educators, engineers, hobbyists, students, industrial users: Our Versatile Interface Module, SYM-1, is a fully assembled, true tested and warranted microcomputer board that's a single-board computer, complete with keyboard and display. All you do is provide a + 5V power supply and SYM-1 gives you the rest.

Key features include:

- Hardware compatibility with KIM-1 (MOS Technology) products.
- Standard interfaces include audio cassette with remote control; both 8 bytes/second (KIM) and 185 bytes/second (SYM-1) cassette formats: TTY and RS232; system expansion bus; TV/KB expansion board interface; four I/O buffers; and an oscilloscope single-line display.
- 28 double function keypad with audio response.
- 4K byte ROM resident SUPERMON monitor including over 30 standard monitor functions and user expandable.
- Three ROM/EPROM expansion sockets for up to 24K bytes total programme size.
- 1K bytes 2114 static RAM, expandable to 4K bytes on-board and more off-board.
- 501/0 lines expandable to 70.
- Single + 5V power requirements.

Price $275 + Tax = $316.25

D2 KIT OUT OF THE MOTOROLA STABLE PROVEN TRACK RECORD

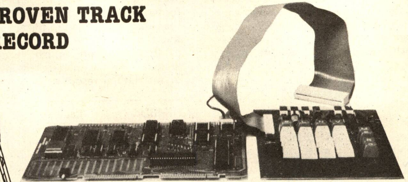

M6800 — FAMILY EVALUATION KIT II

MEK6800D2 provides a useful and expandable tool for those who wish to develop systems with the M6800 Microprocessor without investing in expensive terminals. All parts needed to complete the system and get up and running are provided in the kit with the exception of the power supply. In addition to the expansion available on the basic microcomputer module, additional RAM, ROM and I/O parts can be accommodated at a later date to implement more complex systems. Machine language programmes can be entered through the system keyboard or via a built-in audio cassette interface system. Hexademical LED displays are provided for monitoring data and address information. A crystal-controlled clock generator is used to eliminate timing adjustments.

- JBUG Monitor
  - Trace One Instruction
  - Set up to Five Breakpoints
  - Examine and Change Memory and Registers
- Parallel and Serial Interface Capability
- 161/0 Lines, 4 Control Lines

Price $235 + Tax = $267.25

AVAILABLE AT YOUR NEAREST silicon valley MICRO RANCH

NEW SOUTH WALES

Silicon Valley
Shop 4, PO Arcade, Joyce Street,
Pendle Hill.
Tel: (02) 636 6566

Pre-Pak Electronics
718 Parramatta Road, Croydon.
Tel: (02) 797 6144

Silicon Valley
23 Chandos Street, St. Leonards.
Tel: (02) 439 2965

Madjenk Lighting & Electronics
Shop 5, 246 Princes Highway,
Dapto.
Tel: (042) 61 1785

Martin De Launay
270 Keira Street, Wollongong.
Tel: (042) 28 6020

Applied Technology P/L
109-111 Hunter Street,
Hornsby.
Tel: (02) 476 4758

In-Electronics
84 Ramsey Street, Haberfield.
Tel: (02) 799 3331

Kit-Sets
657 Pittwater Road, Dee Why.
Tel: (02) 982 7500

Rendell Research
Ringwood Road,
Exeter. (Moss Vale)

Serv-U Appliance Centre
107 George Street,
Bathurst.
Tel: (063) 31 1356

A.C.T.

Daicom
29 Colbee Court, Philip.
Tel: (062) 82 3581

KT9500 THE SHORT PRICED FAVOURITE

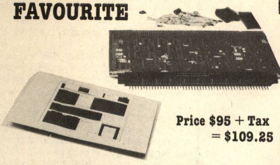

Price $95 + Tax = $109.25

The basic kit consists of a plated-through hole board with component overlay and the mighty 2650 8 Bit Microprocessor, 512 bytes of read/write memory (four 2112 static RAM's), 1K bytes of 2608 ROM with PIPBUB*, two 8T31 1/0 ports and buffering on data, address and control lines. A single + 5 volt supply will be required to power the card and communicate with a serial 20mA current loop terminal.
Modifications to the basic system can be easily made to allow for various memory configurations and operating modes. Unused plated through holes are provided for the PROM memory chips (82S115's). Other options are jumper selectable.

SV640 A SURE WINNER — NO PLACE BETS

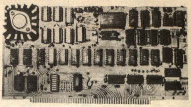

Designed by David Griffiths this superb software controlled V.D.U. kit composes of all components including crystal, IC sockets and top quality plated through hole PCB. Our exclusive 54 page assembly/trouble shooting and software manual is also included. The display format is 16 lines by 64 characters to give upper and lower case letters, reversed video characters (black on white), flashing characters and a graphics resolution of 64 x 128 dot matrix. The unit conforms to the ever increasing popular hobby computer standard S100 bus. **Price $140 + Tax = $149.50**

silicon valley

TM990 /100M-1 A CLEAR WINNER AT 16 FURLONGS

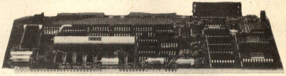

The TM990/100M is an assembled, tested microcomputer module utilizing the powerful NMOS 16 bit TMS 9900 microprocessor as its CPU. With RAM and ROM/EPROM included on board as well as programmable serial and parallel I/0, the TM990/100M is a powerful single board microcomputer. As all address, data and control lines are brought to the board connectors, the board can be expanded to use the entire capabilities of the TMS 9900 in larger systems.

Features

- TMS 9900 16 bit CPU.
- 256 words of 4042-2 (2111-1) Static RAM expandable to 512 words.
- 1K words of 2708 EPROM expandable to 4K words.
- TMS 9901 programmable system interface.
- TMS 9902 asynchronous communications controller.
- EIA or TTY terminal interface option.
- Prototyping area for custom applications.
- Fully expandable bus structure.
- TIBUG operating monitor.

THE BREEDING PASTURE

For the S100 Buss Buff's

PC32KR: 32K Ram Card uses very popular 2114 chips $49.50 + Tax = $54.70

PC16KE: 16K Eprom card takes 2708 $44.75 + Tax = $49.45

PC100MB: 8 Card Motherboard Coming Soon

Literature: We invite you to browse through our extensive range or simply write to us for your free price list.
Software Support: Our growing software library now covers all the above processors right up to high level language on tape for the TM990 and down to simple games packs for the KT9500.

QUEENSLAND
Kit Sets
293 St. Pauls Terrace, Fortitude Valley.
Tel: (07) 52 8391

Hunts Electronics
P.O. Box 546,
Toowoomba.
Tel: (076) 32 9677

Silicon Valley
22 Ross Street, Newstead.
Tel: (07) 52 1339

Technitron
63 Grange Street, Bundaberg.

Southport Electronics Shop
9 Young Street, Southport.
Tel: (075) 32 3632

VICTORIA:
Rod Irving Electronics,
499 High Street, Northcote.
Tel: (03) 489 8131

Stewart Electronics
240b Huntingdale Road, Huntingdale.
Tel: (03) 543 3910

South West Electronics
119 Hopkins Street, Footscray.
Tel: (03) 689 3819

Silicon Valley
380 Bridge Road, Richmond.
Tel: (03) 429 4780

SOUTH AUSTRALIA:
Northern Hi-Fi
Shop 41, Westland,
Whyallm Norrie.
Tel: (086) 45 5766

Kitronics
Peel Street, Adelaide.
Tel: (08) 212 5505

Silicon Valley
170 Sturt Street, Adelaide.
Tel: (08) 51 4080

WESTERN AUSTRALIA:
Atkins Carlyle
1-9 Milligan Street, Perth.
Tel: (09) 321 0101

B.P. Electronics
11 Duke Street, Albany.
Tel: (098) 41 2681

NEW ZEALAND:
Silicon Valley
7-9 Kirk Street, Grey Lynn, Auckland.
Tel: 76 1169

Wind Meter

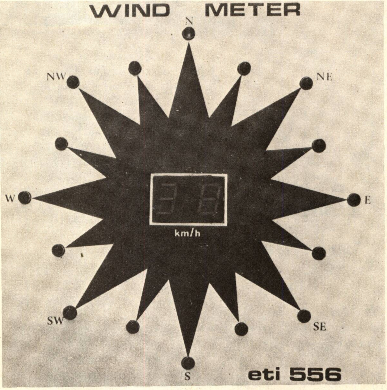

TRADITIONALLY, THE FOUR primary elements are fire, earth, water and air. At ETI, we've designed projects concerned with the first three (temperature meters, soil moisture indicators, rain alarms), but not much for the last. The major property of the air, apart from the fact that it is necessary to support life, is the movement of the air — wind. Light winds generally aren't of terribly much significance except to meteorologists, but stronger winds can be useful as a source of power; for traditional milling, for electricity generation or as a means of propulsion for sailing yachts. Stronger winds such as hurricanes, can be destructive, causing damage to life or property.

So for all the private pilots, yachtsmen, amateur meteorologists and general weather watchers who read ETI, here is a device which will tell you the wind's speed and direction, with a remote indication of both quantities. Our design is, we'd like to think, both stylish and unusual, but there are simpler methods of mechanical construction which you can follow if you wish.

HOW IT WORKS - ETI 556

Wind Direction

Wind direction is indicated by a series of 16 equally spaced LEDs around a circle. These represent the main points on the compass. These are controlled by IC2 and IC4 which are in turn controlled by the direction sensor head.

The sensor head, which is described in fig. 3, consists of a disc which has four optical tracks and four globes and phototransistors. The phototransistors sense either a clear disc (logical "1") or a black disc (logical "0") and thus control IC2 and IC4. The code used is a special one called a "grey" code and is special in that only one bit is changed at each location eliminating gross errors which occur with the binary code if the heads are not perfectly aligned. An example of this is going from location 7 (0111) to location 8 (1000). If this is not done simultaneously almost any location can be specified. With the grey code the same change is from 0100 to 1100. Here there can be no ambiguity as only one bit is changed. Remember these bits are *not* weighted similarly to binary and a lookup table must be used to decide what number (decimal) a particular code is.

The decoder, IC2, is an eight output analogue demultiplexer with the common line joined to the +5v line. When a particular 3 bit code is presented to its control inputs one of the eight outputs will be joined to the +6v line. The fourth output from the sensor head controls IC4 which gives two, inverted, outputs to drive either bank of LEDs. The complete four bit code therefore specifies a particular LED to be lit. By placing the LEDs correctly around the circle the grey code is decoded.

Wind Speed

This is a simple frequency counter measuring pulses from the sensor head. The head consists of a disc with eight holes which breaks a light beam to its associated phototransistor. The output of this phototransistor is squared up by a schmitt trigger formed by IC5 c, d.

The counting is done by IC8a and IC8b (a dual decade counter) with IC6 and IC7 providing the store and LED drivers necessary to drive the seven segment display. Time base is provided by IC3 which gives a 7 ms wide negative pulse about every one second. We say about as it is adjustable by RV1 as individual heads will have different responses and calibration will be necessary.

This negative pulse opens the store to allow the number reached by the counters to be displayed while simultaneously stopping any further counting by disabling the schmitt trigger. On the completion of the 7 ms pulse IC5 a, b generate a $50\mu s$ wide pulse which resets the counter ICs to recommence the sequence.

Power Supply

This is simply a full wave rectified supply with IC1 giving a regulated +6v output. This regulation is needed to ensure that the time base (IC3) remains accurate).

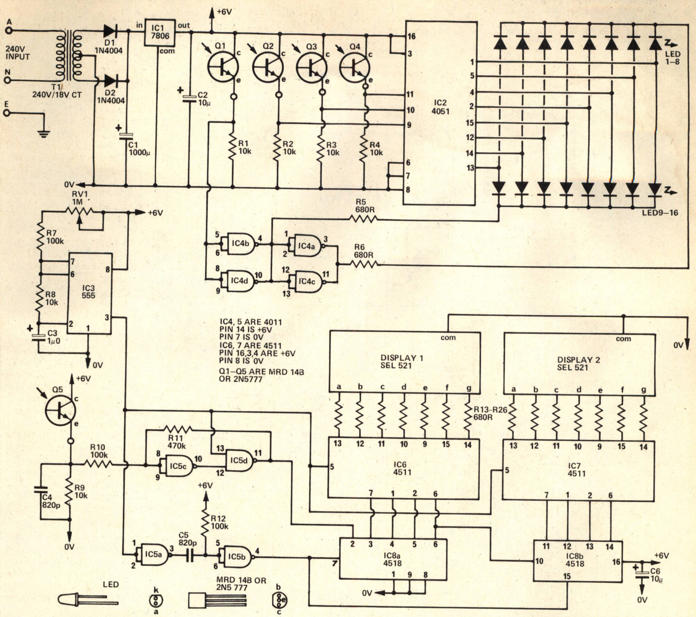

Fig. 1. The circuit diagram of the wind meter.

SPECIFICATION – ETI 556

Wind speed	
Speed range	0 – 99 km/h, knots or mph
Resolution	1 km/h, knot or mph
Display	2 digit LED
Direction	
Resolution	22½ °
Display	16 LEDs
Power supply	240 V ac or 8 to 14 V dc at 350 mA

Fig. 2. The component overlay for the pc board.

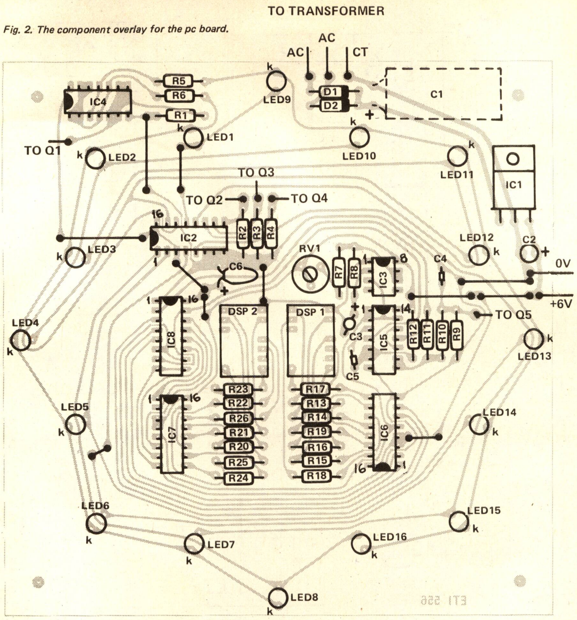

PARTS LIST – ETI 556

Resistors all ½W, 5%

R1–R4	10k
R5,6	680R
R7	100k
R8,9	10k
R10	100k
R11	470k
R12	100k
R13–R26	680R

Potentiometer

RV1	1M trim, type VTP

Capacitors

C1	1000µ 16V electro
C2	10µ 25V "
C3	1µ0 25V "
C4,5	820p ceramic
C6	10µ 25V electro

Semiconductors

IC1	7806 regulator
IC2	4051 multiplexer
IC3	555 timer
IC4,5	4011 NAND gates
IC6,7	4511 decoder-driver
IC8	4518 dual counter
Q1–Q5	2N5777
D1,2	1N4004
LED1–LED16	Red LEDs
Disp. 1,2	SEL521

Miscellaneous

PC board ETI 556
four minature 12V globes
240V/18V CT Transformer
head assembly
front panel and box

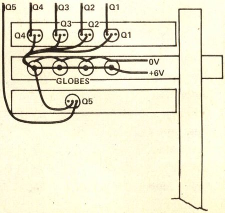

Fig. 3. The connection of the globes and phototransistors in the head.

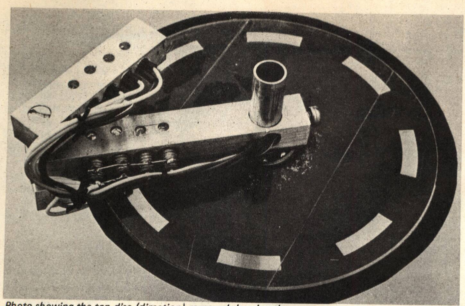

Photo showing the top disc (direction) removed showing the globes and the holes to pass light to the transistor.

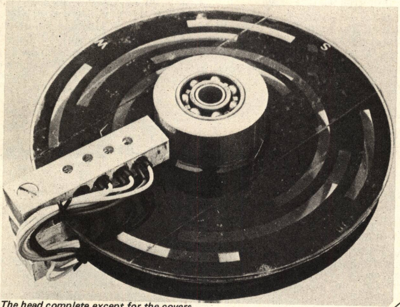

The head complete except for the covers.

The Head

The drawings along with the photos will give the general design that we used. The actual dimensions have to be left to the individual constructor as components such as the ball races and light globes may vary in size.

While we used a single head for both speed and direction, it may be simpler to use separate heads.

The discs we used were 1.5mm thick clear plastic with a piece of photographic film glued onto it. It may be easier to make it out of thin aluminum and cut out the slots. For the speed disc simply drilling holes will suffice.

The most important part of the design, apart from ensuring that the discs rotate with a minimum of friction, is the shielding of the light and preventing light scatter striking a transistor which should be dark. As can be seen from the photos and diagram the globes and transistors are imbedded in aluminum blocks with small holes providing a passage for the light beam.

The wiring of the head is shown in fig. 3. Note that the base lead is not used and can be cut off close to the body. Insulate the joints onto the transistors to ensure that they do not short on the aluminum blocks. The globes may touch the block with their outer connection but this is the 0 volt line and does no harm. In fact it provides some electrical shielding for the leads. The globes we used were 12V but they were bright enough on 6V giving a much longer life.

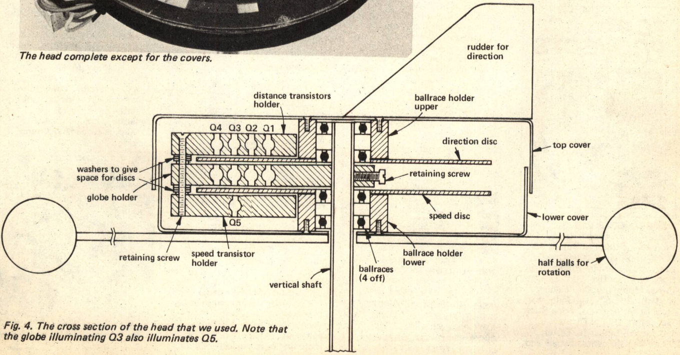

Fig. 4. The cross section of the head that we used. Note that the globe illuminating Q3 also illuminates Q5.

Design Features

When we started design on this project it was to have a digital readout of wind direction with a resolution of either one or two degrees. This would also make it useful in a sailing boat to tell the wind direction relative to the heading.

Difficulties however soon became apparent. The first of these was the sensor head. The only accurate method is a digital head, probably optical. Two methods could have been used, one using a disc with a single optical track of 360 slots and an updown counter and the second using eight or nine tracks in a grey code. The first is simpler in head design but the second is less prone to error. The problem, and the reason for rejecting both, is that with such resolution, the reading would move around so much when the wind is gusty to be unreadable. What is needed is an averaging circuit which unfortunately becomes difficult when the wind is changing from just west of north to just east of north, i.e. 355 to 005. How do you average these (use a microprocessor?).

As this was intended to be a simple project we relaxed our original specification, deleting the use in a boat (we may get back to this problem. A four track 'Grey' scale allows the wind to be given to within 11° of its true heading, without the complexity of a nine track one, and the use of LEDs to give direction solves the problem of averaging as the variations can be seen and averaged by the brain.

Construction

The electronics is relatively simple provided the pc board described is used. Due to a height limitation C1 should be mounted on the rear of the board. The LEDs should be mounted about 7 mm from the board with care being taken not to damage them as the leads have to be bent out slightly. The regulator also has to lie down to give clearance.

We mounted the unit behind an aluminium front panel with the LEDs protruding through holes. If this is to be done it is preferable not to solder the LEDs until after alignment with the front panel.

The head is more difficult as some mechanical ability is necessary to ensure good results. The requirements are basically simple. A disc is to be allowed to rotate, either continuously with the wind or aligning it to the wind, with a globe(s) on one side and phototransistors on the other.

The method used by us is shown in fig 4 with the aluminium blocks providing the shielding necessary to give accurate results. As the unit will be exposed to the weather it must be made waterproof otherwise the ball races will corrode. The races used will normally have to be washed out to give low enough friction with a light spray of WD40 or similar to give some protection.

While our housing is a little ornate, it did work but the more usual half ping pong balls may be more suitable.

Calibration

Wind Speed.

The easiest method for wind speed calibration is to provide the unit with a dc supply (via the common and one of the ac inputs) and to take a drive in the car with the unit supported above the vehicle. Providing there is no wind the potentiometer should be adjusted until the reading corresponds to the speedo.

Direction alignment is simply a matter of aligning the vertical rod so that it gives the correct results.

●●●●●● ETI PROJECTS ●●●●●●

Reprints of many of our most popular projects are available in book form. Top Projects Vols 3 and 4 and our Test Gear book are available from most newsagents or directly from us. Our address is:— Electronics Today International, 15 Boundary Street, Rushcutters Bay, NSW. 2011. The Synthesizer book is available only from us and a limited number of specialist suppliers — it is not sold by newsagents.

TOP PROJECTS VOL 3
Published in October 1976. Projects include FM Tuner. 25 Watt Amplifier, Active Crossover. Crossover Amplifier, Booster Amplifier, 50 Watt Power Module, 400 Speaker System, Audio Noise Generator, Dual Beam Adaptor, Tone Burst Generator, Digital Display, ETI Utiliboard, Linear IC Tester. $2.50 plus 40 cents postage and packing.

TOP PROJECTS VOL 4
Published in June 1977. Projects include Audio Expander/Compressor, 50-100 Watt Amp Modules, Stereo Amplifier, Dynamic Noise Filter, Audio Phaser, Audio Limiter, TV Game, Swimming Pool Alarm, Train Controller, Car 'Scope Testing. Temperature Alarm, Active Antenna, GSR Monitor. $3.00 plus 40 cents post and packing.

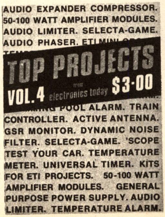
AUDIO EXPANDER COMPRESSOR.
50-100 WATT AMPLIFIER MODULES.
AUDIO LIMITER. SELECTA-GAME.
AUDIO PHASER. ETI MINI ORG
TOP PROJECTS
VOL. 4
from electronics today
$3·00
POOL ALARM. TRAIN
CONTROLLER. ACTIVE ANTENNA.
GSR MONITOR. DYNAMIC NOISE
FILTER. SELECTA-GAME. 'SCOPE
TEST YOUR CAR. TEMPERATURE
METER. UNIVERSAL TIMER. KITS
FOR ETI PROJECTS. 50-100 WATT
AMPLIFIER MODULES. GENERAL
PURPOSE POWER SUPPLY. AUDIO
LIMITER. TEMPERATURE ALARM.

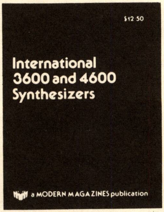

INTERNATIONAL 3600 AND 4600 SYNTHESIZERS
A totally revised and updated reprint of ETI's phenomenally successful music synthesizer book.
This book has been beautifully printed on heavy art paper and has a sturdy cover varnished for protection.
Available only from ETI and some kit set suppliers $12.50 including postage and packing.

TEST GEAR
Published in June 1977. Thirty metering and power supply projects including Audio Level Meter, Impedance Meter, Audio Millivoltmeter, Simple Frequency Counter, Phase Meter, Temperature Meter, Audio Signal Generator, Tone Burst Generator, Cross Hatch/Dot Generator, RF Signal Generator, Logic Probe. $3.00 plus 40 cents post and packing.

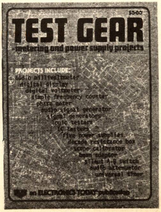

exact original replacement Japan-made semiconductors!

Available in Australia

FUJITSU
PRICE
2SD173
EXACT REPLACEMENT SILICON TRANSISTOR
2SD173
A Quality Product of Japan
369
EPLACEMENT TRANSISTOR
39
TOSHIBA
2SC372
EXACT REPLACEMENT SILICON TRANSISTOR
2SC372
SA672
T REPLACEMENT ILICON TRANSISTOR
2SA672

Now you can obtain exact original replacement Japan-made semiconductors to service CB's, Hi-Fi Equipment, TV's, Car Radio/Stereos, Industrial and Professional Electronic Equipment manufactured in Asia.

Available in large or small quantities, the extensive availability includes over 2,000 items from Japan's leading original manufacturers — Sanyo, Toshiba, Hitachi, NEC, Toyo, Matsushita, Sony, Sanken, Oki, Fujitsu, etc.

Items ex stock will be despatched within 48 hours; items not immediately available will be ordered ex Japan by Air Mail delivery and should be received within max. 4-6 weeks.

CUT OUT THIS PAGE AND KEEP FOR FUTURE REFERENCE

Due to advertising lead times and international exchange rate fluctuations, prices are subject to change without notice.

2SA 329	0.66
2SA 483	7.00
2SA 484	3.91
2SA 493	0.78
2SA 495	0.44
2SA 496	1.24
2SA 550	1.30
2SA 562	0.52
2SA 564	0.40
2SA 606	3.44
2SA 607	3.92
2SA 634	1.28
2SA 640	0.64
2SA 671	1.87
2SA 673	0.56
2SA 678	0.84
2SA 683	0.72
2SA 684	0.73
2SA 697	0.78
2SA 705	1.03
2SA 706	2.12
2SA 715	1.37
2SA 719	0.56
2SA 725	0.54
2SA 733	0.49
2SA 740	4.37
2SB 54	0.52
2SB 56	0.52
2SB 324	0.66
2SB 435	2.10
2SB 507	4.56
2SB 514	2.12
2SB 523	1.51
2SB 526	1.58
2SB 527	1.70
2SB 528	1.84
2SB 529	1.30
2SB 536	1.70
2SC 372	0.32
2SC 380	0.40
2SC 403	0.61
2SC 458	0.40
2SC 461	0.42
2SC 495	0.83
2SC 496	1.08
2SC 509	1.34
2SC 535	0.52
2SC 536	0.37
2SC 538	1.10
2SC 563	1.34
2SC 620	0.61
2SC 645	1.20
2SC 674	0.61
2SC 681	4.90
2SC 710	0.39
2SC 711	0.37
2SC 712	0.39
2SC 730	6.44
2SC 732	0.46
2SC 734	0.61
2SC 735	0.46
2SC 738	0.49
2SC 741	0.42
2SC 756	3.91
2SC 772	0.56
2SC 784	0.52
2SC 789	1.84
2SC 799	9.89
2SC 815	0.73
2SC 828	0.30
2SC 829	0.32
2SC 839	0.40
2SC 840	3.11
2SC 867	12.07
2SC 897	5.48
2SC 930	0.39
2SC 933	0.43
2SC 945	0.28
2SC 959	2.32
2SC 960	2.72
2SC 973	32.20
2SC 995	2.72
2SC 1000	0.46
2SC 1011	16.36
2SC 1013	1.10
2SC 1017	1.42
2SC 1018	1.89
2SC 1030	4.11
2SC 1034	12.65
2SC 1060	1.65
2SC 1061	1.65
2SC 1096	1.42
2SC 1098	1.54
2SC 1114	11.04
2SC 1116	1.17
2SC 1128	1.17
2SC 1129	1.30
2SC 1162	1.30
2SC 1166	0.76
2SC 1169	4.14
2SC 1172B	13.23
2SC 1173	1.17
2SC 1175	0.71
2SC 1195	8.74
2SC 1211	0.54
2SC 1212	1.42
2SC 1213	0.52
2SC 1226	1.15
2SC 1239	4.32
2SC 1243	1.22
2SC 1295	7.13
2SC 1306	2.12
2SC 1307	7.59
2SC 1312	0.37
2SC 1317	0.46
2SC 1318	0.66
2SC 1345	0.54
2SC 1358	15.76
2SC 1364	0.54
2SC 1407	1.10
2SC 1419	1.44
2SC 1444	4.97
2SC 1446	1.54
2SC 1447	1.58
2SC 1448	2.95
2SC 1449	0.86
2SC 1475	1.17
2SC 1509	0.88
2SC 1520	2.08
2SC 1550	1.65
2SC 1624	1.89
2SC 1628	1.70
2SC 1669	2.36
2SC 1674	0.49
2SC 1675	0.37
2SC 1678	2.48
2SC 1728	1.42
2SC 1760	1.39
2SC 1909	4.14
2SC 1951	1.42
2SC 1957	0.98
2SC 1964	0.25
2SC 1969	6.90
2SC 1974	2.76
2SC 1975	2.95
2SC 2028	1.27
2SC 2029	0.24
2SC 2091	1.44
2SC 2092	3.54
2SD 198	3.30
2SD 199	5.06
2SD 213	12.42
2SD 234	1.42
2SD 235	1.77
2SD 313	1.72
2SD 315	2.22
2SD 325	1.34
2SD 330	1.70
2SD 350	9.66
2SD 358	1.75
2SD 359	0.98
2SD 360	1.10
2SD 361	1.58
2SD 380	12.65
2SD 388	6.56
2SD 389	1.68
2SD 525	2.36
2SD 526	1.88
2SK 19	0.90
2SK 30A	0.90
2SK 40	1.03
2SK 49	1.12
3SK 45	2.08
BA 301	1.89
BA 511A	3.54
BA 521	4.14
AN214Q	3.66
AN 214P	3.78
AN 239	11.50
AN 217	3.07
AN 241	3.54
AN 245	7.59
AN 247P	6.90
AN 264	3.30
AN 277	3.54
AN 313	9.78
AN 315	4.26
AN 331	9.66
AN7115	3.68
AN7150	4.26
HA1137W	5.02
HA1156W	3.54
HA1199	3.84
HA1306W	4.44
HA1322	5.02
HA1342AR	4.58
HA1452W	2.90
SAS560S	5.32
SAS570S	5.32
TBA810SH	4.14
M5115AP	7.59
M5152L	2.08
M5153P	8.40
M51513L	3.54
M51515L	6.67
M51841P	3.30
M5320P	1.03
M53273P	1.84
M53274P	1.84
M53393P	5.98
UPC554C	2.95
UPC574J	1.61
UPC575C2	2.79
UPC1009C	6.00
UPC1020H	4.03
UPC1025H	3.11
UPC1028H	2.83
UPC1156H	3.80
TA7045M	3.57
TA7074P	8.51
TA7120P	1.58
TA7200P	5.29
TA7201P	5.59
TA7202P	5.87
TA7203P	5.18
TA7204P	3.80
TA7205P	4.10
TA7214P	9.62
TA7222P	4.56
TA7310P	2.17
LA1201	2.95
LA3300	4.65
LA3301	3.42
LA3350	4.65
LA4030P	3.80
LA4031P	3.68
LA4032P	4.83
LA4050P	3.91
LA4051P	4.32
LA4400	4.95
LA4430	4.14
STK011	9.66
STK015	11.04
STK016	13.62
STK024	20.04
STK433	12.88
STK439	19.55
MB3705	3.45
MB3708	3.45
MB3712	3.30
MB3713	3.30
PLL02AG	12.19
SG613	13.80

Orders over $25, less 10 percent — over $50, less 15 percent — over $100, less 20 percent — over $250, less 25 percent.
Pack, Post and Handling Charge — $2 all orders. All enquiries must include SAE for fast reply.

SEMICONDUCTOR IMPORTS

P.O. BOX 43, NSW
CROYDON 2132

SAVE TIME, TROUBLE
Buy mail order from

East Side Hi-Fi

159 Oxford St,
Darlinghurst,
NSW. 2010.

Should you require a quotation on any hi-fi equipment, please write with details of equipment you wish to purchase.

AMPEX BRAND CASSETTE TAPES AND REEL-TO-REEL TAPE

Size	Type	Ea.	Ctn. of 20 Pcs.
C-45	Plus Series (Low Noise Quality)	$1.70	$32.00
C-60	Plus Series (Low Noise Quality)	$2.00	$36.00
C-90	Plus Series (Low Noise Quality)	$2.50	$48.00
C-120	Plus Series (Low Noise Quality)	$3.50	$68.00
C-45	20/20+ Series (U.D. Quality)	$2.00	$36.00
C-60	20/20+ Series (U.D. Quality)	$2.50	$46.00
C-90	20/20+ Series (U.D. Quality)	$3.25	$60.00
C-120	20/20+ Series (U.D. Quality)	$4.00	$76.00
Cassette	Headcleaner and Demagnetizer	$6.90	T.B.A.
7'' x 1200ft	(Low Noise Quality)	$7.50	T.B.A.
7'' x 1800ft	(Low Noise Quality)	$9.50	T.B.A.
7'' x 2400ft	(Low Noise Quality)	$11.50	T.B.A.
7'' x 1200ft	20/20+ Mastering Tape	$10.00	T.B.A.
7'' x 1800ft	20/20+ Mastering Tape	$12.50	T.B.A.
10'' x 3600ft	20/20+ Mastering Tape	$29.00	T.B.A.
45 min.	Cartridge Tape	$3.80	$70.00
90 min.	Cartridge Tape	$4.50	$80.00

*Please add 10 percent to above prices for orders under $100.00 and 5 percent for orders over $100.00 to cover the cost of Packaging and Freight.

MAIL ORDER ADDRESS:
PO Box 360, Darlinghurst, NSW. 2010.
Ph: 546-7644, 357-6786.
Telex: AA21338.

KNOCK DOWN FURNITURE UNIT

Size: L.1210mm D.395mm H.670mm
Top Quality with adjustable bottom shelves.
Normal Price $139 our Special Price $85
Colour: Walnut
Freight anywhere in Australia $5

Deitron 4 Channel Tuner/Amplifier
10 watts R.M.S. each Channel
AM/FM/FM Stereo Tuner incorporated.
Only $239 Full Warranty
Model DQA-4010.
Freight anywhere in Australia $5

CB ACCESSORIES CLEARANCE **BY MAIL ORDER**
ALL COMPONENTS GUARANTEED 1ST QUALITY MADE IN JAPAN

S0-239 Coax Socket........65c ea. or $5 for 10
PL-259 Coax Plug........65c ea. or $5 for 10
Double Female Joiner........75c ea. or $6 for 10
Lightning Arrester........$1.50 ea. or $12 for 10
Dummy Load — 5 watts........$1.50 ea. or $12 for 10
4 Pin Microphone Plugs........90c ea. or $8 for 10
Right Angle Elbow Joint........$1.50 ea. or $12 for 10
3.5mm Large Body Plug........20c ea. or $1.50 for 10
Magnetic Microphone Holders........50c ea. or $4.50 for 10
2 Amp 3AG Fuse........10c ea. or $8 for 100
100 meter Rolls RG-58 Coax Cable........$25 roll or $100 for 5 rolls
Engine Hot Line Filter........$1.50 ea. or $12 for 10
T.V.I. High Pass Filter........$1.30 ea. or $11 for 10
T.V.I. Low Pass Filter........$4.50 ea. or $40 for 10
CB Lock Mount........$4. ea. or $30 for 10
CB Base Station Antenna........$20 ea. or $90 for 5
Power Supply Chassis Only........$15 ea. or $50 for 4

*Please add 10 percent to above prices to cover packaging and postage for all orders under $100 and 5 percent for orders over $100.

CLEARANCE SALE ON GARRARD TURNTABLES
BY MAIL ORDER

CC-10: Rim Drive Chassis Only w/Ceramic Cart. $15
6200: Rim Drive Chassis Only No Cartridge......$20
65B: Rim Drive Chassis Only No Cartridge.......$35
GT-55: Full Auto Belt Drive w/Shure 756S Cart. $260
DD-75: Direct Drive w/Shure 756S Cart. $250

N.B. GT-55 and DD-75 come complete in base and lid fully imported.

Please add $2 for freight on CC-10, 6200 and 65B and $5 freight on GT-55 and DD-75.

L & D HIGH FIDELITY LOUDSPEAKER **BY MAIL-ORDER**

N.B.: All speaker systems sold by mail subject to customer being satisfied with product within 7 days of delivery. Full refund guaranteed if not satisfied.

10'' 3-way	30 watt R.M.S.	H.610	W.360	D.270	$225 pr
12'' 3-way	40 watt R.M.S.	H.685	W.360	D.270	$270 pr
12'' 4-way	50 watt R.M.S.	H.685	W.390	D.340	$250 pr
15'' 3-way	60 watt R.M.S.	H.795	W.510	D.360	$615 pr

Brand new with 5 year manufacturers guarantee. Please add $10.00 per pair for delivery in N.S.W., Vic., Qld and $15.00 per pair for delivery in S.A., N.T. and W.A.

COMPONENTS SPECIALS —
ALL BRAND NEW

Valve Tuners Black/White ......$2.50 ea
Transistor Tuners B1/Wh.......$5.00 ea
11'' Picture Tubes B1/Wh. ....$12 ea
Yoke for above.......................$5 ea
3 x 4 T.V. Speaker..............$1.50 ea
Dual Base and Lid ....$18 ea
Garrard Base and Lid..........$18.00 ea
B.S.R. Base and Lid..............$18 ea.
C6MR 6'' Midrange Speaker......$8. ea
8'' Goodmans Speaker...........$10 ea
6'' Goodmans Speaker...........$6. ea
DT3 Goodmans Dome Tweeter...$9 ea.
5'' Philips Midrange................$9 ea.

N.B. All above freight free anywhere in Australia.

Project 812

WHEEL OF FORTUNE

Take a gamble on this project.

ELECTRONIC BLACKJACK machines, pinball tables with an MPU at their centre – the world of electronics has a lot to answer for. Is nothing sacred?

The answer to that last question as far as we at ETI are concerned is not a lot. We've taken the liberty of implementing that traditional fairground attraction, the Wheel Of Fortune, in our own electronic fashion. The game usually features a large wooden wheel and ratchet arrangement, the stall either accepting bets on which of the ten numbers will be used the pointer when the wheel stops, or perhaps, suggesting that a message under the pointer will give an indication of what the future holds in store for you – you will meet a tall dark stranger, you will marry young and 2.4 mortages, etc.

Cross My Palm

Our game accurately mimics the real thing, the circle of LEDs similating the spin of the Wheel getting under way as a pair of touch contacts are crossed with your palm (or more likely finger). The movement of the LEDs will then slow down to what seems an excrutiatingly slow speed until it finally stops. All this visual activity is at the same time accompanied by a clicking sound that simulates the ratchet sound of the real game.

It's easy to become a trifle blase about electrical games, particularly in the face of the never ending stream of things that we see in the shops at present, but even the most hardened people, and we've got some fairly hardened people here at ETI, found the Wheel of Fortune to be fun. If you start thinking about building it now it might just get finished for Christmas.

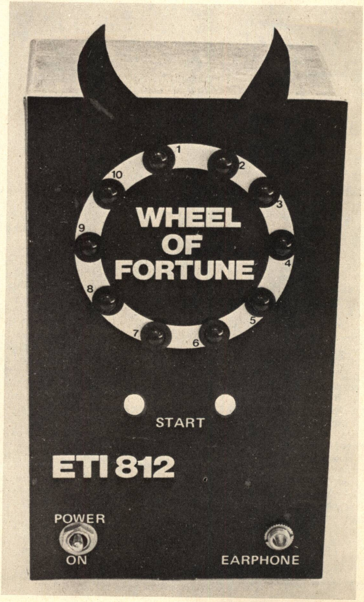

WHEEL OF FORTUNE

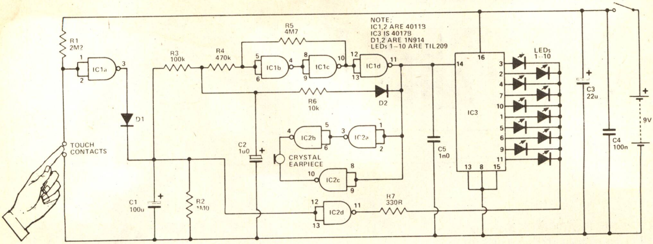

Fig. 1. Circuit diagram of the Wheel of Fortune.

HOW IT WORKS – ETI 812

THE Wheel of Fortune circuit can be broken down into a number of distinct sections; the display circuitry, an audio stage, a VCO, and a touch senstiive/monostable configuration.

In the "off" state R1 holds the input of IC1a high and hence the output of this gate, wired as an inverter, is low and C1 is discharged. Bridging the touch contacts causes the gate's output to go high and C1 to be charged up via D1, When the finger is removed from the touch contacts and the output of IC1a returns low, C1 is prevented from discharging into this gate as D1 is now reverse biased, instead C1 discharges slowly via R2.

The VCO is formed by the components associated with IC1b, c and d. The circuit in fact generates a series of constant duration negative going pulses separated by "spaces" whose duration can be varied by the control voltage.

When the control voltage (the voltage on C1) is below a threshold level that is equal to half supply voltage the circuit will not oscillate. If we now assume that the voltage on C1 rises to supply, as would be the case when the touch contacts are bridged, C2 will start to charge up. The voltage across C2 is applied, via R4, to the schmitt trigger formed by IC1a and b. As the voltage applied to the schmitt crosses its upper switching threshold the output of IC1d, which inverts and buffers the schmitt's output, will go low. This will cause C2 to be rapidly discharged via the relatively low impedance path offered by R6 and D2. As the voltage on C2 crosses the lower threshold of the schmitt the output of IC1d returns high and C2 once more begins to charge. The time taken for the voltage on C2 to reach the schmitt's trigger point is dependent on the voltage across C1. Thus when the voltage on C1 is large, C2 quickly reaches the trigger point and the VCO produces a high frequency, this frequency reducing as the voltage of C1 falls.

The output from the VCO is fed both to IC3 to drive the ring of LEDs and to IC2a, b and c to produce the audio output.

The crystal earpiece that provides the "clicking" is driven from a bridge circuit. This effectively doubles the voltage applied to the transducer and hence, from $P = V^2/R$, quadrouples the audio output.

The LEDs driven by IC3 have their cathodes connected via R7, to the output of IC2d. The output of this gate will normally be high, going low when the voltage on C1 is above half supply. As IC3 outputs are active high the display is thus enabled for a period of time that is slightly longer than the duration of the VCO's oscillation.

C3 and C4 are included to decouple the supply while C5 is needed to prevent any RF interference affecting the circuit's operation.

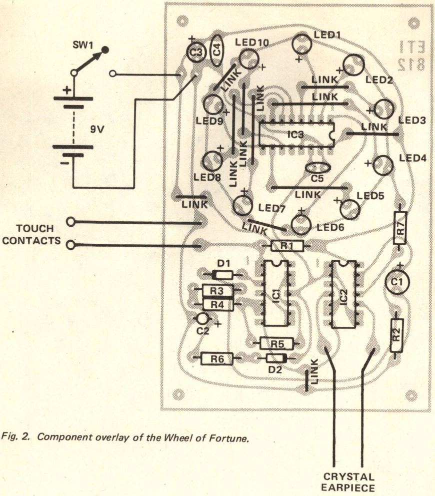

Fig. 2. Component overlay of the Wheel of Fortune.

PARTS LIST – ETI 812

Resistors all ¼W 5%

R1	2M2
R2	1M
R3	100k
R4	470k
R5	4M7
R6	10k
R7	330R

Capacitors

C1	100μ 16 VW
C2	1μ 16 VW
C3	22μ 16 VW
C4	100n Ceramic
C5	1n Ceramic

Semiconductors

IC1, 2	4011B
IC3	4017B
D1, 2	IN914 or similar
LED1- LED 10	TIL 209 or similar

Miscellaneous

9V battery and clip, crystal earpiece, miniature jack socket, box to suit, pcb.

None of the components used in the Wheel of Fortune game should prove hard to find as most will be stock items in many component shops. Make sure that the tantalum capacitors specified for C1, 2 and 3 are used as the circuit makes use of the low leakage characteristics of these components.

Construction

Start by mounting all the components on the PCB with the exception of the LEDs. Pay attention to the orientation of the polarity sensitive devices and, for choice, mount the ICs in sockets.

The touch contacts formed by two drawing pins are glued to the front panel. When the case has been prepared, place, but do not solder, the LEDs into the PCB and offer them up to the case. Solder one lead of each LED. At this stage make sure that all the devices are properly seated, then solder the second lead.

That about completes the construction, just connect up to a battery and place your bets.

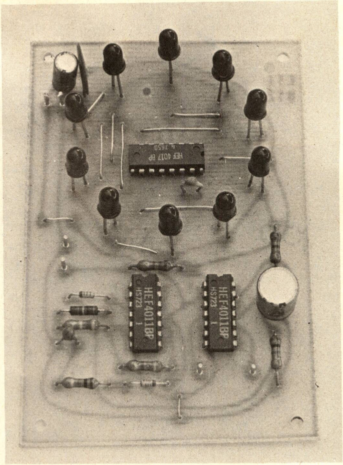

The assembled PCB.

Home Computer Show
Box Hill Town Hall
Box Hill
Victoria

9th-10th December
ETI will be there!

KITS for KIDS!

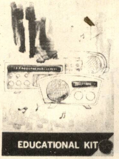

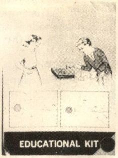

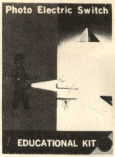

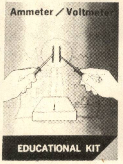

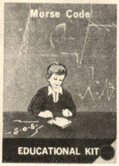

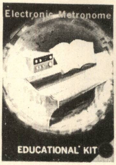

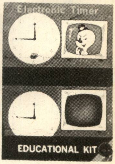

Project kits for the beginner

Completely safe – battery operated* – no mains connection

A. Electric organ	$5.60
B. Electronic flasher	$4.50
C. Electronic sound switch	$4.50
D. Electronic touch switch	$4.50
E. Electronic decision maker	$4.50
F. Electronic sleeping bell	$4.50
G. Electronic magic touch	$4.50
H. Electronic water alarm	$4.50
I. Photo Electric switch	$4.50
J. Electronic singing bird	$4.50
K. Morse code practice set	$4.90
L. Electronic siren	$4.50
M. Electronic water purity tester	$4.50
N. Transistor radio	$4.50
O. Electronic metronome	$4.50
P. Ammeter/voltmeter	$4.50
Q. Electronic Timer	$4.50
R. Electronic mosquito repeller	$4.50
S. Electronic police car siren	$4.90
T. Electronic fan and colour wheel	$4.50
U. Watch kit, 5 functions	$11.50

See July or August '78 ETI for full details.

****Batteries not included in kits A to T.***

KIT BITS DEALERS:

NSW: Electrocraft Pty. Ltd., Whiting St, Artarmon. **Kits Sets Aust.,** Pittwater Rd., Dee Why. **Gordon Toy Shop,** Moree St, Gordon. **Edmunds Moir & Co,** 186 Parry St, Newcastle, and 94 Manning St, Taree. **Madjenk Electronics,** 5.246 Princes Hwy, Dapto. **Lindfield Electrical** Pacific Hwy, Lindfield. **Bergs Hobbies,** 223 Church St, Parramatta. **Allied Communications,** 2 Lockinvar Place, Hornsby. **Kurri Electronics,** Kurri Kurri. **Unique Electronics,** 383 Merrylands Rd, Merrylands. **Manly Toy World,** Shop 5, 74 The Corso, Manly. **Lloyds Hobby Centre,** 24 Railway Ave, Liverpool. **Custom Communications,** Orchardfield St, Yennora. **C.B. Centre,** The Corso, Manly. **Red Ballon Toy World,** 192 Barru Ave, Griffith. **The Toy Box,** Florence St, Hornsby. **In Electronics & Co, 84 Ramsey St, Haberfield. Bladen Brooke Electronics,** 111 Bridge St, West Tamworth. **Sale by Junk,** 282 The Entrance Rd, Erina. **Sheridan Electronics,** 166 Redfern St, Redfern. **Sprint Electronics,** 167 Forest Rd, Hurstville. **Go Electronics,** Hotel Car Park, Bexley.

VIC. DISTRIBUTOR:
Stotts Technical Services, 159 Flinders Lane. Melbourne.
QLD:
St. Lucia Electronics, 9 Young St, Southport.
Mitchell Radio Co, 59 Albion St, Albion.
STH. AUST. DISTRIBUTOR:
International Communications Systems, 77 Dale St, Port Adelaide.
TASMANIAN DISTRIBUTOR:
Tasmanian Hi-Fi Co, 87A Brisbane St, Launceston.

KIT BITS

110 Rosemead Road,
HORNSBY. NSW. 2077.
Phone (02) 476-3975.
Trade enquiries welcome.

To: KIT BITS, 110 Rosemead Rd, Hornsby, NSW. 2077
Please send me Kit/s ....
I enclose Cheque/postal note for $.................................. plus 50c p&p.
NAME ....
ADDRESS ....
.... P/Code..............

ETI data sheet

NATIONAL LM324

The LM124 series op amps operate with only a single power supply and have true-differential inputs. They remain in the linear mode with an input common-mode voltage of 0 V_{DC}.

Precautions should be taken to insure that the power supply for the integrated circuit never becomes reversed in polarity.

electrical characteristics ($V^+ = +5.0\ V_{DC}$

PARAMETER	CONDITIONS	LM324 MIN	LM324 TYP	LM324 MAX	UNITS
Input Offset Voltage	$T_A = 25°C$		±2	±7	mV_{DC}
Input Bias Current	$I_{IN(+)}$ or $I_{IN(-)}$, $T_A = 25°C$		45	250	nA_{DC}
Input Offset Current	$I_{IN(+)} - I_{IN(-)}$, $T_A = 25°C$		±5	±50	nA_{DC}
Input Common-Mode Voltage Range	$V^+ = 30\ V_{DC}$, $T_A = 25°C$	0		$V^+-1.5$	V_{DC}
Supply Current	$R_L = \infty$, $V_{CC} = 30V$, (LM2902 $V_{CC} = 26V$)		1.5	3	mA_{DC}
	$R_L = \infty$ On All Op Amps		0.7	1.2	mA_{DC}
	Over Full Temperature Range				
	$T_A = 25°C$				mA_{DC}
Large Signal Voltage Gain	$V^+ = 15\ V_{DC}$ (For Large V_O Swing) $R_L \geq 2\ k\Omega$, $T_A = 25°C$	25	100		V/mV
Output Voltage Swing	$R_L = 2\ k\Omega$, $T_A = 25°C$ (LM2902 $R_L \geq 10\ k\Omega$)	0		$V^+-1.5$	V_{DC}
Common-Mode Rejection Ratio	DC, $T_A = 25°C$	65	70		dB
Power Supply Rejection Ratio	DC, $T_A = 25°C$	65	100		dB
Amplifier-to-Amplifier Coupling	f = 1 kHz to 20 kHz, $T_A = 25°C$ (Input Referred)		−120		dB
Output Current					
Source	$V_{IN}^+ = 1\ V_{DC}$, $V_{IN}^- = 0\ V_{DC}$, $V^+ = 15\ V_{DC}$, $T_A = 25°C$	20	40		mA_{DC}
Sink	$V_{IN}^- = 1\ V_{DC}$, $V_{IN} = 0\ V_{DC}$, $V^+ = 15\ V_{DC}$, $T_A = 25°C$	10	20		mA_{DC}
	$V_{IN}^- = 1\ V_{DC}$, $V_{IN}^+ = 0\ V_{DC}$, $T_A = 25°C$, $V_O = 200\ mV_{DC}$	12	50		μA_{DC}
Short Circuit to Ground	$T_A = 25°C$		40	60	mA_{DC}
Input Offset Voltage				±9	mV_{DC}
Input Offset Voltage Drift	$R_S = 0\Omega$		7		$\mu V/°C$
Input Offset Current	$I_{IN(+)} - I_{IN(-)}$			±150	nA_{DC}
Input Offset Current Drift			10		$pA_{DC}/°C$
Input Bias Current	$I_{IN(+)}$ or $I_{IN(-)}$		40	500	nA_{DC}
Input Common-Mode Voltage Range	$V^+ = 30\ V_{DC}$	0		V^+-2	V_{DC}
Large Signal Voltage Gain	$V^+ = +15\ V_{DC}$ (For Large V_O Swing) $R_L \geq 2\ k\Omega$	15			V/mV
Output Voltage Swing					
V_{OH}	$V^+ = +30\ V_{DC}$, $R_L = 2\ k\Omega$	26			V_{DC}
	$R_L \geq 10\ k\Omega$	27	28		V_{DC}
V_{OL}	$V^+ = 5\ V_{DC}$, $R_L \leq 10\ k\Omega$		5	20	mV_{DC}
Output Current					
Source	$V_{IN}^+ = +1\ V_{DC}$, $V_{IN}^- = 0\ V_{DC}$, $V^+ = 15\ V_{DC}$	10	20		mA
Sink	$V_{IN}^- = +1\ V_{DC}$, $V_{IN}^+ = 0\ V_{DC}$, $V^+ = 15\ V_{DC}$	5	8		mA
Differential Input Voltage				V^+	V_{DC}

Large differential inputs voltages can be easily accomodated and, as input differential voltage protection diodes are not needed, no large input currents result from large differential input voltages. The differential input voltage may be larger than V^+ without damaging the device. Protection should be provided to prevent the input voltages from going negative more than $-0.3\ V_{DC}$ (at 25°C). An input clamp diode with a resistor to the IC input terminal can be used.

To reduce the power supply current drain, the amplifiers have a class A output stage for small signal levels which converts to class B in a large signal mode. This allows the amplifiers to both source and sink large output currents. Therefore both NPN and PNP external current boost transistors can be used to extend the power capability of the basic amplifiers.

For ac applications, where the load is

connection diagram

Dual-In-Line and Flat Package

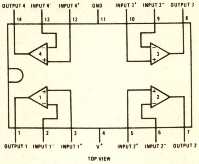

schematic diagram (Each Amplifier)

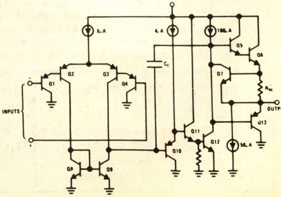

capacitively coupled to the output of the amplifier, a resistor should be used, from the output of the amplifier to ground to increase the class A bias current and prevent crossover distortion. Where the load is directly coupled, as in dc applications, there is no crossover distortion.

Large closed loop gains or resistive isolation should be used if load capacitances over 50 pF must be driven by the amplifier.

Output short circuits either to ground or to the positive power supply should be of short time duration. Putting direct short-circuits on more than one amplifier at a time will increase the total IC power dissipation to destructive levels, if not properly protected with external dissipation limiting resistors in series with the output leads of the amplifiers.

Introducing a pseudo-ground (a bias voltage reference of $V^+/2$) will allow operation above and below this value in single power supply systems.

Common Mode Rejection Ratio

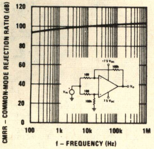

Open Loop Frequency Response

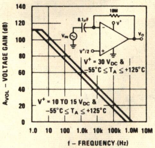

Voltage Follower Pulse Response

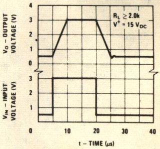

High Input Z Adjustable-Gain DC Instrumentation Amplifier

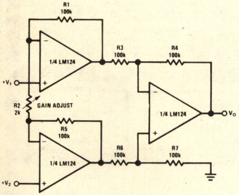

If R1 = R5 & R3 = R4 = R6 = R7 (CMRR depends on match)

$$V_O = 1 + \frac{2R1}{R2}(V_2 \quad V_1)$$

As shown $V_O = 101 (V_2 \quad V_1)$

Driving TTL

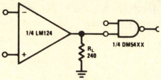

Power Amplifier

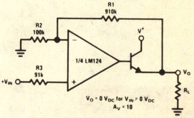

VO = 0 VDC for VIN = 0 VDC
AV = 10

LED Driver

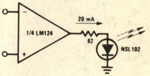

Bandpass Active Filter

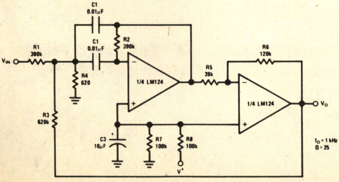

fO = 1 kHz
Q = 25

Lamp Driver

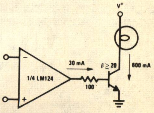

QUICK BE THE FIRST IN YOUR STREET WITH . . . .

THIS INCREDIBLE FAIRCHILD VIDEO ENTERTAINMENT COMPUTER

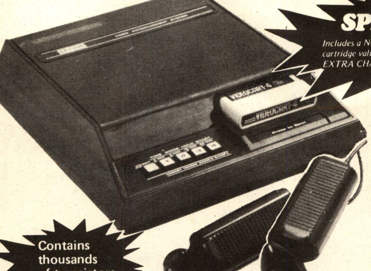

SPECIAL

Includes a NOUGHTS and CROSSES cartridge valued at $24.50 at NO EXTRA CHARGE. . . . . .

Manufactured by FAIRCHILD The US Electronics Giant.

Contains thousands of transistors.

See review in December '78 E.A.

Don't pay $300 or more for others.

This would have to be the most futuristic concept in home entertainment ever devised! Not just another TV video game but a complete computerised home entertainment centre that employs the latest in electronic technology. Just imagine - as new games are devised you simply plug them into the master console for new dimensions of fun and education. The computer console is supplied with two multi-directional hand controllers and has two built-in games (Tennis and Football). For the more adventurous, plug-in any of the 16 fabulous cartridges available separately and listed below (many game cartridges have two games or more!) for hours of colourful fun, learning and skill. Imagine you and your family playing Math games, trying to sink an enemy submarine, shooting the Red Baron out of the sky and even painting - become an electronic artist! The console simply plugs into the aerial socket on your TV and gives all games in glorious colour (if used with a colour TV) plus realistic sound effects from your very own TV set!

$259 **Includes AC adaptor, two built-in games (Tennis and Football) plus a games cartridge with Noughts and Crosses ready to plug in. Cat. X-1200**

SPECIAL 7 DAY TRIAL OFFER

Purchase this Fairchild Channel F Console and 2 game cartridges from one of our stores or by Mail Order. Try it out in your home for 7 days and if not completely satisfied return it to us in the condition you received it and we will refund your money in full.

MAIL ORDERS?

YES! Packing and delivery to anywhere in Australia $5.00. If purchased with the console the cartridges are supplied post FREE - if purchased separately there is a packing and delivery charge of $2.00 per cartridge.

TERMS

To approved applicants we can offer terms on 10% minimum deposit and low monthly repayments. Terms are only available to personal shoppers.

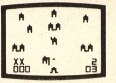

Baseball

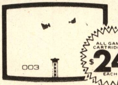

Spitfire

ALL GAMES CARTRIDGES $24.50 EACH

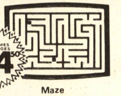

Maze

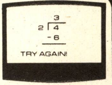

Math Quiz II

BLACKJACK Cat. X-1201
Two games available - you play the TV (the bank) or two players can try and break the bank.

DESERT FOX Cat. X-1203
Two games - Desert Fox where you try and destroy the other tank without being destroyed and Shooting Gallery - the electronic rifle against dead ducks!

MAZE Cat. X-1204
Four great games - Maze, Jailbreak, Blind-man's-bluff, and Trailblazer - games that will test your skill.

BASEBALL Cat. X-1205
All the skills and thrills of the league - for two players.

SPITFIRE Cat. X-1206
Two games - for one player the Red Baron is after you, in the other, two players shoot it out in the sky.

SPACE WAR Cat. X-1207
Laser beams streak towards you - can you outrace and outgun the aliens from outer space.

MATH QUIZ I Cat . X-1208
Addition and subtraction by using your TV screen

MATH QUIZ II Cat. X-1209
Multiplication and division - teach yourself and the kids.

PINBALL CHALLENGE Cat. X-1217
Remove different coloured walls of bricks to become a pinball wizard.

BACKGAMMON Cat. X-1213
All the rules programmed into the cartridge - so no cheating - also has Acey Duecy a variation on Backgammon.

TORPEDO ALLEY Cat. X-1211
Sink as many ships as possible - plus Robot War, try and escape the robots by destroying them in a force field.

SONAR SEARCH Cat. X-1214
Use your ears to try and sink a hidden fleet.

DODGE IT Cat. X-1216
Dodge a varying number of balls to win this game.

MEMORY MATCH Cat. X-1215
Numbers are exposed then disappear try and remember where they are to win this game.

MAGIC NUMBERS Cat. X-1210
Guess the right digits in the right place - race the clock or play for points.

DRAG RACE Cat. X-1212
Don't eat dust, stomp on the accelerator and beat your opponent in a drag race.

DICK SMITH ELECTRONICS

bankcard welcome here

SYDNEY
125 York Street, SYDNEY. Ph. 290-3377
147 Hume Hwy, CHULLORA. Ph. 642-8922
162 Pacific Hwy, GORE HILL. Ph. 439-5311
30 Grose Street, PARRAMATTA. Ph. 683-1133

MELBOURNE
399 Lonsdale Street, MELBOURNE. Ph. 67-9834
656 Bridge Road, RICHMOND. Ph. 42-1614

BRISBANE
166 Logan Road, BURANDA. Ph. 391-6233

ADELAIDE
203 Wright Street, ADELAIDE. Ph. 212-1962

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

SHOPS OPEN 9AM to 5.30PM
(Saturday 9AM – 12 noon)
BRISBANE 1/2 Hour earlier.

- ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

Many lines available from the Dick Smith Electronics Centres at

GRACE BROS ®

Broadway • Bondi • Chatswood • Liverpool
Miranda • Mt Druitt • Parramatta • Roselands
and Warringah Mall

425EA1278

Project 490

Audio compressor

Increase your talk power with this circuit.

THE HUMAN VOICE, being expressive at its best, varies considerably in level, even when one is speaking in a normal conversational voice. The peaks are considerably higher than the lower levels, which can give rise to problems when the speech waveform is being modulated onto a carrier by a transmitter. For example, if the mic gain control is set so that the peaks are just giving 100% modulation, then soft sounds can barely be heard whereas if the gain is turned up to give a higher level on vowel sounds, etc., then plosives (p-sounds) will give overmodulation and consequent splattering and poor speech quality.

A higher ratio of average power to peak voltage can be achieved by several methods, including compression or clipping of the audio signal and compression or clipping of the radio frequency signal. Radio frequency compression or ALC (automatic level control) is often used in the final stages of SSB transmitters.

Radio frequency clipping is the most effective method of increasing the average power; however it requires complex circuitry, since it is necessary to generate an SSB signal, clip, and then insert this signal into the transmitter IF chain.

Almost as effective as RF clipping is a combination of audio compression, clipping and filtering, which is relatively simple and can realise an improvement in signal to noise ratio of up to 5 dB on weak signals.

Compression

When speaking into a microphone it is desirable to keep the voice level as constant as possible. This can be quite difficult as any change in the distance to the microphone will cause a drastic change in its output. To overcome this a variable gain amplifier can be used which senses the average speech level and adjusts its gain accordingly for a constant output voltage. The compressor operates with a fast attack (gain reduction) and a slow decay (gain increase), to quickly respond to the voice while remaining at this level to prevent amplification of background noise during speech pauses.

Clipping

The average power contained in a speech waveform is quite low compared to the peak voltage, and much less than the average power of a sine wave of the same amplitude. If the low energy high voltage peaks are cut off at a preset level the remaining signal can be increased without overdriving the transmitter. The average power is therefore increased. Clipping will slightly change the sound of the voice but will increase the intelligibility of a weak signal, as well as preventing the transmitter from being overdriven by limiting the maximum signal voltage.

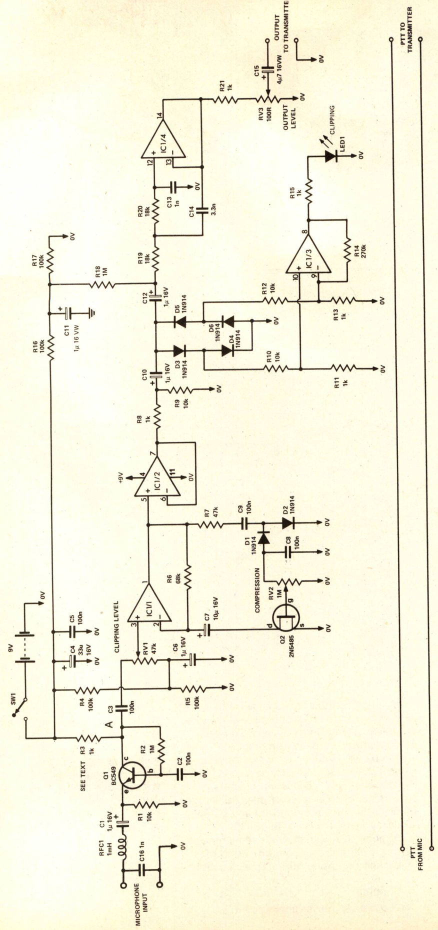

Fig. 1. Circuit of the Audio Processor.

HOW IT WORKS – ETI 490

The input is fed to a common base amplifier (Q1) and then to the gain control, RV1. The signal is then further amplified by IC1/1. Some of the output from IC1/1 is rectified and negatively charges C8. This voltage is then fed to Q2, a depletion mode N – channel FET. As the output of IC1/1 increases the voltage on the gate increases negatively and the impedance of Q2 increases. This increases the ratio of the feed back signal applied to the negative input of IC1/1 and the overall gain is reduced. The attack time is set by the time constant of R7 and C8, while the decay time is set by RV2 and C8.

IC1/1 is a buffer to isolate the peak limiter from the compressor input. R8 limits the output current of IC1/2 on peaks while R9 provides output bias current to prevent crossover distortion in the LM324 when driving capacitive loads. The diodes D3-D6 form the peak limiter by shorting any signal over about 1.5 V. When clipping occurs the voltage across D4 and D6 rises to 0.7 V. This voltage is used to turn on IC1/3 to give an indication of clipping by lighting LED 1.

The active low pass filter, IC1/4, removes the unwanted harmonics produced by clipping. RV3 sets the output level. The low frequency response is limited by the value of the coupling capacitors and C2.

Filtering

When a waveform is clipped high order harmonics are produced which, if allowed to reach the transmitter, would cause splatter and interference to neighbouring stations. A filter must be used after the clipper to rapidly attenuate all frequencies above 3 kHz, which are unnecessary for intelligibility. This is achieved by using an active filter with 12 dB/octave attenuation above 2.5 kHz.

Construction

The speech processor is mounted in a diecast aluminium box to guard against feedback which can be caused by strong RF fields. Our box measured 150 mm x 80 mm x 50 mm deep. Either an internal 9V battery or the 12V transceiver supply can be used. The processor is designed to be used in the line from the microphone to the transmitter without any modification to either. A matching socket to the mic plug is used for the input and the output taken via a lead with a matching plug. The connections for the plug and socket vary between makes of transceivers and will have to be taken from the circuit diagram of the transceiver. The clipping indicator (LED 2) and the power switch are mounted on the front panel.

Setting Up

Turn the compressor control to maximum and speak into the microphone at the greatest distance you are likely to use, (say 30 cm). Increase the gain control until the clipping LED flashes. If this point cannot be reached decrease the compression control and try again. The setting of these two controls is best determined by on-air tests. The output level control should be set so the RF indicator on the transmitter reaches the same peak as with only the microphone plugged in.

For high output, high impedance microphones, such as crystal types, Q1 can be omitted, RV1 replaced with a 1M trimpot and the input fed to point A on the circuit.

The gain of Q1 is proportional to the value of R3. Increasing its value increases the gain. To guard against feedback the lowest value possible should be used.

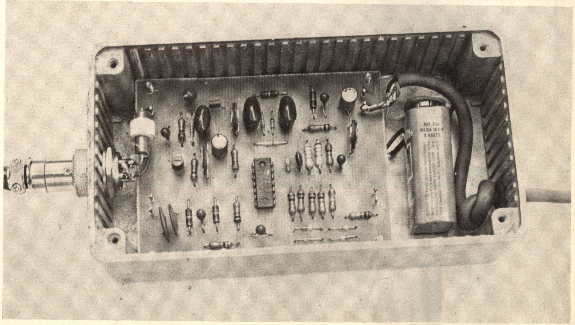

Inside view of the Processor. The RF chock should be mounted as close as possible to the input socket.

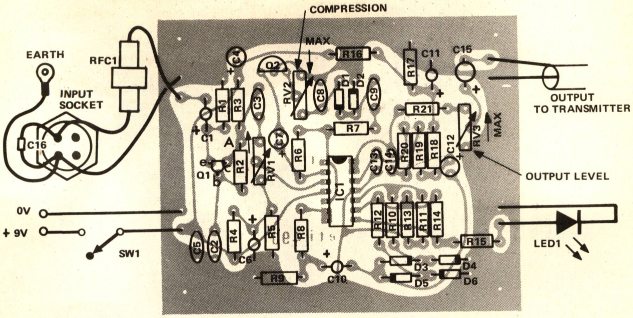

Fig. 2. Component overlay of the Audio Processor. Note the RF chock and capacitor mounted between the PCB and input socket.

PARTS LIST – ETI 490

Resistors all ¼W, 5%

R1	10k
R2	1M
R3	1k
R4, 5	100k
R6	68k
R7	47k
R8	1k
R9, 10	10k
R11	1k
R12	10k
R13	1k
R14	270k
R15	1k
R16, 17	100k
R18	1M
R19, 20	18k
R21	1k

Potentiometers

RV1	47k lin mini trimpot
RV2	1M lin mini trimpot
RV3	100Ω lin mini trimpot

Capacitors

C1	1µ 16 VW electro
C2, 3	100n greencap
C4	33µ 16 VW electro
C5	100n Ceramic
C6	1µ 16 VW electro
C7	10µ 16 VW electro
C8, 9	100n greencap
C10–C12	1µ 16 VW electro
C13	1n greencap
C14	3.3n greencap
C15	4µ7 16 VW electro
C16	1n ceramic

Semiconductors

Q1	BC549 or sim
Q2	2N5485 FET
IC1	LM324N
D1–D6	1N914 or sim
LED1	Red LED

Miscellaneous

RFC1	1mH or higher Radio Frequency Chock
SW1	SPST miniature toggle

Metal box to suit, 9V battery and holder, microphone plug and socket to suit, length multi wire shielded cable.

ETI Staff Vacancy

We are looking for someone to work on ETI's project development staff. Applicants must be capable of, firstly, designing and breadboarding prototype circuits, and secondly, converting the proven circuits into well-built finished projects of the high standard necessary for publication.

Skills required include a good standard of workmanship, both electronically and mechanically. Ability to design pc boards would be an advantage, though limited experience in this area should not deter candidates from applying. A strong background in digital electronics is essential.

The majority of work is design and construction, but it will be necessary to liase with other editorial staff in the presentation of the magazine project article.

The job is in our project development lab at Rushcutters Bay. Salary will depend upon experience and ability, but will be in the region of $12 000.

For further information phone Phil Wait on (02) 33 4282, or write, enclosing a complete resume, to *Staff Vacancy, Electronics Today International, 15 Boundary Street, Rushcutters Bay, NSW 2011.*

TASMAN ELECTRONICS

12 VICTORIA STREET, COBURG 3058 Ph. (03) 354-5062
Open Mon – Thurs. 9.00 – 5.30pm. Fri. 9am – 9pm. Sat. 9am – 12.00 noon
Mail orders — please add 70c minimum post and pack.

• TRANSISTORS

BC318	22
BC319	22
BC320	22
BC548	19
BC557	19
BC558	19
BC559	19
BC139	50
BD140	50
MP102	45
MJ2955	80
TIP31	89
TIP31C	69
TIP32C	72
2N2219	45
2N2646	1.15
2N2647	1.15
2N2904	50
2N2905	50
2N2905A	50
2N2907	45
2N3017	1.00
2N3053	50
2N3054	1.15
2N3000	75
2N3702	29
2N3740	1.70
2N3904	29
2N4030	90
2N4032	95
2N4033	1.30
2N4036	1.50
2N4037	1.30
2N4231	98
2N4234	1.80
2N4238	1.65
2N5088	30
2N5871	1.50
2N5872	2.00
2N5873	1.50
2N5874	1.65
2N6124	90
2N6126	1.10
2N6129	1.30
2N6130	1.45
2N6132	1.45
2N6134	1.60
PN2222A	25
PN3565	18
PN3566	18
PN3567	18
PN3568	18
PN3569	18
PN3638	17
PN3638A	22
PN3641	20
PN3642	20
PN3643	20
PN3644	22
PN3645	22
PN3646	22
PN3693	29
PN3694	29
PN4121	35
PN4248	22
PN4250	29
PN4355	29

• 74LS

74LS00	25
74LS01	28
74LS02	25
74LS03	25
74LS04	30
74LS05	30
74LS08	25
74LS09	28
74LS10	25
74LS11	28
74LS12	28
74LS14	1.15
74LS20	28
74LS21	28
74LS27	28
74LS28	35
74LS30	28
74LS32	30
74LS37	38
74LS38	38
74LS40	32
74LS42	95
74LS73	60
74LS74	46
74LS75	55
74LS78	50
74LS85	1.20
74LS86	48
74LS90	70
74LS92	1.10
74LS93	80
74LS95	1.00
74LS109	45
74LS113	50
74LS114	50
74LS125	70
74LS133	30
74LS138	1.30
74LS151	1.15
74LS157	75
74LS160	90
74LS163	1.15
74LS164	155
74LS169	1.50
74LS174	70
74LS175	85
74LS190	1.25
74LS191	1.20
74LS192	1.15
74LS193	1.10
74LS194	1.95
74LS195	1.00
74LS196	1.30
74LS197	1.35
74LS221	1.15
74LS251	80
74LS253	80
74LS257	70
74LS259	3.20
74LS279	55
74LS290	1.15
74LS365	70
74LS366	70
74LS367	70
74LS368	65

• CMOS

4001	25
4002	30
4007	30
4008	1.20
4011	25
4012	25
4013	52
4014	1.30
4015	1.45
4016	55
4017	1.30
4018	1.20
4020	1.40
4021	1.30
4022	1.30
4023	30
4024	90
4025	35
4027	65
4028	95
4040	1.30
4042	1.10
4043	95
4044	95
4046	1.55
4049	55
4050	55
4051	1.20
4052	1.20
4053	1.20
4066	75
4068	35
4069	30
4070	35
4071	35
4072	35
4076	1.75
4077	35
3078	35
3081	35
3082	35
4510	1.40
4511	1.40
4518	1.40
4520	1.40
4528	1.20
4553	6.75
4555	1.10
4584	75
74C00	35
74C02	35
74C04	40
74C08	40
74C10	40
74C14	1.55
74C20	45
74C48	2.45
74C73	1.10
74C76	1.15
74C90	1.50
74C93	1.50
74C175	1.75
74C192	1.85
74C193	1.85
40097	90
40098	90
40014	60

• TTL

7400	28
7401	28
7402	28
7403	28
7404	35
7405	37
7408	30
7409	34
7410	30
7413	54
7414	1.29
7416	50
7420	30
7421	30
7422	30
7426	40
7427	40
7430	30
7432	40
7437	46
7440	30
7442	83
7447	1.20
7448	1.20
7450	30
7451	30
7453	30
7454	30
7460	30
7470	50
7472	50
7473	50
7474	50
7475	72
7476	55
7480	95
7483	1.10
7485	1.40
7486	50
7490	40
7491	1.04
7492	75
7493	40
7494	1.05
7495	92
74107	55
74121	55
74132	1.15
74151	1.10
74153	1.10
74154	1.65
74160	1.40
74173	2.20

• VOLT. REGS.

7805-12-15-18-24	All 1.20
7905-12-15-18-24	All 1.60
78L05-12-15-18-24	All 40
79L05-12-15-18-24	All 80
78CB	2.30
723	50
309	2.00
317	2.95

• DIODES

0A90	15
0A91	15
IN4002	8
IN4004	8
IN4007	16
IN5404	35
IN4148	6
W02 BRIDGE	90
VM48 DIL BRIDGE	1.25
IN3493	1.70
IN3493R	1.70

• ZENERS

BZX79 Series	19
BZY88	40
BZX70	65

• RESISTORS

½ WATT E24 VALUES	3
1 WATT E12 VALUES	7
5 WATT W/W	25
MINIATURE PRESETS, ALL	18
MINIATURE TRIMPOTS, ALL	48
93448 MICRO.	10.20
T03 SOCKETS	22

• LINEAR

741	35
747	1.15
3900	99
301	45
307	86
311	85
324	1.20
555	35
RC4136	1.35
9368	1.90
308	1.35
TL080	1.15
TL081	52
TL082	95
380	2.00
381	2.00

• OPTO

MCT2	65
FND357 c/c	1.40
LED-RED	20
LED-GREEN	30
LED-AMB	43

• SCR's

C106YI	39
C106DI	62
C103YY	99

• ELECTROLYTICS PCB TYPE

6.3V.	470uf	20
10V.	4.7uf	8
	22uf	10
	100uf	12
16V.	10uf	8
	22uf	12
	47uf	12
	100uf	15
	220uf	15
	470uf	23
	640uf	42
	1000uf	37
	2500uf	62
25V.	1.5uf	8
	2.2uf	8
	3.3uf	8
	10uf	8
	25uf	12
	100uf	18
	220uf	24
	330uf	24
	470uf	32
	1000uf	48
35V.	2.2uf	8
	3.3uf	8
	10uf	11
	100uf	18
	220uf	21
	1000uf	53
	2000uf	71
	2200uf	88
50V.	0.47uf	8
	2.2uf	8
	22uf	13
	33uf	15
	220uf	23
63V.	0.47uf	8
	1uf	8
	2.2uf	8
	4.7uf	10
	10uf	12
	25uf	15
	47uf	16
	100uf	23
	220uf	37
	330uf	40
	470uf	77

• TANTALUMS TAD-35V.

0.1 TO 1uf	15
1.5uf	20
2.2uf	25
3.3uf	25
6.8uf	30
15uf	55
22uf	55
4.7uf 16V	20

• CERAMICS

1pf TO 0.0047	5
0.0068 TO 0.01	8
0.1	12
0.22	18
0.47	24

Other lines in stock include:- Battery chargers and adaptors, instrument cases and boxes, wire and cable, audio and TV leads — plugs — sockets, dmm's, potentiometers, switches, stylii, transformers, etc, etc. **We are dealers for "AIWA" quality products.**

PM/RM SERIES PANEL METERS

LARGEST RANGE OF PANEL METERS AVAILABLE!

PM-4 4 digits

RM-351 3½ digits

PM-350 3½ digits

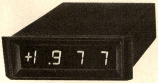

PM-351 3½ digits

Features:
- MOS/LSI Construction.
- Smallest package available anywhere (Less than 1" high).
- Lowest power requirements — less than 0.8 watts.
- Reliability enhanced by burn-in at elevated temperature.
- Multiple ranges, ± 1V to ± 1000V F.S. (± 0.1V range optional on PM-3 & PM-4).
- No zero adjustment.

Features:
- MOS/LSI construction.
- Fits DIN or NEMA cutouts.
- Large 0.6" LCD or 0.5" LED display.
- No zero adjustment.
- Input voltage protection.
- Plug-in range change capability.
- Programmable decimal.
- Overload indication.
- Automatic polarity.
- 0.2V, 2V, 20V, 200V or 1000V range.

Features:
- MOS/LSI construction.
- Less than 1" high.
- Large LCD or LED display.
- Programmable decimal.
- No zero adjustment.
- Overload indication.
- Low power requirement.
- Display blanking.
- Automatic polarity.
- Input voltage protection.
- 0.2V, 2V, 20V, 200V or 1000V range.

Trade enquiries welcome

NON LINEAR SYSTEMS, (AUST) PTY LTD
61 Lothian St, W. Melbourne, Vic. 3015.
Phone (03) 329-9951, 329-9377

DISTRIBUTED BY:
Vic. Radio Parts, 329-7888.
NSW. Radio Despatch, 211-0816.
SA. Protronics, 51-4713.
QLD. Electronic Components, 371-5677.

NEW ZEALAND READERS

THE ELECTRONICS CENTRE — NOW OPEN — 179 HOBSON ST, AUCKLAND

The one-stop components shop

Stockists of:

RESISTORS
CAPACITORS
DIODES
TRANSISTORS
CMOS
TTL
LINEAR

REGULATORS
ROMS
RAMS
LEDS
7 SEGMENT DISPLAYS
CLOCK MODULES

SWITCHES
POTENTIOMETERS
POWER SUPPLIES
AERIALS
MULTIMETERS
SOLERING IRONS
IC SOCKETS

CASES & CABINETS
CABLE & WIRE
SPEAKERS
KNOBS
TRANSFORMERS
WIRE WRAP TOOLS

PLUS — too many to list — all devices by NATIONAL TEXAS, FAIRCHILD.

TV GAMES — **Teletennis with GI AY-3-8550 plus joysticks.**
Tank Battle with GI AY-3-8710.
Chips available, AY-3-8500, AY-3-8550, AY-3-8710 etc.

PLUS A HUGE RANGE OF KITS.

MUSICOLOUR — Colour Organ — let there be light in your music.

RADAR DETECTORS
Super Orbit, built-up and kitsets.

Send for our FREE PRICE LIST (please include SAE)
or our ORBIT CATALOGUE — only $2.00.
To: ORBIT ELECTRONICS LTD., PO Box 7176, Wellesley Street, AUCKLAND, 1.

Q Where should you start in your search for better sound?

A At the beginning. With a new Audio-Technica Dual Magnet stereo phono cartridge.

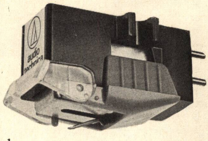

Our AT12XE, for instance. Tracking smoothly at 1 to 1-¾ grams, depending on your record player, Delivers smooth, peak-free response from 15 Hz to 28,000 Hz (better than most speakers available). With a minimum 24 dB of honest stereo separation at important mid frequencies, and 18 dB minimum separation even at the standard high-frequency 10 kHz test point. At just $42.95 suggested list price, its an outstanding value in these days of inflated prices. Audio-Technica cartridges have been widely-acclaimed for their great sound, and for good reason. Our unique, patented* Dual Magnet construction provides *separate* magnetic system for *each* stereo channel. A concept that insures excellent stereo separation, while lowering magnet mass. And the AT12XE features a tiny 0.3 x 0.7-mil nude-mounted elliptical diamond stylus on a thin-wall cantilever to further reduce moving mass where it counts. Each cartridge is individually assembled and tested to meet or exceed our rigid performance standards. As a result, the AT12XE is one of the great bargains of modern technology . . . and a significant head start toward more beautiful sound. Listen carefully at your Audio-Technica dealer's today.

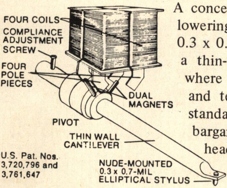

FOUR COILS
COMPLIANCE ADJUSTMENT SCREW
FOUR POLE PIECES
DUAL MAGNETS
PIVOT
THIN WALL CANTILEVER
NUDE-MOUNTED 0.3 x 0.7-MIL ELLIPTICAL STYLUS

*U.S. Pat. Nos. 3,720,796 and 3,761,647

Australian distributor: **MAURICE CHAPMAN AUST. PTY. LTD.**
44 Dickson Ave, Artarmon. 2064. Tel: 438-3111

audio technica
INNOVATION PRECISION INTEGRITY

LEADER AUDIO FREQUENCY RESPONSE RECORDER LFR-5600

The LFR-5600 is a frequency response recorder designed to graphically record frequency response, wow-flutter, drift, voltage and temperature parameters of audio equipment.

The unit consists of two instruments: A pen recorder and audio sweep oscillator. The sweep oscillator may be used separately for direct reading of frequency response on an oscilloscope.

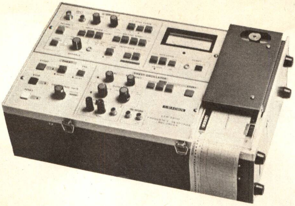

FEATURES:

- Automatic start circuitry allows easy measurement of tape recorder response.
- Standard signal frequencies of 1kHz and 333Hz (with less than 0.1% distortion) may be selected for reel to reel or cassette recorder measurement.
- Selectable 25dB, 50dB or linear scales.
- Sweep oscillator output has 20dB and 40dB attenuation allowing high sensitivity measurements.
- External signals may be used for response checks.
- Meter may be used as sweep frequency indicator or input/output voltage indicator for voltage calibration.
- Chart section may be used as a direct current recorder (10 mV/cm).
- A slow speed range of 0.1 mm/cm allows long term drift measurements.

APPLICATIONS:

● Tape recorder/Cassette frequency & signal to noise ratio ● Audio amplifier frequency response & signal to noise ratio ● Cartridge frequency response ● Wow-flutter & drift ● Filter frequency response ● Direct observation of low frequency response

For further information contact:—

WARBURTON FRANKI

● ADELAIDE 356-7333 ● BRISBANE 52-7255 ● HOBART 23-1841
● MELBOURNE 699-4999 ● PERTH 277-7000 ● SYDNEY 648-1711
● AUCKLAND N.Z. 79-7781 ● WELLINGTON N.Z. 698-272

WF 587/77

●●●●●●●●●●●●●● **state of the art in audio monitoring** ●●●●●●●●●●●●●●●

Chromatec announces the TVD100 SERIES MULTICHANNEL PEAK PROGRAM MONITORS AND REAL TIME SPECTRUM ANALYZERS

(See front cover pic "Hi-Fi and Music, August '78)

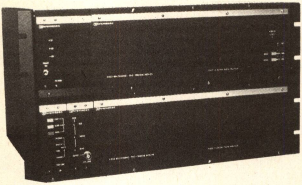

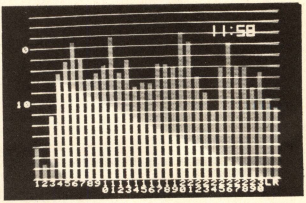

- Australian Designed and manufactured
- Units display information on a standard PAL colour monitor
- Coloured display with alphanumeric character labelling
- Professional specifications: BBC Peak Program Response on up to 32 channels, Third octave filter set for Real Time Spectrum Analysis
- Many customer specified variations including a variety of bar formats
- Quality from around $3000 for each type, or around $5000 for combined Peak Program Monitor/Real Time Spectrum Analyzer (TV monitor not included)

Brief Technical Specifications:

- Logarithmic response — i.e. a linearized dB scale
- Electronically generated graticule and character information
- Standard R,G,B & Sync. outputs to a suitable monitor
- Balanced audio inputs with or without transformers
- Options include: Input bridging transformers; standard PAL colour encoder; on screen clock; pink noise generator; microphone input preamplifier; (the latter two for use with the Spectrum Analyzer), and others

DESIGNED AND MANUFACTURED BY CHROMATEC VIDEO PRODUCTS PTY. LTD. 3 Withers Ave., Mulgrave, Vic. 3170. Tel: (03) 546-2259

●●

Colour Sequencer

This unit interfaces with the ETI 592 Light Show Controller to give a rainbow sequence of colours.

BY MIXING THE THREE primary colours in the right proportions any colour of the rainbow, including white, can be made. A good example of this is a colour TV set, which uses only red, green and blue phosphors. When creating special effects with lights it is often desirable to have a colour which changes with time be it for a spot on a disco wall or lighting up a fountain.

This unit allows three light dimmers (the ETI 592 is ideal) to be controlled in a preset sequence giving eight different colour mixes. The rate of change from one sequence to the next is also variable.

Design Features

When we first examined the different ways of designing this project we had the choice of a simple system using a multitude of potentiometers or one which uses digital techniques with a RAM and D-A converters. Due to the complexity of the digital approach we chose the simple analogue system.

Construction

This is simply a matter of following the component overlay in fig. 2. Note that the trimpots are staggered to allow adjustment or to allow the larger type to be used without interfering with the adjacent pot.

Check the orientation of the ICs before soldering and solder the power supply rails first (especially for the CMOS ICs).

SPECIFICATION — ETI 593

Number of channels	3
Speed	3 — 30 seconds per step
Output Voltage	0 — +7V
Power Supply	∓ 12V @ 10mA

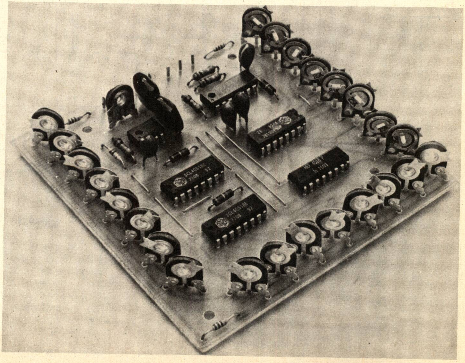

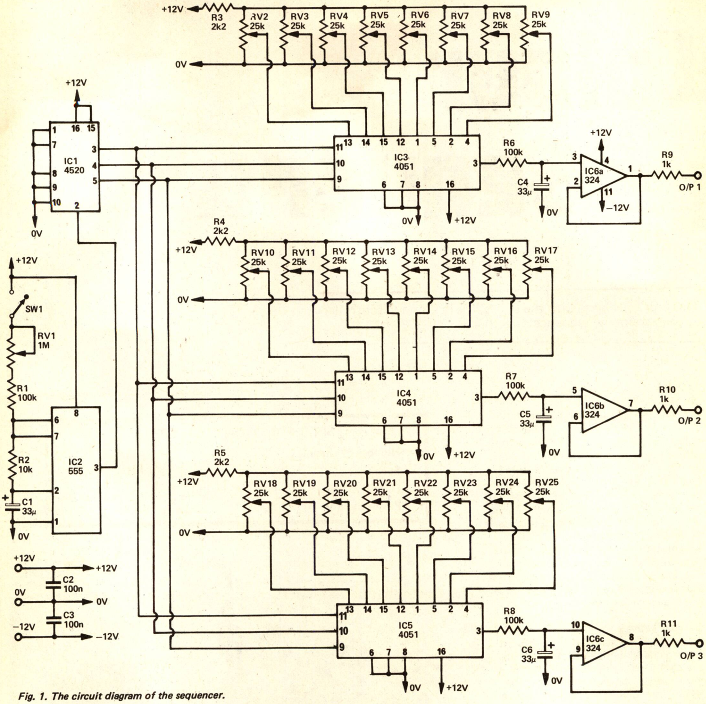

Fig. 1. The circuit diagram of the sequencer.

How It Works - ETI 593

The unit consists of three identical channels controlled by a master selector. There are eight potentiometers associated with each channel which are used simply as voltage dividers. The 4051 IC associated with each set of potentiometers is a one of eight analogue multiplexer which means that one of the potentiometer outputs will be connected through to the output of the IC (pin 3) depending on the binary code presented to the control inputs (pins 9, 10 and 11).

The output from the 4051 is buffered by an op-amp with an RC network to give a slow change from one level to the next. The value of the capacitor can be reduced if the response is too slow. As the op-amp cannot swing to its supply rail a dropping resistor is used in series with the potentiometers limiting the maximum voltage to the op-amps to 7 volts.

The channel selection is done by IC1 which is a dual 4 bit binary counter. We are only using it as a single 3 bit counter with the unused inputs terminated to the supply rails. This IC is clocked by the 555 timer IC2 with the rate being determined by RV1. Again if the rate is wrong C1 can be changed in value.

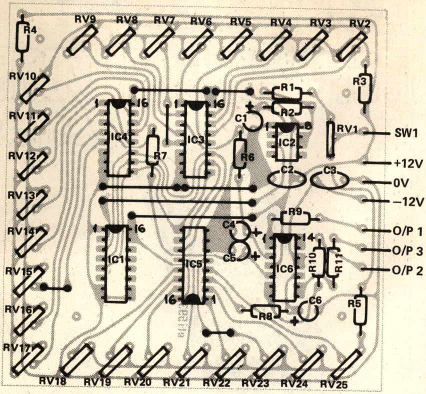

Fig. 2. The component overlay.

PARTS LIST – ETI 593

Resistors	all ½W, 5%
R1	100k
R2	10k
R3–R5	2k2
R6–R8	100k
R9–R11	1k
Potentiometers	
RV1	1M trim
RV2–RV25	25k trim
Capacitors	
C1	33µ 16V electro
C2,3	100n polyester
C4–C6	33µ 16V electro
Semiconductors	
IC1	4520 counter
IC2	555 timer
IC3–IC5	4051 multiplexer
IC6	324 quad op amp
Miscellaneous	
PC board ETI 593	
single pole switch	

The power for the unit comes from an external supply. If it is to be used with the ETI 592 dimmer power can be taken from that unit. Otherwise a supply giving a positive voltage of between 10V and 15V (regulated) and a negative voltage of −2V to −15V is needed. Supply current on the positive supply is about 10mA while it is only about 3mA on the negative side.

Setting Up

Connect the unit up and switch on. On switching SW1 on the unit should sequence through its cycle. Stop the unit and check to see which potentiometer in each bank controls the light. Adjust the level of the three dimmers to give the desired colour and intensity.

Close the switch until the next stage is selected, open the switch, and adjust the next colour. Proceed until all eight stages of the sequence have been programed.

electronics today INTERNATIONAL

BINDERS

HOLDS
12 COPIES
OF ETI

Protect and file your back issues of Electronics Today with these attractive binders. Price $4.50 plus postage and packing (90c NSW, $2.00 other states)

Write enclosing cheque/postal note/money order to:

SUBSCRIPTION DEPARTMENT,
ELECTRONICS TODAY INTERNATIONAL,
3rd Floor, 15 Boundary Street,
Rushcutters Bay, NSW. 2011.

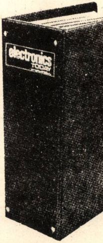

HERE IT IS!

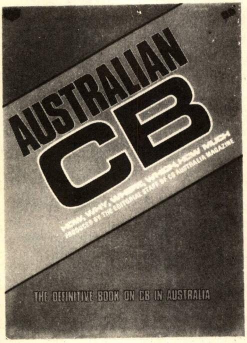
AUSTRALIAN CB
HOW, WHY, WHERE, WHICH, HOW MUCH
PRODUCED BY THE EDITORIAL STAFF OF CB AUSTRALIA MAGAZINE
THE DEFINITIVE BOOK ON CB IN AUSTRALIA

THE AUSTRALIAN CB BOOK – it's the one Australian CBers have been waiting for! Compiled by the editor and staff of CB Australia, this book is the most important publication for CBers yet published in this country. We hope you come to regard it as the 'bible' of the Australian CB scene. It is backed by the technical expertise of its sister publication Electronics Today International.

Author, Roger Harrison, is a freelance technical journalist with many years experience in electronics and communications. His highly regarded technical articles have been published world wide in several languages.

Australian CB is written in a language that the ordinary person interested in CB can understand. Its 22 chapters cover virtually every aspect of CB in Australia, from how to read rig specs to how to install antennas to what UHF is all about.

ON SALE NOW AT YOUR NEWSAGENT – $3.95

COMING!

SIMPLE PROJECTS

Volume 2

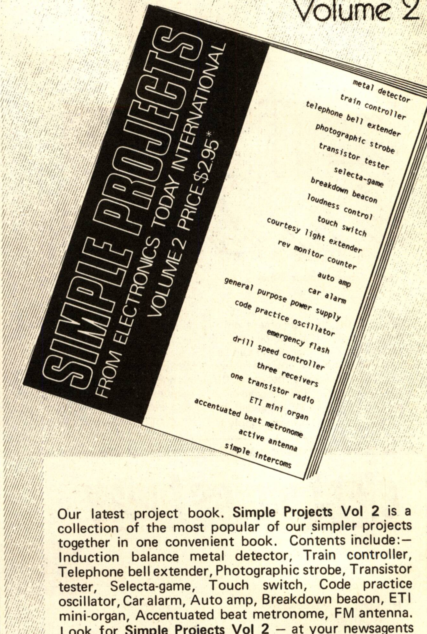

SIMPLE PROJECTS
FROM ELECTRONICS TODAY INTERNATIONAL
VOLUME 2 PRICE $2.95*

metal detector
train controller
telephone bell extender
photographic strobe
transistor tester
selecta-game
breakdown beacon
loudness control
touch switch
courtesy light extender
rev monitor counter
auto amp
car alarm
general purpose power supply
code practice oscillator
emergency flash
drill speed controller
three receivers
one transistor radio
ETI mini organ
accentuated beat metronome
active antenna
simple intercoms

Our latest project book. **Simple Projects Vol 2** is a collection of the most popular of our simpler projects together in one convenient book. Contents include:– Induction balance metal detector, Train controller, Telephone bell extender, Photographic strobe, Transistor tester, Selecta-game, Touch switch, Code practice oscillator, Car alarm, Auto amp, Breakdown beacon, ETI mini-organ, Accentuated beat metronome, FM antenna. Look for **Simple Projects Vol 2** – at your newsagents next month. Recommended retail price is $2.95 or you can order directly from Electronics Today, 15 Boundary Street, Rushcutters Bay. 2021. (Add 45 cents for post and packing).

SEMCON MICROCOMPUTERS PTY. LTD.

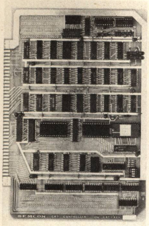

CRT INTERFACE CARD

This powerful unit has been designed to efficiently interface the memory of excorciser compatible systems directly to a CRT display. It is software driven and with appropriate program can be made to emulate the majority of functions of currently available intelligent terminals.

- No page buffer — the card has a line buffer that is continuously refreshed from processor memory on a DMA basis; a) Phase 2 when CPU VMA is low, or, b) Phase one. This is completely transparent to the processor resulting in a flicker free display without halting or slowing processor.
- Displays up to 32x2k pages simply by changing contents of 8 bit page register.
- Hardware scrolling controlled by scroll register.
- Displays full 128 ASCII character set. (Control characters optional).
- Inverse video (may be mixed with normal video).
- Coarse graphics.
- Link programmable character/line (48, 64, 80).
- Link programmable lines/page (20, 22, 24).
- Additional line at bottom of page for status information — uneffected by scrolling.
- Dot rate controlled by phase locked loop — automatically adjusts to different formats.

FOR FURTHER INFORMATION ON THIS VERSATILE DEVICE PLUS ASSOCIATED SOFTWARE PACKAGES SEND S.A.E. TO SEMCON.

PRICE
$285
PLUS TAX

Card cage/backplane

- Designed for Motorola Cards.
- Anodised Aluminium chassis.
- Sturdy Construction.
- Tin Plated Backplane.
- Accommodates 8 cards.

$74

POWER SUPPLY

- plus 5V 5 amps.
- ± 12V ½ amp.
- – 5V ½ amp.
- Designed to fit onto end plate of Card Cage

$149

EDGE CONNECTORS

43 x 2 x 0.156", **$8.50** each. Eight for **$59.** S100 Connectors **$8.50.**

8K/16K EPROM MODULE **$135**

8K STATIC RAM 350 n.s. Kit now only **$199**
Built $250.

Semcon has several special offers for customers on our regular mailing lists. To join it, simply send S.A.E. together with name, address, occupation and, if you wish, details on your current system.

Please add 15 percent S/T to all prices
SHOWROOM: 1 Chilvers Rd, Thornleigh, NSW. 2120.
MAIL ORDER: PO Box 61, Pennant Hills. NSW. 2120.
PHONE: 848-0800. Add 15 percent S/T. P&P $1.50. Goods valued over $100 will be sent by courier, standard charges for freight and insurance, Syd. metro — $2.50, NSW country and interstate — $7.00

HEATHKIT

Digital Wind Speed and Direction Indicator

KIT ID-1590E—$120.00

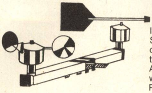

ID-1590E SPECIFICATIONS: Wind Speed: 0-99 in miles per hour, knots or kilometres per hour (choice of two). Response Threshold: 3 mph Accuracy ± 1 digit or ± 10%, whichever is greater. Direction Response Threshold: approx 2 mph. Power Requirement: 240V AC, 50 Hz.

Outstanding accuracy and easy-to-read digital display make this kit a "must" for pilots, boaters—anyone whose activities are affected by the wind. Pick the two readout modes you want from the three available: miles or kilometres per hour, or knots. Switches select mode and front-panel lights show which is in use. Incandescent bulbs mark the 8 principal compass points, providing 16-point resolution. The transmitter boom clamps on to any 1" to 1½" TV aerial mast and connects to the receiver with optional cable.

Digital Indoor / Outdoor Thermometer

KIT ID-1390AE—$97.00

You'll never have to "gauge-guess" again! This fun-to-build kit monitors indoor/outdoor (or any two temperatures) with a big, bright, ½" high digital readout. The readout includes plus and minus signs as well as indoor and outdoor indicator lights, so you know at a glance which temperature is being monitored. Switches select Fahrenheit or Celsius and let you choose continuous readings of one temperature or alternate readings of both. The 85' of cable included lets you place the temperature sensors just about anywhere for a variety of custom applications—home freezer, hot house, garage, basement, pump house, swimming pool, aquarium, almost any temperature.

ID-1390AE SPECIFICATIONS: Temperature Range: Fahrenheit –40 to +120°. Celsius –40 to +50°. Power Requirement: 240V AC, 50 Hz.

ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the Heathkit of my choice. My cheque for $........... is enclosed plus $5.00 for package and post.

Name...
Address..
....
P/code...

☐ **KIT ID-1590E** plus one of either:
  ☐ IDA-1290-1, 50' Cable—$13.00
  ☐ IDA-1290-2, 100' Cable—$23.00
  & choose two of:
    ☐ m.p.h.
    ☐ k.p.h.
    ☐ knots
☐ **KIT ID-1390AE**

Send to: WF Heathkit Centre
220 Park St, South Melb. 3205. Phone 699-4999.

WF 586/77

INTERSIL

HIGH PERFORMANCE C MOS 8-DIGIT COUNTER — ICM7216

ICM7216A Universal Counter, Drives Common Anode LED's
ICM7216B Universal Counter, Drives Common Cathode LED's
ICM7216C Frequency Counter, Drives Common Anode LED's
ICM7216D Frequency Counter, Drives Common Cathode LED's

The ICM7216A and B can function as a frequency counter, period counter, frequency ratio (fA/fB) counter, time interval counter or as a totalizing counter. The counter uses either a 10 MHz or 1 MHz quartz crystal timebase. An external timebase input is also provided. For period and time interval, the 10 MHz timebase gives a 0.1 usec resolution. In period average and time interval average, the resolution can be in the nanosecond range. In the frequency mode, the user can select accumulation times of 0.01 sec, 0.1 sec, 1 sec and 10 sec. With a 10 sec accumulation time, the frequency can be displayed to an accuracy of 0.1 Hz in the least significant digit. There is 0.2 seconds between measurements in all ranges.
The ICM7216C and D function as frequency counters only, as described above.

All versions of the ICM7216 incorporate leading zero blanking. Frequency is displayed in KHz. In the ICM7216A and B, time is displayed in usec. The display is multiplexed at 500 Hz with a 12.5 percent duty cycle for each digit. The ICM7216A and C are designed for common anode display with typical peak segment currents of 25mA. The ICM7216B and D are designed for common cathode displays with typical peak segment currents of 12mA. In the display off mode, both digit drivers and segment drivers are turned off, enabling the display to be used for other functions.

Soon to be released in kit form!

Designated ICM7226 EV Kit, it contains a 10 MHz quartz crystal, 8 each 7 segment .3" LED's, P.C. board, resistors, capacitors, diodes, switches, socket: everything needed to quickly assemble a functioning Universal Counter System.

R&D

R & D ELECTRONICS

VICTORIA
23 Burwood Rd., Burwood.
P.O. Box 206, Burwood 3125
Tel.: 288-8232, 288-8262

N.S.W.
133 Alexander St., Crows Nest.
P.O. Box 57, Crows Nest 2065
Tel.: 439 5488

QLD.
56 Raynham St.,
Salisbury Nth. 4107
Tel.: 275-3188.

AUDITEC POWER 25-250 WATTS

001 Mk.2 30/50 Watts R.M.S. Power Amplifier Module. Load 8/4 ohms. Less than 0.05 percent T.H.D. Fully short-circuit protected.

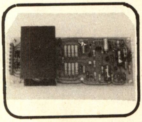

018 60 Watts R.M.S. at less than 0.1 percent T.H.D. Fully short-circuit protected.

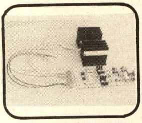

009 120 Watts R.M.S. at less than 0.1 percent T.H.D. Fully short-circuit protected.

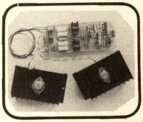

033 Very high quality 100 Watts R.M.S. Power Amplifier for studio work etc. Distortion almost unmeasurable. T.I. distortion almost nil. Produces a subtle difference in sound which has to be heard to be appreciated.

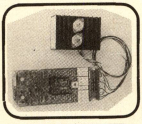

027 250 Watts R.M.S. power amplifier module at less than 0.2 percent T.H.D. Fully short-circuit protected. 8 ohm balanced output.

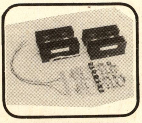

019 25 Watts R.M.S. power amplifier at less than 0.1 percent T.H.D. Powered directly from 12 volt car battery.

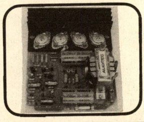

AGENTS:
MELBOURNE: Zephyr Products, phone 568-2922.
BRISBANE: Delsound Pty Ltd, phone 229-6155.
ADELAIDE: Neil Muller Pty Ltd, phone 74-1162.
PERTH: Willis Trading Co., phone 321-7609.
CANBERRA: Musique Boutique, phone 82-2553.
BUNDABERG: Bundaberg Hi-Fi, phone 71-3176.
DARWIN: Darwin Communications Systems, phone 85-3184.
ALICE SPRINGS: Farmer & Davies Electronics, phone 52-2967.
ALBURY: Ray Walsh Systems, phone 21-1502.
TAMWORTH: Hi-Fi Gallery, phone 66-2525.
SURFERS PARADISE: Beno's Musical Supplies, phone 38-1568.
MERMAID BEACH: Rave, 38-3331.
NSW: President Sound, Wentworthville, phone 631-6689; WMR Electronics, Glenfield, phone 605-1203; Dawes Sound System, Blaxland, phone 39-4421.

For descriptive leaflets on these modules call phone or write to:

AUDITEC AUSTRALIA
PTY. LTD.
10 Waitara Avenue,
WAITARA, NSW. 2077.
Phone 48-4116.

(Pacific Highway side of Waitara Station)

A FULL RANGE OF PREAMPLIFIERS, MIXERS AND COMPLETE AMPLIFIERS FOR PUBLIC ADDRESS, STUDIO AND HI-FI IS ALSO AVAILABLE

WHERE
IN MELBOURNE DO YOU PAY MUCH LESS FOR YOUR COMPONENTS

NOW AVAILABLE EX STOCK:

The new SINCLAIR DM 235 Digital Multimeter.

Large 3½ digit display reading to plus/minus 1999. Six functions in 26 ranges. DC volts, 1mV to 1000V, AC volts, 1mV to 750V. DC current, 1uA to 1A. AC current, 1uA to 1A Resistance, 1 ohm to 20M ohms. Diode test, 0.1uA to 1mA. Impedance, 10M ohms. 12 month guarantee. P&P $2.

ONLY **$145** incl tax. ($132 tax exempt)

Also available; The ideal pocket size digital multimeter, the SINCLAIR PDM 35, for only **$61.50** incl. tax. ($56 tax exempt) P&P $2.

We also stock Soar, Sanwa and Arlec multimeters and Trio oscilloscopes, signal generators, etc.

- Philips AD12 K 12 TK 3 way 12" 40 watt speaker kits, complete, $279.50 pr inc tax.
- Philips AD 8K 40 3 way 8" 40 watt speaker kits, complete, $195 pr inc tax.
- Philips AD 8K 30 2 way 8" 30 watt speaker kits, complete, $137.50 pr inc tax.
- Philips ADO 160 T8 stereo tweeter kits incl crossover caps, $26.75 pr inc tax.
- Large range of Philips, Plessey-Foster and CTS speakers in stock.
- Philips EUY-10E 023LE Tape Printers,$71.25 plus tax.
- South West Tech Keyboard kits, $85 ea inc tax.
- Micro Honeywell Hall Effect Keyboards, $120 ea inc tax.
- Daneva Keyboards (63 keys) $45 ea inc tax.

WE NOW STOCK a huge range of semiconductors (incl micro chips) by all leading manufacturers at most competitive prices. Also a full range of capacitors, resistors, plugs, sockets, cables, connectors, instrument cases, transformers, Vero and Blob board, Continental breadboard, ETI and EA project boards, Chart Pak, potentiometers, in fact, just about everything electronic at Melbourne's leading electronic centre.

Send 30c stamp for catalogue. All components can be supplied tax exempt through our new wholesale division, Ellistronics Wholesale P/L.

ELLISTRONICS

289 LATROBE ST, MELBOURNE 3000

Phone (03) 602-3282

INFORMATIVE SYSTEMS —

3 BANK STREET, SOUTH MELBOURNE
A DIVISION OF CAE P/L. PHONE 690-2284

– are proud to be dealers of:

ALTOS Computer systems.
WESTERN TELEMATIC word processing systems.
CROMEMCO system 3 microcomputers and peripherals — full range.
SPACE-BYTE computers.
PROBLEM SOLVER systems.
SOLID STATE MUSIC.
ADDS TERMINALS — full range.
CENTRONICS PRINTERS — full range.
QUME PRINTERS.
INTEGRAL DATA SYSTEM PRINTERS.

– high level languages available:

3k integer Basic.
Basic Compiler.
Multi-user Basic.
16K extended disc Basic.
COBOL.
Data-base management system.
Fortran-IV.
Color graphics.
Macro-Assembler.
Pascal.
Word processing and text formatter.

– business software available from:

Serendipidity Systems Inc.
Microware.
Speakeasy Software.
Software records.
CP/M users group.
Administrative Systems Inc.

– business software available or under development includes:

Motel/Hotel management.
Clinical Accounts Receivable and Billing.
General ledger (accounting).
Payroll (personnel).
Job order control/invoicing:
Commercial Accounts Receivable.
Commercial Accounts Payable.
Inventory control (manufacturer).
Inventory control (retailer).
Professional Appointments (group).
Professional Appointments (individual).
Professional Clinet Billing.
Rental Property management.

We also have software available for: TRS-80, Apple II. We specialise in writing custom software to suit your particular requirements.

O.E.M. DISCOUNTS AVAILABLE

Australia's top ham radio suppliers....with a comprehensive range of the finest gear !

KENWOOD

SPECIALS WITH TRADE-IN

TS520S	HF TRANSCEIVER 10–160M, 240 Vac
TS820S	HF TRANSCEIVER 10–160M, 240 Vac
AT200	ANTENNA TUNER
SM220	STATION MONITOR
BS-5	PAN ADAPTER FOR TS820 SERIES
BS-8	PAN ADAPTER FOR TS520 SERIES
TL922	LINEAR AMPLIFIER
SP520	MATCHING SPEAKER TS520S
SP820	MATCHING SPEAKER TS820S
DG5	DIGITAL DISPLAY TS520
DS-1A	DC/DC CONVERTER TS820
HC-2	WORLD CLOCK 24 HOUR
MC-10	HAND MIC, HIGH Z
MC-35S	HAND MIC, NOISE CANCELLING
MC-50	DESK MIC, HIGH/LOW Z
TS-120V	HF MOBILE TRANSCEIVER
PS-20	AC POWER SUPPLY FOR ABOVE
R-300	COMMUNICATIONS RECEIVER
R-820	COMMUNICATIONS RECEIVER
VFO520S	REMOTE VFO TS520S
VFO820	REMOTE VFO TS820S
YG88C	CW CRYSTAL FILTER TS820

PLENTY IN STOCK

NEW TS-120V HF MOBILE

INTRODUCTORY PRICE $630

BALUNS

BL50A RAK 50 ohm, 4 Kw model for dipoles	$32.00
BL70A RAK 70 ohm, 4 Kw model for dipoles	$32.00
AS-BL ASAHI 50 ohm, ideal for beams	$36.00

CW FILTERS

FT101E	filter $49.00
TS520S	$57.00
TS820S	$57.00

VICOM

hy-gain Amateur Radio Systems.

TH6DXX	beam	$299
TH3Jr	beam	$219
TH3MK3	beam	$239
203Ba	beam	$189
204Ba	beam	$249
HyQuad		$269
18AVT	vert.	$149
14AVQ	vert.	$109

MFJ 40T QRP transmitter. Work the world with 5 watts on 40 meter CW. No tuning. Matches 50 ohm load. Clean output with low harmonic content. Power amplifier transistor protected against burnout. Switch selects 3 crystals or VFO input. 12 V DC operation. **$49**

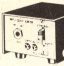

new !

vfo option $49

5w

TRAP DIPOLES

Midy VNB 80 thru 10m trap dipole, 23m long	$111.00
AL24DXN 20 and 40m trap dipole	$70.00
A4VPN 40m dipole kit	$27.00

PARABOLIC DISH

PARABOLIC DISH FOR 432 & 1296 MHz A professionally engineered dish with 12 db and 20 db gain on 70 cm and 1.2 GHz. $349

DISCONES

GDX-1 80 thru 480 MHz commercial discone	$85.00
SCAN-X 65 thru 530 MHz receive only	$39.00

ICOM

The Ultimate!

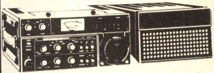

State of the art

ICOM IC-701 HF transceiver

The NEW 701 features: • Solid-state • 100W continuous on all bands, all modes • USB, LSB, CW, CW-N, RTTY operation • Double balanced Schottky Diode Mixer used in both RX/TX • Dual built-in digital VFO and much more!

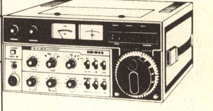

ICOM IC-211 2m transceiver

Features: • 144 to 148 MHz coverage • Modes: SSB, CW, FM • LSI synthesizer PLL • 4-digit LED readout • Pulse-type noise blanker • VOX, antivox • Semi-break-in CW • Built-in SWR bridge • CW monitor and much more!

HF transceiver, solid-state	$1,480.00	IC701
AC power supply	$253.00	IC701PS
2m all-mode transceiver	$799.00	IC211
Remote control head	$169.00	RM3

PORTABLES

IC215	2m fm incl. 5 channels	$245.00
IC402	70 cm ssb portable	$469.00
IC202S	2m ssb portable USB/LSB	$357.00
IC202E	2m ssb portable	$239.00

ACCESSORIES FOR THE PORTABLES

LC025	Leather case	$12.00
FA-1	Rubber ducky antenna	$12.00
MMB-B	Mobile mount	$22.00
BC-20	Nicad pack	$69.00

Well, it had to happen !

2m hand-held

800ch Synthesised

144–148 MHz **Palm size**

Sooner or later it had to happen. Now Vicom are proud to introduce the first ham hand-held synthesised 2m rig with thumbwheel dial-up of frequencies 144–148 MHz. The palm size (40 x 62 x 165 mm) and 400 gram weight of this NiCd rig makes it ideal for the ham on the go!

RF output power : 1.5w
Harmonics : –60 dB
Spurious : –70 dB
Repeater offset : +600 KHz or –600 KHz
Sensitivity : 0.3 uV 20 dB SINAD

The unit features high quality construction with double sided glass-epoxy pcbs.

And your new hand held comes complete with VICOM 90 day warranty and service back-up.

$399.

1.5w

WOW

NEW!

TUBES

6JS6c	$12.50
6KD6	$13.00
12BY7A	$ 3.50
6146B	$13.50
572B	$61.00

Stacks of quality accessories

USED GEAR Call or Order By Mail

bankcard

DINERS CLUB AUSTRALIA

ICOM 2M FM

IC-22S

The famous IC22S transceiver – more of these sold in Australia than any other 2m Rig. Price: $330.00

2m mobile

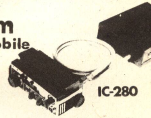

IC-280

The popular remotable 2m fm Rig. Price: $450.00

VICOM

68 Eastern Rd.
Sth Melb. 3205 ph 699.6700

Perth	446-3232	Sydney	681-3544
Adelaide	43-7981	Brisbane	38-4480
Gold Coast	32-2644	Hobart	43-6337
Canberra	82-3581		

Amateur News

Auroral Scatter

The first reported auroral scatter contacts in about 20 years for this part of the world occurred on the night of 28th August last. Contacts between Victoria (VK3), South Australia (VK5) and Tasmania (VK7) were reported with about a dozen stations involved. Both the six metre and two metre bands were used during the period of the opening.

An auroral formation was visible to the south of Tasmania at about 1900 hrs. First contacts via auroral scatter were on CW at around 2000 hrs between VK7JG and VK7AH who maintained contact for about an hour. The aurora flared up at 2230 hrs, the formations moving north. It was subsequently visible from as far north as Birchip in Victoria and Albury in southern NSW. The predominant aurora was a light-coloured arc visible in the south-western sky.

VK30T and VK3ATN in north-western Victoria made contact at 2300 hrs and were successful on SSB apart from CW, despite the heavy 'buzz' on the signal – the most noticeable characteristic of auroral scatter signals.

The visible aurora faded around 2330 hrs, signals dropping at the same time. The opening faded at around 2345 hrs.

From reports it seems that high erp greatly assists propagation and the successful stations were running between 100 and 400 watts PEP on six metres to beams ranging from four elements to 11 elements (VK3ATN). On two metres, stations running high power into large arrays were reportedly the most successful.

Auroras peak during the winter months and could provide some welcome excitement and a boost to wintertime activity which is traditionally very low in Australia in contrast to the summer 'DX' season.

Stations reported to be involved in the 28th August opening were: VK3ATN, VK30T, VK5KK, VK5ZMO, VK7AH, VK7AK, VK7BC, VK7JC, VK7LZ, VK7MC and VK7ZAH.

There should be many more opportunities to explore this mode of propagation over the coming solar cycle peak, so gentlemen of the amateur fraternity, dig out your reference books, sharpen up your wits and keep a sharp lookout for all the indications (solar flares, magnetic storms, watery HF signals etc).

The Channel 5A/0 Battle

Now that there's a 'leg in the door' towards the introduction of UHF television, as reported last issue, now is the time to press your local politician and the Minister for P & T (the Right Honourable A.A. Staley) for the removal of Australia's non-standard TV channels – 0 and 5A.

There's a wealth of material to support the amateurs' case for the removal of 0 and 5A in local amateur publications and from the WIA. See your local Member of Parliament, discuss the *basics* of the issue in a *clear, concise* manner and let him know that radio amateurs exist, what we are and what we do – stress the aspects of the radio amateur as a community resource. If you can organise, get other amateurs who live in the same electorate to go along, either singly or maybe en masse, if you can arrange it!

The fight has just begun!

The "Gosford Field Day"

This most-famous of annual amateur radio events will recur next year (that's 1979!) on Sunday 18 February. Commencing at 0800 (Daylight Saving Time) and ending at 1615 on the appointed day, the Gosford Field Day (as it is colloquially known) will include the 'usual' range of events: scrambles, foxhunts, demonstrations and *new* this time – *a workshop.* This will be run by Des Clift, VK2AHC, and the workshop facilities will include:

Sweep gen. with VSWR attachments, 10 MHz – 2 GHz
Deviation meter, 5.5 MHz – 1 GHz
Power meters, 10 MHz – 12.4 GHz
Frequency measurement up to 12.4 GHz.

The registration fee is a mere $4 for men, $2 for women (that's sexist discrimination!), $1 for children 16 years and under with a pensioner concession of 50%.

The event will be staged at the familiar venue: the Gosford Showground, Showground Road, Gosford (amazing address!).

To the uninitiated the Gosford Field Day is organised by the Central Coast Amateur Radio Club and is probably the biggest amateur event of its type in this country attracting some 700 registrants each year.

For full details and program, write to (including SAE): *The Secretary, CCARC, P.O. Box 238, GOSFORD 2250.*

Dick Smith Covers Yaesu

Dick Smith Electronics advise that they have available a heavy duty PVC cover to suit Yaesu amateur equipment – the popular FT101E transceiver, FL2100B linear, FRG-7 and FRG-7000 general coverage receivers and the FT901D transceiver.

Recommended for keeping out dust, creepy-crawlies (except those tenacious ones that crawl up from underneath) and to prevent scratching of the equipment, the cover should help to maintain the appearance and resale value.

The covers are supplied free with the purchase of any major piece of Yaesu equipment or they may be purchased separately for $3.95 each (catalogue number D-9050).

More Auroral Scatter – stop press!

The excitement of August 28th returned on the evening of 29 September when stations in VK3, VK5 and VK7 were treated to a seven hour opening.

The fun started a little before 0730 z when VK7DA, Dan, worked VK30T on CW on 52.050 MHz promptly followed by VK5PB who worked Steve VK30T but could not hear the VK7. During the following hour the following stations cashed in on the opportunity: VK3AAK, VK3AQR, VK3ATN and VK3OT with VK5KK, VK5PB, VK5ZMH, VK5ZMO and VK7DA, VK7JG, VK7KJ and VK7LZ.

The aurora flared up around 1030 z when the following stations mixed it on six metres with signals at very good strength – VK1RK and VK1VP; the VK3's mentioned previously were this time joined by VK3AXV, VK3AZY, VK3BKF and VK3BMV. The VK7's were joined by VK7AZ, VK7FA, VK7JG, VK7KJ, VK7MC, VK7ZAH, VK7ZIE and VK7ZIF.

Most everybody gave it away around 1430 z (well after midnight local).

Long distance TEP

In between the first and second bouts of auroral scatter on 29 September reported above, the KH6EQI beacon, from Hawaii, was heard for a considerable period and over a wide area in Australia from around 0900 z. Stations in VK4, VK5 and VK3 reported hearing the beacon, running at strengths over S9 on occasions. No contacts were made despite frantic phone calls to Hawaii and attempts to drum up 50 MHz operators on the 21 MHz band.

However, on October 16, at 0915 z, VK2YDY and VK2BXT, later joined by VK5KK and VK5LP worked KY6EQY, Hawaii. This is the first Hawaii-Australia contact for around 20 years.

WOW! Feast your

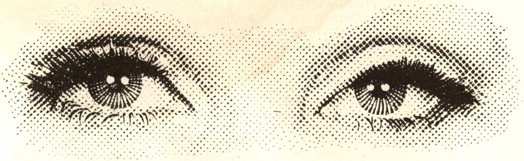

on this new Kenwood gear!

TS-120V

HF SSB-CW Mobile Transceiver: 30W PEP, Digital display, full 10M coverage, plus 80, 40, 20, 15 meters, Noise Blanker, RIT, Vox, WWV, and 25 kHz marker. Rugged construction with diecast front panel and finished with usual KENWOOD quality features. Size: 241mm W x 94mm H x 235mm D.

TR-7600

VHF FM 800 Channel, 10 watt Transceiver: Over 10 watts output, full repeater coverage, provision for external Microcomputer control and scanning. Pushbutton memory with Hi-Low power. Frequency range, 144 MHz to 148 MHz. Size: 60mm H x 160mm W x 220mm D.

KENWOOD

TRIO-KENWOOD (AUSTRALIA) PTY. LTD.

31 Whiting Street, Artarmon, Sydney. NSW. Australia. 2064. Tel: (02) 438-1277.

Interstate Distributors:
VIC: Vicom Imports Pty Ltd (03) 699-6700
QLD: Mitchell Radio Co (07) 57-6830
SA: International Communications Systems P/L (08) 47-3688
WA: Willis Trading Co. (09) 321-7600
TAS: Advance Electronics (003) 31-5688
NT: R.J. Klose (089) 81-8704

CB News

K40 Magnamount

President Electronics (Aust.) markets the popular American Antenna Company's K40 base-loaded mobile whip here in Australia. The parent company recently released a magnetic mount to suit their K40.

Called the "K40 Magnamount", it features a toroidal magnet 116 mm in diameter – considerably larger than the magnets in the biggest magnetic mounts currently available in Australia. These latter usually measure around 90 mm in diameter.

The manufacturers indicate that the magnet used consists of eight magnets set around the circumference of the ring to produce a powerful magnetic seal. They claim this construction assists the radiation pattern of the K40.

The K40 Magnamount will retail here for $21.95 and is distributed by *President Electronics Australia, 506 Miller Street, Cammeray, NSW, 2062;* phone (02) 922-3827.

CB Australia 21 and Glossy!

Sister publication, CB Australia's 21st issue was the November one with which it commences printing on quality gloss paper throughout the magazine.

The change is an effort to further boost its standing in the market place (already held in high regard for its technical accuracy and news content) and to effect a change in the 'image' of CB – now being referred to increasingly as 'personal communications' and similar phrases by the trade. It is felt that an improved quality publication will reflect and/or lead an emerging trend towards more sane on-air activities, particularly on the UHF band, and marketing attitudes.

Catering to wider reader interests, and expanding the existing interests of readers, is a new feature of CB Australia. It has provided articles of interest to novices (many of whom 'step up' from the CB ranks) since the July issue, and in recent issues has highlighted shortwave listening. Simple electronic construction projects of interest to CBers have become a regular part of CB Australia as many CBers have had an interest in electronics sparked from their hobby.

CB Australia continues to grow. It's come a long way since the first issue, published as a supplement to the February 1977 edition of ETI, running to 32 pages – Australia's first national CB publication.

NZ CBers Get Boost

New Zealand CBers received a welcome increase in channels and power output in recent months and are now allowed to use an *extra four channels* and transmitter output power has been increased from 0.5 watt to 2 watts. The four extra channels are:–

26,600 MHz
26,625 MHz
26,650 MHz
26,675 MHz.

In addition, NZ Government Departments, public bodies and 'approved' (?) operators are allowed to use a further three channels on 26.700, 26.725 and 26.750 MHz.

New Zealand's first CB magazine has appeared also – CB World.

CB Invention Now 'Secret'

The four inventors of a new CB voice scrambler have had a secrecy order slapped on them by a US Intelligence agency responsible for eavesdropping on communications of foreign governments and decoding such messages.

The four inventors, Carl Nicolai, Carl Quale and David Miller – all from Washington, and William Raike of Monterey, California, can't sell their device because it's considered a threat to national security!

When they applied for a patent for their device the Patent Office, part of the US Commerce Department, issued a secrecy order instead of a patent! This forbids the inventors from discussing or manufacturing their device under threat of prosecution.

The invention uses an unrevealed (naturally!) technique that scrambles the voice at the transmitter, reversing the procedure in the receiver, it was reported (that's the way most scramblers work!).

Dick Smith Enters UHF Market

Dick Smith has announced that he will be marketing a UHF CB rig under Midland label in Australia, due for release this month.

Although designed as only a 'basic rig' – no LED display or preselected channel options – Dick Smith claims the rig features better adjacent channel rejection than 'current' UHF equipment (i.e.: the Philips FM320).

It is believed that the rig will retail for less than $300.

SWL News

Compiled by Peter Bunn, on behalf of the Australian Radio DX Club (ARDXC).

All times are given in GMT (Greenwich Mean Time); all frequencies are in kiloHertz (kHz).

Summertime Signals On 60 Metres

With summer now upon us, you will discover that the 60 metre band – that part of the frequency spectrum from 4750 to 5060 kHz – such a rich source of exotic reception from Latin America during our winter months, trends towards better reception of Asian broadcasters. By systematically scanning this band during our evenings, many countries can be heard, so let's present a brief rundown of some of them:

Indonesia has a great array of shortwave broadcasters serving the different areas of this vast archipelago, often broadcasting with humble facilities in small towns for their local audiences. Programs are therefore almost invariably in the Indonesian language. Most evenings you should be able to hear some of the stations of the closest province, Iran Jaya, but about 0930. The best of these should be Radio Republik Indonesia at Sorong operating on 4875. The station gives station identification fairly regularly, and will start like this: "Inilah Radio Republik Indonesia Sorong", with "Inilah" meaning "this is". Shortly after 0930 you should also be able to hear the station in the provincial capital of Irian Jaya, Jayapura, on 4980 but the Jayapura outlet will suffer bad interference from a Venezuelan station which opens transmission on the same frequency at 1000, but don't be deterred, as Jayapura will still be there when the Latin station fades out soon after 1130, and will be audible through to evening closedown at 1400. Yet another Irian Jaya station is located at the small town of Fak Fak on the western side of the province, operating on 4790 and this station should also be audible by 1000.

Soon after 1000, you will be able to hear some of the stations in the central area of Indonesia. Two of the strongest signals are usually those emanating from Radio Republik Indonesia at Surakarta on 4932, and Radio Republik Indonesia at Yogyakarta on 5047, both cities located in Central Java. Yogyakarta is quite unusual, in that it is one of the few regional stations in Indonesia to broadcast an English program, which is currently heard each night at 1130-1145. By around 1030, some of the stations in the island of Sumatra will become audible, and the best of these is usually Radio Republik Indonesia at Palembang, operating on 4855. For night-owls, this one is audible right through to 1600 closedown.

A special note regarding those regional Indonesian stations. Do not be surprised if you hear a station identification on any of the above stations for "Radio Republik Indonesia dari Jakarta". All stations carry the news on relay from Jakarta each night at 1200.

Moving further west a little, we reach **Malaysia**. Malaysian stations come in three varieties: penninsula Malaysia or West Malaysia, and the provinces of Sarawak and Sabah, located on the island of Borneo. Penninsular Malaysia has shortwave outlets carrying Home Service programs from Kuala Lumpur operating on 4845, which is audible most nights by 1100. You can also hear the transmitter located at the northern centre of Penang, on 4985 which becomes audible by about 1030 nightly, and carries some English programs as well as programs in Malay. Moving to the other Malaysian states, the small state of **Sabah** has a transmitter at Kota Kinabalu which operates on 4970, and generally is heard from about 1100 when the Venezuelan station also operating on the frequency fades. In **Sarawak**, there are shortwave transmitters at three centres, at Kuching, Sibu and Miri. Best signals are provided by the Kuching outlets operating on 4835, 4950 and 5030, and the Sibu transmitter on 5005, most of these outlets carrying programs in Malay and local languages, though 4950 carries English programs. Malay has a very similar sound to that of the Indonesian language, and again the key word in station identification announcements is "Inilah" followed by "Radio Malaysia" and the name of the town where the studio is located. Regional stations often relay the news from Kuala Lumpur, and these take place most nights at 1130 and 1530, so at these times you are likely to hear the station identification from Kuala Lumpur, regardless of which station you are tuned to.

Finland

Radio Finland has a daily English program for Australia and the Far East between 0930 and 1000, using 21495. On Sundays, there is the special weekly magazine program for Australia between 0800 and 0930, also on 21495, which is known as "Radio Finland in its Sunday Best". A new program this summer is DX Editor Davis Mawby's "World of Radio" which will be heard on the Sunday Best program every fortnight. The program will include reviews of different sections of the radio spectrum telling about its particular characteristics, who broadcasts there, and how you may best tune in.

Tropical Band Survey Now Available

This survey, published annually by the Danish Shortwave Clubs International, provides a comprehensive listing of stations broadcasting in the "tropical bands" between 2000 and 5900 kHz. It is highly recommended and perfect in aiding you in your reception of the many exotic Asian signals over these summer months, not to mention its value for next March or April when signals from Africa and Latin America begin to reach their peak on this part of the spectrum. If you would like a copy, just write to the ARDXC asking for the "DSWCI Tropical Bands Survey" and enclosing 8 International Reply Coupons.

Turkey

Voice of Turkey has been observed on two new channels for the Foreign Service with the French program noted on 11955 and 6185, followed by the English service between 2130 and 2300 daily. Other frequencies announced as carrying this service are 9515 and 7170.

Spain

Radio Exterior de Espana at Madrid has added the new outlet of 9790 for programs in Spanish every day between 0800 and 1130, this outlet being in parallel with both 9520 and 11730. This constitutes a new out-of-band channel for Madrid, as the normal 31 metre shortwave broadcast band ends at 9750. This is yet another example of an international broadcaster resorting to the technically illegal practice of going outside the designated bands in order to find a vacant frequency.

Portugal

Voice of Hope (Adventist World Radio) had introduced a the new channel of 9665 for the special Sunday services via the facilities at Sines in Portugal. Good signals are noted at present, with German programs at 0730; English programs are scheduled for broadcast between 0900 and 1000.

Ethiopia

An interesting station providing excellent reception at present is the Voice of Revolutionary Ethiopia in Addis Ababa. The station has a daily English service between 1500 and 1600, which is carried on both 9615 and 7165. Much local and western music is presented, along with current affairs talks.

Singapore has two transmitters operating in the 60 metre band, on 5010 and on 5052. Both these channels carry the English language service, and usually provide good reception during summer from around 1030 until sign-off at 1630.

Vietnam is a country with a host of shortwave transmitters in various regional centres throughout the country, but possibly the best reception on 60 metres will be of the Home Service programs carried on 4943 with the first program, and on 4995 with the second network, all in Vietnamese. Incidentally, in our mornings, the 4943 channel carries an English segment daily at 2130-2145, taken up largely with language lessons.

Cambodia has a powerful transmitter located at Phnom Penh, which may be heard every night from sign-on at 1100 on 4908. The music from this station is something quite distinctive.

By about 1130, you should also be able to hear the home service program of **Radio Thailand** in Bangkok, operating on 4830 with a 10 kilowatt transmitter. The key word to listen for, which precedes all station identifications, is "Thiini" and the station name is given.

Probably the ultimate in exotic listening is Radio Ulan Bator, in **Mongolia**, which has a transmitter which operates on approximately 5053, varying to 5055 on occasions. During summer, Ulan Bator may be heard from about 1100, but you may have to be a little persistent to hear this one!

There are many more obscure and exotic stations to hear on the 60 metre band during summer, such as the small Laotian and Vietnamese regional stations which seldom seem to operate on exactly the same frequency every night, and utilise transmitters which could perhaps be best described as "home made"! All these stations, with the exception of Cambodia and some of the smaller Vietnamese stations, will verify listeners' reception reports. Many of the smaller stations will require reports to be written in their local language, especially those in Indonesia. To aid listeners in forwarding reports to such stations, the Australian Radio DX Club has a publication called the "Indonesian Reporting Guide" which sets out in detail all information you will need for writing reports to Indonesian stations, including complete translations with glossaries of words, phrases and sentences used. Write to the ARDXC if you are interested in obtaining a copy.

Norway

Radio Norway in Oslo has supplied details of its schedule for the period November to March (that is, period "D" -78) and this shows programs to Australia, New Zealand and the Far East broadcast daily from 0700-0830 on 9590, 11850 and 21730. A further service to Australia, Indonesia and the Far East is listed between 1100 and 1230 on 21730, and 17840. Both these services include an English segment for the last half-hour of the Sunday program. All other programs are in Norwegian.

Greece

The Voice of Greece at Athens provides its schedule for "D"-78, effective until March 1979, showing programs in Greek and English beamed to Australia 0900-0950 daily on 15160 and 9655. The morning service for Australia is on the air 2100-2150 on 9760, 9655, and 6140 with programs continuing in Greek on 9655 until sign-off at 2250. The morning service carries English news at 2115, while in the evenings a bulletin of news in English may be heard at 0915.

The Australian Radio DX Club is a non-profit body with headquarters in Melbourne and members Australia-wide. For further information regarding shortwave radio and the ARDXC, please write to the General Secretary, PO Box 67, Highett, Vic. 3190, enclosing a 30c stamp.

YAESU

FRG -7

RECEIVER

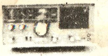

for amateurs,
novices
and
short-wave
listeners

Latest model includes fine-tune adjustment

MANUFACTURER'S TECHNICAL DATA

- Electronic band changing.
- 0.5-29.9 MHz continuous coverage.
- Uses Wadley loop (drift cancellation circuit) to derive synthesized hetrodyne oscillator signal.
- LSB, USB, AM and CW.
- Frequency readout better than 10 KHz (readable to 5 KHz).
- Stability within 500 HZ during any 30-minute period after warm-up.
- Better than 0.7 V for 10 dB S N/SSB and CW. Better than 2 V for 10 dB S N/N AM.
- Selectivity 3 KHz at -6 dB, 7 KHz at -50 dB.
- Input Impedance high 0.5-1.6 MHZ. 50-75 ohm 1.6-29.9 MHz.
- 234V AC 50-60 Hz or 12V DC external.
- Internal dry cell operation optional.
- Size 340 mm x 153 mm x 285 mm.
- **Price $389.00**
- YAESU FRG 7 internal battery holder for 8 size 'D' cells, $10.
- Prices include S/tax, freight extra. Prices and Specs subject to change.

Explore the wonderful world of short-wave listening.
Hear broadcast stations, amateurs, ships, aircraft and morse code from stations all over the globe.
Provides an introduction into many aspects of electronics and communications, CB'ers upgrade and widen your scope of operation. The FRG-7 will provide the means of listening to the amateur bands so that you can get the "feel" of amateur "ham" radio.
You can tune into the morse practice transmissions and broadcasts conducted by the Wireless Institute of Australia; the Radio Amateurs representative Society in Australia.
Write for a descriptive brochure.
Remember, BAIL has been the authorised agent for the YAESU MUSEN CO LTD since 1963. Our experience gathered over these yearyears, and a lifelong participation in electronics, places us in a superior position to handle warranty, after sales service and advice on the wide range of Yaesu amateur radio equipment.
Avoid unauthorised handlers of equipment as it generally results in the supply of non-export 110V sets with 2-core AC power cables, instruction manuals printed in Japanese, lack of service etc.
Consult us for advice on your requirements in the field of short-wave listening and amateur radio.
For further information call or write to the Amateur radio specialists.

Australian YAESU Agents since 1963.

bail ELECTRONIC SERVICES
60 Shannon St., Box Hill North
Vic., 3129
Ph 89 2213

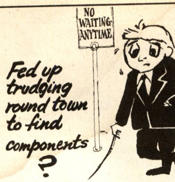
NO WAITING ANYTIME
Fed up trudging round town to find components ?

VESCO

ELECTRONIC SUPPLIES

318 Huntingdale Rd, Huntingdale.
Vic. 3166. Cnr. of Hume St.
Phone 543-4826.
Open Fri night till 9pm & Sat morn.

KENWOOD

THIS MONTH'S OFFER

KA 3700 22 watts per channel, $185.
KA 5700 40 watts per channel, $315.
KT 5500 AM-FM Tuner, $215.
KD 2000 B-D Turntables, $199.
KR nh90 Tuner-Amp, $275.
LS-30 SP System, $149.
KS 3000 System, $520.
KH-33 Headphones, $29.

THE AUDIBLE DIFFERENCE

* SPECIAL!

LEDS RED	20c ea.
BC 548	20c ea.
BD 139	60c ea.
NE 555	45c ea.
CD 4011	40c ea.
74107	50c ea.
1 WATT RESISTORS	6c ea.
BC 558	20c ea.
BD 140	60c ea.
741	45c ea.
4012	40c ea.
9N07	50c ea.

- ¼/½ WATT RESISTORS 4c ea. or 100 for $2.20
- .0033 100V GREENCAPS 20c ea.
- 16V 100mfd rb ELECTRO'S 20c ea.
- 16V 220mfd rb ELECTRO'S 25c ea.
- 16V 2200mfd ELECTRO'S 50c ea.
- SOLDER PACKS 60c ea. SOLDER WICK $2.40
- PC BOARD $1.00 per sheet.
- INSTRUMENT CASES FROM $2.00
- P.V.C. INSULATION TAPE 20 yard roll for 40c.
- TDK C90 CASSETTES $2.80 ea.
- RALMAR C90 CASSETTES $1.50 or 10 for $1.40 ea.
- RALMAR AUDIO ACCESSORIES.
- HIRSCHMAN AUDIO CONNECTORS.
- FERGUSON LOW PROFILE TRANSFORMERS.

MAIL ORDER FOR COUNTRY & INTERSTATE AREAS.

bankcard welcome here

ELECTRONIC AGENCIES

NOW OWNED AND OPERATED BY

BILL EDGE

Experts in

ELECTRONIC COMPONENTS
SPEAKERS and
SPEAKER BOXES
CB's
PLUGS and SOCKETS
CAPACITORS, RESISTORS
INTEGRATED CIRCUITS
TRANSISTORS
KITS, KNOBS
AERIALS and
ACCESSORIES
WIRE, BOOKS
HI-FI EQUIPMENT
CASSETTES
AUDIO ACCESSORIES
TOOLS
PC BOARDS
ETCHING EQUIPMENT
TRANSFORMERS
TEST EQUIPMENT
CALCULATORS
BURGLAR ALARM
ACCESSORIES
ELECTRICAL
ACCESSORIES, ETC.

9am-5.30pm Mon-Fri. 9am-Noon Sa

115-117 Parramatta Rd, Concord.
PHONE: 747-6472
PO Box 1005, Burwood Nth. NSW. 2134.

HiFi CiTY

269 ELIZABETH ST, SYDNEY

251 CHURCH ST, PARRAMATTA

10%

DISCOUNT TO ETI READERS

Stylus and cartridge

- EMPIRE • KENWOOD
- AUDIO TECHNICA • NORD
- ADC • EEI • DYNAVECTOR
- SURE • DENON
- AKG • STAX
- STANTON • SHARP

tone arms

- ADC • DYNAVECTOR
- SME • AUDIO TECHNICA

headphones

- MARUNI • KENWOOD
- SENNHEISER • STAX
- CORAL • AUDIO TECHNICA

speaker kits

- HARMONIX • CORAL
- PHILIPS

MAIL ORDERS

ENQUIRIES WELCOME

TEL: (02) 235-7863, 235-8401

Electronics Today International

4600 and 3600 SYNTHESIZERS

Complete plans for the Electronics Today International 4600 Synthesizer are now available in book form. Many hundreds of these remarkable synthesizers have been built since the series of construction articles started in October 1973 issue of Electronics Today.

Ensure your copy!

Send $12.50 to Electronics Today International,
15 Boundary Street, Rushcutters Bay, 2011.

INTERESTED IN ELECTRONICS?

TAFE

MOORABBIN TECHNICAL COLLEGE

OFFERS THE FOLLOWING COURSES FOR 1979

TAFE ADULT ELECTRONICS

BASIC ELECTRONICS

Pre-requisites: 4th Form (Year 10) Maths, Science & English.
A 2 year course of 8 Hours (2 nights) per week.

SPECIALIST

RADIO
AUDIO & HI-FI
COMMUNICATIONS
DIGITAL
TELEVISION

Pre-requisites: successful completion of Basic Electronics Course or equivalent.

HOBBY

AMATEUR RADIO
AUDIO & HI-FI
HOBBY ELECTRONICS
DIGITAL HOBBY
HOBBY MICROCOMPUTER

ADVANCED AND TECHNICIAN

RADIO – AM & FM
AUDIO & HI-FI
COMMUNICATIONS
DIGITAL
MONOCHROME TELEVISION
COLOUR TELEVISION

MOORABBIN TECHNICAL COLLEGE IS A NEW COLLEGE OFFERING TRAINING WITH THE LATEST EQUIPMENT IN MODERN, WELL EQUIPPED CLASSROOMS.

ELECTRONICS TRADE DEPT
Audio Communications Digital Electronics Radio TV

FOR FURTHER INFORMATION

PHONE 95 9300 Ext. 11 or 36

TAFE COMPONENT:
15 FLETCHER ST.,
MOORABBIN,
VIC. 3189.

predictions

The Ionospheric Prediction Service have kindly developed propagation predictions for us, in the form of a computer printout, which we can reproduce directly. These predictions are known as GRAFEX and contain a lot more information than those we published previously.

The left hand vertical column of each printout lists the frequency, in MHz, for each horizontal row of characters. Each vertical column of characters represents one hour, commencing at 00 UT on the left-most column going to 23 UT on the extreme right column.

Each printout is for a particular path, named at the bottom. The month to which the predictions apply, the mean path distance and the great circle bearing are also listed beneath each printout.

A variety of up to ten characters may appear on the printout and their meanings are listed in the table reproduced here.

The form of the GRAFEX predictions allows the indication of several 'modes' of propagation. The *first* mode is that requiring the least number of 'hops'. This will mean *two* hops on paths of length 4000 to 6000 km or so, *three* hops on paths around 7000 to 10,000 km in length, and so on. The *second* mode for a path will be the next integral number of hops that may be required to propagate a signal over the path.

Thus, the second mode for paths around 4000 to 6000 km in length will involve *three* hops and for paths 7000 to 10,000 km long will involve *four* hops, and so forth.

Mixed modes may also be indicated (symbols M, S and X). That is, a combination of hops involving both first and second modes perhaps (this indicates that considerable fading may be experienced on signals); a mixture of hops involving both the E and F layers of the ionosphere, etc. (See "Propagation, a Closer Look", the July 1978 issue of ETI, pages 112 to 114.).

For ultra-reliable predictions follow the times and frequencies indicated by the F characters on the printouts. For a bit of adrenalin in your operating, use the % symbols area of the printouts. But, for a real 'buzz' look to the do symbols area and hang around during the month of the predictions for those magic days when the higher frequency DX starts pouring through!

Six metre band amateur enthusiast should scan the printouts for those tha have characters extending into th 40 MHz region and operate accordingly.

Co-ordinated Universal Time (UT) i used on all predictions. For mos people's purposes that's equivalent t the well-known GMT. Thus, times fo Eastern Australia will be 10 hours ahea (Eastern Australian Standard Time c E.A.S.T.); for central Australia, 9 hours ahead and for Western Australia 8 hours ahead. Don't forget to take int account Daylight Saving Time wher and when it applies. Oh, heck, sav yourself all the hassle and run a cloc in the shack set to Universal Time!

For information on the areas serve by the prediction charts, see ETI Jul 1978, page 113.

' '	A blank means no propagation is possible by a normal first or second mode.
'.'	A dot indicates that propagation is possible but probably on less than 50% of the days of the month. This normally applies for the first F mode but under some circumstances the first mode may not be propagated because the layer is too low (usually for hops greater than 3000 kilometres) in which case the symbol applies to the second mode.
'%'	Propagation is possible between 50% and 90% of the days of the month. It should be noted that the median F MUF for each hour lies between the lowest ' . ' and the highest ' % ' for that hour.
'F'	Propagation is possible by the first F mode on at least 90% of the days of the month unless there is a severe ionospheric disturbance. For frequencies on the highest 'F' for the hour the probability is 90% but this will increase slightly on lower frequencies.
'E'	Propagation is possible by the first E mode and on less than 50% of days by the first F mode. This symbol overrides ' . ' if present.
'P'	Propagation is possible by the first E mode and between 50% and 90% of days by the first F modes. This symbol overrides ' % '.
'B'	Propagation is possible by the first E mode and by the first F mode on more than 90% of the days. This symbol overrides 'F'.
'M'	Propagation is possible by both the first and second F modes. The strongest mode is normally the first mode but the vertical aerial pattern may influence the mode received. It should be noted that the second F mode MUF is just about the highest frequency showing 'M'.
'S'	Propagation is not possible by the first mode but it is possible by the second mode. It should be remembered that propagation may be possible by other modes, e.g.: the third F or mixed E and F modes at these frequencies. This symbol does not occur very often.
'A'	High absorption i.e.: above the ALF but probably too close to it for good communication.
'X'	Complex mixture of modes including the second E mode (the vertical angles of the first F and the second E modes are often very close).

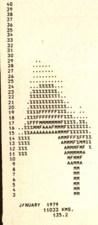

East Coast — South Africa (also serves South Central)

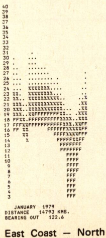

East Coast — North Africa (also serves South Central)

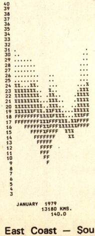

East Coast — South America (also serves South Central)

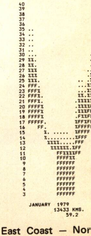

East Coast — Nor America (also NE a South Central)

SWL and AMATEUR COMMUNICATIONS

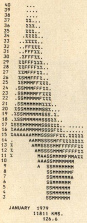

East Coast — Japan (also serves NE and South Central)

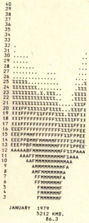

East Coast — South Pacific

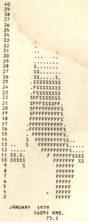

East Coast — Europe (Short Path)

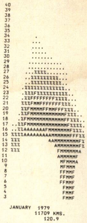

North East — South Africa

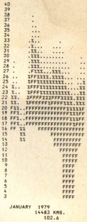

North East — North Africa

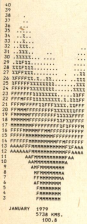

North East — South Pacific (also serves South Central)

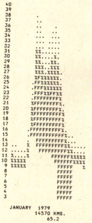

North East — Europe (Short Path)

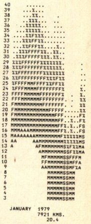

West Coast — Japan

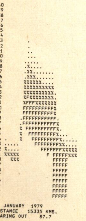

outh Central — Europe
Short Path)(also West
oast)

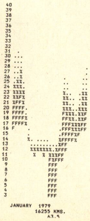

West Coast — North America

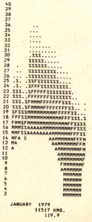

West Coast — North Africa

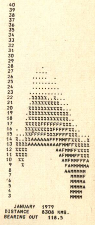

West Coast — South Africa

(Advertisement)

OUR XMAS SPECIAL OFFER FOR ETI READERS

ELAC BELT DRIVE-PLUS TURNTABLE

FOR ONLY $199 (RRP $389)

ELAC
high fidelity

If you missed our previous offer this is now your chance!

It's hardly necessary to state that the PC 830 exceeds DIN 45 500. It leaves it way behind!
The 830 is a unique unit which combines the vibration decoupling advantages of belt drive units with the trouble free running of the classic idler wheel design.

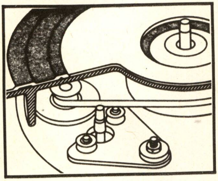

In essence the 830 may be seen as a belt-drive unit but with an idler wheel drive which automatically aids the drive belt whilst running up to speed and also during the inward and outward movement of the pick-up arm. In addition the mechanism ensures that the drive belt is slackened off whenever the turntable is switched off thus preventing belt stretching unevenly.
The result of all this is extraordinary smoothness reflected in a wow and flutter figure of 0.08 percent. Rumble is down to 44 dB and signal noise 64 dB.
Naturally the unit operates in both manual and fully automatic modes and has a record repeater plus auto changer mechanism.
It is supplied with ELAC's STS 355-17 magnetic cartridge and has all the features you'd expect to find on a near-$400 unit.

ELAC TURNTABLE XMAS SPECIAL OFFER

Please forward .... ELAC PC. 830 Turntable complete with deluxe base and hinged lid including ELAC STS 355/17 magnetic cartridge for $199.00 each. (plus $5 post/packing in NSW, plus $7 post/packing interstate.)

NAME ....

ADDRESS ....

.... Postcode..............................

Please allow a minimum of 2 weeks for delivery. Please make cheques etc. payable to "ATRAM OFFER" and post together with order form to:

"ATRAM OFFER" c/o P.O. Box 465 North Sydney N.S.W. 2060 Tel. 92-4177

MXR

Dual Fifteen Band Equalizer
Thirty-One Band Equalizer

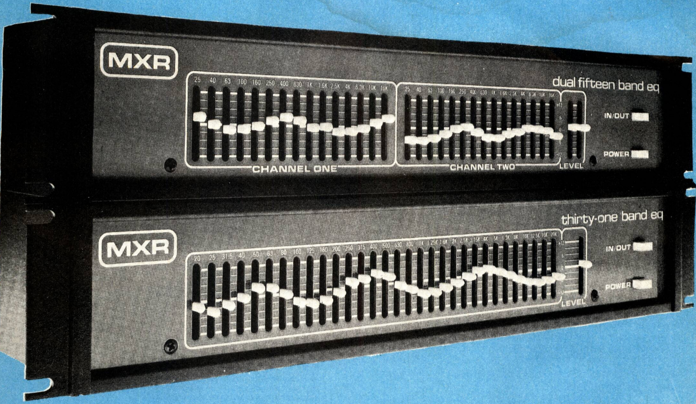

MXR is proud to present two additions to our Professional Products Group—the Dual Fifteen Band Equalizer and the Thirty-One Band Equalizer.

The Dual Fifteen Band Equalizer is a professional, two-channel frequency equalizer offering 15 bands of discreet adjustment per channel. Each of the bands, spaced at 2/3 octave intervals, has a range of -12 to +12 decibels and can be independently adjusted using the slide controls. In addition, each channel has its own level control slider.

The Thirty-One Band Equalizer is a professional, single channel graphic equalizer providing precise control over thirty one discreet frequency bands spaced at 1/3 octave intervals. Like the Dual Fifteen Band Equalizer, each band has a range of -12 to +12 decibels. In addition, there is a broadband level control to provide optimum dynamic range and ease of operation.

Due to their advanced design and high quality construction, both units are reliable, versatile instruments, that can be utilized in a wide variety of situations. Adjustments can be made in the basic tonal characteristics of any instrument to suit one's taste or needs. Specific portions of program material may be accented or diminished. A room can be "tuned" by adjusting for tonal discrepancies caused by room acoustics. Compensation for inadequacies in microphones, speakers, or even hearing is easily accomplished.

The Dual Fifteen Band and Thirty-One Band Equalizers are graphic units in that their response is illustrated on the front control panel. The outline of the frequency response curve is reflected in the positions of the slide controls. This visual representation facilitates duplication of the desired effects.

Both units can be easily mounted in any standard EIA 19" rack for studio installation, or in the optional road case for portable use.

As with every MXR product, the Dual Fifteen Band Equalizer and the Thirty-One Band Equalizer are designed and manufactured with all of the care and attention given to our products used around the world in recording studios and musical performances.

Distributed by:
The Music Distillery,
503 Pittwater Road,
Brookvale. NSW.
938-4095 938-2372

MXR **Professional Products Group**

The last time you saw a really new bench/portable DMM was

1972

THAT'S the year our 8000A was introduced. Its custom LSI and solid owner benefits quickly established it as the world's leading DMM. Now, look at the new 8010A and 8012A: single-chip CMOS designs for problem solving in the eighties!

RAZOR-SHARP LCD for large, no-strain answers at first glance — in any light.

TOUCH AND HOLD probe option, so you can thread your way through a component jungle and capture the readings you need.

FUNCTION POWER: 22 ranges of AC and DC volts and current, six ranges of resistance, and three ranges of conductance — the missing function on other bench multimeters.

CONDUCTANCE RANGES for noise-free leakage measurements to 10,000 M ohms. A valuable function for bench-testing boards and components, conductance also measures transistor beta (using a bias resistor) and light intensity (by using a photocell).

OVERLOAD PROTECTED — like no other DMM, including rejection of 6000V transients and up to 600V applied to the current terminals.

HONEST AC ANSWERS derived from a Fluke hybrid true rms converter. You'll even see the difference on your AC line between the correct value and what your average-responding meter reads. And 50 kHz bandwidth won't let any significant distortion products go unmeasured. Plus, 10 times the basic response you may be limited to now!

SPECS YOU EXPECT from Fluke — like 0.1 percent on DC for one year. Both models available with rechargeable batteries, and backed by the same solid warranty and worldwide service that helped make the 8000A the industry standard.

LEADERSHIP HAS TO BE EARNED. And we're committed to keeping the price of your confidence as realistic as possible. Like $255* for the 8010A with a 10A current range, and $315* for the 8012A with two extra-low ohms ranges that allow measurements from 0.001 ohms to 10,000M ohms — making it the widest range ohmmeter available!

**** Excluding sales tax (add 15 percent).***
Rechargeable Battery Model – add $45.
Quantity discounts available.

FLUKE ®

ELMEASCO
Instruments Pty. Ltd.

NSW: PO Box 30, Concord, NSW. 2137. 13-15 McDonald St, Mortlake, NSW. 2137. Phone: (02) 736-2888. Telex: 25887.
VIC: PO Box 107, Mt. Waverley, Vic. 3149. 21-23 Anthony Drive, Mt. Waverley, Vic. 3149. Phone: (03) 233-4044. Telex: 36206.
ADELAIDE: 51-3521, Brisbane: 229-3161, Perth: 325-3144.

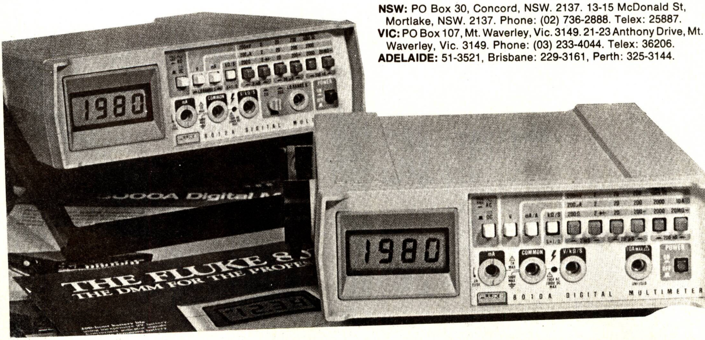

KITS FOR ETI PROJECTS

We get many enquiries from readers wanting to know where they can get kits for the projects we publish. The list below indicates the suppliers we know about and the kits they do.

Any companies who want to be included in this list should phone LES BELL on 33-4282.

Key to companies:

A Applied Technology Pty. Ltd. 109 - 111 Hunter St, Hornsby. 2077. NSW.

D Dick Smith Pty. Ltd. of Crows Nest, NSW. (see Ads. for address).

E All Electronic Components (formerly ED & E Sales), 118 Lonsdale Street, Melbourne, Victoria 3000.

J Jaycar Pty. Ltd. 405 Sussex St., Sydney 2000.

L Delsound Pty. 1 Wickham Terrace. Queensland.

M Mode Electronics. PO Box 365, Mascot 2020.

N Nebula Electronics Pty. Ltd. 15 – 19 Boundary St., Rushcutters Bay 2011. NSW.

P Pre-Pac Electronics. 718 Parramatta Rd., Croydon NSW 2132.

T Townsville Electronics Centre.
281E Charters Towers Rd,
Rising Sun Arcade, Hermit Park. 4812

PROJECT ELECTRONICS

ETI 041	Continuity Tester	DS
ETI 043	Heads or Tails	DATSE
ETI 044	Two-Tone Doorbell	DATSE
ETI 045	500 Second Timer	DS
ETI 047	Morse Practice Set	DS
ETI 048	Buzz Board	DS
ETI 061	Simple Amplifier	DATS
ETI 062	Simple Amplifier Tuner	DSE
ETI 063	Electronic Bongo's	DS
ETI 064	Intercom	ATS
ETI 065	Electronic Siren	DS
ETI 066	Temperature Alarm	ADTSE
ETI 067	Singing Moisture Meter	DS
ETI 068	Led Dice	ADSE
ETI 072	2-Octave Organ	DS
ETI 081	Tachometer	E

TEST EQUIPMENT

ETI 102	Audio Signal Generator	E,DS
ETI 105	Lab Power Supply	E
ETI 107	Widerange Voltmeter	E
ETI 108	Decade Resistance Box	ES
ETI 109	Digital Frequency Meter	E
ETI 111	IC Power Supply	ES
ETI 112	Audio Attenuator	ES
ETI 113	7-Input Thermocouple Meter	P,E
ETI 116	Impedance Meter	ES
ETI 117	Digital Voltmeter	E,AS
ETI 118	Simple Frequencv Counter	E,AS
ETI 119	5V Switching Regulator supply	ETS
ETI 120	Logic Probe	L,ES
ETI 121	Logic Pulser	L,ES
ETI 122	Logic Tester	ES
ETI 123	CMOS Tester	ES
ETI 124	Tone Burst Generator	ES
ETI 128	Audio Millivoltmeter	L,ES
ETI 129	RF Signal Generator	L,ES
ETI 130	Temperature Meter	E
ETI 131	General Purpose power supply	E,N
ETI 132	Power Supply	NSE
ETI 133	Phase Meter	E
ETI 134	True RMS Voltmeter	E

SIMPLE PROJECTS

ETI 206	Metronome	T
ETI 218	Monophonic Organ	ET
ETI 219	Siren	ET
ETI 220	Siren	ET
ETI 222	Transistor Tester	ETS
ETI 234	Simple Intercom	T
ETI 236	Code Practice Oscillator	E
ETI 239	Breakdown Beacon	E
ETI 240	High Powered Emergency Flasher	E

MOTORISTS' PROJECTS

ETI 301	Vari-Wiper	ET
ETI 302	Tacho Dwell	ET
ETI 303	Brake-light Warning	E
ETI 305	Car Alarm	E
ETI 309	Battery Charger	P,E
ETI 312	CDI Electronic Ignition	P,ET
ETI 313	Car Alarm	E,DT
ETI 316	Transistor Assisted Ignition	E
ETI 317	Rev. Monitor	E

AUDIO PROJECTS

ETI 401	Audio Mixer FET Four Input	E
ETI 406	One Transistor Receiver	T
ETI 408	Spring Reverb. Unit	E
ETI 410	Super Stereo	E
ETI 413	100 Watt Guitar Amp	P,L,J,DT
ETI 413	x 200 Watt Bridge Amp	SE
ETI 414	Master Mixer	E,J
ETI 416	25 Watt Amplifier	E
ETI 417	Amp Overload Indicator	E
ETI 419	Guitar Amp Pre-Amp	P.E.DT
ETI 420	Four-channel Amplifier	L,E
ETI 420E	SQ Decoder	E
ETI 422	International Stereo Amp	S L,D
ETI 422B	Booster Amp	E
ETI 422	50 Watt Power Module	E
ETI 423	Add-on Decoder Amp	E
ETI 424	Spring Reverberation Unit	S L,E
ETI 425	Integrated Audio System	E
ETI 426	Rumble Filter	E
ETI 427	Graphic Equaliser	S L,E,J
ETI 429	Simple Stereo Amplifier	E
ETI 433	Active Crossover	J
ETI 435	Crossover Amp	J
ETI 438	Audio Level Meter	L,ES
ETI 440	Simple 25 Watt Amp	L,E
ETI 441	Audio Noise Generator	L,ES
ETI 443	Compressor-Expander	E.J.
ETI 444	Five Watt Stereo	ES
ETI 445	Preamp	J,E,D
ETI 446	Audio Limiter	J
ETI 447	Phaser	E.J
ETI 449	Balanced Mic Preamp	JE
ETI 480	50 W. 100 W Power Amp	A
ETI 480P	Power Supply	DAT
ETI 481	12V to 40V DC Inverter	E
ETI 482A	Preamp Module	AE
ETI 482B	Tone Controller	AE
ETI 484	Compressor Expander	E
ETI 485	Graphic Equalizer	JSE
ETI 480	50W, 100W Power Amp	ADBE

MISCELLANEOUS

ETI 502	Emergency Flasher	E
ETI 503	Burglar Alarm	ET
ETI 505	Strobe	L,E,D
ETI 506	Infra-Red Alarm	E
ETI 509	50-Day Timer	E
ETI 512	Photographic Timer	E
ETI 513	Tape Slide/Synchroniser	E
ETI 514	Flash Unit — Sound Operated	E
ETI 515	Flash Unit — Light operated	E
ETI 518	Light Beam Alarm	ET
ETI 525	Drill Speed Controller	E
ETI 528	Home Burglar Alarm	P,ET MS
ETI 529	Electronic Poker Machine	E
ETI 532	Photimer	E
ETI 533	Digital Display	L,E,AS
ETI 534	Calculator Stopwatch	A,D
ETI 539	Touch Switch	E
ETI 540	Universal Timer	ES
ETI 541	Train Controller	ET
ETI 543	Double Dice	A
ETI 544	Heartrate Monitor	AE
ETI 546	GSR Meter	E
ETI 547	Telephone Bell Extender	E
ETI 548	Photographic Strobe	E
ETI 549	Induction Balance Metal Locator	E
ETI 581	Dual Power Supply	E
ETI 582	House Alarm	E
ETI 583	Gas Alarm	ME
ETI 586	Shutter Speed Timer	E

ELECTRONIC MUSIC

ETI 601		
4600	Synthesiser	J
3600	Synthesiser	J
ETI 602	Mini Organ	E,A,D
ETI 604	Accentuated Beat Metronome	E

COMPUTER PROJECTS

ETI 630	Hex Display	AE
ETI 631	VDU Keyboard Encoder	AE
ETI 632	VDU 1 k x 8 Memory Card	AE
ETI 633	VDU Sync Generator	AE

RADIO PROJECTS

ETI 701	TV Masthead Amplifier	E,D
ETI 702	Radar Intruder Alarm	DE
ETI 703	Antenna Matching Unit	E
ETI 704	Crosshatch/Dot Generator	L,A,D,ES
ETI 706	Marker Generator	ES
ETI 707	Modern Solid State Converters	E
ETI 708	Active Antenna	E
ETI 709	RF Attenuator	E
ETI 710	2 metre Booster	E
ETI 711B	Single Relay Remote Control	AE
ETI 711C	Double Relay Remote Control	AE
ETI 711R	Receiver	AE
ETI 711AR	Remote Control Transmitter	AE
ETI 711DR	Remote Control Decoder	AE
ETI 712	CB Power Supply	E
ETI 740	FM Tuner	AE
ETI 780	Novice Transmitter	E

ELECTRONIC GAMES

ETI 804	Selecta-Game	O,A,DS

PCB's

Using ETI PCB Artwork

This method can be used to make negatives of ETI artwork from October 1977 on, provided the reverse of the page is printed in blue. The film used is Scotchcal 8007 which is UV sensitive and can be used under normal subdued light.

Cut a piece of film a little larger than the PC board and expose it to UV light through the magazine page. The non emulsion side should be in contact with the page. This surface can be detected by picking the film up by one corner - it will curl towards the emulsion side. Exposures of about 20 minutes are normally necessary.

The film can now be developed by placing it emulsion side up on a table, pouring some Scotchcal 8500 developer on the surface and rubbing it with a clean tissue.

Further information on Scotchcal and PCB manufacture can be found in the September and December 1977 issues of ETI. Please note also, that occasionally pressure on space may unfortunately prohibit the printing of blue type behind all PCB's, in which case the reader must resort to more conventional photographic techniques for PCB manufacture.

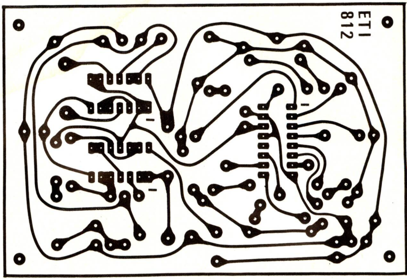

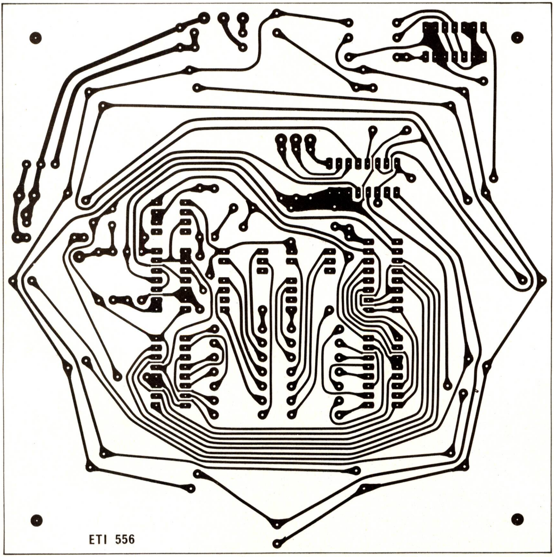

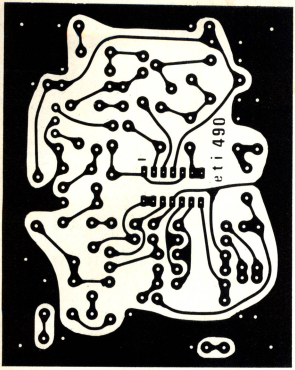
eti 490

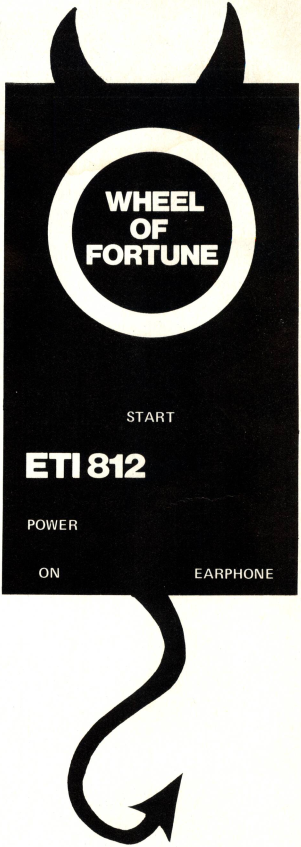
WHEEL
OF
FORTUNE
START
ETI 812
POWER
ON
EARPHONE

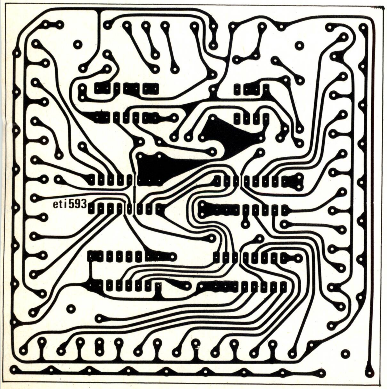
eti593

Mini-Mart

We'll print your 24 words (maximum) totally free of charge. Copy must be with us by the 7th of the month preceding the month of issue. Please, **please** write or preferably type your adverts clearly, using BLOCK LETTERS.

CONDITIONS

Name and address plus phone number (if required) must be included within the 24 words allowed.

Reasonable abbreviations, such as 25 Wrms, count as one word.

Private adverts only will be accepted. Please let us know if you find a commercial enterprise using this service.

Every effort will be made to publish all adverts received — however, no responsibility for so doing is accepted or implied.

Adverts must relate to electronics or audio — general adverts cannot be accepted.

QTY 2SD200 POWER TRANS. 1500V/3A SUIT HOR. O/P $2.50 ea. NI-CAD BATTERIES 6v/1.2A.H. NEVER USED $3.50. OTHER BITS. PHONE SYDNEY 929-3944. A.H. JOHN, WAVERTON N.S.W.

SELL COMPLETE ETI (VOL I, No 1 TO CURRENT ISSUE) $70. OR EXCHANGE FOR A SIMILAR NUMBER R.Tv&H. PRE-DEC 64. E. GRABIS, 3 DAVID STREET, COROMANDEL VALLEY, SOUTH AUST. 5051.

SELL: 4600 SYNTHESIZER KEYBOARD CONTROLLER $75, TRANSIENT 1 $20. PHILIPS MICROPHONE $10. MIC STAND $10 2-STATION INTERCOM $8. CARL VINE, 33 PALMERSTON STREET, VAUCLUSE (02) 337-4681.

BWD 506 CRO 5mV, 19 mHz B.W. WITH FLOATING BNC INPUT. AS NEW CONDITION PHONE LINDSAY SMITH ANY TIME (07) 273-1351.

AUSTRALIAN RADIO DX CLUB, FOR SHORTWAVE AND MEDIUMWAVE DXERS. MONTHLY MAGAZINE PUBLISHED. WRITE FOR DETAILS WITH 30c STAMP TO, PO BOX 67 HIGHETT, VICTORIA 3190 OR PO BOX 79 NARRABEEN NSW 2101.

ESTABLISHED TELEVISION AND RADIO REPAIR SERVICE, WITH SOME REPAIR STOCK, PLUS OLDER TYPE CONSISTING, TWO SELF CONTAINED FLATS ON DOUBLE BLOCK OF GROUND, PENRITH DISTRICT, $28,000 PHONE 623-5181.

FOR SALE — 2650 IC $20 ea, 2114 $7.00 ea. BOTH NEW NEVER USED. WRITE PO BOX 166 PARKHOLME. S.A.

SELL. ADVANCE SIG/GEN SG62B 150KHz 220 MHz $120. MARCONI CARRIER DEVIATION METER TF791D 4-1,024 MC/S $400. HANDBOOKS EXC. CONDITION. CONTACT EDWARDS (086) 42-4262 OR EDGE (08) 268-7952.

SALE: TRIO AG 202A AUDIO GENERATOR —85:00 TRIO SG 402 R.F. GENERATOR — 65:00 TEKTRONIX D61 OSCILLOSCOPE WITH 2x10 PROBES 350:00 R.L. ARMSTRONG 27 ROBERTS AVE, BARRACK HEIGHTS 2528 PH. 95-1592.

MINISCAMP WITH NATIONAL MANUALS $90 ONO SIXTY KEY KEYBOARD $45 ONO TWO 2112 256x4 BIT RAM $2 EACH J.MUIR, 32 CLARKE STREET, BENDIGO 3550. PHONE (054) 43-2979.

2650 MICRO BASIC USES 1.5K RAM. INTER GER ±32K + — x ÷ LET, IN, PR, GT, GS, RND, IF, END. A—Z VBLES. FULL SOURCE LISTING + CUTS TAPE. $7. A. PEEK 10 GALE ST., WOOLWICH. 2110 SYDNEY 89-1450.

SELL 12 COPIES E.T.I. AND 12 EA. IN NEAR MINT COND. ALL FROM 76—78 $25.00 JAMES COTTERILL, CHADSTONE, PHONE MON-FRI A/H (03) 56-5011.

SURPLUS CONV. MANUALS RADIO ASTRONOMY WEATHER SATELLITE BOOK'S HAM MAG'S MISC ITEM'S LARGE S.A.E. FOR LIST'S PHONE A/H (03) 546-3940 JEFF SILVESTER 9 GOODWOOD DRIVE, SPRINGVALE 3171.

WANTED CRO IN GOOD CONDITION WITH CALIBRATED INPUT AND T.B. 4" SCREEN OR LARGER A.RETTKE 52 MAYHEW ST., SHERWOOD QLD. 4075.

FOR SALE, LICENSABLE 23 CH BETA CB RADIO, RFGAIN, SQUELCH, DELTA TUNE, INT/EXT SPEAKER, P.A. SWITCH, ANL, PROVISION FOR 24TH CH. $80. COLIN, Ph 787-7640. FRANKSTON, AFTER 6.00 PM.

FOR SALE. LEADER LSW 250 SWEMAR GENERATOR. AS NEW $150. ONO. C. BROOKES BOX 117 GOOMALLING W.A. 6460. OR PHONE GOOMALLING 147.

URGENT SALE ARLUNYA COLOUR TV PATTERN GENERATOR PG31 AS NEW WITH ALL LEADS $325 ONO. GOING OVERSEAS N. LADSON 467 GEORGE ST., DENILIQUIN N.S.W. 2710.

HP 25/33 CLOCK-TIMER PROGRAM $2. SEND S.A.E. TO P.O. BOX 275 WENTWORTH BLDG. UNI. OF SYDNEY 2006. (MAY SUIT HP19/29).

SELL HEATH H8 MICRO 16K RAM, SERIAL, PARALLEL I.O. BOARD. H10 PAPER TAPE SYSTEM. PROFESSIONALY BUILT. K. POWER 35 FREDA ST. MT. GRAVATT BRISBANE. 349-9983.

send your ad to —
ETI MiniMart,
Modern Magazines,
15 Boundary Street,
Rushcutters Bay,
NSW 2011.

GLASS FIBRE COPPER LAMWATE, SINGLE SIDE SIZES 3" x 3" TO 19" x 18", DOUBLE SIDED 2½" x 1½" TO 19" x 13". FOR PRICES AND SIZES, PHONE COLIN, FRANKSTON, 787-7640.

C.B. RADIO CLUB AND QSL SWAP BUREAU. FOR FREE POSTAL MEMBERSHIP SEND 20c STAM. LAKESIDE C.B. RADIO CLUB. BOX 114, TOUKLEY, NSW 2263.

MELBOURNE HI-FI AND TAPE-FANS. THE RECORDING SOCIETY OF AUSTRALIA MEETS MONTHLY. YOU ARE INVITED TO COME ALONG. FOR INFORMATION RING OR WRITE TO DON PATRICK, 36 ARGYLE ST., MCLOED, 3085. (03) 459-1717.

CB. FERRIS CB SSB-5000. 5/8 WAVE GROUND PLANE ANTENNA. ISE CB 345 AM-SSB POWER SUPPLY. TANDY HEAVY DUTY COAX CABLE. TVI FILTER. PHONE (08) 2951270.

SELL MOTOROLA M6800 D2 MICROPROCESSOR KIT FULL DOCUMENTATION ASSEMBLED AND WORKING, 640 BYTES RAM $230 ALSO EX-PMG BAUDOT TELETYPE WITH MANUAL $60 O.N.O. P O'FARRELL BRISBANE 209-8696.

PENNYWISE PERIPHERALS STACKABLE 4K x 8 BIT RAM PLANE WITH 32 21LO2'S AS NEW. J. BILLS, 29 BERKLEY ROAD RINGWOOD, VICTORIA, 3134. PHONE (03) 876-3231 A.H.

F.M. TRANSCEIVER 6M F.M. NET. CONVERTED WITH XTALS. WITH 6M ANTENNA AND MOBILE MOUNT $35 MR. ANDERS (03) 630-5317 B.H.

PROGRAMMABLE CALCULATOR. SHEEN SCIENTIFIC PROGRAMMABLE MODEL 2000. 100 STEP PROGRAMMING FACILITY SELL — $50, INLCUDING ADAPTOR. GUY TEMPLETON, 65 BRENTWOOD AVENUE TURRAMURRA 2074. PHONE 44-7593.

COSSOR VALVE VOLTMETER MODEL 1044K. OLD BUT STILL VERY GOOD $20. TEL (02) 89.4645 EVENINGS/WEEKENDS.

LABORATORY WEIGHTS, POLISHED BRASS SET IN HARDWOOD CASE WITH LID, FORCEPS AND FRACTIONS 1 MG THROUGH 500 GRAMMES. BRAND NEW NEVER USED. $17.50, TEL (02) 89 4645 EVENINGS/WEEKENDS.

VACUUM GAUGE - BADENBERG 0-30 IN HG 5 3/4 INCH DIAL. $17.50, TEL (02) 89 4645 EVENINGS/WEEKENDS.

HISTORICAL BOOK. HANDBOOK OF TECHNICAL INSTRUCTION FOR WIRELESS TELEGRAPHISTS BY HAWKHEAD AND DOWSETT, WIRELESS PRESS PUBLISHED IN 1915. $12.50, TEL (02 89 4645 EVENINGS/WEEKENDS.

DELSOUND
PTY LTD

BRISBANE

1 Wickham Tce (Cnr, Wharf St) 229-6155 (park at rear). 35 Logan Rd, Woolloongabba. 391-7048.

IF WE CAN'T BEAT THE OPPOSITION PRICE, WE WILL TRY TO MATCH IT . . . IF WE DON'T STOCK IT, WE WILL TRY TO GET IT FOR YOU.

(Guess who's now a Dick Smith dealer?)

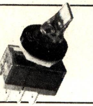

PRINTED DRESS NUTS show each switch and warning light's function, including spot, demist, temp., fog, etc.
***DUCKBILL GLOW SWITCHES.** Red, amber, blue or green. Provides protection against battery drain if equipment is left on. Fits standard 12.5 mm dia.

HAZARD FLASHER, simple and compact, easy to fit. Only 3 wires to connect. Patented.

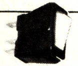

***ROCKER GLOW SWITCHES.**
In-button illumination. Ideal rear screen demister replacement switches, no need for warning light. Red, amber, blue, green. Mtg. bracket available.

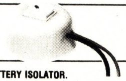

ANTI-THEFT IMMOBILISER. Effective against thieves. Adhesive backed to hide anywhere in car.

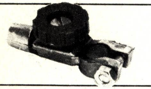

BATTERY ISOLATOR.
Anti-theft, quick battery disconnect and emergency cut-out. A must to avoid battery drain and electrolysis. No tools or dirty hands. Rated 100 amps at 12 or 24 volts.

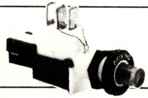

***PUSH-BUTTON GLOW SIWTCH.**
Update with attractive illuminated push-buttons. Red, amber, blue, green.

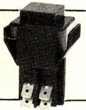

***PUSH-BUTTON SWITCHES.**
Illuminated or non-illuminated. Red, amber, blue, green.

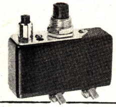

CIRCUIT BREAKER.
Does away with need for a separate switch or fuse.

**** All switches extra-heavy-duty and have been tested in excess of 28 amps at 12 volts.***

Qld. distributor for:

RCA Semiconductors and Swan Electronic Components.
Wholesale, trade and mail order welcome. Add 10 percent post and pack. Stocks and prices valid at 1.10.78.

BUILD MUSIC AND SOUND

Expand your talent with the SH1 synthesizer; let it take you into areas previously reserved for musicians. Roland, the world's largest maker of electronic musical equipment, now provides you with a comprehensive operator's manual which will show you how to enjoy and understand the never-ending creative possibilities.

Simply hook up the SH1 with your hi-fi system and play your favourite electronic, pop or orchestral sounds — or sound effects like surf, rain, wind, etc.

$750* **gets you into the exciting world of electronics and sound**

*recommended retail

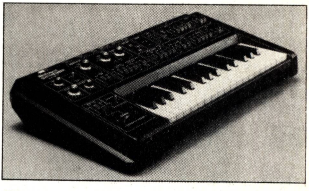

SH-1

- ■ KEYBOARD (32 keys, 2-½ octaves)
- ■ VCO (voltage controlled oscillator)
  - ● Modulator
  - ● Autobend Depth
  - ● Autobend Time (8-360 msec)
  - ● VCO Range (32', 16', 8', 4', 2')
  - ● Waveform (⩘ , ⎍ , ∿)
  - ● Pulsewidth Modulation (Min-50%)
  - ● PWM Mode Switch (Env-1/Manual/LFO)
- ■ Sub-oscillator
  - ● 1 oct Down /2 oct Down /2 oct Down
- ■ AUDIO MIXER
  - ● VCO
  - ● Sub-oscillator
  - ● Noise Generator
  - ● Ext Sig
  - ● Overload Indicator
- ■ NOISE GENERATOR
  - ● White/Pink Selector
- ■ HIGH PASS FILTER
  - ● Cutoff Frequency Control (25Hz-5KHz)
- ■ VCF (Voltage Controlled Filter)
  - ● Cutoff Frequency Control (5 Hz-20KHz)
  - ● Resonance (Min-Self Oscillation)
  - ● ENV-1 Control Depth
  - ● Modulator
  - ● KYBD Control
  - ● Envelope Follower Control
- ■ VCA (Voltage Controlled Amplifier)
  - ● Hold Control
  - ● Envelope Switch (ENV-1/ENV-2)
- ■ ENVELOPE GENERATOR 1
  - ● Attack Time Control (1.5 msec-2.5 sec)
  - ● Decay Time Control (1.5 msec-8 sec)
  - ● Sustain Level (0-100%)
  - ● Release Time (1.5 msec-8 sec)
  - ● Gate Trigger Selector Switch (Gate + Trig/Gate/LFO)
- ■ ENVELOPE GENERATOR 2
  - ● Attack Time Control (1.5 msec-3 sec)
  - ● Release Time (1.5 msec-8 sec)
  - ● Gate Selector Switch (Gate/LFO)
- ■ Modulator
  - ● Mode Switch (Random / ⎍ / ∿)
  - ● Rate Control (0.2 Hz-25Hz)
  - ● Delay Time Control (0-3 sec)
  - ● Rate Indicator
- ■ Controller
  - ● KYBD/Ext CV GATE Selector Switch
  - ● Total Tuning (+700 cents or over)
  - ● Portamento Time Control (0-2.5 sec)
  - ● Total Volume
  - ● Transpose Switch (L/M/H)
  - ● Bender Level
  - ● Bender Sensitivity (VCO, VCF)
- ■ CONNECTION JACKS
  - ● Output Jack
  - ● Output Level Switch (L/M/H)
  - ● Phones Jack (8 ohm stereo)
  - ● Phones Output Level Switch (L/M/H)
  - ● External Input Jack
  - ● External Signal Input Level Switch (L/M/H)
  - ● External Control Voltage Input Jack (1 V/1 Oct)
  - ● External Gate Voltage Input Jack (ON with +7.5 V or over)
  - ● Keyboard Control Voltage Output Jack (1 V/1 Oct)
  - ● Keyboard Gate Output Jack (OFF-0 V, ON-14 V)
- ■ POWER CONSUMPTION: 10W
- ■ DIMENSIONS: 610(W) x 370(D) x 135(H)mm 24.0(W) x 14.6(D) x 5.3(H) in
- ■ WEIGHT: 6.4 kg, 14 lbs
- ■ ACCESSORY: 2.5m Connection Cord

Super Fat Sound from a New 24dB/oct Filter

*Specifications are subject to change without notice.

Write or call for more information.

Roland
Roland Corporation (Australia) Pty. Ltd.
13 Chard Road, Brookvale, N.S.W. 2100.
Telephone (02) 938 3911.

OPTOELECTRONICS

If you hang this up, your opto supplier can't hang you up.

When you need this*:	Order this:
MONSANTO PART #	**FAIRCHILD PART #**
LAMPS	LAMPS
MV5050 through MV5056	MV5050 through MV5056
MV5152 through MV5154	MV5152 through MV5154
MV5252 through MV5254	MV5252 through MV5254
MV5353 through MV5354	MV5353 through MV5354
MV5752 through MV5754	MV5752 through MV5754
DIGITS	DIGITS
MAN71A	MAN71A
MAN72A	MAN72A
MAN73A	MAN73A (3Q '78)
MAN74A	MAN74A
COUPLERS	COUPLERS
MCA230	MCA230
MCA231	MCA231
MCA255	MCA255
MCT2	MCT2
MCT26	MCT26
MCT2E	MCT2E
TI PART #	**FAIRCHILD PART #**
LAMPS	LAMPS
TIL209A	TIL209A
TIL211	TIL211
TIL213	TIL213
COUPLERS	COUPLERS
TIL111 through TIL119	TIL111 through TIL119
LITRONIX PART #	**FAIRCHILD PART #**
COUPLERS	COUPLERS
IL1	IL1
IL12	IL12
IL15	IL15
G.E. PART #	**FAIRCHILD PART #**
COUPLERS	COUPLERS
H11A1 through H11A4	H11A1 through H11A4
H11B1 through H11B2	H11B1 through H11B2

*Parts listed in the column on the right meet the published guaranteed performance criteria of parts listed in the column on the left.

Fairchild is a major supplier of optoelectronic products. We make a full line of our own proprietary opto parts. Plus all the parts you buy from the other guys. (See chart)

The biggest difference between our line and theirs is this: Ours are available now. In quantity.

FAIRCHILD

Distributors:
GEORGE BROWN & CO. PTY. LTD. 174 Parramatta Road, Camperdown. N.S.W. 2050. Telephone: 519-5855. TOTAL ELECTRONICS, Darmin House, 155 Willoughby Road Crows Nest, N.S.W. 2065 Telephone: 439-6722. BROWNTRONICS PTY. LTD 93 Sackville Street, Collingwood, Vic. 3066 Telephone: 419-3355. WARBURTON FRANKI (MELB.) PTY. LTD. 220 Park Street, Sout Melbourne, Vic. 3205 Telephone 699-4999. TOTAL ELECTRONICS, 239 Bay Street, North Brighton 3186. Telephone: 596-2891 ELECTRONIC COMPONENTS (QLD.) Suite 16, 205 Moggill Rd, Taringa Qld. 4068 Telephone: 371-5677. TOTAL ELECTRONICS, 316 Adelaide Street, Brisbane, Qld. 4001 Telephone: 229-1633. PROTRONICS PTY. LTD. 174-180 Wright Street, Adelaide S.A. 5000. Telephone: 212-3111. GEORGE BROWN & CO. PTY. LTD. 23 Whyalla Street, Fyshwick, A.C.T. 2609 Telephone: 95-0455. WARBURTON FRANKI (PERTH), 98 Belgravia Street, Belmont, W.A. 6104 Telephone: 65-7000. **NZ:** FOUNTAIN MARKETING, 1 Maidstone Street, Auckland, N.Z. Telephone: 763-064

The best speaker kit isn't a kit at all!

The best speaker kit is a system designed by Electro-Voice that allows you to choose your own level of performance; from a studio monitor to a modest bookshelf system, from a wide selection of woofers, tweeters, mid-range drivers and crossovers.
The Electro-Voice provides detailed plans on how to construct the enclosures designed specifically for the drivers you chose.
Only Electro-Voice gives you all the options. But, then, Electro-Voice is known for their superb quality speakers — not for kits.
To get your component speaker catalogue and construction plans package, just send $1.00 to Electro-Voice Australia Pty. Ltd., 174 Taren Point Road, Taren Point, NSW. 2229.

EV Electro-Voice®
a gulton company

Electro-Voice Australia Pty Ltd
174 Taren Point Road,
Taren Point, NSW 2229.

Please send me .... E-V component speaker packages. I have enclosed $1.00 for each package ordered.

Name..

Address..

....P/Code..............................

CARTRIDGES & STYLI

CARTRIDGES

ADC ZLM	$125
ADC XLM MK3	$99
ADC VLM MK3	$82
ADC QLM 36 MK3	$75
ADC QLM 34 MK3	$58
ADC QLM 32 MK3	$42
ADC QLM 30 MK3	$30
DENNON DL107	$75
DENNON DL109R	$85
DENNON DL 109D	$112
DENNON DL103	$120
AU310 Trans for DL103	$70
DENNON DL103S	$155
AU320 Trans for DL103S	$90
Shure V15 Type IV	$159
Shure V15 Type III	$125
Shure M95ED	$58
Shure M91ED	$39
Shure M70EJ	$16
Shure M55E	$25
Shure M44E	$22
Shure M24H	$79
Shure M70B	$12
Shure M75CS	$19
Shure M44-7	$21
Jelco MC9	$12
Jelco MC-14D	$24
Jelco MC-14E	$39
Jelco MC-45E	$80

STYLI

Shure VW35E	$56
Shure N95ED	$49
Shure N91ED	$39
Shure N70EJ	$11
Shure N55E	$21
Shure N44E	$18
Shure N24H	$52
Shure N70B	$7
Shure N75C	$15
Shure N44-7	$16
Jelco ND-9	$8
Jelco ND-14D	$12
Jelco ND-14E	$28
Jelco ND-45E	$45

TONE ARMS

ADC LMF-1	$179
ADC LMF-2	$189
Grace 707	$89
Jelco SA50	$39
Jelco SA200	$69

ACCESSORIES

Headshell JS-10 Blk A1	$8.50
Headshell JS-20W Nat A1	$9.50
Headshell JS-50 Solid Blk A1	$11.75
Stylus Press Gauge	$4.95
Static Discharge mat	$7.95
Stylus Microscope	$4.00
Static Eliminator Gun	$19.95

Goods listed are offered subject to availability. Prices include postage anywhere in Australia. Write, phone or call in. Send SAE for full cartridge and styli price list.

CAMPBELLTOWN HI-FI
107 Macquarie Ave,
Campbelltown, NSW 2560
Open all day Saturday
Ph. (046) 25-6067

TWO BYTES ARE BETTER THAN ONE

ANYTHING EIGHT CAN DO THIS CAN DO BETTER

QUESTION: The majority of microcomputers now being sold to hobbyists, researchers, and small businesses, use 8-bit microprocessors. Why then have virtually all the makers of 8-bit microprocessors (Intel, Fairchild, Motorola, Zilog, etc) announced that they are working on the production of 16-bit microprocessors?

ANSWER: Because users of 8-bit equipment are becoming aware of its limitations and of the advantages offered by the 16-bit microcomputer: greatly increased calculating capacity, increased addressing efficiency in programming, and so on. More and more of the experts in the field are becoming convinced that for the serious users of microcomputers, the future lies with the 16-bit processors.

PONDER: While the others are working hard to catch up, Texas Instruments remains the world leader in microprocessors with its 64-pin, 16-bit TMS9900. Anything 8 bits can do, this can do better. And it can do many things that are completely beyond the capability of any 8-bit microprocessor. It has separate data and address lines (no multiplexing), hardware multiply and divide, and a host of other features. May we tell you more about them?

THE COMPLETE SYSTEM AVAILABLE NOW: IMPACT can, from stock, supply you now with a fully assembled and tested Technico T-9900-SS Single-board, Stand-alone microcomputer for $575 (model T-1.5K-SS) or $795 (model T-6K-SS), built around the TMS9900 chip. Also available: a wide range of additional boards and peripherals to go with it. Just tell us you would like to receive details and prices. (Warning: You must expect to pay a little more, of course, than for an 8-bit machine).

I.M.P.A.C.T. LTD.,
P.O. Box 177, PETERSHAM
NSW 2049. Ph: 560-7603.

15
Yes, I would like Technico details and prices.

NAME..

ADDRESS..

....

STATE..............................POSTCODE..............................

RELIABLE SOAR DIGITAL MULTIMETERS

ME SERIES

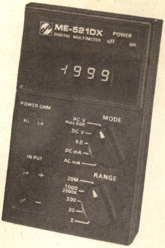

ME-521 DX
3½ DIGIT LCD DISPLAY

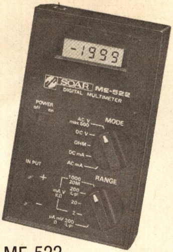

ME-522
3½ DIGIT LCD DISPLAY

ME-523
3½ DIGIT ¾" HIGH LCD
WITH MODE DISPLAY

Digital Multimeter at an Analog price! Send for detailed specifications and compare before buying

Available from: **NSW;** David Reid Electronics, 516-3544. Radio Despatch Service, 211-0191. Electronics (Distributors), 636-6052. Martin D Launay, 29-5834. Standard Components, 660-6066. **VIC:** Radio Parts, 329-7888. Stewart Electronics, 543-3733. Arlin Instruments, 569-698 **SA:** Protronics, 212-3111. **WA:** Reserve Electronics, 328-3116. **QLD;** Wilber Sales, 391-5136.

AMPEC ENGINEERING CO. Tel: (02) 818-1166.

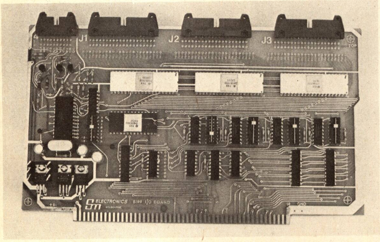

See us at Computer Show, December 9 and 10.
Box Hill Town Hall, Melbourne.

S100 STATIC RAM BOARD

Available in Jan: 16K, 2114's, 450 Ns, low power. 4K block addressing, bank select, 4K block mem. write protect, plated thru holes, solder mask, wait states, Australian made.

KIT PRICE — 16K $346 plus 15 percent s/t.
— 8K $196 plus 15 percent s/t.

S100

I/0 PORT BOARD

NEW FROM S.M. ELECTRONICS

- 9 Programme parallel ports (8255).
- 1 Programme serial port (8251) selectable as 20 m current loop for TTY, RS232 or 5V TTL.
- Xtal controlled baud rate generator from 75 to 960 baud.
- Baud rate switch selected.
- Fully decoded addressing for ports via Dil switches
- Sockets supplied for main chips (5).
- 3 x 36 way and 1 x 10 way flat cable sockets.
- Plated thru holes with solder resist mask.
- Fibreglass board with gold plated edge connector.
- Fully buffered with LS chips.
- Australian made.

KIT PRICE $164 plus 15 percent S/T.

Sm ELECTRONICS
MELBOURNE

10 Stafford Crt., Doncaster East. Victoria. 3109.
Box 19, Doncaster East. 3109. Ph (03) 842-3950.
Built & tested prices and tax free prices on application.

Fig. 5. The direction disc used shown full size. Note that this is the top surface of the disc.

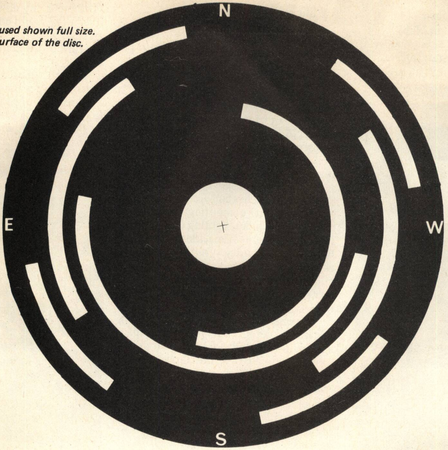

Fig. 6. The wind speed disc shown full size.

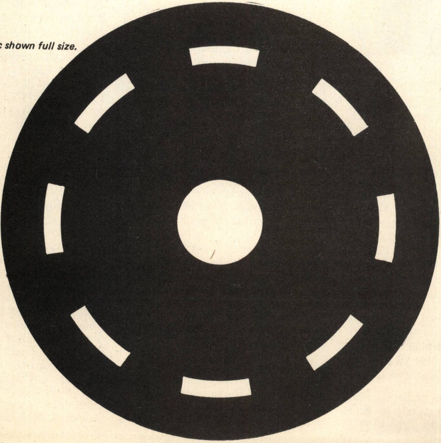

News Digest

Attention, Mr. S. Campbell

Would Mr. S. Campbell of Mill Park, Victoria, who won the September ETI/ Unitrex Calculator Contest, please contact us, as we have mislaid his address and we are unable to send him his Unitrex calculator?

374 kW Triode

The new Philips YD1432 metal-ceramic triode, intended for use as an industrial oscillator in rf heating equipment, supplies high power of typically 374 kW at a low anode voltage of only 12 kV. This means that conventional components can be used in the power supply and the rf circuitry with consequent cost savings.

Featuring a high anode efficiency of 80%, the YD1432 bridges the gap between the other well-known Philips tubes, the YD1212 (240 kW) and the YD1342.

The YD1432 incorporates similar component parts to the other Philips rf heating tubes with proven reliability and is fitted with an integral helix for water cooling. The new tube follows the current market requirements in the trend to the use of lower voltage anode supplies.

Further information available from Philips Electronic Components & Materials, 67 Mars Road, Lane Cove.

C E Show Diversifies

The organisers of the Consumer Electronics Show this week announced details of a substantially diversified C E Show in 1979. The 4th Australian CES will be staged at the Sydney Showgrounds from Wednesday, 18 July to Sunday, 22 July.

Whilst previous C E Shows have drawn wide support from the hi fi industry, organisers next year are looking to a greater range of products fully justifying the "consumer electronics" title.

Amongst the projected list of displays are: digital watches and clocks, computer games, personal computing equipment, dictating machines, lighting equipment, records, amusement machines, antennas, PA systems, security systems, electronic calculators, microwave ovens, batteries, photo systems, professional sound recording equipment and electronic radios.

The organisers weren't quite ready to release full details, but whispers of space age equipment and a CE Wiz Kid promotion were heard at the Showgrounds.

World Eye on Australian Exhibition

In October 1980 the world computer spotlight will turn to Melbourne for the biggest single computing activity ever to be staged south of the equator. IFIP – The International Federation of Information Processing – has selected the Exhibition Building, Melbourne for the 8th World Computer Congress, incorporating an Exhibition of the likes never before seen in Australia.

World Computer Congress' are held once every three years, Congress 80 being shared between Tokyo, Japan and Melbourne, Australia.

Going on the 1977 Congress in Toronto, Australian exhibitors can expect between 2000-3000 registered delegates representing every technologically advanced country in the world to visit the Exhibition.

The exhibition is certain to attract virtually the entire computing profession in Australia.

A Personal Computing Fair will be a major drawcard within the Exhibition, particularly for the thousands of Australians to visit the Exhibition Building on a day set aside for the public.

The organisers of the Congress 80 Exhibition, Riddell Exhibition Promotions Pty Ltd have allocated over 5,500 square metres (60,000 square feet) for exhibition purposes only.

According to Riddell's general manager, Mr Bryan Humphris, the Congress 80 Exhibition will dwarf all previous computer exhibitions held in Australia. "If there is any doubt about Australia's role in the world computer stakes, Congress 80 will cement our foothold until the turn of the century," Mr Humphris said.

Riddell's have been contracted to organise and promote the Exhibition by Congress 80 organisers, The Australian Computer Society.

For further information please contact Riddell Exhibition Promotions Pty Ltd, 166 Albert Road, South Melbourne, Vic, 3205.

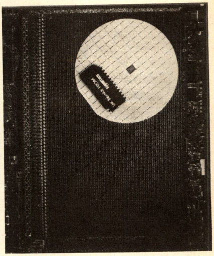

16K Bipolar PROM

What is believed to be the world's first 16K bipolar PROM to go into production has been announced by Signetics. Designated 82S190 (open collector output) and 82S191 (three-state output), the new 16K PROM is the latest addition to a range of PROMs which has already set new industry standards. Samples are now available through Philips Electronic Components and Materials, and production build-up is planned to meet a full-scale demand next year.

The 82S190/191 offers a great deal more than just extra storage. Despite having double the capacity of its 8K counterpart, it has the same power dissipation as the smaller PROM and is almost as fast. Its access time is guaranteed at 80 ns, with 50 ns as the typical value, while the power dissipation is 650 mW typical and 875 mW maximum.

The manufacturing process is the reliable diffused isolation, michrome fuse system utilizing dual-layer aluminium interconnect. The programming circuitry is unchanged from Signetics PROMs currently in production, so new programming equipment is not needed.

For further information, contact Philips Electronic Components and Materials, 67 Mars Road, Lane Cove.

SUPER SPECIALS

BD 139 — 50c ea.
BD 140 — 50c ea.
BC 547/8/9 — 15c ea.
20 555 Timers for $5
MJ2955 — 80c
2N3055 — 75c
T03 Mounting Kits — 5c ea.

CANNON CONNECTORS

XLP-3-11	$2.30
XLP-3-12c	$3.25
XLP-3-31	$3.25
XLP-3-32	$3.00
XLR-LNE-11c	$3.05
XLR-LNE-32	$4.30

Weller cordless soldering iron kit, model WC100DKW — includes batteries, solder, 4 interchangeable tips, battery charger and instructions for only **$29.50.**

TTL

7400	20
7401	25
7402	28
7403	28
7404	37
7405	37
7406	50
7407	50
7408	34
7409	34
7410	20
7411	37
7413	54
7414	90
7416	60
7417	60
7420	30
7422	30
7426	45
7427	45
7430	30
7432	43
7437	50
7438	50
7440	30
7441	1.50
7442	70
7447	60
7448	60
7450	35
7451	35
7453	35
7454	30
7460	35
7470	65
7472	45
7473	60
7474	65
7475	65
7476	45
7480	1.25
7483	1.25
7485	1.45
7486	65
7490	35
7491	1.00
7492	75
7493	35
7494	1.10
7495	95
74100	2.45
74107	65
74121	60
74123	60
74132	1.25
74150	1.80
74151	1.10
74153	1.10
74154	1.70
74157	1.10
74160	1.55
74164	1.55
74165	1.55
74173	2.75
74175	1.65
74180	1.35
74192	1.40
74193	1.40
74221	1.50
74367	1.40

74LS

74LS00	30
74LS01	30
74LS02	30
74LS03	30
74LS04	35
74LS05	35
74LS08	30
74LS09	30
74LS10	30
74LS11	30
74LS12	30
74LS14	1.20
74LS20	30
74LS21	30
74LS27	30
74LS28	40
74LS30	30
74LS32	33
74LS37	45
74LS38	45
74LS40	30
74LS42	1.20
74LS73	1.20
74LS74	50
74LS75	70
74LS78	50
74LS85	1.50
74LS86	50
74LS90	1.20
74LS92	1.20
74LS93	1.20
74LS95	1.50
74LS109	50
74LS113	55
74LS114	55
74LS138	1.20
74LS151	1.20
74LS154	1.60
74LS157	90
74LS163	1.20
74LS164	1.30
74LS174	1.00
74LS175	1.00
74LS191	1.20
74LS192	1.20
74LS193	1.20
74LS194	1.20
74LS195	1.20
74LS196	1.20
74LS221	1.20
74LS253	1.85
74LS279	65
74LS365	80
74LS367	80
74LS368	80

CMOS

4000	20
4001	25
4002	25
4006	1.40
4007	25
4008	1.25
4011	25
4012	25
4013	55
4014	1.35
4015	1.20
4016	50
4017	1.40
4018	1.40
4019	75
4020	1.60
4021	1.40
4022	1.60
4023	25
4024	90
4025	40
4027	80
4028	1.25
4029	1.90
4030	40
4040	1.30
4041	1.25
4042	1.25
4043	1.50
4044	1.50
4046	1.95
4049	60
4050	60
4051	1.20
4052	1.20
4053	1.20
4060	2.65
4066	1.00
4068	40
4069	35
4070	40
4071	40
4072	40
4073	40
4074	40
4076	1.85
4077	40
4078	40
4081	40
4082	40
4510	1.30
4511	1.30
4518	1.30
4520	1.30
4528	1.20
4555	1.20
14553	7.50
14584	1.25
74C00	40
74C02	40
74C04	40
74C08	40
74C10	40
74C14	1.90
74C48	2.55
74C73	1.20
74C75	1.20
74C76	1.35
74C90	2.25
74C93	2.25
74C175	1.85
74C192	2.25
74C193	2.25

LINEAR

301	35
307	65
308	1.35
311	85
324	1.35
339	90
349	2.25
356	1.65
380	1.20
381	2.00
382	2.00
386	1.95
555	35
556	85
565	1.95
566	2.50
567	2.65
709	75
723(VR)	55
741	35
747	1.25
3900	90
3909	1.25
CA3130	1.95

VOLTAGE REGS.

309	1.50
317	2.90
323	8.25
325	2.60
723	55
7805	90
7806	1.30
7808	1.30
7812	90
7815	1.30
7818	1.30
7824	1.30
7905	1.50
7912	1.50
7915	1.50
78L05	50
78L12	50
78L15	50
79L05	85
79L12	85
79L15	85

OPTO

FND507 C/A	1.70
FND 357C/C	1.40
FND 500C/C	1.40
Red LED	22
Green LED	35
Yellow LED	35

DIODES

IN4148	6c — 5c/100
IN4004	9c
IN5625 5A 400V	45c

I.C. SOCKETS

8 PIN DIL	25
14 PIN DIL	33
16 PIN DIL	35

Also in stock Multimeters, relays, veroboard, solder, solderwick, soldering irons, transformers. All components brand new by top companies. Prices current till end of January.

ROD IRVING ELECTRONICS

Shop 499, High Street, Northcote. Vic. 3070. Ph (03) 489-8131. Open Mon-Thurs 8 am — 5.30 pm, Fri 8am — 7 pm. Sat 9 am — 1 pm. Mail Orders: PO Box 135, Northcote. Vic.3070. Minimum 75c post and pack. Send 30c stamp for free condensed catalogue

DISCUS I™

Full-size Floppy Disk Memory for S-100 Systems.

UP IN MINUTES INSTEAD OF MONTHS.

AND STILL UNDER $1,000.

COMPUTER BITS

47 Birch Street,
BANKSTOWN. NSW. 2200.

A DIVISION OF AUTOMATION
STATHAM PTY. LTD.

(02) 709-4144. Telex AA26770.
Trade Enquiries Welcome.

allf
RANGE
EXTENDED
allf

LOW PROFILE TRANSFORMERS

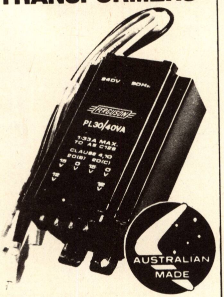

20VA CHASSIS OR FRAME MOUNTED

Type No.	Series Connections	Parallel Connections
PL12/20VA	12 volts at 1.67 amps	6 volts at 3.33 amps
PL15/20VA	15 volts at 1.33 amps	7.5 volts at 2.67 amps
PL18/20VA	18 volts at 1.11 amps	9 volts at 2.22 amps
PL24/20VA	24 volts at 0.83 amps	12 volts at 1.67 amps
PL30/20VA	30 volts at 0.67 amps	15 volts at 1.33 amps
PL40/20VA	40 volts at 0.50 amps	20 volts at 1.00 amps

40VA CHASSIS OR FRAME MOUNTING

Type No.	Series Connections	Parallel Connections
PL12/40VA	12 volts at 3.33 amps	6 volts at 6.67 amps
PL15/40VA	15 volts at 2.67 amps	7.5 volts at 5.33 amps
PL18/40VA	18 volts at 2.22 amps	9 volts at 4.44 amps
PL24/40VA	24 volts at 1.67 amps	12 volts at 3.33 amps
PL30/40VA	30 volts at 1.33 amps	15 volts at 2.67 amps
PL40/40VA	40 volts at 1.00 amps	20 volts at 2.00 amps

60VA CHASSIS OR FRAME MOUNTING

Type No.	Series Connections	Parallel Connections
PL12/60VA	12 volts at 5.00 amps	) single secondary
PL15/60VA	15 volts at 4.00 amps	) winding only
PL18/60VA	18 volts at 3.33 amps	9 volts at 6.67 amps
PL24/60VA	24 volts at 2.5 amps	12 volts at 5.00 amps
PL30/60VA	30 volts at 2.0 amps	15 volts at 4.00 amps
PL40/60VA	40 volts at 1.5 amps	20 volts at 3.00 amps

Made in Australia and Guaranteed by:

FERGUSON

FERGUSON TRANSFORMERS PTY.LTD.
331 HIGH STREET, CHATSWOOD. N.S.W. 2067.

FT4

ELECTROCRAFT
PTY. LTD.
68 Whiting Street, Artarmon, 2064
Telephone 438-4308. 438-3266

We have the largest range of TV antenna accessories in Sydney.
CHECK OUR PRICES

TRADE AND WHOLESALE SUPPLIED

FM ANTENNA'S	
Channelmaster 5 el H. Gain 700FM	19.68
Hills FM1 Local	11.51
Hills 353 3.el Met	14.72
Matchmaster FMG/2 Semi fringe	21.51
Matchmaster FMG/6 Outer fringe	40.64
T.V. ANTENNA'S	
Hills outer fringe CA.16 phase array	48.28
Hills 215 (Australia's best selling high gain 8.el antenna at a new low price)	25.2
Hills EFC.3 (The best of the colour 75 ohm antennas, very high gain, good anti-ghosting	62.41
Channel master 3111 A 300-75 ohm (Best metropolita anti-ghosting antenna)	41.98
Channel master 3110 300-75 ohm local anti-ghosting	27.9
Belling Lee plugs	.8
Belling Lee Coaxial wall sockets	1.7

Ecraft TV FM Distribution Amplifiers and Amplifier Splitters

R.F. Amplifiers. Masthead and Distribution for FM & T from 16 dB Ecraft	45.0
25 dB Ecraft	53.5
Hills MH1 Masthead 300 ohms	61.0

PROJECT KITS for the beginner
Completely safe — battery operated — no main connection. See ADVERTISERS INDEX: KIT BIT AUST.

- **IDEAL XMAS GIFTS**

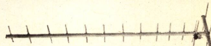

THE TM/13 UHF/CB BEAM

$35.94

BASIC SPECIFICATIONS
ELECTRICAL

Nominal Impedance	50 ohn
Power Handling Cap	5 Wat
Input Termination	Co-Axi
V.S.W.R.	less than 1.3
Bandwidth	10 perce
Forward Gain	15 dB (Ref. Dipol
Frequency response	467 to 477

MECHANICAL
Rugged but lightweight aluminium construction, elipso dal boom shape combines strength with accurate eleme alignment, point of gravity mounting for optimum use wi masthead rotator.

- President Grant SSB 23 ch: with 18 ch Mod. kit. 1 ONLY.......$229
- Rotators CDE AR22XL.......$124
- Build your own CB power supply. Black vinyl case, $3. holes drilled for Ferguson transformer 240V to 18V60 $8.95. Regulator 13.8V 2.2amp $2.94. Circuit supplied.

Please enclose postage with all orders.

WE ARE THE EXPERTS — 30 YEARS
THE ANTENNA BUSINESS

Open Mon. to Fri. 8-5. Sat. 8.30-12

RAVE

PROFESSIONAL

SOUND & LIGHT
SOUND & LIGHT
SOUND & LIGHT
SOUND & LIGHT

Importers of Quality Electronic Equipment

Complete HIRE • SALES • DESIGN service to the entertainment industry.

OFFICE and SHOWROOMS
2388 Gold Coast Highway,
Mermaid Beach. Qld. 4218.
Phone (075) 38-3331.

DJ S77 STEREO DISCOMIXER

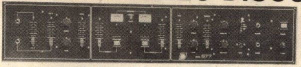

SUPERIOR DESIGN CLEAN, CRISP SOUND REPRODUCTION.

Automatic voice overide • tape-in, tape-out • 2 microphone in • 2 x turntables in • T.T. start buttons • slave out • 2 year guarantee.

Available separate or in console C/W turntables and 200 watt power amp built-in. Mono or stereo. Size (mixer only) 17cm x 86.5cm x 9cm. Weight 4.5kg.

LITO 250 PROFESSIONAL EFFECTS PROJECTOR

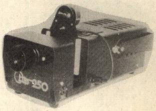

• New 250W Quartz Iodine Effects projector for use with effects from spectacular Lightomation range • Lens system totally enclosed to eliminate light spill • Cool, quiet operation, high efficiency tangential air blower • Used free-standing or suspended with adjustable handle • Supplied as "Main-Frame Unit" with 50mm lens, 60, 85 & 100mm avail. • 14 attachments available — changed by slide-in rotator system — wide selection of cassettes & 6" Effect Wheels • Mains voltage selector gives range of 6 input voltages.

• STROBES • SOUND TO LIGHT UNITS • DRY ICE FOG MACHINES • ROPELITES • LIGHTING STANDS • BEACONS • JBL SPEAKERS & CABINETS • Brochures available on request.

EPROM ERASERS

COMPLETE WITH
20 MINUTE TIMER

ERASES UP TO **30** EPROMS IN **10** MIN
$120 INC SALES TAX P&P
10 EPROM VERSION **$95** INC

PROGRAM TMS2716
for just $20.40 WITH YOUR

2708 PROGRAMMER	
TMS 2716 ADAPTOR BOARD	**$20,40**
WITH ZERO INSERTION FORCE SOCKET	**$28,60**

EAROM ELECTRONICS
PO BOX 40, NTH. BALWYN, 3104

ALSO AVAILABLE FROM

MACKAY ELECTRONIC DISTRIBUTORS PTY. LTD.
Regd. Office: 32 Woodhouse Road, Doncaster East, Victoria, 3109 – Phone: 842 3465
SALES AND SERVICE **Allen** DIGITAL COMPUTER ORGANS

AUDIO ENGINEERING & PRODUCTION

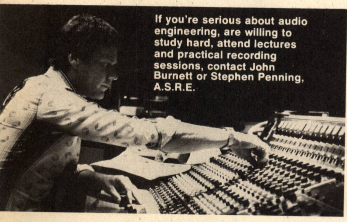

If you're serious about audio engineering, are willing to study hard, attend lectures and practical recording sessions, contact John Burnett or Stephen Penning, A.S.R.E.

SCHOOL OF BASIC ELECTRONICS

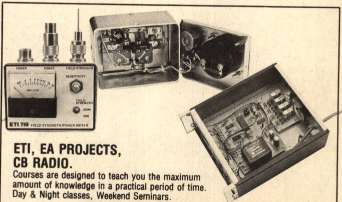

ETI, EA PROJECTS, CB RADIO.

Courses are designed to teach you the maximum amount of knowledge in a practical period of time. Day & Night classes, Weekend Seminars.

. . Sydney 922-6301. . . Canberra 80-4446. . . Adelaide 261-1383. . . Newcastle 69-4021

Fast dependable mail order service
Prime devices at low prices

THE ELECTRONIC MAILBOX
P.O. BOX 97
PENNANT HILLS N.S.W. 2120

1. PROVEN QUALITY * prime factory devices, money back guarantee.
2. SAME DAY SHIPMENT * all orders cleared within 24 hours of receipt. Immediate credit or refund out of stock items.

74LS

74LS00	30
74LS01	30
74LS02	30
74LS03	30
74LS05	35
74LS08	30
74LS09	30
74LS10	30
74LS11	30
74LS12	30
74LS14	1.20
74LS20	30
74LS21	30
74LS27	30
74LS28	40
74LS30	30
74LS32	33
74LS37	45
74LS38	45
74LS40	40
74LS42	1.20
74LS73	1.20
74LS74	50
74LS75	70
74LS78	50
74LS85	1.50
74LS86	50
74LS90	1.20
74LS92	1.20
74LS93	1.20
74LS95	1.50
74LS109	50
74LS113	55
74LS114	55
74LS138	1.20
74LS151	1.20
74LS154	1.60
74LS157	90
74LS163	1.20
74LS164	1.30
74LS174	1.00
74LS175	1.00
74LS191	1.20
74LS192	1.20
74LS193	1.20
74LS194	1.20
74LS195	1.20
74LS196	1.20
74LS221	1.20
74LS253	1.85
74LS279	65
74LS365	80
74LS367	80
74LS368	80

TTL

7400	28
7401	28
7402	28
7403	28
7404	37
7405	37
7406	50
7407	50
7408	34
7409	34
7410	30
7411	37
7413	54
7414	1.03
7416	60
7417	60
7420	30
7422	30
7426	45
7427	45
7430	30
7432	43
7437	50
7438	50
7440	30
7441	1.50
7442	70
7447	1.25
7448	1.25
7450	35
7451	35
7453	35
7454	30
7460	35
7470	65
7472	45
7473	60
7474	65
7475	65
7476	45
7480	1.25
7483	1.25
7485	1.45
7486	65
7489	1.20
7490	75
7491	1.00
7492	75
7493	75
7494	1.10
7495	95
74100	2.45
74107	65
74121	60
74123	1.10
74132	1.25
74150	1.80
74151	1.10
74153	1.10
74154	1.70
74157	1.10
74160	1.55
74164	1.55
74165	1.55
74173	2.75
74175	1.65
74180	1.35
74192	1.40
74193	1.40
74221	1.50

CMOS

4000	25
4001	25
4002	25
4006	1.40
4007	25
4008	1.25
4011	25
4012	25
4013	55
4014	1.35
4015	1.20
4016	50
4017	1.40
4018	1.40
4019	75
4020	1.60
4021	1.40
4022	1.60
4023	25
4024	90
4025	40
4027	80
4028	1.25
4029	1.90
4030	40
4040	1.30
4041	1.25
4042	1.25
4043	1.50
4044	1.50
4046	1.95
4049	60
4050	60
4051	1.20
4052	1.20
4053	1.20
4060	2.65
4066	1.00
4068	40
4069	35
4070	40
4071	40
4072	40
4073	40
4074	40
4076	1.85
4077	40
4078	40
4081	40
4082	40
4510	1.50
4511	1.50
4518	1.50
4520	1.45
4528	1.20

MICROPROCESSOR CHIPS

All devices supplied complete with data.

Z80 2MC/S	$29.95
PIO for Z80	$15.95
CTC for Z80	$15.95
2650A	$19.75
260 PIPBUG	$17.25
SC/MP 11	$12.75
8080A	$12.75
6800	$22.50

OPTOELECTRONICS

FND500 .5" C/C	$1.25
FND 507 .5" C/A.	$1.50
FND 357 .3" C/C.	$1.30
RED LED. .2". 5 for	$1.00
GREEN LED	.35
YELLOW LED	.35

MEMORY IC'S

2101 256 x 4 STATIC RAM.	$3.75
2102-4 1K STATIC.	$1.45
2114 4K STATIC.	2 for $19.95
4116 250NS DYNAMIC.	$22.00

CRYSTALS

(± .005% @ 25°C)

1.000Mhz	7.95
1.843Mhz	7.95
2.000Mhz	7.95
4.000Mhz	7.95
5.000Mhz	7.95
6.000Mhz	7.95
10.000Mhz.	7.95
12.000Mhz.	7.95
18.000Mhz.	7.95
20.000Mhz.	7.95

LINEAR

301	40
307	65
308	1.35
311	85
324	1.35
339	90
349	2.25
356	1.65
380	2.00
381	2.00
382	2.00
386	1.95
555	35
556	85
565	1.95
566	85
567	2.65
709	75
723 (VR)	55
741	35
747	1.25
3900	90
3909	1.25

CAPACITORS

Ceramic disc:

10pf 50V	10
47pf 50V	10
100pf 50V	10
220pf 50V	10
330pf 50V	10
470pf 50V	10
.001mfd 50V	10
.0047mfd 50V	10
.01mfd 50V	10
.022mfd 50V	10
.047mfd 50V	10
.1mfd 50V	10

Polyester:

.001 100V	15
.0015mfd 100V	15
.0022mfd 100V	15
.0047mfd 100V	15
.01mfd 100V	15
.022mfd 100V	15
.047mfd 100V	15
.1mfd 100V	20
.15mfd 100V	25
.22mfd 100V	25

Electrolytic:

1mfd 50V	10
4.7mfd 50V	10
10mfd 50V	10
22nfd 25V	15
47mfd 25V	15
100mfd 25V	20
220mfd 25V	30
470mfd 25V	45
1000mfd 25V	55
2200mfd 16V	85

Tantalum:

.1mfd 35V	35
.22mfd 35V	35
.33mfd 35V	35
.47mfd 35V	35
.68mfd 35V	35
1mfd 35V	35
1.5mfd 35V	35
2.2mfd 25V	35
3.3mfd 25V	35
4.7mfd 25V	35
6.8mfd 25V	35
10mfd 25V	40
22mfd 25V	45
33mfd 16V	50

¼W RESISTORS

Full E12 range from 10HM to 10MEG .... .04

Each decade includes: 1.0, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2

SWITCHES

SPST min tog	1.20
ADDT min tog	1.45
SPDT mon push.	1.75
DIPSWITCH 16pin.	2.50

PLEASE ALLOW $2.00 postage and handling on all orders.

Ideas for experimenters

These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.
Electronics Today is always seeking material for these pages. All published material is paid for – generally at a rate of $5 to $7 per item.

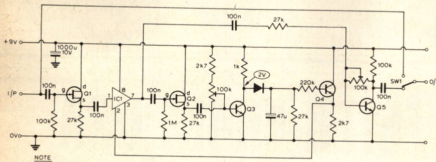

NOTE
Q1, 2 are 2N3819
Q3,4,5 are BC109C
D1 is OA91
IC1 is MC3340

Guitar Sustain Unit

The sustain to be described here holds the output at a constant level over a vide range of input levels. It was designed to use with electric guitars and has a naximum effect with the guitar pick-up full up.

The principle employed is that of an AGC, whereby the circuit output is nonitored by a DC voltage follower which controls the gain of the VCA through which the signal passes. The advantages of this circuit are that, unlike many such devices, it does not use opto-coupling which draws too much current for battery powered equipment; it produces no audible distortion; components are easily obtained – and cost is low.

Construction method is not critical.

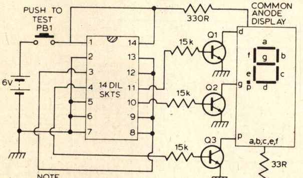

NOTE
Q1–3 ARE BC109

MOS Gate Identifier

he circuit can be used to distinguish our types of dual input gates – AND, R, NAND, NOR – it is also a quick ethod of checking IC function. If an AND gate is inserted into the socket, an A appears on the LED. An O denotes an OR gate. The decimal point is used to denote inverted function, i.e. A is an NAND gate.

TELEX®

PUSH BUTTON – INSTANT CASSETTE COPIERS

Desk top units to suit every need

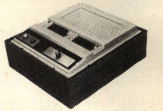

ECONOMY COPIER
- High speed, copies a C60 in 2 minutes
- Two button operation, automatic rewind.

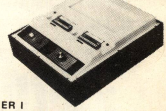

COPIER I
- High speed, copies a C60 in 2 minutes
- Two button operation
- Track selectable erase, automatic rewind.

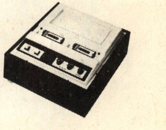

STEREO COPIER IV
- High speed, copies a C60 in less than 3 minutes.
- High fidelity stereo copies. Track selectable recording and erase for four channel operation.
- Two button operation – automatic rewind.

SLAVE COPIER
- When plugged into the Copier I or Copier IV, provides an additional two copies simultaneously.
- Two slave copiers can be connected.

FOR FURTHER INFORMATION:
AUDIO TELEX COMMUNICATIONS PTY. LTD.

SYDNEY
54-56 Alfred Street,
Milsons Point 2061
Telephone: 929-9848

ADELAIDE
Werner Industries,
28 Gray Street,
Kilkenny 5009
Telephone: 268-2801

BRISBANE
294 Montague Road
West End, 4101
Tel.: 44 6328

MELBOURNE
828 Glenferrie Road,
Hawthorne 3122
Telephone: 819-2363

PERTH
Electro Acoustic Co.
55 Frobisher Street
Osborne Park, 6017
Tel.: 444 8688

HOBART
Video & Sound Services
11-13 Andrew Street
North Hobart, 7000
Tel.: 34 1180

TELEVISION REPLACEMENTS CHRISTMAS SPECIALS

REAR 139 UNION ROAD, SURREY HILLS, VIC. 3127. PHONE: 89-1019.

$85

BSR P157 belt driven semi-automatic. For the first time a belt drive player under $100. This player, without cartridge, would make a beaut disco unit.

PHILIPS MINIWATT TECH DATA BOOK

A great deal of information at a sensible price. Contains information on 1700 valves, 160 semiconductors, 68 picture tubes. From Philips with love

ONLY $3

S-DEC

With free matching ZB5D Blob Board and leaflet describing 9 circuits.

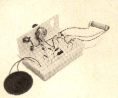

Build your projects on this remarkable, resusable Breadboard, if you wish to make them permanent, transfer them to the matching Blob Board.

$8.12

GM5 AERIAL

Latest metropolitan aerial from Hills. GM5 will out-perform most primary signal aerials. Has to be seen.

ONLY

$10.13

Yes, we do have a large range of aerials

CUTTER & PLIERS

West German quality, 4½" or 110 mm Cutters and 5" or 130 mm Snub Nose Pliers. Just the thing for the electronic technician.

$9 the set.

SCOPE 240V 60 WATT IRON

Automatic temperature controlled, change temperature without changing tips. Try it now!

ONLY

$29.95

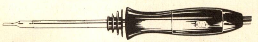

Non Linear Systems Mini Oscilloscope $379.50

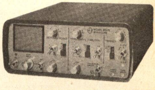

PIEZO TWEETER FROM USA

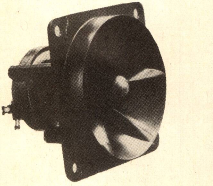

Frequency Response: 3.8 to 28 KC.
No Crossover needed.
35V RMS (100W 4 ohm system).

As used by major musical instrument manufacturers.

LARGE DISCOUNT FOR QUANTITY

WRITE or PHONE FOR RE-AN CATALOGUE.

HOLDEN WASP INTERNATIONAL
PO Box 532, MARRICKVILLE. 2204. Phone 560-3488.

SOME OF AUSTRALIA'S LOWEST COMPONENT PRICES

NOTE: REGULAR PRICES – NOT TEMPORARY SPECIALS – KEEP US IN MIND FOR THAT NEXT ORDER

POTS 38c CAPS 5c

POLYESTER FILM CAPS

E12 10% 100V
All values .001 to .01 — 5c ea.

.01	5c	.1	10c
.012	6c	.12	11c
.015	6c	.15	12c
.018	6c	.18	14c
.022	6c	.22	15c
.027	6c	.27	16c
.033	7c	.33	18c
.039	7c	.39	19c
.047	7c	.47	20c
.056	8c		
.068	8c		
.082	9c		

All values in uF

10% off 100 same uF

SUPERB LEDS $12/100

BC108—13c, 10 for $1.20

ELECTROCAPS (UPRIGHT)
(per 100 prices in brackets)

Cap.	16V	25V	50V
0.47 uF thru to	all	all	all
10 uF	5c($3½)	6c($3¾)	7c($4)
22 uF	6c($3¾)	7c($4)	8c($5)
33 uF	8c($4)	9c($5)	10c($6)
47 uF	9c($5)	10c($6)	11c($7)
100 uF	10c($6)	12c($7)	14c($11)
220 uF	12c($8)	16c($10)	35c($17)
470 uF	16c($12)	22c($16)	45c($30)
1000 uF	22c($18)	30c($25)	75c($50)

1000 uF/16V axial — 20c ea. $8 per 50
2200 uF/50V axial — 95c ea. $8 per 10
Full axial price list — SAE

2c RESISTORS — our 2 year old price still current. Opposition hoped we would go broke but our price remains at 2c ea.
1 Ohm to 10 M ¼W 5% E12 carb. film $1.80 per 100 same value (or ½W 3c, $2.50 per 100 same value)

LEDs: $12 a 100, $110 a 1000, or 17 each, 10 for $1.50. LEDs superb 5mm red well difused wide viewing angle Quality mtg. clips 5c ea. $4 a 100.

Potentiometers: 38c ea. rotary carb linear 500 Ohm, 1K, 5K, 10K, 25K, 50K 100K, 250K, 500K, 1M, 2M (¼" alum shafts) Log: 50c ea except no 500 Ohm or 2M Trimpots: 15c ea 100 Ohm to 2M

ZENER DIODES: 15c each 400mW 5% E24 values 3V to 33V

Trade/govt./S.T. exempt: welcome. Sen for special lists (eg. $26 a 100 pots plu tax if applic.)

Keep electronics a hobby and not a luxury compare our prices and buy from u Same day turnaround service (unle swamped). All goods top quality and new No minimum order. One P/P charge 45c regardless of quality. Advert curren 3 months for late readers.

SCRs:				TRIACS:		DIODES:	
0.8A	30V	C103Y	35	2A 400V ESP240	65	1N4001	7c (1A 50
0.8A	200V	C103B	60	6A 400V SC141D	$1.30	1N4002	8c (1A 100
4A	30V	C106Y1	40	10A 400V SC146D	$1.50	1N4004	9c (1A 400
4A	400V	C106D1	75	25A 400V SC260D	$2.50	1N4007	12c (1A 1000
8A	400V	C122D	$1.05	DIAC ST2	35	1N4148	5c, $4/C, $30/
8A	500V	C122E	$1.20	Chart to identify leads			
25A	400V	C37D	$2.50	Plus trigger info.	10c		

DIGGERMAN ELECTRONICS

P.O. BOX 33, CORAMBA NSW. 2466.

Ideas for experimenters

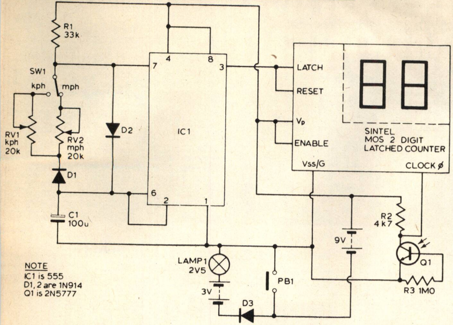

Digital Bike Speed

This unit provides push-bike speed measurement between zero and 100 km hr or 100 mph! The circuit is based on the Sintel MOS counter block, which counts the pulses from the photo transistor Q1.

The pulses are provided by fixing 18 aluminium 'barriers' to the wheels. Q1 was an unmarked type in the prototype, n a TO 18 package. This mounts in an old felt-tip pen case opposite the lamp so that the barriers interrupt the beam in operation. The counter operates whilst PB1 is pressed, but latches after a time determined by RV1 or RV2. IC1 and associated components. IC1 forms a square-wave oscillator with variable mark-space ratio. The time for which pin 3 is taken low is determined by RV1/RV2 — this enables the counter.

The speedo accuracy is determined by the accuracy of setting of controls RV1 and/or RV2.

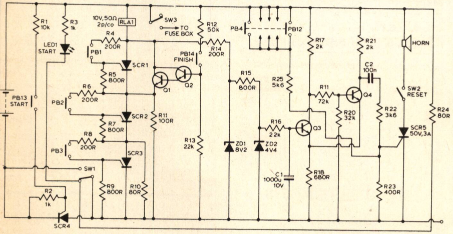

lectronic Ignition Switch

/hen used with a calculator type keyoard, this circuit provides a 'combination lock' ignition switch which nly activates if the correct sequence of hree numbers is keyed in. The keyboard as 14 keys numbered 1 to 12, 'START' nd 'FINISH'. To start the car, the tart' key is pressed and the start LED ill light. The correct sequence of 3 numbers is then keyed in. If the sequence is wrong, the cars horn will be sounded. If the right sequence is entered, the 'START' LED will extinguish and the ignition will be energised. The correct sequence will be PB1, PB2, PB3, but these can be arranged amongst the other keys in the keyboard and given any numbers.

RADCOM
constructor components

EVERYTHING FOR
THE CONSTRUCTOR
AT ONE SHOP
AT PRICES TO SUIT
YOUR BUDGET

SPECIAL!
Make your own PCB's
with our super kit.
ONLY $8·50

SILICON VALLEY
stockists

— CAPACITORS —
— RESISTORS —
— POTS —
— SWITCHES —
— PLUGS —
— SOCKETS —
— PANEL LAMPS —
— TRANSISTORS —
— DIODES —
— BOXES —
— LEDS —
— IC's —

Try us for the
hard-to-get components
Block Capacitors
Silver Micas
High Voltage
etc, etc

Ask at the counter
for our stock list

Cnr. Eldridge & Willfox Rds.
BANKSTOWN, NSW.
709-4706

DISCOUNT COMPONENTS

10 RED LEDS	$1.50
7805	90c
7812	90c
LM317K	$2.90
TIL209	18c
10 BC547	$1.20
IN4003	7c
IN4002	7c

100 RED LEDS	$13.00
10 4016	$4.50
6 LUG TAG STRIPS	5c
309K	$1.50
10 GREEN LEDS	$2.90
10 YELLOW LEDS	$2.90
10 4011	$2.00

10 74LS00	$2.00
10 uA301	$3.30
4N28	$1.00
4N29	$1.10
10 7490	$3.00
10 74123	$5.00
10 741	$2.90
LED CLIPS	2c
10 723	$4.50

ULTRASONIC TRANSDUCERS

as used in ETI 585R/T ultrasonic switch

40T	$5.95
40R	$5.95
As a pair	$11.00

ZENERS

400mW E24 Values 3.3v to 33v	0.20
1 Watt Zeners 3.3v to 33v	0.33

TRIACS

SC141D	$1.30
SC151D	$2.10

DIACS

ST2	0.35
ST4	0.80

CLOCK MODULES

MA1002B	$11.50
MA1003	$21.50

MICRO'S

2708 EPROM	$15.00
2114	$14.00
2102 450nS	$2.10
2650	$26.00
8080A	$13.00
9305	$3.30
9317	$3.75
9334	$3.75
9350	$1.80
9368	$1.80

PCB'S PRECISION DRILLED FIBREGLASS

ETI 043	$1.40
ETI 044	$1.30
ETI 047	$1.50
ETI 061	$1.40
ETI 062	$1.80
ETI 063	$1.70
ETI 064	$1.70
ETI 065	$1.70
ETI 067	$1.80
ETI 068	$1.40
ETI 071	$1.40
ETI 072	$1.80
ETI 083	$1.80
ETI 084	$1.70
ETI 085	$1.30
ETI 130	$1.90
ETI 134	$1.90
ETI 135	$1.90
ETI 245	$1.60
ETI 417	$1.80
ETI 445	$1.50
ETI 446	$1.90
ETI 449	$1.50
ETI 450A	$1.90
ETI 450B	$1.90
ETI 480	$2.20
ETI 480PS	$2.20
ETI 481M	$2.00
ETI 481PS	$2.50
ETI 483	$2.20
ETI 484	$3.90
ETI 485	$2.90
ETI 486	$2.90
ETI 528	$2.20
ETI 541	$2.20
ETI 581	$2.20
ETI 583	$2.20
ETI 585R	$1.60
ETI 585T	$1.40
ETI 586	$2.30
ETI 603	$2.50
ETI 604	$1.60
ETI 635	$2.90
ETI 708	$1.90
ETI 713	$3.90
ETI 714	$1.90

RESISTORS

	1-99	100-999
½ watt Metal Glaze		
1 ohm to 1M (E12 values)	**3c**	**2.5c**
1.2m — 10m (carbon)	**5c**	**4c**
1 watt carbon 1 ohm to 1M	8c	7c
5 watt 1 ohm to 100 ohm	.40	.35

TANTALUMS Resin Dipped

	1-9	10-99
.1, .15, .22, .33, .47, .68uF (all 35V)	.25	.20
1uF 35V	.25	.20
2.2uF 25V	.23	.20
2.2uF 35V	.25	.20
3.3uF 25V	.25	.20
4.7uF 35V	.25	.22
6.8uF 35V	.30	.25
10uF 16V	.25	.23
10uF 35V	.30	.28
15uF 16V	.30	.25
15uF 35V	.50	.45
22uF 16V	.38	.35
47uF 16V	.65	.60
68uF 16V	1.20	1.10
100uF 6.3V	.70	.65

MINIATURE TRIMPOTS

	1-9	10 up
0.1 watt, .1" spacing 100, 250, 500, 1K, 2K, 5K, 10K,	.20	.17
25K, 50K, 100K, 250K, 500K, 1M	.20	.17

I C SOCKETS

0	1-9	10 up
8 Pin DIL	.25	.23
14 Pin DIL	.33	.30
16 Pin DIL	.35	.30
18 Pin DIL	.55	.50
24 Pin DIL	.90	.85
40 Pin DIL	1.40	1.20
28 Pin DIL	1.20	1.10

POTENTIOMETERS

.25 watt rotary carbon single gang, Log or Lin.

1K, 5K, 10K, 25K, 50K	.50
100K, 250K, 500K, 1M, 3M (Lin)	.50

CERAMICS

10pF to 680pF	.05c
820pF to .0015uF E12 Values	.06c

Include 30c postage for free catalogue.

ELECTROLYTICS

			1-9	10 up
4.7 uF	25v	PCB	0.08	0.07
10 uF	25v	PCB	0.09	0.08
10 uF	50v	PCB	0.10	0.09
22 uF	16v	PCB	0.08	0.07
22 uF	35v	PCB	0.10	0.09
33 uF	16v	PCB	0.09	0.08
33 uF	50v	PCB	0.11	0.10
47 uF	16v	PCB	0.10	0.09
47 uF	35v	PCB	0.12	0.11
100 uF	10v	PCB	0.11	0.10
100 uF	16v	PCB	0.12	0.11
220 uF	25v	PCB	0.15	0.14
470 uF	16v	PCB	0.17	0.16
1000 uF	25v	PCB	0.38	0.36
2500 uF	50v	Axial	1.95	1.85
2200 uF	25v	PCB	0.55	0.90
6800 uF	50v	LUG	4.75	
5600 uF	40v	PCB	2.90	
4700 uF	35v	Axial	2.10	

KITS

ETI 480 100W Module Kit includes Heat Sink Bracket	$19.75
ETI 480 50W Module Kit includes Heat Sink Bracket	$16.00
12 volt Electronic Siren Kits	
1. "Whip"	$8.00
2. "Wail"	$8.00
3. "Flying Saucer"	$8.00
Horn Speaker to suit	$8.50

SILICON VALLEY

Products in stock. Also available mail order as per the Silicon Valley catalogue and price list.

Also in stock: Multimeters, relays, veroboard, solder, solderwick, soldering irons, transformers. All components brand new by top companies. Prices current till end of January.

ROD IRVING ELECTRONICS

Shop 499, High Street, Northcote, Vic 3070. Ph (03) 489 8131. Open Mon-Thurs 9.00-5.30, Sat 9.00-1.00. Mail Orders: PO Box 135, Northcote Vic. 3070, Minimum 75c post and pack. Send 30c stamp for free condensed catalogue.

Ideas for experimenters

Half-Wave Control

One of the most common applications for SCR phase control systems is speed control of commutator motors — such as those used for food mixers, sewing machines, pottery wheels etc.

However one of the disadvantages of controlling motor speed by varying input power is that as the effective power input is reduced to slow down the motor — the torque available is reduced as well.

This may be overcome by using a feedback signal to advance the firing angle in proportion to the load on the motor — thus increasing the power input if more torque is required.

The circuit shown (right) achieves this load compensating function by deriving a feedback signal from the armature back-emf (produced by the residual field of the motor). In this circuit, the SCR is triggered when the voltage on the wiper arm of potentiometer R2 rises to a high enough value to forward bias diode D2 — thus allowing gate current to flow. As the back emf tends to reverse bias D2, the firing point of the SCR depends largely upon the back emf and this in turn is a function of speed. If the motor is loaded, the speed reduces, thus also reducing the back emf — hence D2 becomes forward biased earlier in the cycle (triggering the SCR earlier in the cycle), and thereby supplying the motor with more power to offset the effect of the loading.

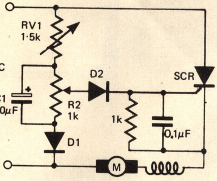

The component values shown are suitable for most fractional horse-power motors — for optimum results it will be necessary to adjust component values to suit the motor used.

The circuit described above will provide stepless speed control over a wide range of motor speed — but tends to cause jerky operation at low speeds.

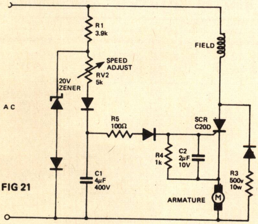

FIG 21

nproved Half-Wave

s may be seen from the circuit diagram t is necessary to bring out separate onnections from the armature and field vindings. This is generally a simple peration and providing it can be done he circuit will provide stepless speed control down to virtual standstill. In this circuit the 20 V zener diode provides a constant voltage for the discharge of C1. Capacitor C2 and resistor R4 are connected from gate to cathode of the SCR to stabilize the circuit by preventing the SCR from being triggered by extraneous signals.

NORTRONICS®

AUDIO & DIGITAL TAPE HEADS

for long life extended response

- Replacement heads for cassette decks, reel to reel decks, cartridges and cassette recorders. Also professional recorders and duplicators.
- Will fit AMPEX, SCULLY, TEAC, ATC, GATES, PENTAGON, IFONICS and many more.
- Complete range of Alignment tapes for cassette, reel to reel and cartridge decks.
- REGULAR MAINTENANCE ENSURES CONTINUED OPTIMUM PERFORMANCE. Nortronics manufacturers a full range of audio care products.

- NORTRONICS audio care products are designed to care for and maintain your valuable recording equipment.
- SEND TWO 20c STAMPS FOR OUR FREE BROCHURE ON THE COMPLETE NORTRONICS RANGE.

E.I. EMAC INDUSTRIES Pty.Ltd.

9 Meriton Place, Clayton South,
3169. Tel: 544-5157

COLOUR TV GAMES

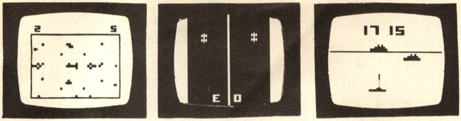

teleplay AUSTRALIA

KITS

Colour TANK BATTLES	$48.50
B&W ROAD RACE	$35.00
COLOUR WARFARE	POA

(available late October send SAE for details)

CHIPS

AY-3-8610 (10 GAMES)	$15.50
AY-3-8603 (ROAD RACE)	$15.80
AY-3-8605 (WARFARE)	$ POA
AY-3-8710 (TANKBATTLES)	$16.40
COLOUR ENCODER	$9.80
CRYSTALS	
1 MHz	$7.10
3.579MHz	$2.60
4.433MHz	$4.10

Kits include all parts, just add controls and case

PRICES INCLUDE POSTAGE IN AUST

PO Box 90,
EAST KEW, 3102.
VICTORIA.

EXPAND YOUR M6800 D2 KIT

16K RAM CARD Using 2114L (see ETI Sept '78)

PCB plus support IC's Kit	$111.80
8K assembled & tested (450 nS low power)	$295.80
16K assembled & tested (450 nS low power)	$451.25

16K RAM/PROM Using 2102s & 2708s (see ETI Oct '78)

16K Memory Mother Board Kit	$49.20
4K RAM PLANE KIT (450 nS)	$75.25
4K ROM PLANE Kit (2808s extra)	$33.90
RAM or ROM PLANE PCB	$16.75
Set of sockets for stacking RAM/ROM PLANE on Mother Board (included with kits but not PCBs)	$3.40

BACKPLANES & EDGE CONNECTORS

5 slot backplane	$27.60
11 slot backplane	$35.90
Edge connectors (PCB mounting or solder eye) each	$8.50 or 5 for $39.75; or 11 for $84.70

BUFFER ICS

2 x 8T26, 3 x 8T97, 1 x 7430	$13.80

CDB-150 FAST AUDIO CASSETTE INTERFACE

In case (software driver included)	$199.00

SPECIAL 2708 EPROM PROGRAMMER $136

(See ETI Nov.)

Offer open till 31.1.79. All prices include tax. Add P&P: $1 — cost under $50, $2 — $50 to $150, $3 — over $150.

PP Pennywise Peripherals 19 Suemar St, Mulgrave, Vic
3170. Ph (03) 546-0308.

DICK WOODS ELECTRONICS

77 EDGEWORTH DAVID AVENUE,
HORNSBY, NSW 2077. PH. 487-3111

TTL

7400	$0.23
7401	0.23
7402	0.23
7403	0.23
7404	0.23
7405	0.33
7408	0.28
7410	0.25
7413	0.43
7414	0.95
7416	$0.43
7420	0.25
7430	0.25
7442	0.65
7447	1.10
7473	0.43
7474	0.50
7475	0.60
7476	0.65
7485	1.20
7486	0.50
7490	0.65
7491	$0.95
7493	0.65
7495	0.95
7496	1.15
74107	0.50
74121	0.55
74123	0.85
74125	0.95
74141	1.25
74191	1.35
74192	1.10
74193	1.65

REGULATORS

7805	$1.20
LM340T12	1.20
LM340T15	1.20
LM340T24	1.20
LM320K5	2.00
LM320K12	2.00
LM320T15	2.00

EPROM

2708	16.00

DIODES

EM401 1A	$0.12
1N4720R 100PIV 3A	0.36
1N4721R 200PIV 3A	0.40
1N4722R 400PIV 3A	0.47
Bridge Rectifier 25A	2.90

TRANSISTORS

2N2222A NPN 500mW	0.45
2N2907A PNP 400mW	0.45
2N3567 NPN 300mW	0.40
TIP3055 NPN 115W	0.60

CAPACITORS

0.01 uF 400V	$0.20
0.047 uF 400V	0.30
0.1 uF 400V	0.40
0.47 uF 400V	0.65
TAG Tantalum 35V	0.40
ELECTROLYTICS from	0.18

SWITCHES

SPST standard	0.80
DPST standard	0.95
DPDT standard	1.15

Resistors ½W all values	$0.04
Potentiometers from	0.25
12 way two screw connectors	0.70
IC sockets 8 to 40 pin from	0.22
SWR Meters JD110	15.00
SWR Meters JD175	19.50
SWR Meters JD176	23.00
C.B. ELECTRO-LOCK mounts	12.00
U.H.F. Lightning Arrestor	2.00
U.H.F. 259 T connector	1.90
T.V. Hi-pass filter	0.99
JD150 Hi-pass filter 1KW	22.50
Instrument Case 255x135x130	14.00
Instrument Case 350x240x120	18.00

PLESSEY FOSTER LOUDSPEAKERS

TWEETERS from	$6.85
MIDRANGE from	$8.00
WOOFERS from	$22.95

Soan digital multimeter-liquid crystal display $109

20p.c. off Ultilux & Molex connectors. Large range of antennae & fittings. Wirewrap supplies and sockets.

METAL THREADS C5&RH

⅛:½" to 3" pack 25 from	0.40
5/32":¼" to 1" pack 25 from	0.40
3/16":½" & ¾" pack 25 from	0.50
¼":⅝" to 3" packs from	0.50
5/16":1¼" to 2¼" pack 10 from	0.45
Nuts and washers packs from	0.20

When it comes to electronics, come to ***DICK WOODS***

ETI SPECIALS

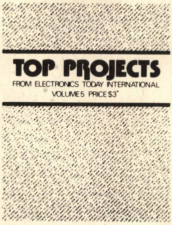

TOP PROJECTS VOL 5
Our latest project book. All the most popular projects which have been published recently in Electronics Today. Includes Bucket Brigade Audio Delay Line, Howl-round Stabilizer, Transmission Line Speakers . . . . . . $3.00.

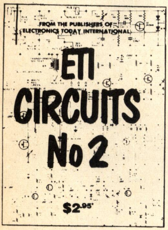

ETI CIRCUITS NO 2
Ideas and data for experimenters. There are about 200 circuit ideas in this book. It's not for the beginner. But someone with a fair bit of experience in electronics will get a lot of use from this book. Invaluable for ideas and inspiration.. . . . . $2.95.

PROJECT ELECTRONICS
If you're just getting interested in electronics this is the book for you. There are lots of projects to build. They're simple, educational and useful too. And there's advice about constructional methods and electronics components . . . . $4.75.

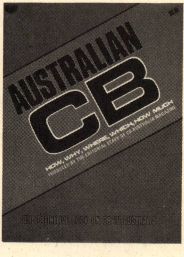
AUSTRALIAN
CB
HOW, WHY, WHERE, WHICH, HOW MUCH
PRODUCED BY THE EDITORIAL STAFF OF CB AUSTRALIA MAGAZINE
THE DEFINITIVE BOOK ON CB IN AUSTRALIA

AUSTRALIAN CB
All about CB. . How to buy and install a rig. How to work interstate on skip. What UHF CB is like. How to build accessories. Australian CB is a thorough, simple yet authoritative guide to CB in Australia 1978 . . . . $3.95.

If your newsagent has sold out, order directly from us at Modern Magazines, 15 Boundary Street, Rushcutters Bay, 2011. Just add 45 cents to the price for post and packing

electronics today SERVICES ADVERTISERS INDEX

READERS' LETTERS

No charge for replies but a foolscap-size stamped addressed envelope must be enclosed. Project queries can only be answered if related to item as published. We cannot assist if project is modified nor if components are otherwise than specified.

We regret we cannot answer readers' enquiries by telephone.

SUBSCRIPTIONS AND BACK ISSUES

ETI subscriptions cost $17.00 per year (inc. postage) within Australia. Cost elsewhere is $17.65 (inc. postage — surface mail). Airmail rates on application.

Back issues cost $1.25 each plus 45 cents post and packing.

We can supply **only** the following issues.

1976: Nov., Dec.
1977: All issues except Jan, Feb, March.
1978: All issues.

Photostats are available of any article ever published in ETI. We charge a flat $1.00 regardless of page quantity from any one issue of ETI. Thus if the article is in three issues the cost is $3.00 Send orders to address below.

Binders $4.50 plus 90c post NSW, $2.00 other States.

Microfiche editions of this publication are available by annual subscription from Microsystems Pty Ltd, PO Box 188, North Sydney, NSW. 2060.

COPYRIGHT

The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

LIABILITY

Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any component parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid.

A MODERN MAGAZINES PUBLICATION

PRODUCTION

Art Director:	Sheila Tonsic
Assembly:	Bill Crump/Simon Bracken
Production Manager:	Bob Izzard
Subscriptions & Circulation:	John Oxenford
Project Design:	Nebula Electronics
Acoustical Consultants:	Louis A. Challis & Assoc.

Sydney: **Modern Magazines**
Bob Taylor (Manager), Geoff Petschler (NSW Manager), 15 Boundary St., Rushcutters Bay 2011. Tel: 33-4282.

Melbourne: **Modern Magazines**
Tom Bray (Manager), Poppe Davis, Suite 24, 553 St. Kilda Rd, Melbourne.
Tel: 51-9836

Brisbane: **Modern Magazines**
Geoff Horne, 60 Montanus Drive, Bellbowrie, Qld. 4070.
Tel: 202 6229.

Adelaide: **Harry Hastwell Media**
399 Glen Osmond Rd, Glen Osmond, S.A. 5064.
Tel: 79-1869.

Perth: Aubrey Barker, 133 St. George's Terrace, Perth. 6000.
Tel: 322 3184.

Hobart: H.W. Lincone, 23 Lord St, Sandy Bay. Tasmania. 7005.

Tokyo: Genzo Uchida, Bancho Media Service, 15 Sanyeicho, Shintuku-Ku, Tokyo 160.

London: Electronics Today International, 25-27 Oxford St, London, WIR 1RF. Tel: 01-434-1781/2.

U.S.A.: Elmatex International, PO Box 34607. Los Angeles, CA. 90034. Tel: (213) 821 8581. Telex: 18 1059 (Elmatexint USA)

Electronics Today International is published by Modern Magazines (Holdings) Ltd, 15 Boundary St., Rushcutters Bay, NSW 2011. It is printed (in 1978) by Wilke & Co., Browns Rd, Clayton, Victoria and distributed by Australian Consolidated Press.

ADVERTISERS INDEX

Applied Technology 63
Advanced Computer Products 43
Acoustic Research 8
Auditec 94
Automation Statham 120
Audio Telex 123
Ampec Engineering 116
Atram 106
Bail Electronics 102
Convoy 11
Cema 64-65
Centaur Industries 38
Chloride Batteries 56
Chromatec Video 88
Campbelltown Hi-Fi 115
Computer Art & Education 95
Dick Smith 54-55, 80
Defense Recruiting 10
Dicker, J.W. 44
Delsound 113
Diggerman Electronics 124
Dick Woods 128
Electronic Mailbox 122
Emona 53
Elmeasco 108
Ellistronics 95
Electrocraft 120
Electro-Voice 115
Emac 127
Earom 121
Electronic Agencies 102
Fairchild 114
Fhone Audio 30
Ferguson Transformers 120
Hagemeyer 2, 131
Harmonix Acoustix 20
Holden Wasp Industries 124
Hi-Fi City 103
IC's Unlimited 36
Impact 115
Jade Computer Products 50
Jaycar 28
Kit Bits 77
Lendan 72
Maurice Chapman 87
Moorabin Tech. College 103
National Panasonic 132
Non-Linear Systems 86
Orbit Electronics 86
Professional Products 107
Pre Pak 49
Philips Elcoma 35
Pennywise Peripherals 128
Pioneer 22
Rod Irving 119, 126
Roland Australia 113
R & D Electronics 94
Rave 121
Radcom 125
Semiconductor Imports 71
Soundring Distributors 28
SM Electronics 34, 116
Semcon 93
School of Basic Electronics 121
Tandy 12
Trio-Kenwood Aust. 98
Tasman Electronics 85
TV Replacements 124
Teleplay Australia 125
University Grahame 48
Vicom 90
Vesco Electronics 10
Vanfi 24-2
Warburton Franki 88, 9

THE JVC RECEIVER.

Every bit as revolutionary as they look, and then some.

In our case, looks are never deceiving. Because all our new DC integrated stereo receivers combine unprecedented, revolutionary styling with unique electronic design features that reflect JVC's more than 50 years' experience in audio development and innovation.

DC Power Amplifier Design

All four new JVC receivers feature DC amplifier circuitry. They offer virtually distortion-free performance (0.03% THD) throughout the entire audible spectrum. As a result, the sound you hear is clearer, cleaner and crisper. In addition, your speakers are protected with the Triple Power Protection circuit and you can monitor output wattage with dual power meters. Choose from 120, 85, 60 and 35 watts/channel.*

SEA all the way

All four receivers offer JVC's exclusive built-in SEA five-zone graphic equalizer for more complete control of the music spectrum than conventional tone controls. You can attenuate or accentuate any of five separate musical bands, and as an added feature, we've incorporated a special button so that the SEA circuit can be switched to your tape deck.

Pushbutton Source Selectors

A horizontal panel of pushbuttons provides total control over all functions. And brilliantly illuminated LEDs instantly indicate the program source. Professional-type slider controls set volume and balance.

Combine all these exclusive features with high sensitivity and tuning precision, thumb control tuning wheel and accurate dual-metering and you'll see just how revolutionary the new JVC DC integrated stereo receivers are. Play one at your JVC dealer soon.

Top JR-S401
Left JR-S201 Right JR-S301

For details on all JVC Hi-Fi Equipment, write to
JVC Advisory Service,
Box 307, North Ryde,
N.S.W. 2113.

For pure Hi-Fi entertainment!

JVC
the right choice

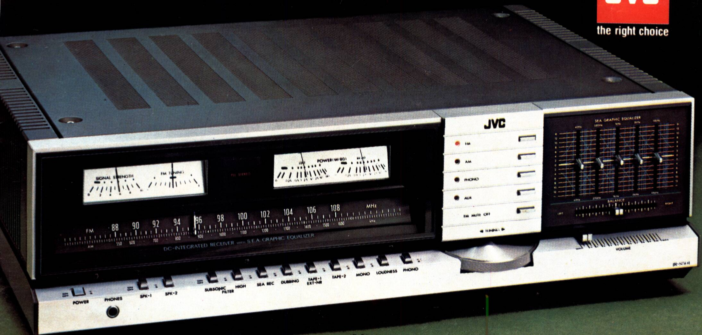

JR-S501

* @ 8 Ohms, both channels driven from 20Hz-20 KHz, with no more than 0.03% THD.

TECHNICS SU8080 INTEGRATED DC AMPLIFIER: AMPLIFIES...NOT MODIFIES.

The first and foremost function of an amplifier is to amplify. To amplify all the incoming signals as accurately as possible. Technics terms this "waveform fidelity" which simply means that the music that's put in will be the music that comes out, neither adding nor subtracting fr[illegible] the original.

In the SU8080 Technics have ac[illegible]form fidelity by eliminating capacitors—the cause of very low frequency signal blocking—from the signal path stages and all connections in between. Their elimination made DC (Direct Current) in the power amplifier possible, resulting in ultra-wide frequency response and phase fidelity.

Rated power output of the Technics SU8080 is 72 watts per channel, RMS at 8 ohms, from 20Hz-20kHz with no more than 0.02% total harmonic distortion. Real power for real sound. And there's a totally independent power supply for each channel to eliminate transient crosstalk.

The phono equalizer input is equipped with Technics developed ultra-low noise transistors, giving an extremely high signal to noise ratio of 88dB at a sensitivity of 2.5mV. The SU8080 amplifier. Achieving waveform fidelity.

For a National Technics catalogue, please write to:
National Technics Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033.

National Technics
hi-fi

T78.1